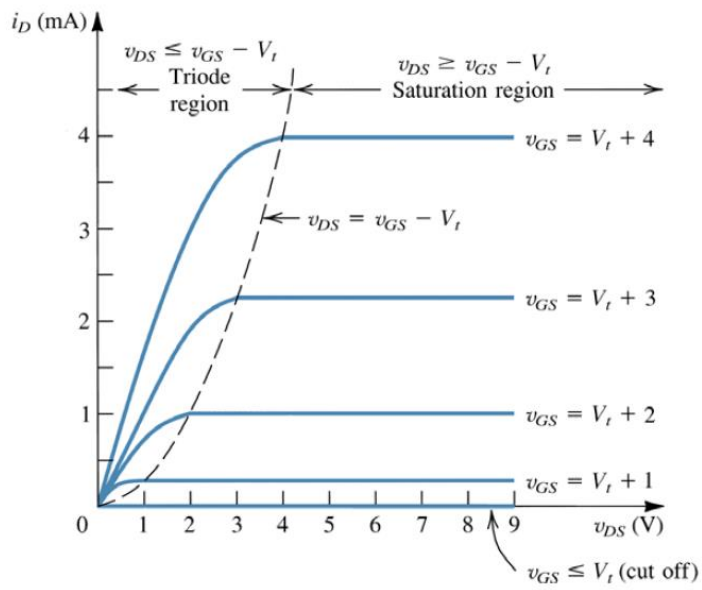


1. (需說明原因與產生的影響)


- (a) 參考講義 2-66
- (b) 參考講義 2-62
- (c) 參考講義 2-39
- (d) 參考講義 2-33
- (e) 參考講義 2-63-65

2.

(a)(b)(d)



(c)

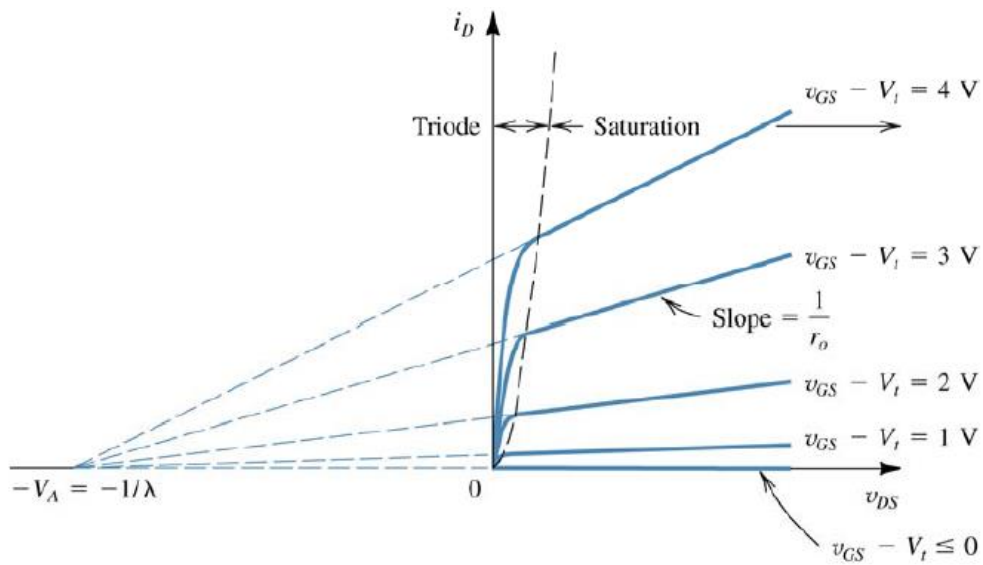

3.

(a)


$0V \leq V_x \leq 1.3V$  triode

$$C_{EF} = C_{EN} = \frac{1}{2}WLC_{ox} + WC_{ov} = 6fF$$


$1.3V \leq V_x \leq 3V$  saturation

$$C_{EF} = WC_{ov} = 1fF$$
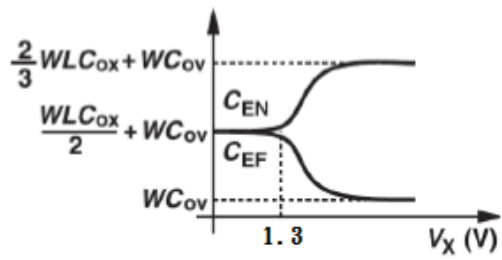
$$C_{EN} = \frac{2}{3}WLC_{ox} + WC_{ov} = 7.67fF$$




(b)

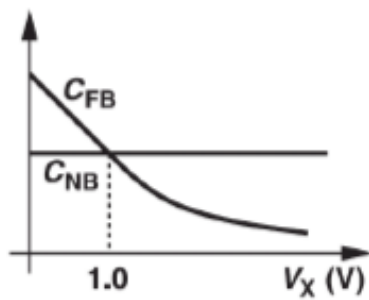

4. 參考講義 1-70~79

(a)

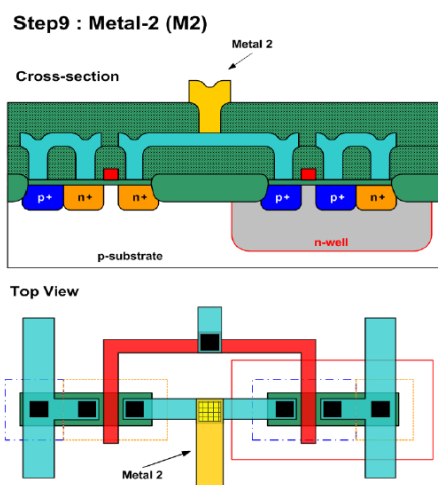


(b)

p-sub => 1. NW 2. OD 3. PO 4. PP 5. NP 6. CO 7. M1 8. Via1 9. M2

5.

(a)

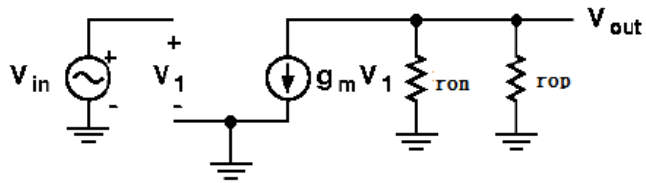


(b)

$$A_v = -g_m \langle r_{on} // r_{op} \rangle$$

6.

(a)  $g_{mb} = 0$

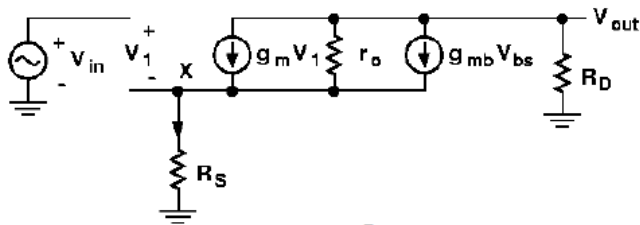

(b)

$$\begin{aligned} R_{out} &= [1 + g_m r_o] R_S + r_o \\ &= 1.2 \text{M}\Omega \end{aligned}$$

7.

Triode region:


$$I_D = \mu C_{ox} \frac{W}{L} [(V_{GS} - V_{TH}) V_{DS} - \frac{1}{2} V_{DS}^2]$$

Saturation region:

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

8.

(a)

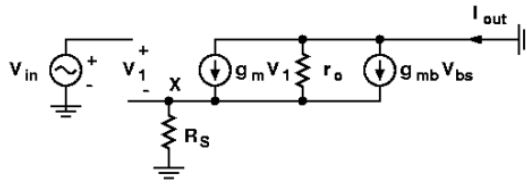

(b)

$$A_v = \frac{V_{out}}{V_{in}} = \frac{g_m R_S}{1 + (g_m + g_{mb}) R_S}$$

$$= 0.83 \text{ V/V}$$

9. (方向錯誤,沒寫單位:0 分)

(a)  $A_{v,DM} = -g_m (R_D \parallel r_o) = -133 \text{ V/V}$

(b)

$$A_{v,CM} = \frac{V_{out}}{V_{in,CM}} = -\frac{R_D / 2}{1 / (2g_m) + R_{SS}}$$

$$= -0.24 \text{ V/V}$$

(c)

$$\Delta V_{in} = \sqrt{2I_{SS} / (\mu_n C_{ox} W / L)}$$

$$= 283 \text{ mV}$$

(d)

$$V_{GS1} + (V_{GS3} - V_{TH3}) \leq V_{in,CM} \leq \min \left[ V_{DD} - R_D \frac{I_{SS}}{2} + V_{TH}, V_{DD} \right]$$

$$1 \text{ V} < V_{in,CM} < 1.4 \text{ V}$$

10.

(a)

$$\frac{I_{D2}}{I_{D1}} = \frac{(W/L)_2}{(W/L)_1} \frac{1 + \lambda V_{DS2}}{1 + \lambda V_{DS1}}$$

$$V_{DS2} = 0.5 \text{ V}, V_{DS1} = 0.7 \text{ V}, I_{out} = 39.842 \text{ uA}$$

(b)  $V_{out} > V_{ov} = 0.2 \text{ V}$

11.

(a)  $V_b = V_{th} + 2V_{ov} = 0.9 \text{ V}$

$$V_{out} = 2V_{ov} = 0.4 \text{ V}$$

(b)  $(W/L)_5 = 0.25 * (W/L)_1 = 0.5 \text{ um} / 4 \text{ um}$

(只寫 ratio: 0 分)

12. (gain 算成-200V/V or 沒寫單位:0 分)

(a)

$$A_v = -g_m(R_D \parallel r_o) = -100V/V$$

$$C_{in} = C_{GS} + C_{GD}(1 - A_v) = 510 fF (\approx 505 fF)$$

$$C_{out} = C_{DB} + C_{GD}(1 - \frac{1}{A_v}) = 7.05 fF (\approx 7 fF)$$

(b)

$$\omega_{in} = \frac{1}{R_{in} \cdot C_{in}} = \frac{1}{R_s \cdot C_{in}} = 1.96 \times 10^8 \text{ rad/sec}$$

$$\omega_{out} = \frac{1}{R_{out} \cdot C_{out}} = \frac{1}{(R_D \parallel r_o) \cdot C_{out}} = 2.84 \times 10^9 \text{ rad/sec}$$

13.

(a) (方向錯誤:0 分)

$$V_{in,min} = V_{ov5} + V_{GS1} = 2V_{ov} + V_{th} = 1V$$

(b)

$$\text{max. swing} = V_{DD} - V_{ov4} - V_{ov2} - V_{ov5} = 1.2V$$

(c)

$$V_{out} / (V_{in1} - V_{in2}) = g_m(r_{o4} \parallel r_{o2}) = 50V/V$$

(d)

$$CMRR = \frac{A_{v,DM}}{A_{v,CM}} = \frac{g_m(r_o \parallel r_o)}{\frac{1}{2g_m r_o}} = (g_m r_o)^2 = 10000$$

14.

(a) F, before  $\rightarrow$  after

(b) T

(c) T

(d) T,  $C_j$  is proportional to A, where A is width\*depth

(e) T

(f) F, low power  $\rightarrow$  double power

(g) F,  $I \uparrow, V_{ov} \uparrow, \text{swing} \downarrow$

(h) F, chemical vapor deposition  $\rightarrow$  photolithography

(i) F,  $g_m = \sqrt{2\beta I}$ , proportional to **square root** of width

(j) F, larger  $\rightarrow$  smaller, because mobility  $\mu_p < \mu_n$

(k) T

(l) T

(m) F, after 0hz → after pole frequency

(n) F, voltage swing is decreased

(o) F, length modulation effect → impact ionization