

- Answer definitions of the following effects and explain the physical mechanisms. (10%)
  - Junction breakdown. (2%)
  - Channel length modulation effect. (2%)
  - Mobility degradation. (2%)
  - Hot carrier effect. (2%)
  - Velocity saturation. (2%)

2. A source follower as shown in Fig. 2 with  $g_m = 1\text{mA/V}$ ,  $g_{mb} = 0.2g_m$ ,  $R_S = 500\text{k}\Omega$ , and  $r_o = 100\text{k}\Omega$ . (5%)

- Sketch the small signal equivalent circuit. (2.5%)
- Find the voltage gain  $V_{out}/V_{in}$ . (2.5%)

 


Fig. 2

3. Sweep  $V_{GS}$  of nMOS with a constant  $V_D$ , the  $C_{GS}$  and  $C_{GD}$  curves are shown in Fig. 3. (10%)

- Find values of C1, C2, and C3 in W, L,  $C_{ox}$ , and  $C_{ov}$ . (6%)
- Define the operation regions I, II, and III. (4%)

 


Fig. 3

4. Write down the drain current equations of MOSFET in triode and saturation region with channel length modulation effect. (5%)

5. The  $r_o$  vs.  $V_{DS}$  characteristic of MOSFET is shown in Fig. 5. Please identify and explain the effects at the three regions. (5%)

 


Fig. 5

6. Derive the equation of voltage gain  $V_{out}/V_{in}$  of amplifier as shown in Fig. 6 in terms of  $g_{m<n>}$ ,  $g_{mb<n>}$ ,  $g_{m<p>}$ ,  $g_{mb<p>}$ ,  $r_{o<n>}$  and  $r_{o<p>}$ . (5%)

 


Fig. 6

7. Assume  $g_{mb} = 0$ ,  $r_o = \infty$ ,  $g_m = 1\text{mA/V}$ ,  $R_S = 20\text{k}\Omega$ , and  $R_D = 100\text{k}\Omega$  in the circuit of Fig. 7. (5%)

- Find the short circuit transconductance  $G_m$  of this amplifier. (2.5%)
- Find the voltage gain  $V_{out}/V_{in}$ . (2.5%)

 


Fig. 7

8. Fig. 8 is a layout of CMOS inverter. (5%)  
 (a) Draw the cross section from A-A'. (2.5%)  
 (b) Identify and index all the name of layers. (2.5%)

 


Fig. 8

9. A differential pair is shown in Fig. 9. Assume all the MOSFETs are biased with  $|V_{ov}| = 200\text{mV}$  and  $|V_{th}| = 0.6\text{V}$ . The  $I_D(M_3) = 50\mu\text{A}$ ,  $g_{m1} = g_{m2} = 1\text{mA/V}$ ,  $R_{D1} = R_{D2} = 100\text{k}\Omega$ ,  $r_o(M_1) = r_o(M_2) = r_o(M_3) = 100\text{k}\Omega$ , and  $V_{DD} = 1.8\text{V}$ . (10%)  
 (a) Find the differential gain  $A_{v,DM}$ . (2.5%)  
 (b) Find the common-mode gain  $A_{v,CM}$ . (2.5%)  
 (c) Find the maximum differential input signal range. (2.5%)  
 (d) Find the input common mode range. (2.5%)

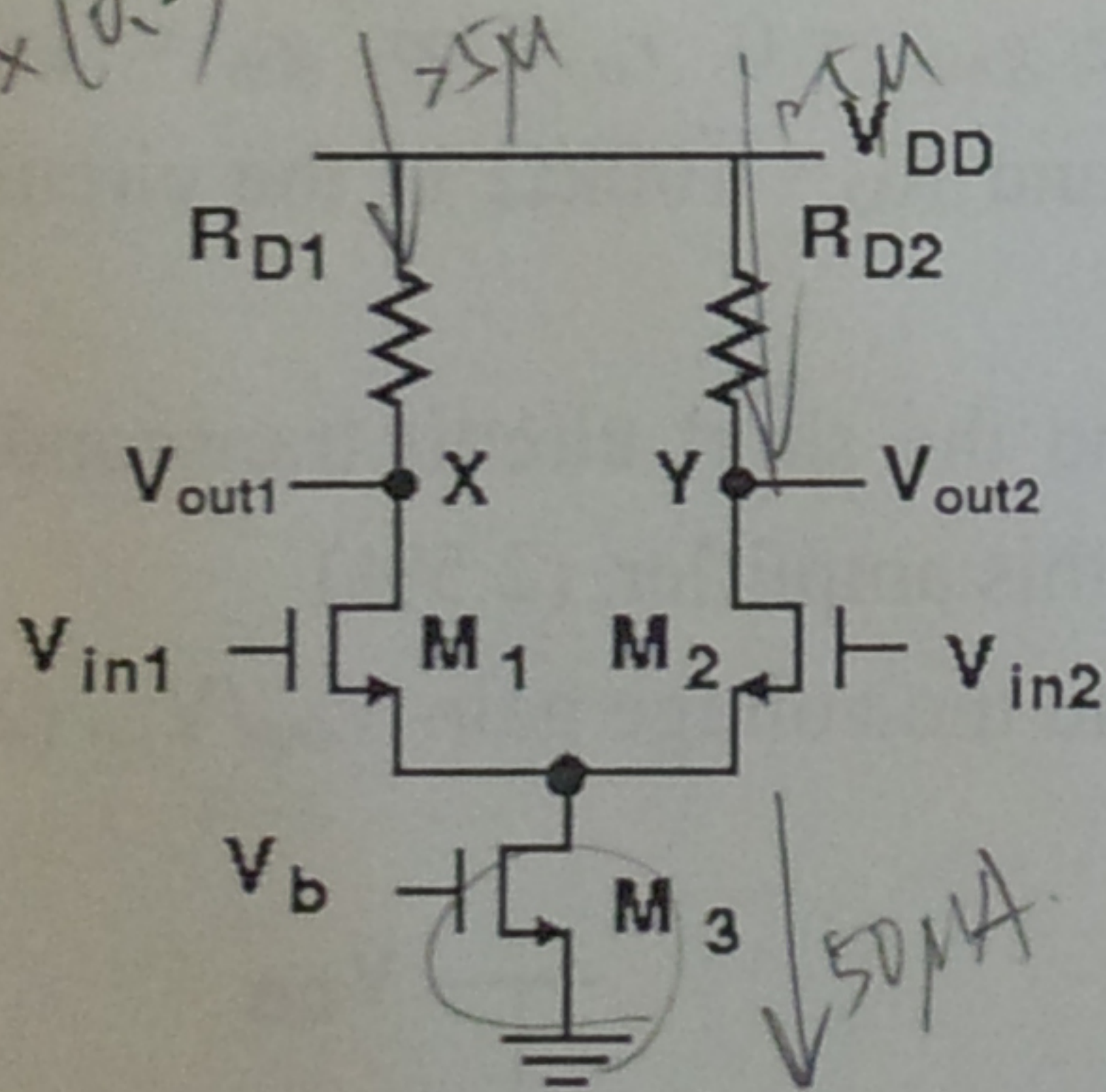


Fig. 9

10. Use the amplifier and bias condition in Fig. 9, assume  $R_{D1} = 100\text{k}\Omega$  and  $R_{D2} = 110\text{k}\Omega$ . (5%)  
 (a) Find the common mode to differential mode gain  $A_{v,CM-DM}$ . (2.5%)  
 (b) Assume  $A_{v,DM}$  = the value in 9(a), find the CMRR. (2.5%)

11. Assume  $g_m = 1\text{mA/V}$ ,  $g_{mb} = 0.2 g_m$ ,  $R_S = 10\text{k}\Omega$ , and  $R_D = 100\text{k}\Omega$  in the circuit of Fig. 11. (5%)  
 (a) With  $r_o = \infty$ , find input impedance. (2.5%)  
 (b) With  $r_o = 100\text{k}\Omega$ , find the output impedance. (2.5%)

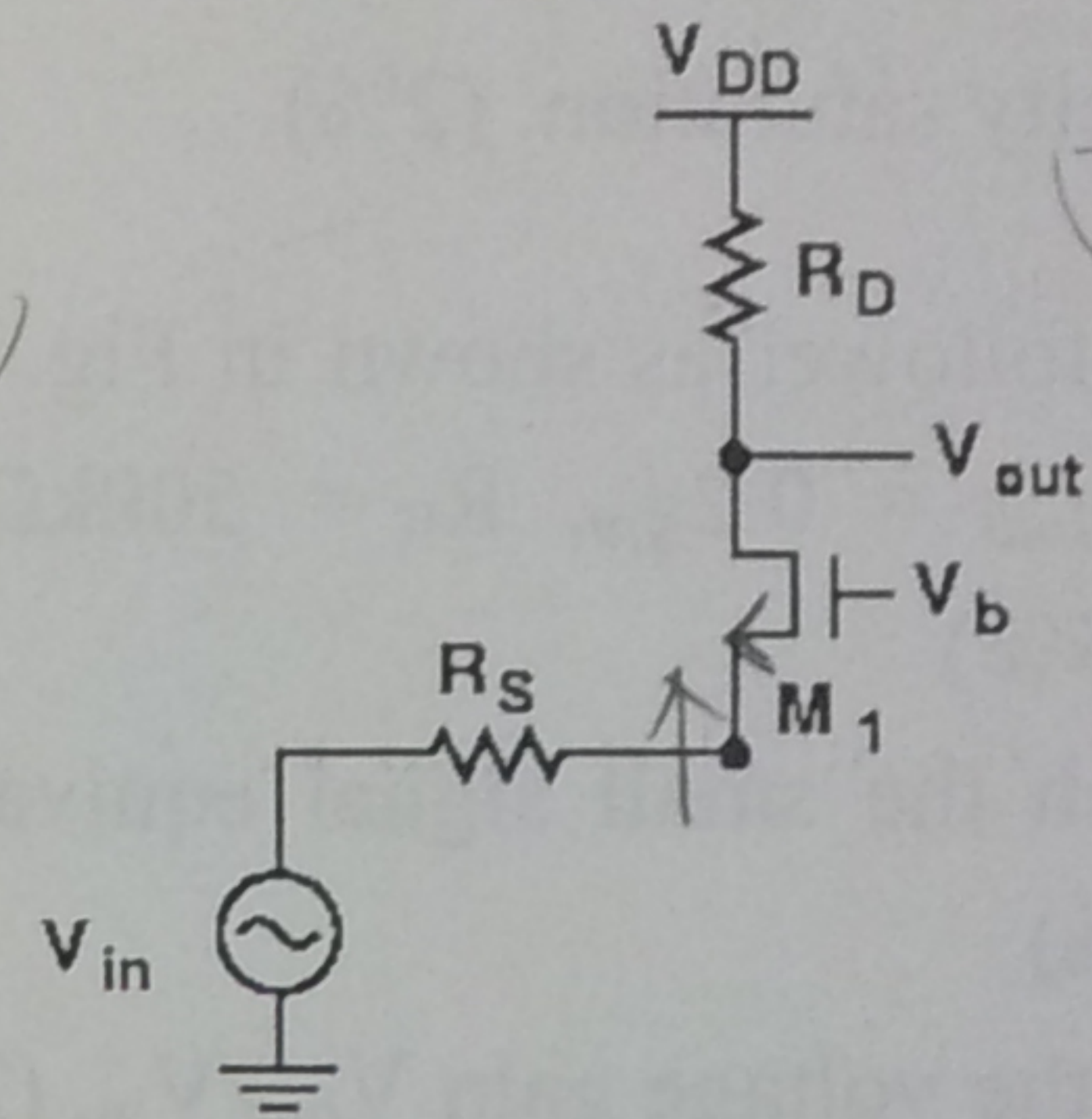


Fig. 11

12. A cascode current mirror as shown in Fig. 12, assume  $M_1$  and  $M_2$  are biased with  $|V_{ov}| = 200\text{mV}$ ,  $|V_{th}| = 0.6\text{V}$ ,  $I_{REF} = 10\mu\text{A}$ ,  $g_{m1} = g_{m2} = 1\text{mA/V}$ ,  $r_{o1} = r_{o2} = r_{o3} = r_{o4} = 100\text{k}\Omega$ ,  $(W/L)_3/(W/L)_1 = (W/L)_4/(W/L)_2 = 4$ , and  $V_{DD} = 1.8\text{V}$ . (10%)

- (a) Find the  $g_{m3}$  and  $g_{m4}$ . (2.5%)  
 (b) Find the minimum  $V_b$  and related output voltage  $V_{out}$  for proper current mirror operation. (2.5%)  
 (c) Find the output resistance  $R_{out}$ . (2.5%)  
 (d) Sketch a circuit to generate the required optimal bias  $V_b$  in (b). (2.5%)

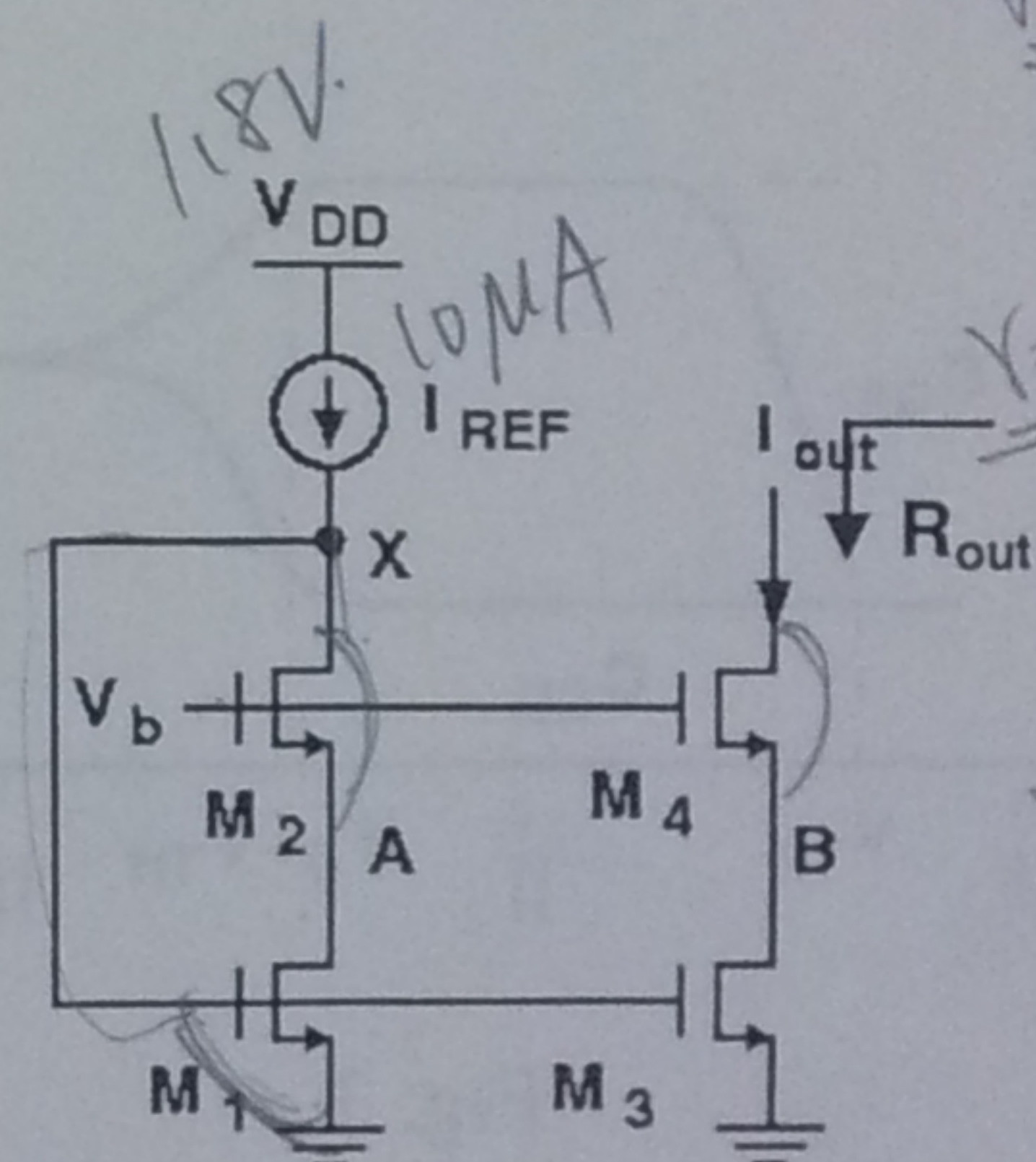


Fig. 12

2014 Analog IC: Midterm Examination (100%)

13. A differential to single-ended amplifier is shown in Fig. 13. Assume all the MOSFETs are biased with  $|V_{ov}| = 200\text{mV}$ ,  $|V_{th}| = 0.6\text{V}$ ,  $r_o = 100\text{k}\Omega$ , and  $u_n C_{ox} = 0.001\text{F/V}\cdot\text{S}$ . The  $I_D(M_5) = 80\mu\text{A}$  and  $V_{DD} = 1.8\text{V}$ . (5%)

(a) Find the minimum input DC bias voltage. (2.5%)

(b) Find the voltage gain  $V_{out}/(V_{in1}-V_{in2})$ . (2.5%)

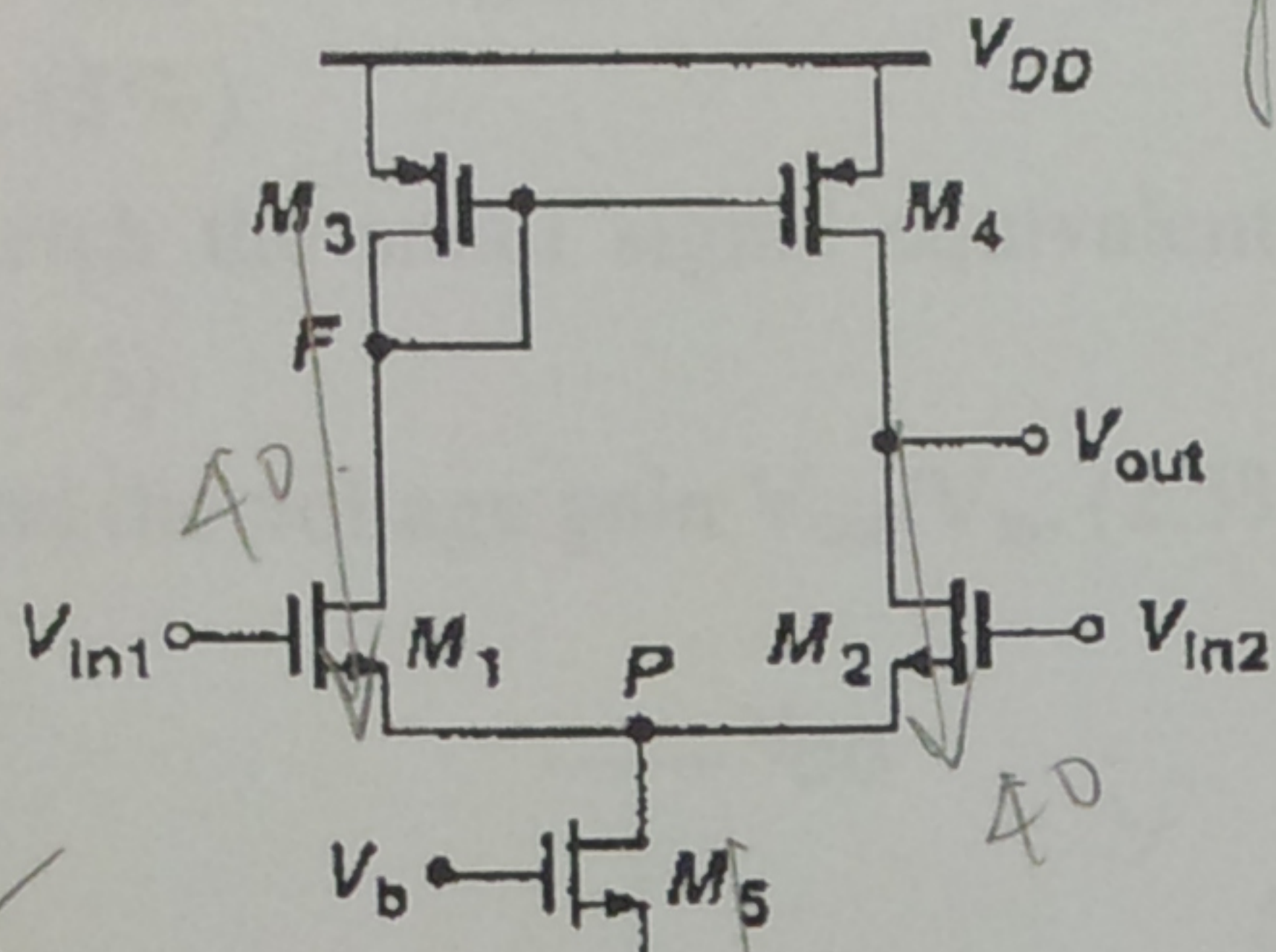


Fig. 13

- (i) The threshold voltage of nMOS is increased by n+ channel implantation. (1%)
- (j) The depletion width of p/n ratio ( $W_p/W_n$ ) in diode is correlated to doping concentration ( $N_A/N_D$ ) as  $W_p/W_n = N_A/N_D$ . (1%)
- (k) The transconductance  $g_m$  of MOSFET is proportional to  $V_{ov}$  at known constant biasing current. (1%)
- (l) The channel charge of MOSFET is proportional to  $W\cdot L$  and overdrive voltage  $V_{ov}$  as well. (1%)
- (m) The output resistance of MOSFET at saturation region is inversely proportional to bias current. (1%)
- (n) The addition of source resistor on common-source amplifier improves the gain and linearity. (1%)
- (o) The output impedance and available swing of current source can be increased by cascode structure. (1%)

14. Answer the following questions with TRUE or FALSE: (15%)

(a) The angle of ion implant is "zero" degree for better depth control. (1%)

(b) Chemical vapor deposition is a common process for metal formation in IC manufacturing. (1%)

(c) Annealing is for crystal lattice reforming after oxidation. (1%)

(d) Shallow trench isolation is used in advanced technology for its higher precision. (1%)

(e) Junction capacitance is proportional to reverse biasing voltage. (1%)

(f) The main free carrier in channel of MOSFET is from body. (1%)

(g) Silicide is used to reduce the sheet resistance of diffusion. (1%)

(h) The voltage gain of source follower is smaller than unity and decreased by body effect. (1%)

$$W_n N_D = W_p N_A$$

$$\frac{W_n}{W_p} = \frac{N_A}{N_D}$$

$$\frac{W_p}{W_n} = \frac{N_D}{N_A}$$

$$R_s \parallel \frac{1}{g_m} = \frac{R_s}{1 + g_m R_s}$$

$$\frac{R_s \parallel \frac{1}{g_m}}{1 + g_m (R_s \parallel \frac{1}{g_m})} = \frac{R_s}{1 + g_m R_s}$$