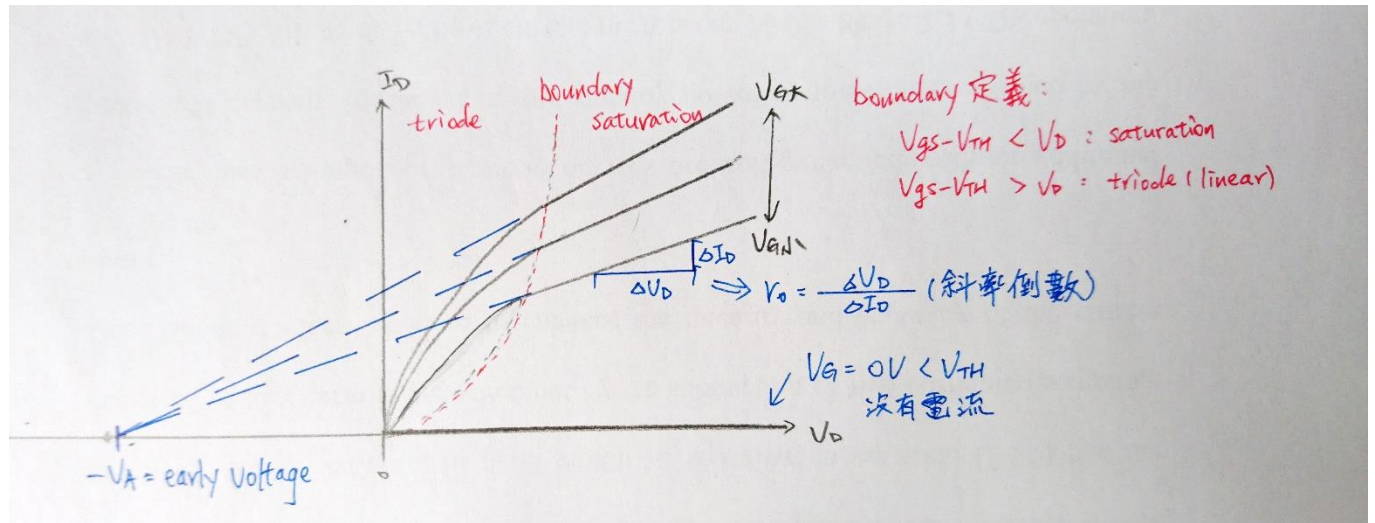



1. Definitions. Please refer the textbook: Design of Analog CMOS Integrated Circuits, Razavi.

- (a) **Channel length modulation:** see textbook p.25-27.
- (b) **Body effect:** see textbook p.23-25
- (c) **Punch through:** In short channel devices, an excessively large drain source voltage widens the depletion region around the drain so much that it touches around the source, creating a very large drain current.
- (d) **Velocity saturation:** see textbook p.587-589
- (e) **Mobility degradation:** see textbook p.585-587

2. Plot



3.

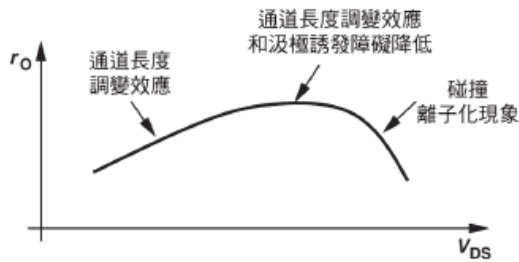

See textbook p.591

I: Channel-length modulation  
ionization

II: Channel-length modulation + DIBL

III: Impact

4.

(a)  $I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$

$$(b) I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$(c) g_m = \mu C_{ox} \frac{W}{L} V_{OV}$$


$$(d) g_m = \sqrt{2 \mu C_{ox} \frac{W}{L} I_D}$$

$$(e) g_m = \frac{2I_D}{V_{OV}}$$

5. text book introduction p69-p78

6. 不考慮 M1, M2 的 body effect  $A_v = -g_{m1}(r_{o1} // r_{o2})$

7.

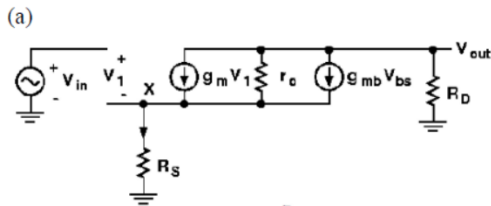

(b)

$$G_m = \frac{I_{out}}{V_{in}} = \frac{g_m}{1 + (g_m + g_{mb})R_S + R_S / r_o}$$

$$\approx 8.32e-6(A/V)$$

(c)

$$\begin{aligned} \frac{V_{out}}{V_{in}} &= -\frac{g_m r_o R_D}{R_D + R_S + r_o + (g_m + g_{mb})R_S r_o} \\ &= -\frac{g_m r_o}{R_S + r_o + (g_m + g_{mb})R_S r_o} \cdot \frac{R_D [R_S + r_o + (g_m + g_{mb})R_S r_o]}{R_D + R_S + r_o + (g_m + g_{mb})R_S r_o} \\ &= -G_{meff} R_O = -G_{meff} \{R_D \parallel [R_S + r_o + (g_m + g_{mb})R_S r_o]\} \end{aligned}$$

$$= 0.832(V/V)$$

8.

(a)

$$C1 = \frac{2}{3} WLCox + WCov$$

$$C2 = WCov$$

$$C3 = \frac{1}{2} WLCox + WCov$$


(b)

I: Cut off

II: Saturation

III: Triode

9.

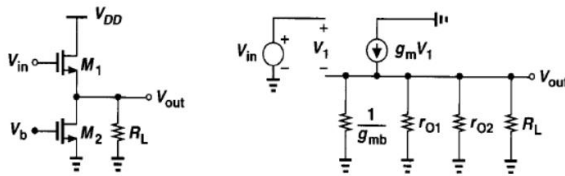

$$R_{out} = g_{m1} // g_{mb1} // r_{o1} // r_{o2} = 166.113 \Omega$$

(b)

$$A_v = \frac{\frac{1}{g_{mb}} // r_{o1} // r_{o2} // R_L}{\frac{1}{g_{mb}} // r_{o1} // r_{o2} // R_L + \frac{1}{g_m}}$$

$$= 0.83$$

10.

$$(a) \frac{I_{out}}{I_{ref}} = 4 \frac{1 + \lambda V_{ds2}}{1 + \lambda V_{ds1}} \Rightarrow I_{out} = 41.51 \mu A$$

$$(b) r_o = 1 / \lambda I_d = 240.9 k\Omega$$

11.

$$(a) V_b = 0.2 + 0.5 + 0.2 = 0.9 V \quad V_{outmin} = 0.2 + 0.2 = 0.4 V$$

$$(b) (0.7 - 0.5)^2 \times 1/2 = (0.9 - 0.5)^2 \times X \Rightarrow X = 0.25 \mu m / 2 \mu m$$

12.

$$(a) V_{swing} = V_{DD} - 4V_{ov} = 2.5 V$$

(b)  $A_v = -g_m(g_{m_{r_1}} r_{o_1} // g_{m_{r_2}} r_{o_2}) = -125000$

13.

(a)  $A_{vdm} = -g_m(R_d // r_o) = 45.45$

(b)  $A_{vcm} = \frac{-R_d/2}{\frac{1}{2g_m} + R_{ss}} = -50/1001$

(c)  $V = \sqrt{2} \times 200mV = 282.84mV$

(d)  $0.9V \sim 1.8V$

14.

(a)  $g_m$

(b)  $r_o // r_{o_1} = 50k\Omega$

(c)  $A_v = g_m(r_o // r_{o_1}) = 250$

(d)  $A_v = -1/(1 + 2g_m R_{ss}) = -1/1001$  (or textbook 5.34)

15.

FTTTF FFFTF