

A close-up, high-angle photograph of a green printed circuit board (PCB) with intricate white and silver traces and components. The lighting is dramatic, highlighting the texture and complexity of the board.


CHAPTER 8

Feedback

Outline

- 1. General Consideration**
2. Feedback Topologies
3. Effect of Loading
4. Effect of Feedback on Noise

General Consideration

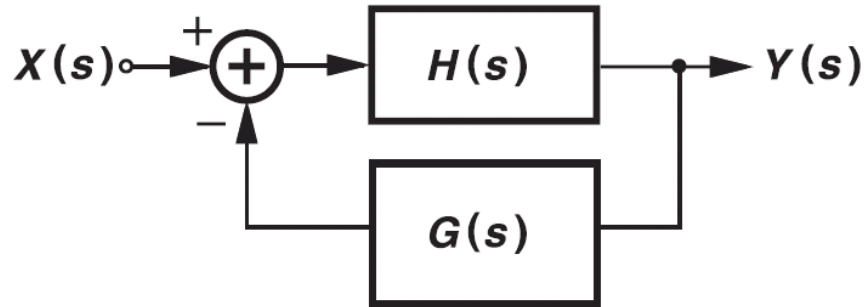


- $H(s)$: Feedforward network (Represents an amplifier)
- $G(s)$: Feedback network (β , feedback factor, freq. independent)

$$Y(s) = H(s)[X(s) - G(s)Y(s)], \quad \frac{Y(s)}{X(s)} = \frac{H(s)}{1 + G(s)H(s)}$$

- $X(s) - G(s)Y(s)$: The input to $H(s)$, also called feedback error
- $H(s)$: open loop transfer function
- $Y(s)/X(s)$: closed loop transfer function

General Consideration

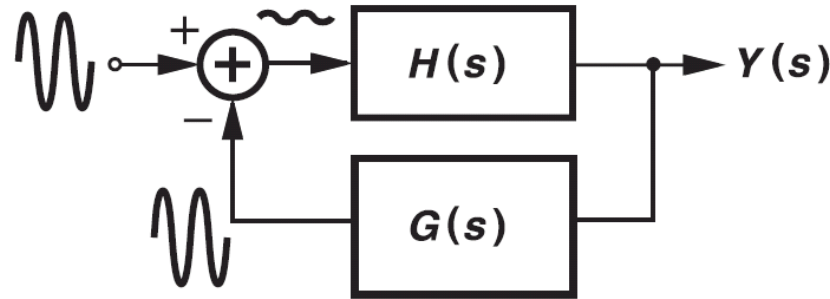

- In a well designed negative feedback system, the error term is minimized, making the output $G(s)$ an accurate copy of the input.
- Input of $H(s)$ as “virtual ground”.
- Four elements in the feedback system
 - The feedforward amplifier.
 - A means of sensing the output.
 - The feedback network.
 - A means of generating the feedback error.

Properties of Feedback Circuits

- Gain Degeneration
- Terminal Impedance Modification
- Bandwidth Modification
- Nonlinearity Reduction

Properties of Feedback Circuits

Negative Feedback properties :

1. Desensitize the gain :

- *make gain less sensitive to variations.*

2. Reduce nonlinear distortion :

- *make gain independent of signal level.*

3. Reduce effect of noise :

- *minimize unwanted signal contribution to output.*


4. Control the input and output impedance :

- *use feedback to control impedance.*

5. Extend bandwidth of the amplifier.

*The basic idea of negative feedback is to **trade off gain** for other desirable properties, like increased input impedance, extended bandwidth... etc.*

Terminologies

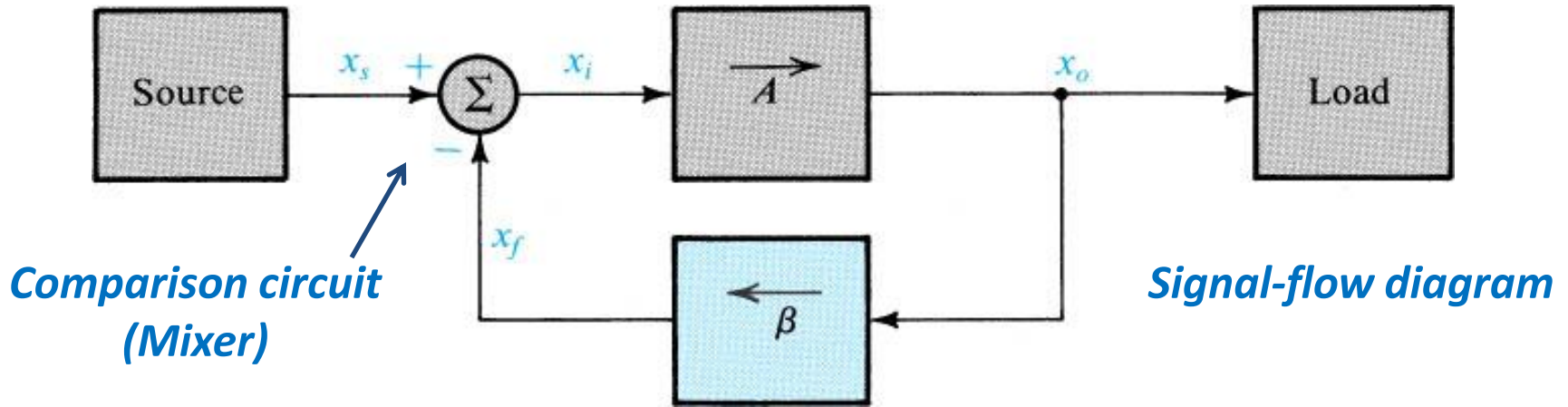

1. Open-loop Gain : A
2. Feedback Factor : β
3. Loop Gain : $A\beta$
4. Amount of Feedback : $1 + A\beta$
5. Closed-Loop Gain : $A_f = A / (1 + A\beta)$

$$x_o = Ax_i \quad x_f = \beta x_o \quad x_i = x_s - x_f$$


$$A_f \equiv \frac{x_o}{x_s} = \frac{A}{1 + A\beta} \quad A\beta \gg 1, A_f \cong \frac{1}{\beta}$$

$$x_f = \frac{A\beta}{1 + A\beta} x_s \cong x_s \quad x_i = \frac{1}{1 + A\beta} x_s \cong 0$$

1. A_f is almost determined by β and **independent** of A , that is, the process variation.
2. β can be implemented by passive component and **accurate, predictable, stable**.
3. x_i : negative feedback **reduces** the input signal of the basic Amp by **(1+Aβ)**


Gain Desensitization

- Gain desensitization

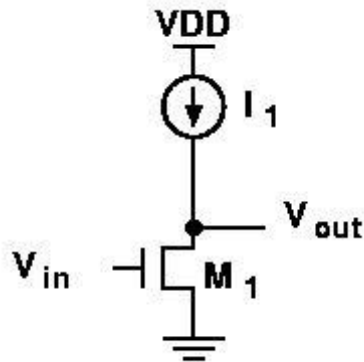

$$A(v) = -g_{m1}r_{o1}$$

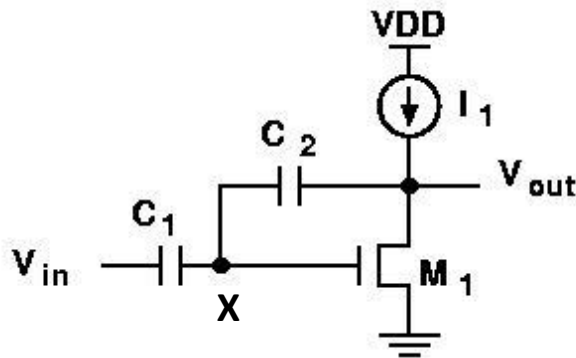- Poor definition of the gain : both g_{m1} and r_{o1} vary with process and temperature.
- For the CS amplifier with feedback (C_1 & C_2)
- The overall voltage gain of the circuit at low freq. such that C_2 does not load the output node




$$A(v) = \frac{V_{out}}{V_X} = -g_{m1}r_{o1} \gg 1$$

$$(V_{out} - V_X)C_2s = (V_X - V_{in})C_1s$$

$$\frac{V_{out}}{V_{in}} = -\frac{1}{\left(1 + \frac{1}{g_{m1}r_{o1}}\right)\frac{C_2}{C_1} + \frac{1}{g_{m1}r_{o1}}} \approx -\frac{C_1}{C_2} = -\frac{1/sC_2}{1/sC_1}$$

- Compared to $g_{m1}r_{o1}$, this gain can be controlled with much higher accuracy because it is given by the *ratio* of two capacitors – **gain desensitization**.

Gain Desensitization


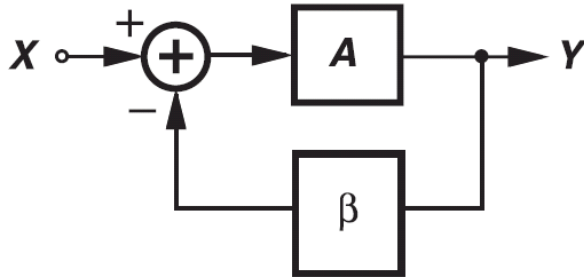


$$\frac{Y}{X} = \frac{A}{1 + A\beta} \approx \frac{1}{\beta} \left(1 - \frac{1}{A\beta} \right) \approx \frac{1}{\beta} \quad \text{if } A\beta \gg 1$$

- In a feedback system, the closed-loop gain is much less sensitive to device parameters than the open-loop gain is.
- The closed loop gain varies by a small percentage even if the open loop gain A varies a lot if the loop gain $(\beta A) \gg 1$.
- The higher the **loop gain** (βA) , the less sensitive Y/X will be to variations in A .
 - We begin with a high-gain amplifier and apply feedback to obtain a low, but less sensitive closed-loop gain.

Loop Gain


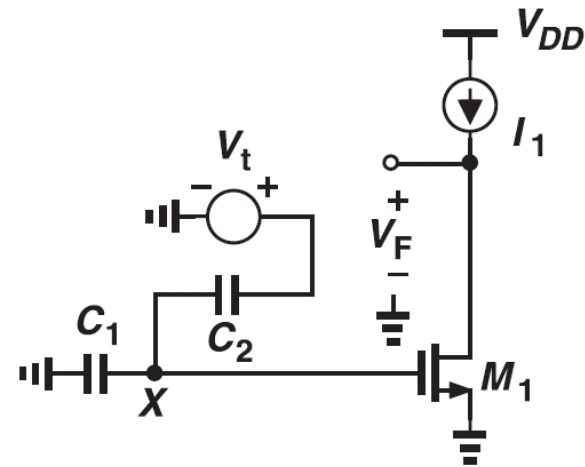
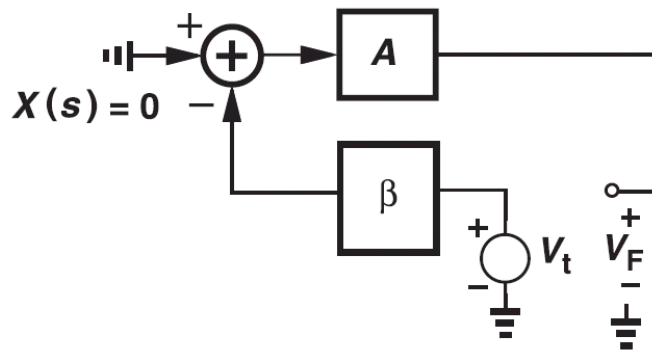
- Calculation of loop gain
 - Set the main input to zero.
 - Break the loop at some point.
 - Inject a test signal in the right direction.
 - Obtain the value that returns to the break point.



$$V_t \frac{C_2}{C_1 + C_2} (-g_{m1} r_{O1}) = V_F, \quad \frac{V_F}{V_t} = -\frac{C_2}{C_1 + C_2} g_{m1} r_{O1} = -A\beta$$

Input Impedance Modification

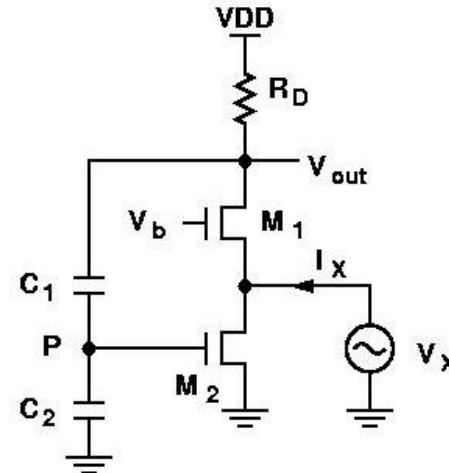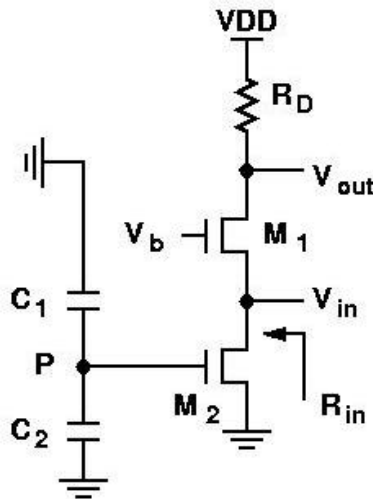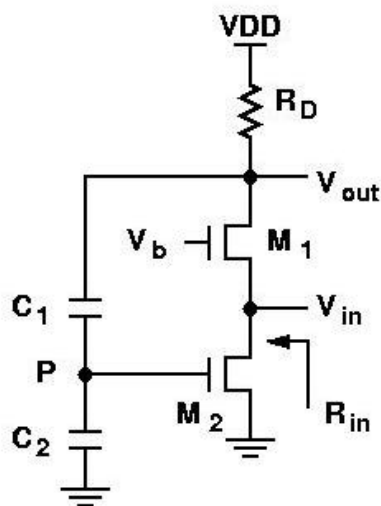- Common gate circuit with feedback (capacitive voltage divider).



- The input resistance without feedback** $R_{in,open} = (g_{m1} + g_{mb1})^{-1}$

- Consider the **input resistance with feedback**, as

$$V_{out} = (g_{m1} + g_{mb1})V_X R_D, \quad V_P = V_{out} \frac{C_1}{C_1 + C_2} = (g_{m1} + g_{mb1})V_X R_D \frac{C_1}{C_1 + C_2}, \quad I_{M2} = g_{m2}(g_{m1} + g_{mb1})V_X R_D \frac{C_1}{C_1 + C_2}$$


$$I_X = (g_{m1} + g_{mb1})V_X + g_{m2}(g_{m1} + g_{mb1}) \frac{C_1}{C_1 + C_2} R_D V_X, \quad R_{in,closed} = V_X / I_X = \frac{1}{g_{m1} + g_{mb1}} \frac{1}{1 + g_{m2} R_D \frac{C_1}{C_1 + C_2}}$$

- The Loop gain**

$$g_{m2} R_D \frac{C_1}{C_1 + C_2} = A\beta$$

$$= R_{in,open} \frac{1}{1 + A\beta}$$

Loop Gain


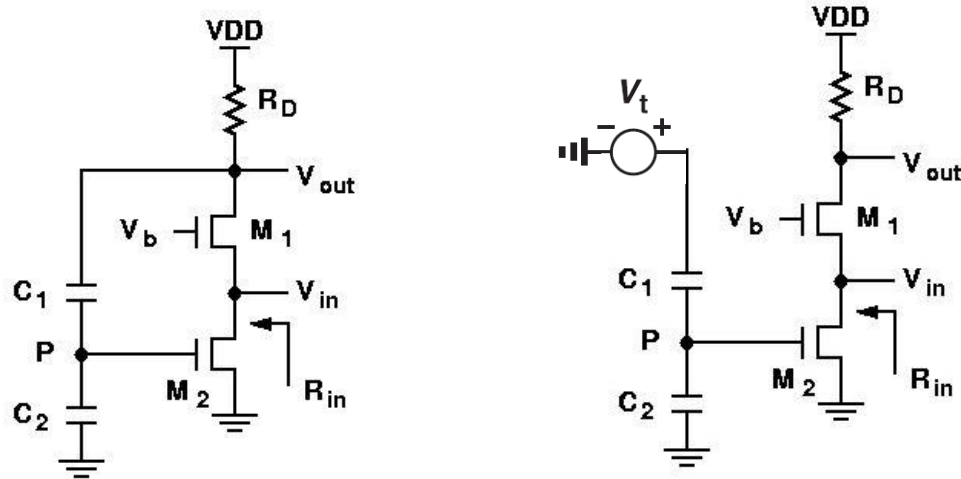


- The feedforward amplifier : M_1 and R_D ($A = R_D$)
- Output sensed by C_1 and C_2 .
- The feedback network : C_1 , C_2 and M_2 ($\beta = g_{m2} \frac{C_1}{C_1 + C_2}$)
- The subtraction occurs in the current domain at the input terminal.
- Loop gain = $A\beta$

$$A\beta = R_D g_{m2} \frac{C_1}{C_1 + C_2}, \quad \left(\frac{V_{out}}{V_t} = -A\beta \right)$$



Output Impedance Modification

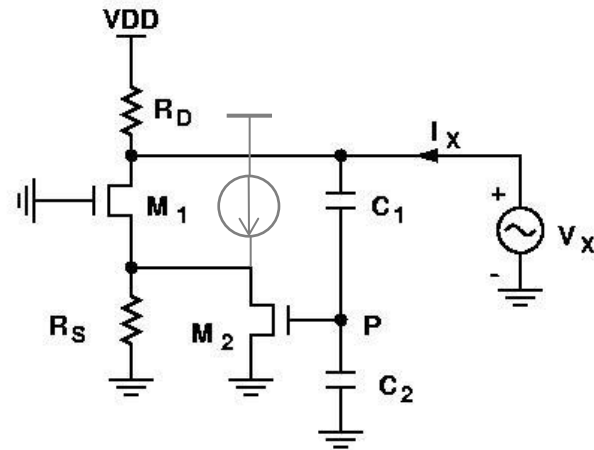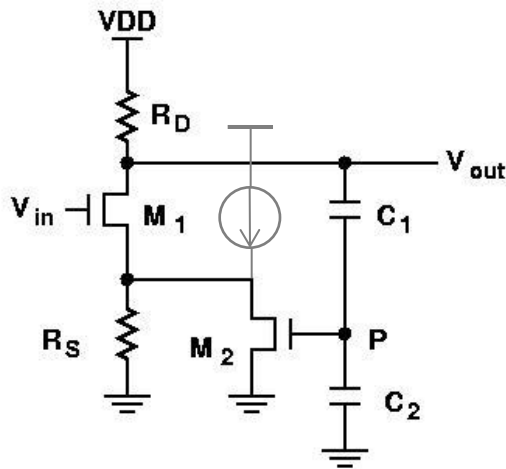- Common source stage with feedback.
- Common source stage: M_1 , R_S and R_D .
- Feedback network sense the V_{out} , returning a current equal to $\left[\frac{C_1}{C_1 + C_2} \right] V_{out} g_{m2}$
- To find the output resistance at relatively low frequencies



$$I_{D1} = V_X \frac{C_1}{C_1 + C_2} g_{m2} \frac{R_S}{R_S + \frac{1}{g_{m1} + g_{mb1}}}, \quad I_X = \frac{V_X}{R_D} + I_{D1}, \quad \frac{V_X}{I_X} = \frac{R_D}{1 + \frac{g_{m2} R_S (g_{m1} + g_{mb1}) R_D}{(g_{m1} + g_{mb1}) R_S + 1} \frac{C_1}{C_1 + C_2}} = \frac{R_D}{1 + A\beta}$$

Bandwidth Modification

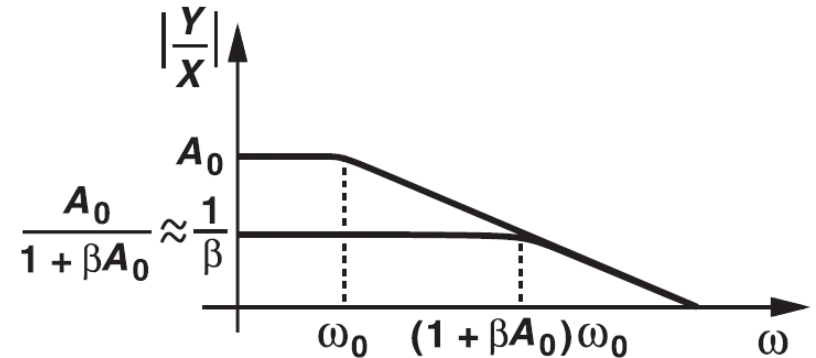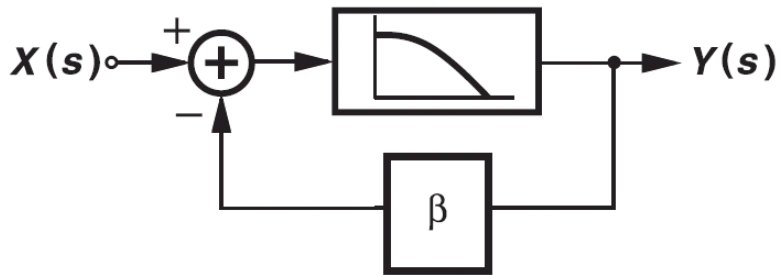

- Suppose the feedforward amplifier has a one-pole transfer function $A(s) = \frac{A_0}{1 + s/\omega_0}$
- The transfer function of the closed loop system is

$$\frac{Y}{X}(s) = \frac{\frac{A_0}{1 + s/\omega_0}}{1 + \beta \frac{A_0}{1 + s/\omega_0}} = \frac{A_0}{1 + \beta A_0 + \frac{s}{\omega_0}} = \frac{\frac{A_0}{1 + \beta A_0}}{1 + \frac{s}{\omega_0(1 + \beta A_0)}}$$



- The -3dB bandwidth has increased by a factor $1 + \beta A_0$, albeit at the cost of a proportional reduction in the gain.
- If A is large, the closed loop gain remains approximately equal to $1/\beta$

Bandwidth Modification Example

- Suppose we need to amplify a 20-MHz square wave by a factor of 100 and maximum bandwidth but we have only a single-pole amplifier with an open loop gain of 100 and -3 dB bandwidth of 10 MHz.









(a) With open-loop amplifier, the risetime and falltime is long: $\frac{1}{2\pi f_{3-dB}} \approx 16ns$

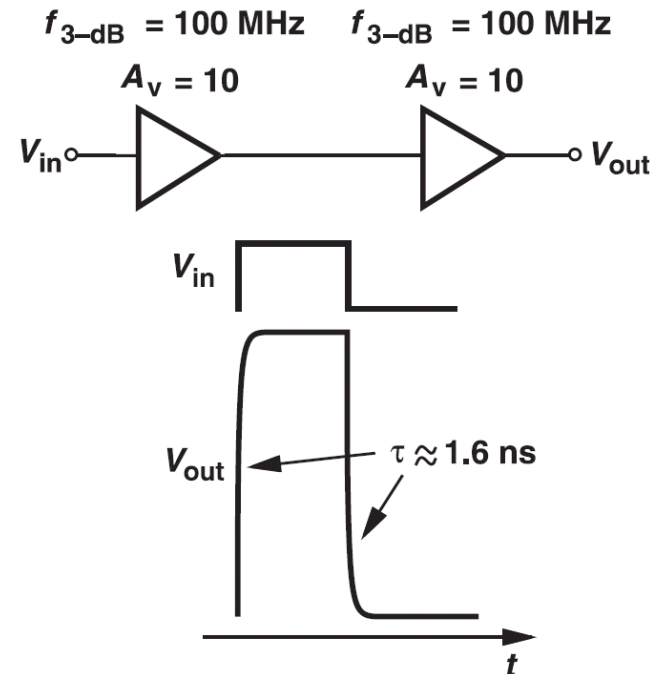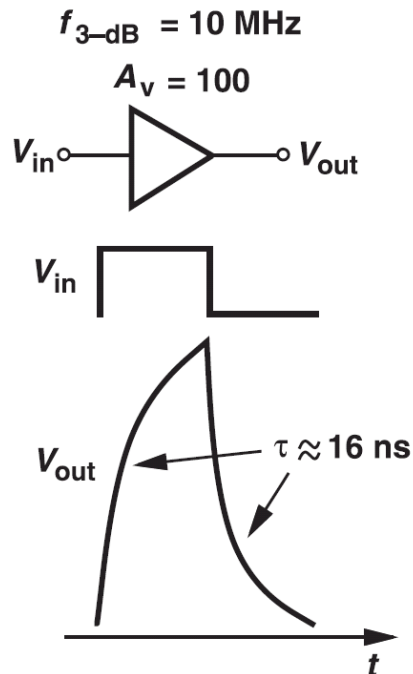(b) Placing two of the amplifiers with feedback in cascade to achieve the same gain. The power dissipation is doubled.











Types of Amplifiers

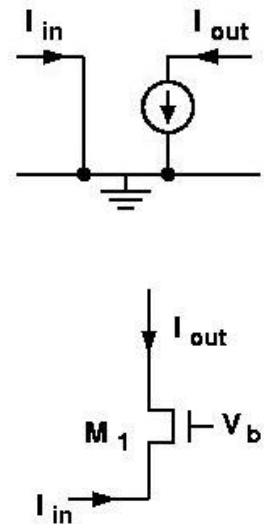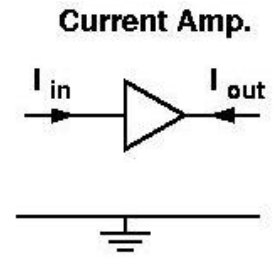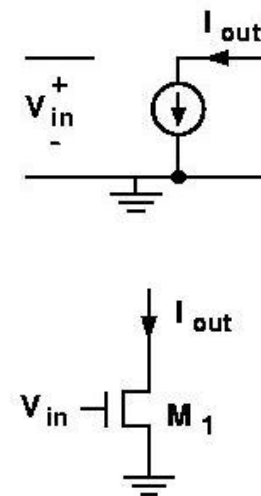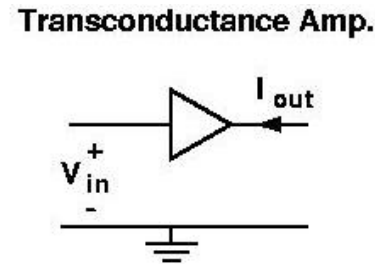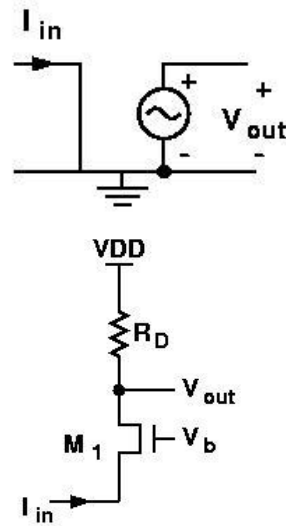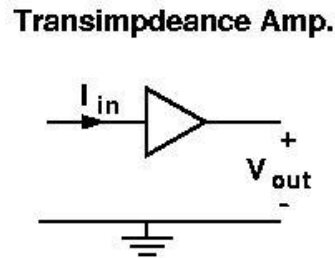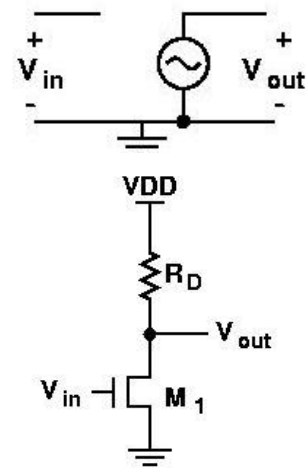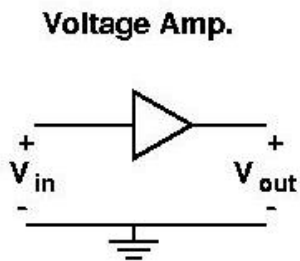- Circuits sensing a voltage must exhibit a high Z_{in} (as a voltmeter), circuits sensing a current must provide a low Z_{in} (as a current meter).
- Circuits generating a voltage must exhibit a low Z_{out} (as a voltage source), circuits generating a current must provide a high Z_{out} (as a current source).



Amplifiers with Improved Performance

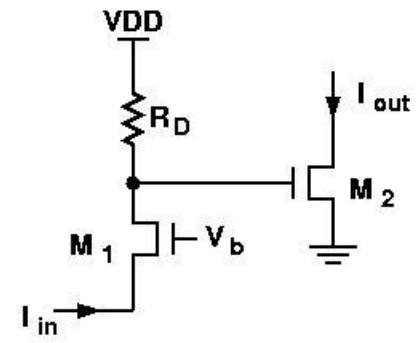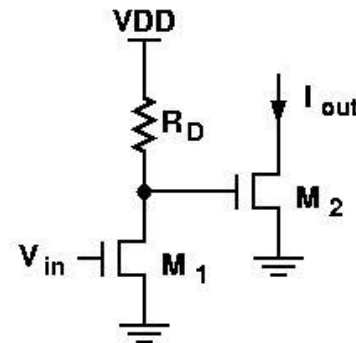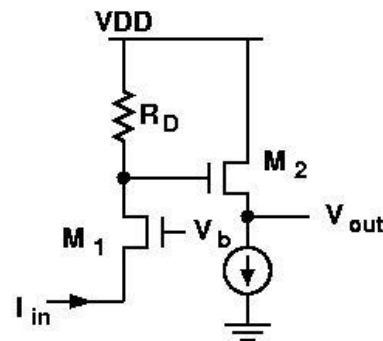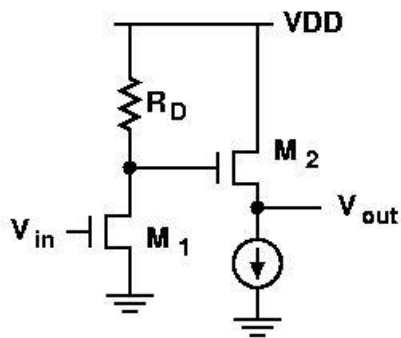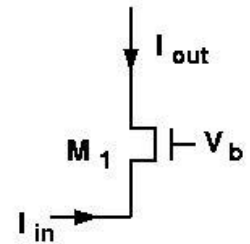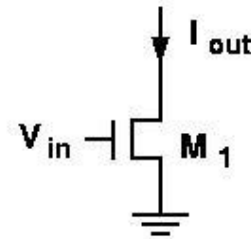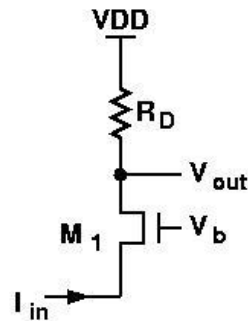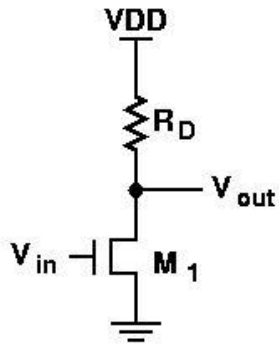
- The basic circuits may not provide adequate performance in many applications.
- Use modified circuits to alter the output impedance or increase the gain.




Sense and Return Mechanisms

- Four type of feedback : voltage-voltage (series-shunt), voltage-current (shunt-shunt), current-current (shunt-series), and current voltage (series-series).
- The **first** entry in each case denotes **the quantity sensed at the output** and the **second** the type of **signal returned to the input**.


➤ Sensing a voltage by a voltmeter

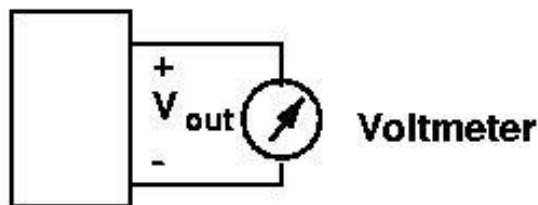

➤ Sensing a current by a current meter

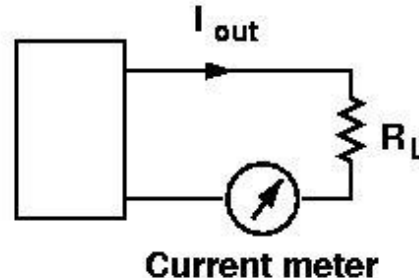


➤ Sensing a current by a small resistor

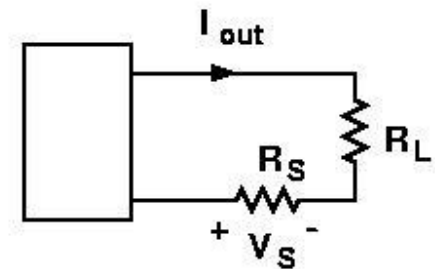


- To sense a current, a current meter is inserted in series with the signal.
- The addition of the feedback signal and the input signal can be performed in the voltage domain or current domain.

Return Mechanisms

➤ Voltage mode addition

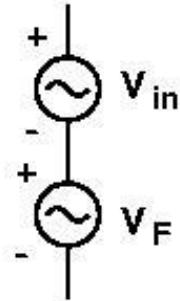


➤ Current mode addition

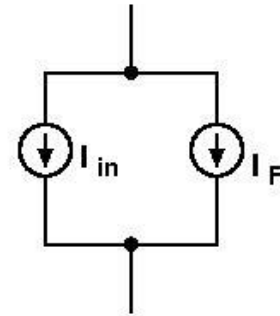


- To add two quantities, we place them in series if they are voltages and in parallel if they are current.
- The feedback network in reality introduces loading effects that must be taken into account.

Practical Examples

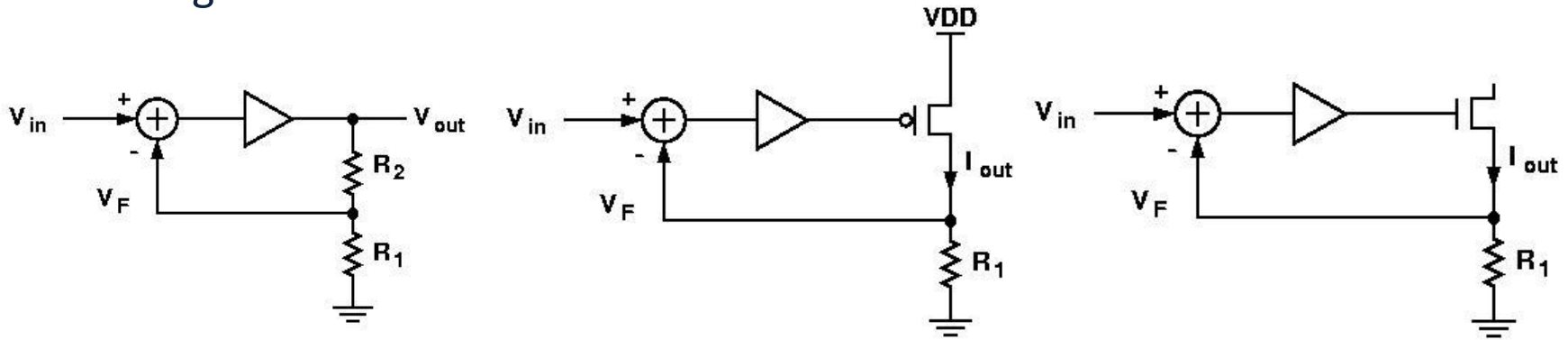- Voltage can be sensed by a resistive / capacitive divider in parallel with the port.
- A current can be sensed by placing a resistor in series with the wire and sensing the voltage across it.





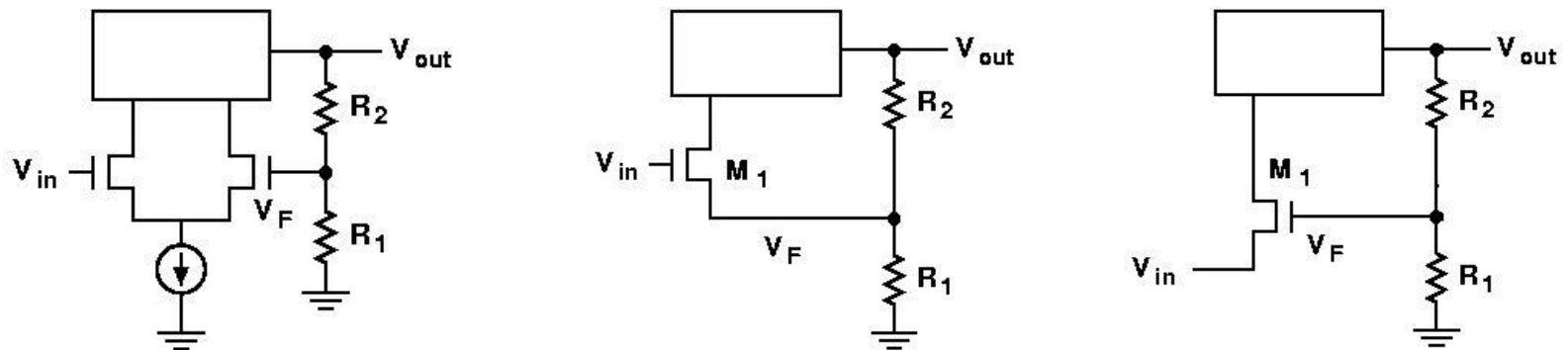- To subtract two voltages, a differential pair or a single transistor can be used.



Sense and Return Mechanism

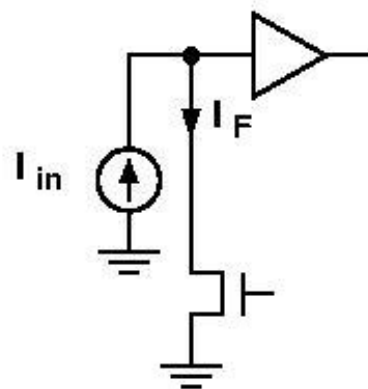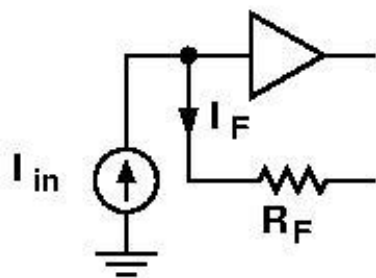- Subtraction of currents can be accomplished as follows.




- In summary
 - For voltage subtraction, the input and feedback signals are applied to two distinct nodes.
 - For current subtraction, they are applied to a single node.
 - It help to identify the type of feedback

Outline

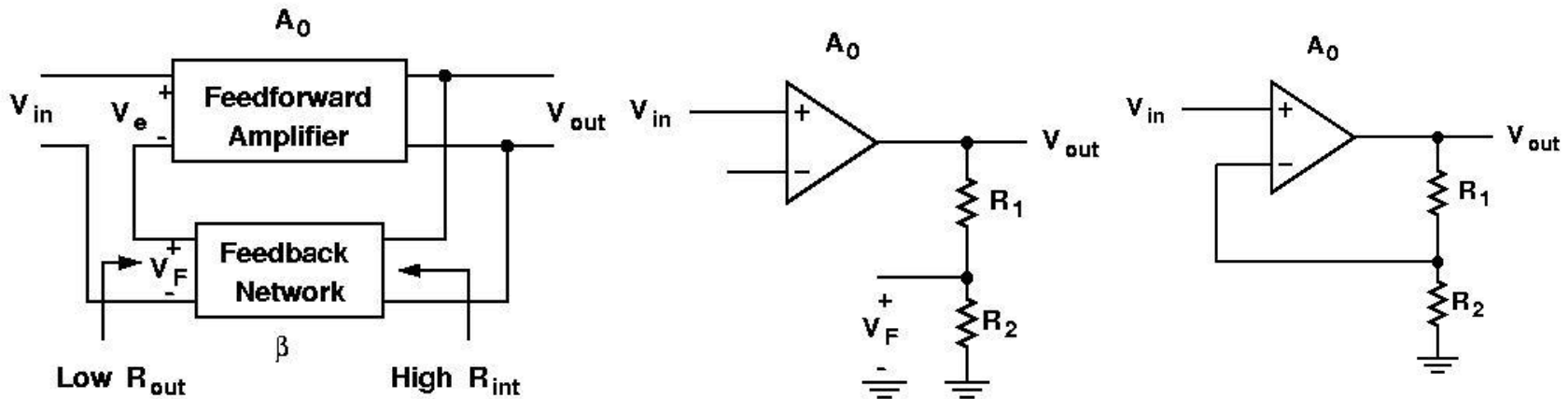1. General Consideration
- 2. Feedback Topologies**
3. Effect of Loading
4. Effect of Feedback on Noise

Voltage-Voltage (V-V) Feedback



- Voltage-voltage feedback (**series - shunt**)
 - samples the output voltage and returns the feedback signal as a voltage.



- The feedback network is connected in parallel with the output and in series with the input port.
- An ideal feedback network in this case exhibits infinite input impedance and zero output impedance.

$$V_F = \beta V_{out} \quad V_e = V_{in} - V_F \quad V_{out} = A_0(V_{in} - \beta V_{out}) \quad \frac{V_{out}}{V_{in}} = \frac{A_0}{1 + \beta A_0} \quad \beta = \frac{R_2}{R_1 + R_2}$$

Effect of V-V Feedback on R_{out}

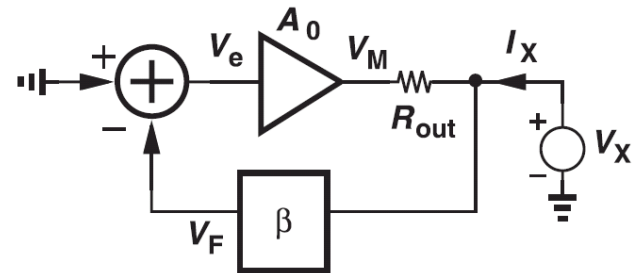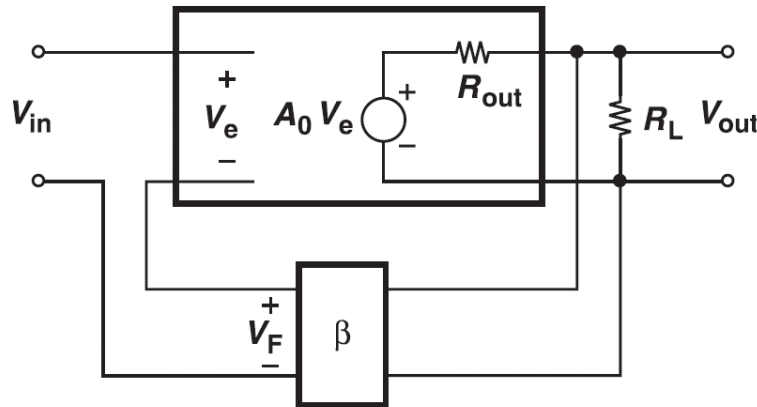


- If the amplifier is loaded by a resistor R_L
 - Consider a voltage amplifier without feedback (*open-loop* configuration), the output would drop in proportional to $R_L / (R_L + R_{out})$
 - Consider a feedback amplifier, if loop gain remains much greater than unity


$$V_{out} / V_{in} \approx 1 / \beta$$
 - The circuit stabilizes the output voltage amplitude despite load variations, it behaves as a voltage source, thus exhibiting a low output impedance.

$$V_F = \beta V_X \quad V_e = -\beta V_X \quad V_M = -\beta A_0 V_X \quad I_X = [V_X - (-\beta A_0 V_X)] / R_{out} \quad \frac{V_X}{I_X} = \frac{R_{out}}{1 + \beta A_0}$$

Effect of V-V Feedback on R_{in}

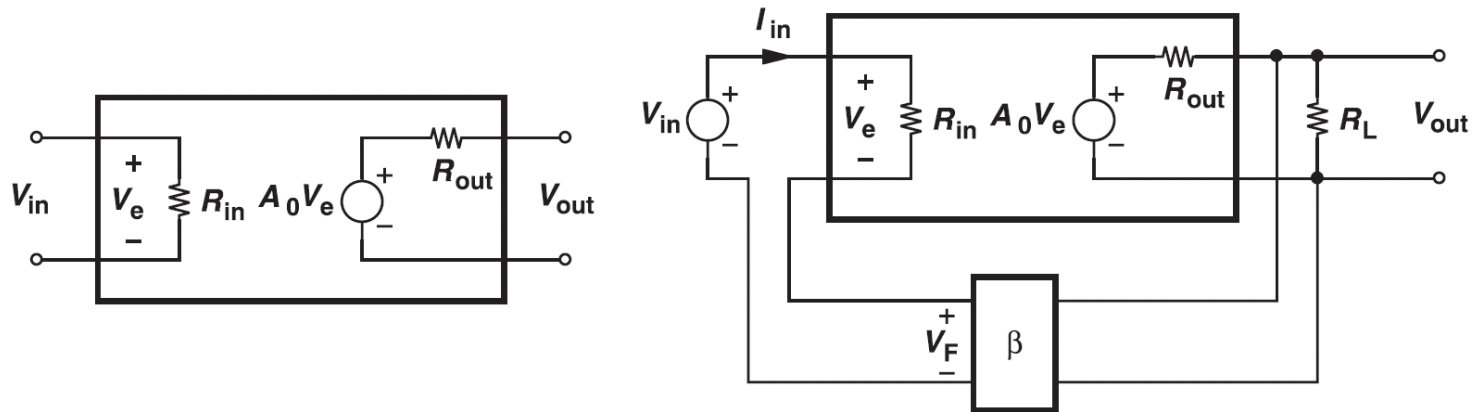

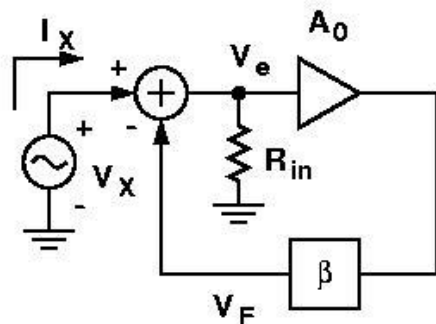- For the open loop Amp, the R_{in} of the FF Amp sustains the entire V_{in} .
- For the closed loop Amp, the R_{in} of the FF Amp sustains only a fraction of V_{in} .
- The $I(R_{in})$ in the FB topology is less than that in the open-loop system.
- Returning a voltage quantity to the input increases the input impedance.



$$V_e = I_X R_{in}$$



$$V_F = \beta A_0 I_X R_{in}$$

$$V_e = V_X - V_F = V_X - \beta A_0 I_X R_{in}$$

$$I_X R_{in} = V_X - \beta A_0 I_X R_{in}$$

$$\frac{V_X}{I_X} = R_{in} (1 + \beta A_0)$$

Current-Voltage (I-V) Feedback

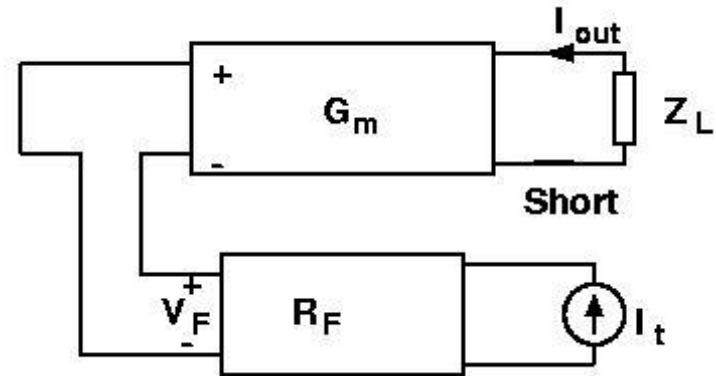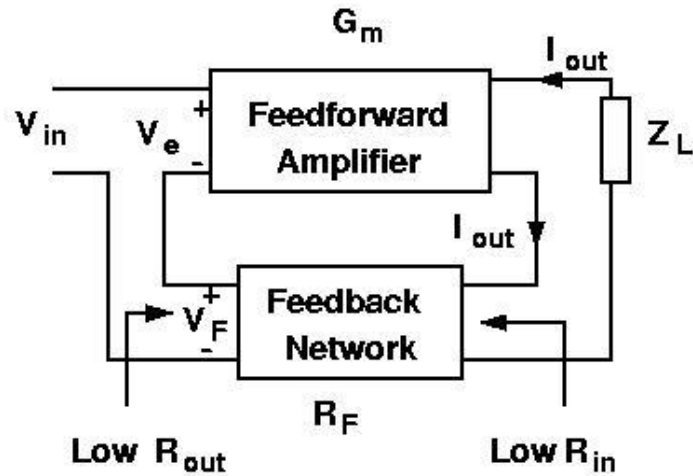

- Sense the output current to perform feedback. (series – series)
- The current is usually sensed by placing a small resistor in series with the output and using the voltage across the resistor as the feedback information.
- The feedback factor β (R_F).

$$V_F = R_F I_{out}, \quad V_e = V_{in} - R_F I_{out}, \quad I_{out} = G_m (V_{in} - R_F I_{out}) \quad \frac{I_{out}}{V_{in}} = \frac{G_m}{1 + G_m R_F}$$

- An ideal FB network in this case exhibits zero input and output impedance.
- The loop gain = $G_m R_F$. $V_F = R_F I_t$, $I_{out} = -G_m R_F I_t$, $-\frac{I_{out}}{I_t} = G_m R_F$

R_{in}/R_{out} of I-V Feedback Amplifier

- Output resistance of a current-voltage feedback amplifier

$$V_F = R_F I_X$$

$$-R_F I_X G_m = I_X - V_X / R_{out}$$



$$\frac{V_X}{I_X} = R_{out} (1 + G_m R_F)$$

- Input resistance of a current-voltage feedback amplifier


$$R_{in} I_X G_m = I_{out}$$

$$V_e = V_X - G_m R_F I_X R_{in}$$
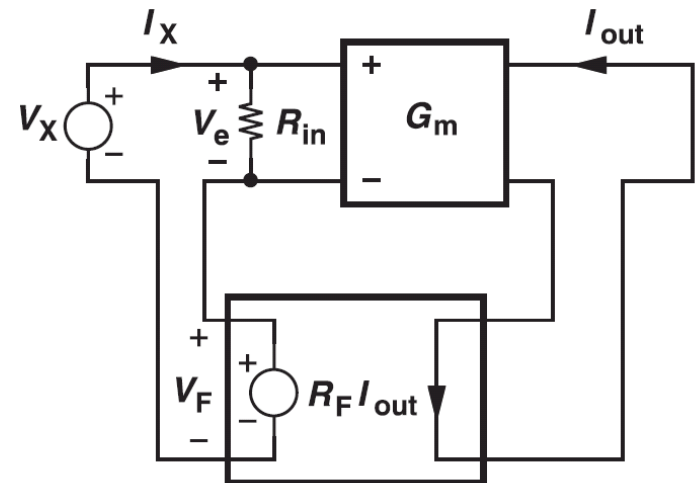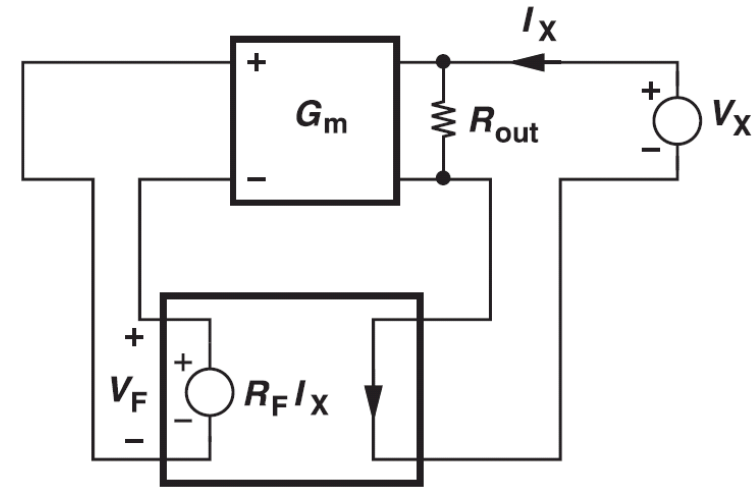
$$\frac{V_X}{I_X} = R_{in} (1 + G_m R_F)$$



Voltage-Current (V-I) Feedback

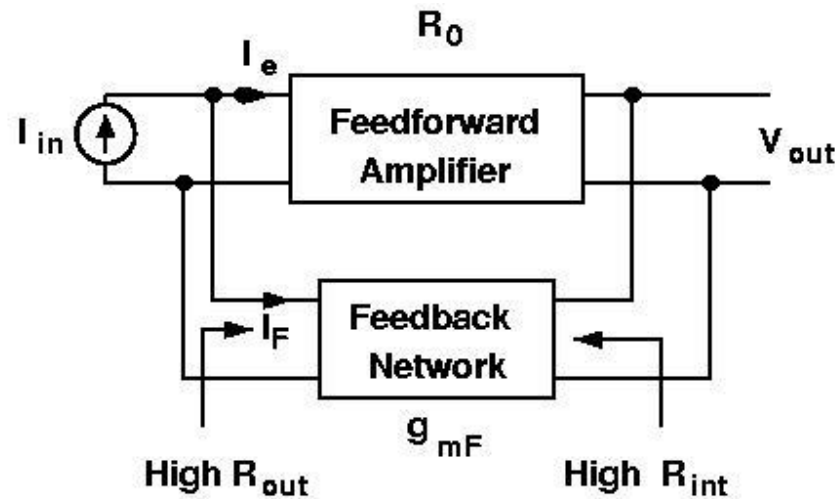

- The output voltage is sensed and a proportional current is returned to the summing point at the input. (shunt – shunt)
- The feedforward path incorporates a transimpedance amplifier with gain R_0 .
- The feedback factor has a dimension of conductance.
- The feedback network ideally exhibiting infinite input and output impedance.

$$I_F = g_{mF} V_{out} \quad I_e = I_{in} - I_F \quad V_{out} = R_0 I_e = R_0 (I_{in} - g_{mF} V_{out}) \quad \frac{V_{out}}{I_{in}} = \frac{R_0}{1 + g_{mF} R_0}$$

- The Loop gain : $g_{mF} R_0$

R_{in}/R_{out} of V-I Feedback Amplifier

- R_{in} of a voltage-current feedback amplifier.
- The R_{in} of R_0 is placed in series because an ideal transimpedance amplifier exhibits a zero input impedance.

$$I_F = I_X - V_X / R_{in} \quad (V_X / R_{in})R_0 g_{mF} = I_F$$



$$\frac{V_X}{I_X} = \frac{R_{in}}{1 + R_0 g_{mF}}$$

- Output impedance of a voltage-current feedback amplifier.



$$I_F = V_X g_{mF} \quad I_e = -I_F \quad V_M = -R_0 g_{mF} V_X$$

$$I_X = (V_X - V_M) / R_{out} = (V_X + g_{mF} R_0 V_X) / R_{out}$$
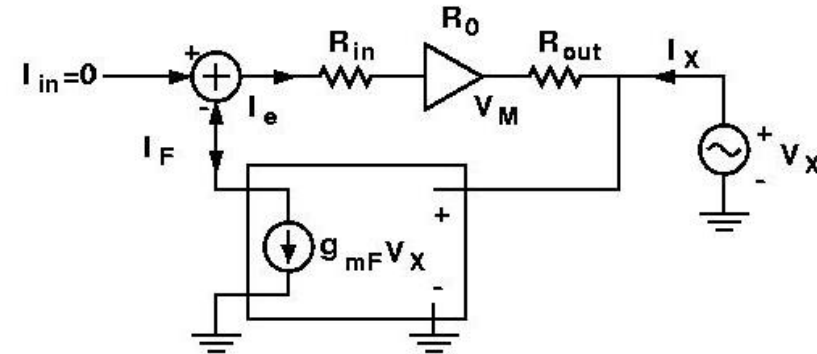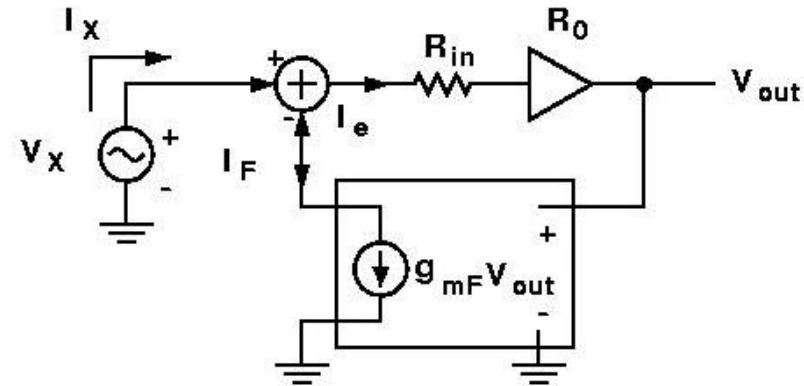
$$\frac{V_X}{I_X} = \frac{R_{out}}{1 + g_{mF} R_0}$$



Current-Current (I-I) Feedback

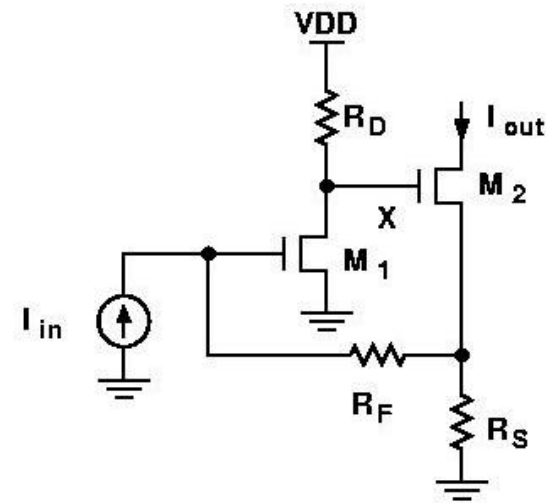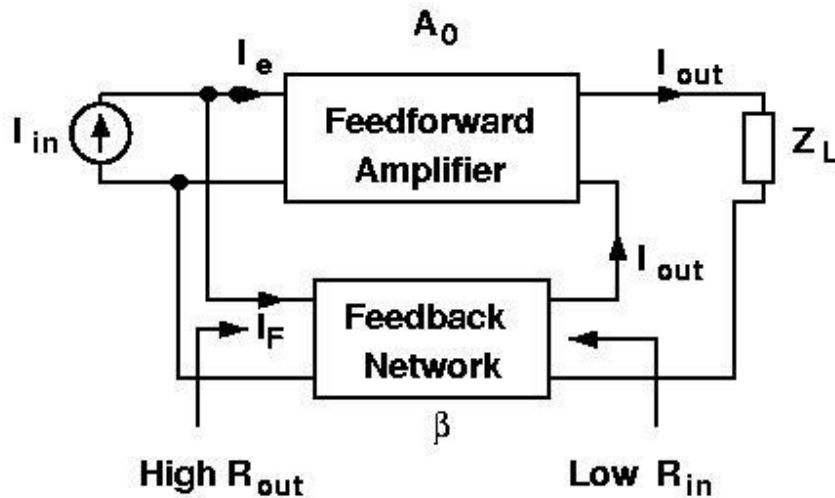

- The feedforward amplifier is characterized by a current gain A_i . (shunt – series)
- The feedback network by a current ratio β .

- The closed loop current gain is
$$A_{if} = \frac{A_i}{1 + A_i \beta}$$

- The input resistance is
$$R_{if} = \frac{R_i}{1 + A_i \beta}$$


- The output resistance is
$$R_{of} = (1 + A_i \beta) R_{out}$$

Outline

1. General Consideration
2. Feedback Topologies
- 3. Effect of Loading**
4. Effect of Feedback on Noise

Two-Port Network Models


- For current-voltage feedback (Z)

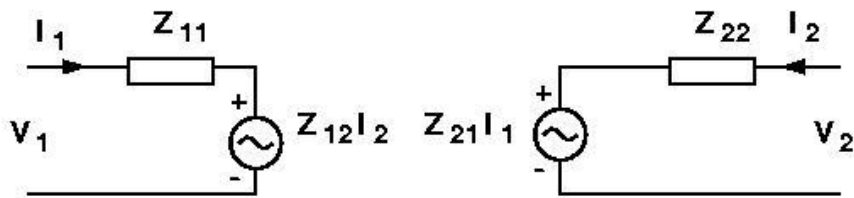

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$


- For voltage-current feedback (Y)

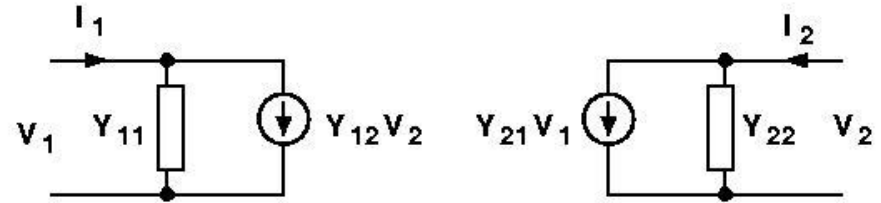

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$


- For current-current feedback (H)

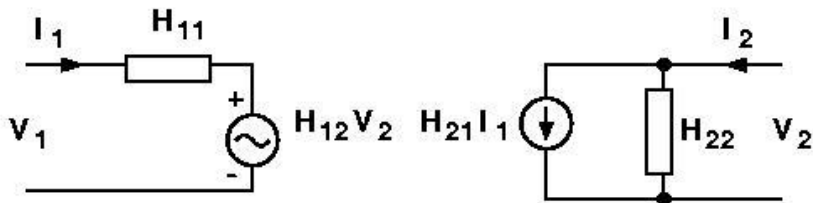

$$V_1 = H_{11}I_1 + H_{12}V_2$$

$$I_2 = H_{21}I_1 + H_{22}V_2$$


- For voltage-voltage feedback (G)

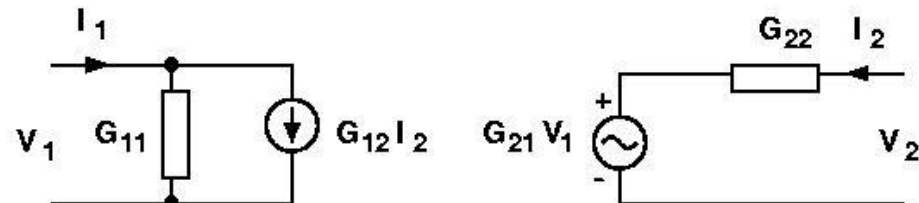


$$I_1 = G_{11}V_1 + G_{12}I_2$$

$$V_2 = G_{21}V_1 + G_{22}I_2$$

Loading in V-V Feedback

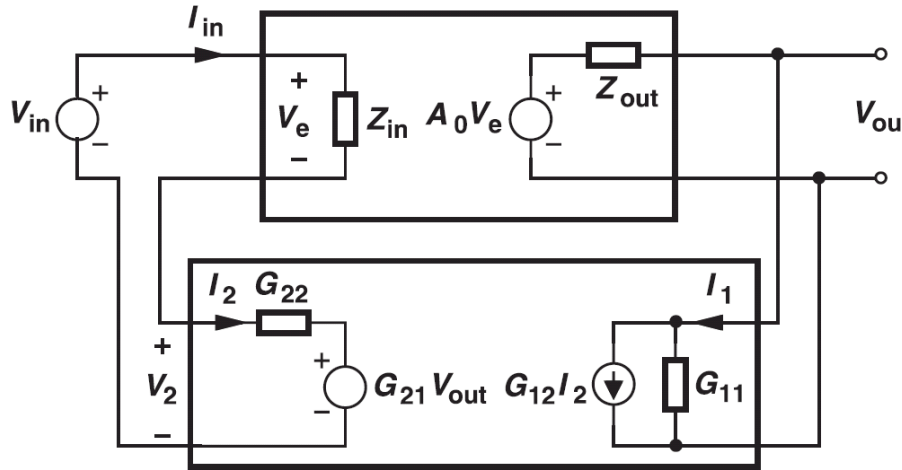

(a)

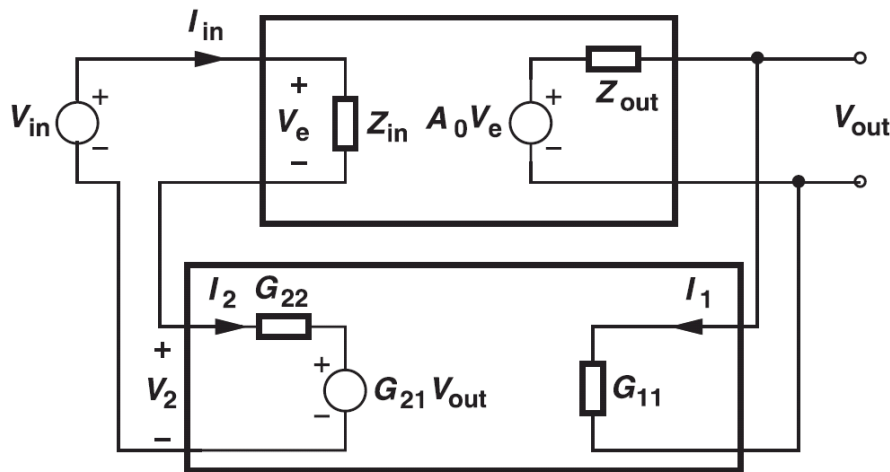

(b)

- If A_0 is large, the signal amplified by A_0 is much greater than the contribution of $G_{12}I_2$.

$$V_e = (V_{in} - G_{21}V_{out}) \frac{Z_{in}}{Z_{in} + G_{22}}$$

$$(V_{in} - G_{21}V_{out}) \frac{Z_{in}}{Z_{in} + G_{22}} A_0 \frac{G_{11}^{-1}}{G_{11}^{-1} + Z_{out}} = V_{out}$$

$$\frac{V_{out}}{V_{in}} = \frac{A_0 \frac{Z_{in}}{Z_{in} + G_{22}} \frac{G_{11}^{-1}}{G_{11}^{-1} + Z_{out}}}{1 + \frac{Z_{in}}{Z_{in} + G_{22}} \frac{G_{11}^{-1}}{G_{11}^{-1} + Z_{out}} G_{21} A_0}$$


$$\text{If } G_{11}^{-1} = \infty, \quad G_{22} = 0,$$

$$V_{out}/V_{in} = A_0 / (1 + G_{21}A_0)$$

Loading in a V-V Feedback Circuit

- If we define the open-loop gain in the presence of loading as
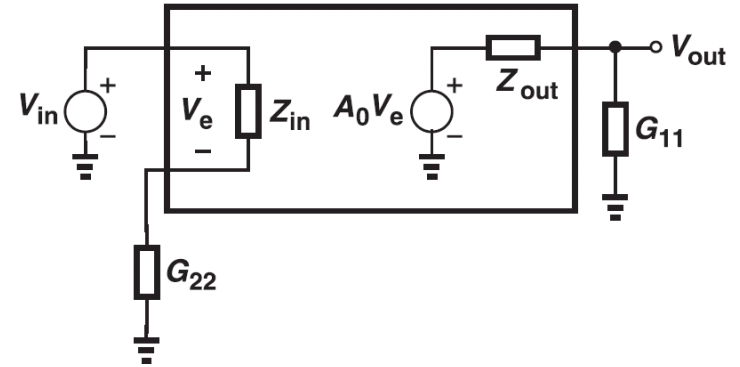
$$A_{v,open} = \frac{Z_{in}}{Z_{in} + G_{22}} \frac{G_{11}^{-1}}{G_{11}^{-1} + Z_{out}} A_0$$



- The finite input and output impedances of the feedback network reduces the output voltage and the voltages seen by the input of the main amplifier.
- G_{11} is obtained by leaving the output of the feedback network open.


$$G_{11} = \left. \frac{I_1}{V_1} \right|_{I_2=0}$$

- G_{22} is calculated by shorting the input of the feedback network.




$$G_{22} = \left. \frac{V_2}{I_2} \right|_{V_1=0}$$

- Consider the loading effect
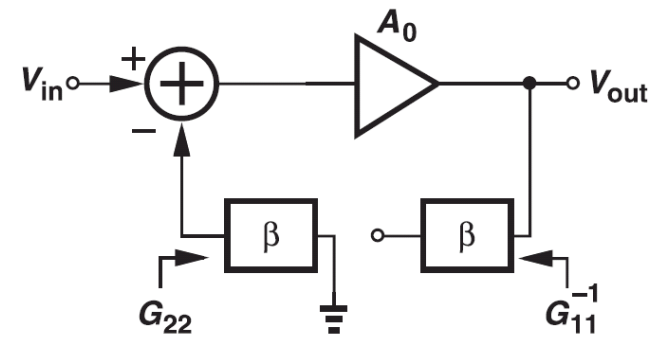
$$\frac{V_{out}}{V_{in}} = \frac{A_{v,open}}{1 + A_{v,open} G_{21}}$$



Example of V-V Feedback

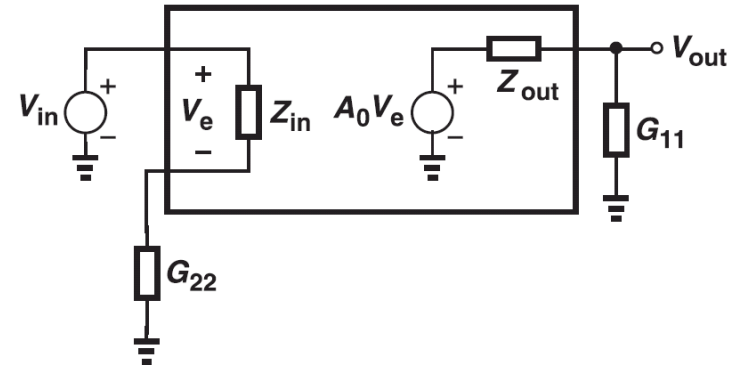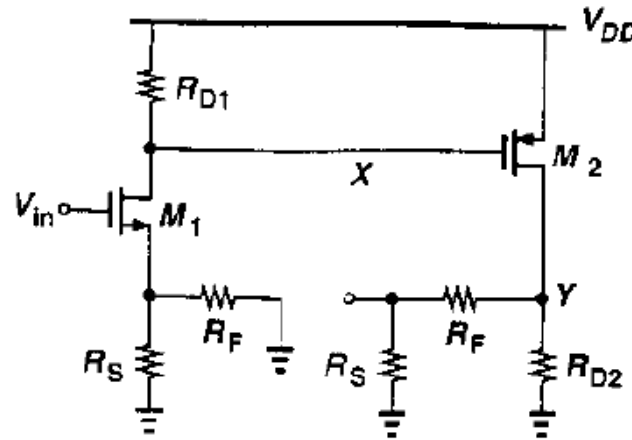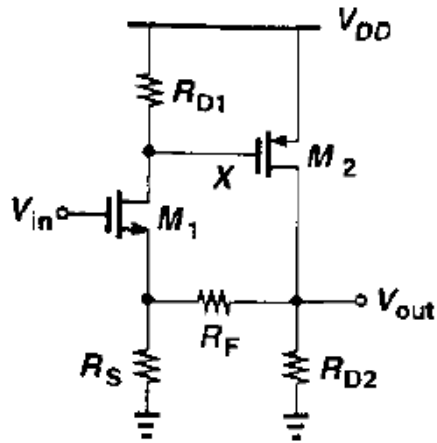


$$G_{22} = \left. \frac{V_2}{I_2} \right|_{V_1=0} = R_S \parallel R_F \quad G_{11} = \left. \frac{I_1}{V_1} \right|_{I_2=0} = (R_S + R_F)^{-1}$$

$$G_{21} = \left. \frac{V_2}{V_1} \right|_{I_2=0} = \frac{R_S}{R_S + R_F} = \beta$$

$$A_{v,open} = \frac{-R_{D1}}{R_F \parallel R_S + 1/g_{m1}} \{g_{m2} [R_{D2} \parallel (R_F + R_S)]\}$$

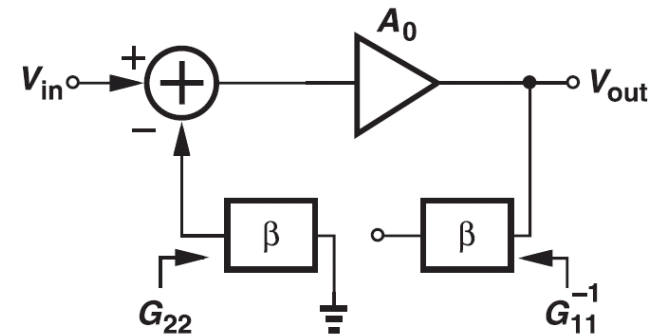
$$A_{v,closed} = \frac{A_{v,open}}{1 + G_{21} A_{v,open}}$$



$$G_{22} = \left. \frac{V_2}{I_2} \right|_{V_1=0} \quad G_{11} = \left. \frac{I_1}{V_1} \right|_{I_2=0}$$



Loading in I-V Feedback

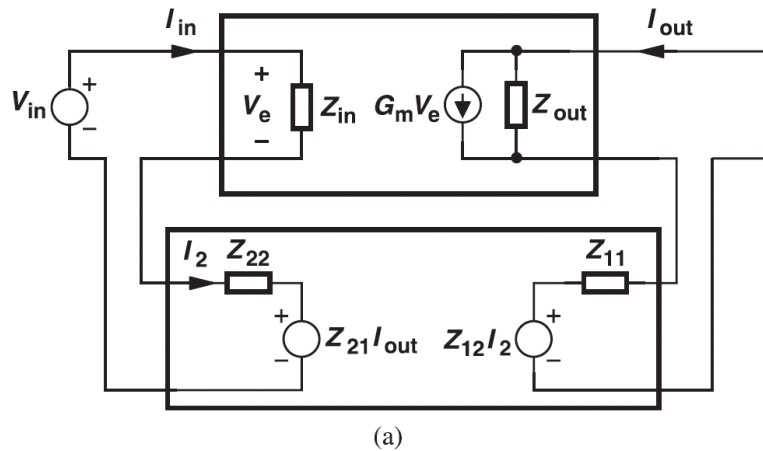- Replacing the feedback network by a Z model, and neglect the source $Z_{12}I_2$



$$(V_{in} - Z_{21}I_{out}) \frac{Z_{in}}{Z_{in} + Z_{22}} G_m \frac{Z_{out}}{Z_{out} + Z_{11}} = I_{out}$$
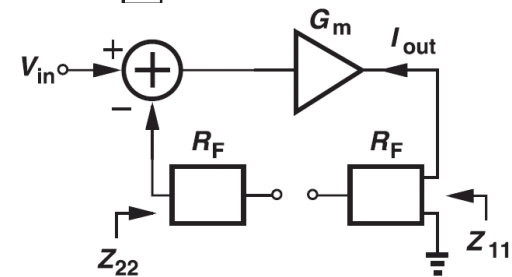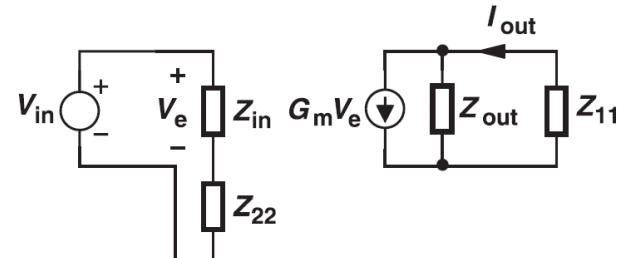
$$\frac{I_{out}}{V_{in}} = \frac{\frac{Z_{in}}{Z_{in} + Z_{22}} \frac{Z_{out}}{Z_{out} + Z_{11}} G_m}{1 + \frac{Z_{in}}{Z_{in} + Z_{22}} \frac{Z_{out}}{Z_{out} + Z_{11}} G_m Z_{21}}$$




- The loaded open loop gain is equal to


$$G_{m,open} = \frac{Z_{in}}{Z_{in} + Z_{22}} \frac{Z_{out}}{Z_{out} + Z_{11}} G_m$$

Loading in V-I Feedback

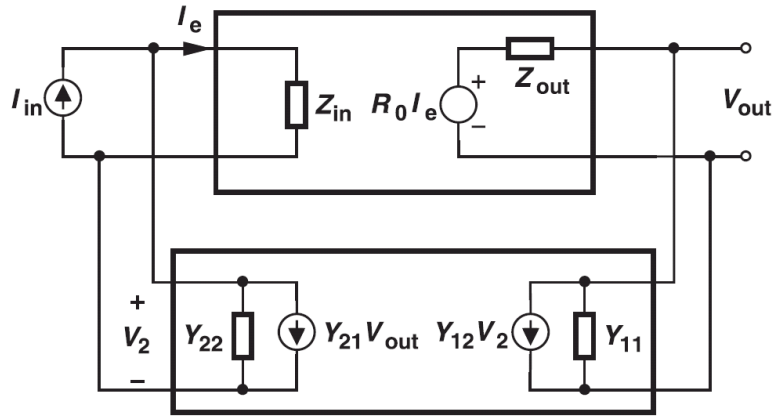- Replacing the feedback network by a Y model, and neglect the source $Y_{12}V_2$




(a)

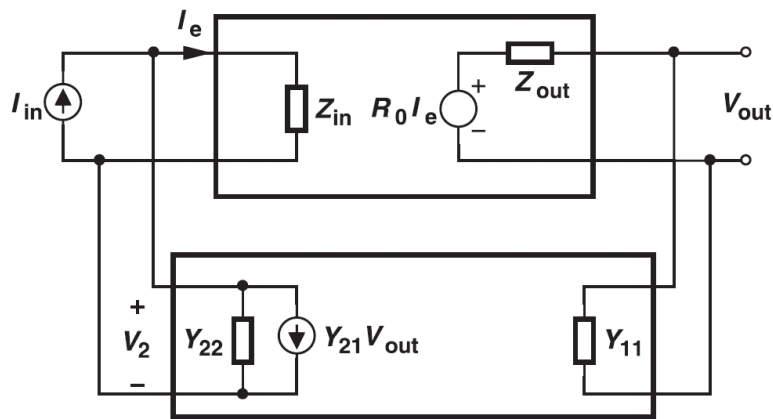

$$\frac{V_{out}}{I_{in}} = \frac{\frac{Y_{22}^{-1}}{Y_{22}^{-1} + Z_{in}} R_0 \frac{Y_{11}^{-1}}{Y_{11}^{-1} + Z_{out}}}{1 + \frac{Y_{22}^{-1}}{Y_{22}^{-1} + Z_{in}} R_0 \frac{Y_{11}^{-1}}{Y_{11}^{-1} + Z_{out}} Y_{21}}$$



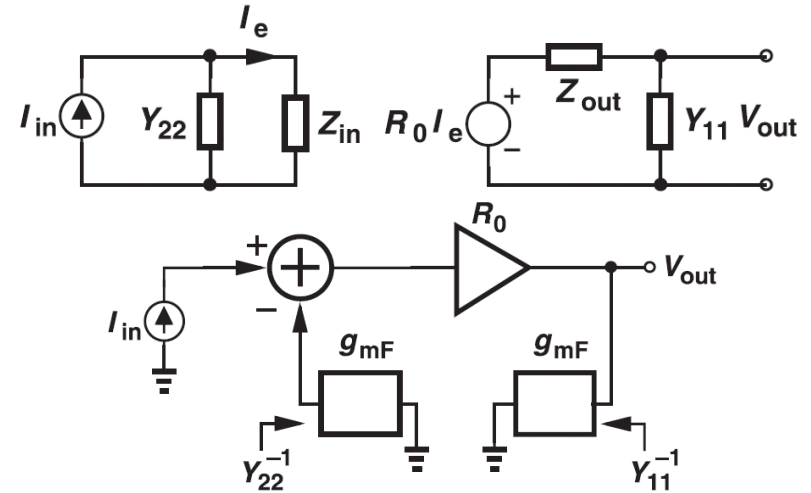
$$(I_{in} - Y_{21}V_{out}) \frac{Y_{22}^{-1}}{Y_{22}^{-1} + Z_{in}} R_0 \frac{Y_{11}^{-1}}{Y_{11}^{-1} + Z_{out}} = V_{out}$$



- The loaded open loop gain is equal to

$$R_{0,open} = \frac{Y_{22}^{-1}}{Y_{22}^{-1} + Z_{in}} \frac{Y_{11}^{-1}}{Y_{11}^{-1} + Z_{out}} R_0$$

Example of V-I Feedback

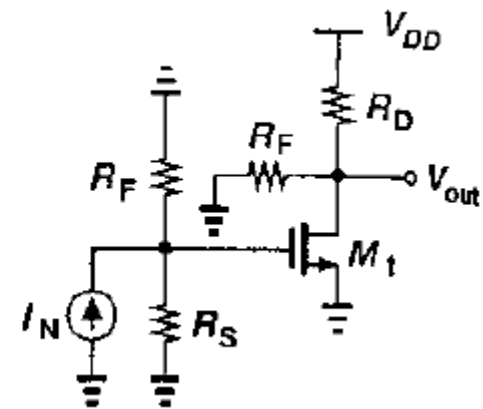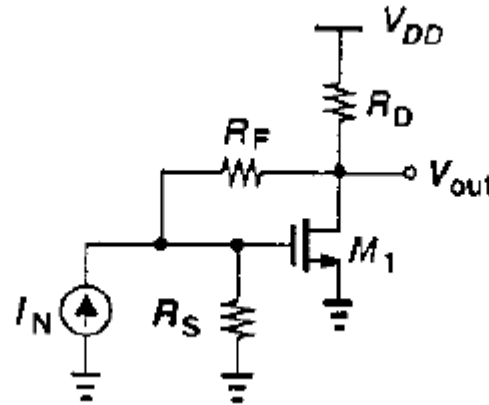
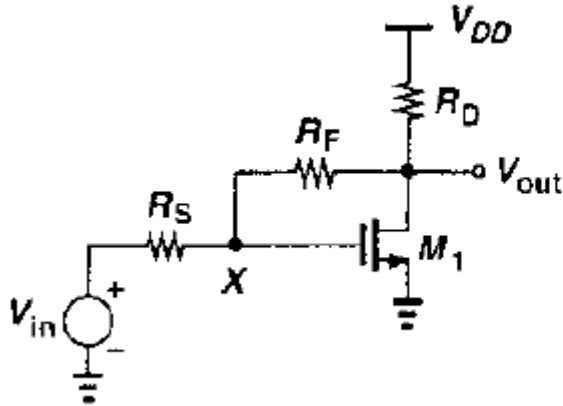


$$Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = 1/R_F, \quad Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = 1/R_F, \quad Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = -1/R_F,$$

$$R_{0,open} = \left. \frac{V_{out}}{I_N} \right|_{open} = -(R_S \parallel R_F) g_m (R_F \parallel R_D)$$


$$R_{0,closed} = \frac{R_{0,open}}{1 + Y_{21} R_{0,open}} = \frac{-(R_S \parallel R_F) g_m (R_F \parallel R_D)}{1 + g_m (R_F \parallel R_D) R_S / (R_S + R_F)}$$
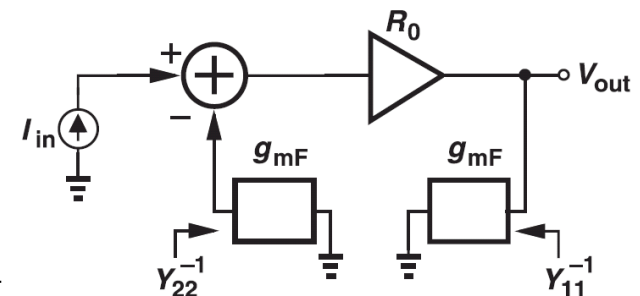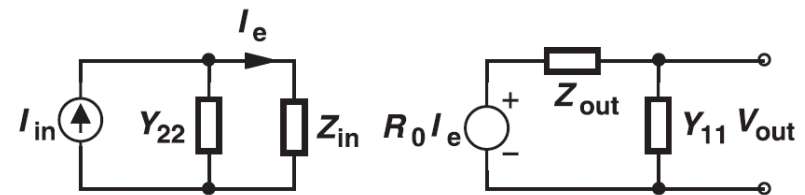
$$\frac{V_{out}}{V_{in}} = \frac{V_{out}}{I_N} \frac{1}{R_S} = \frac{R_{0,closed}}{R_S} = \frac{1}{R_S} \frac{-(R_S \parallel R_F) g_m (R_F \parallel R_D)}{1 + g_m (R_F \parallel R_D) R_S / (R_S + R_F)}$$




Loading in I-I Feedback

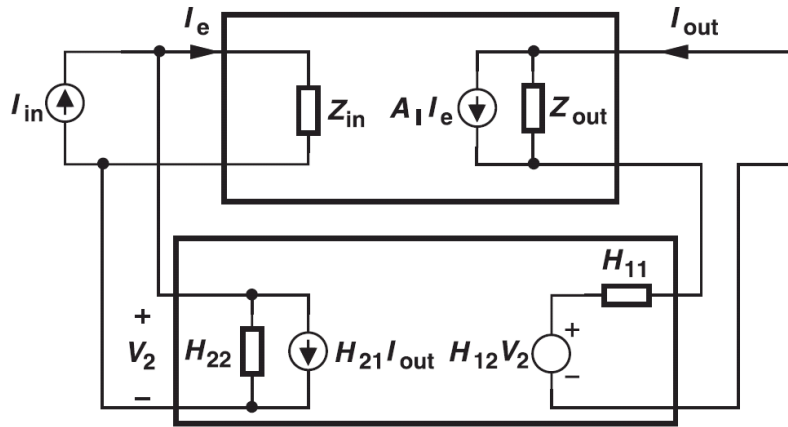- Replacing feedback network by an H model. Neglecting the effect of $H_{12} V_2$




(a)

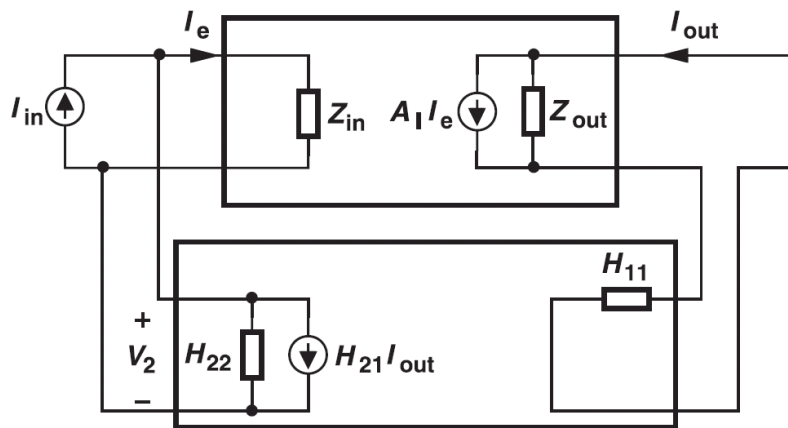

- The loaded open loop gain is equal to

$$(I_{in} - H_{21} I_{out}) \frac{H_{22}^{-1}}{H_{22}^{-1} + Z_{in}} A_I \frac{Z_{out}}{H_{11} + Z_{out}} = I_{out}$$

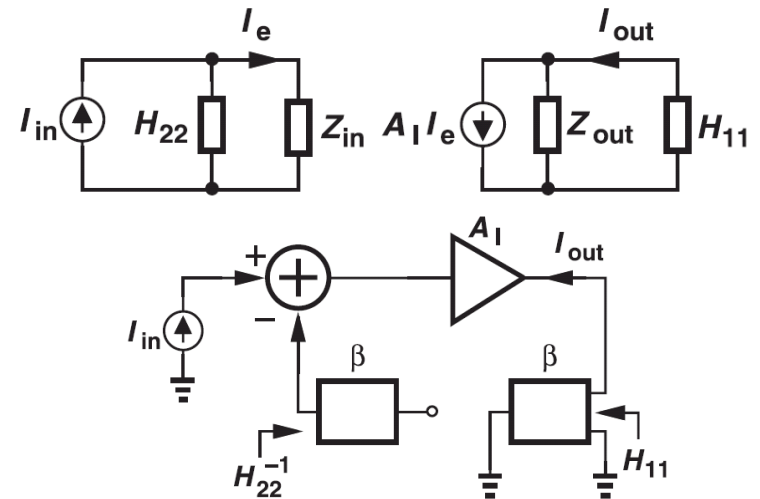
$$\frac{I_{out}}{I_{in}} = \frac{\frac{H_{22}^{-1}}{H_{22}^{-1} + Z_{in}} A_I \frac{Z_{out}}{H_{11} + Z_{out}}}{1 + \frac{H_{22}^{-1}}{H_{22}^{-1} + Z_{in}} A_I \frac{Z_{out}}{H_{11} + Z_{out}} H_{21}}$$



$$A_{I,open} = \frac{H_{22}^{-1}}{H_{22}^{-1} + Z_{in}} A_I \frac{Z_{out}}{H_{11} + Z_{out}}$$

Summary of Loading Effects

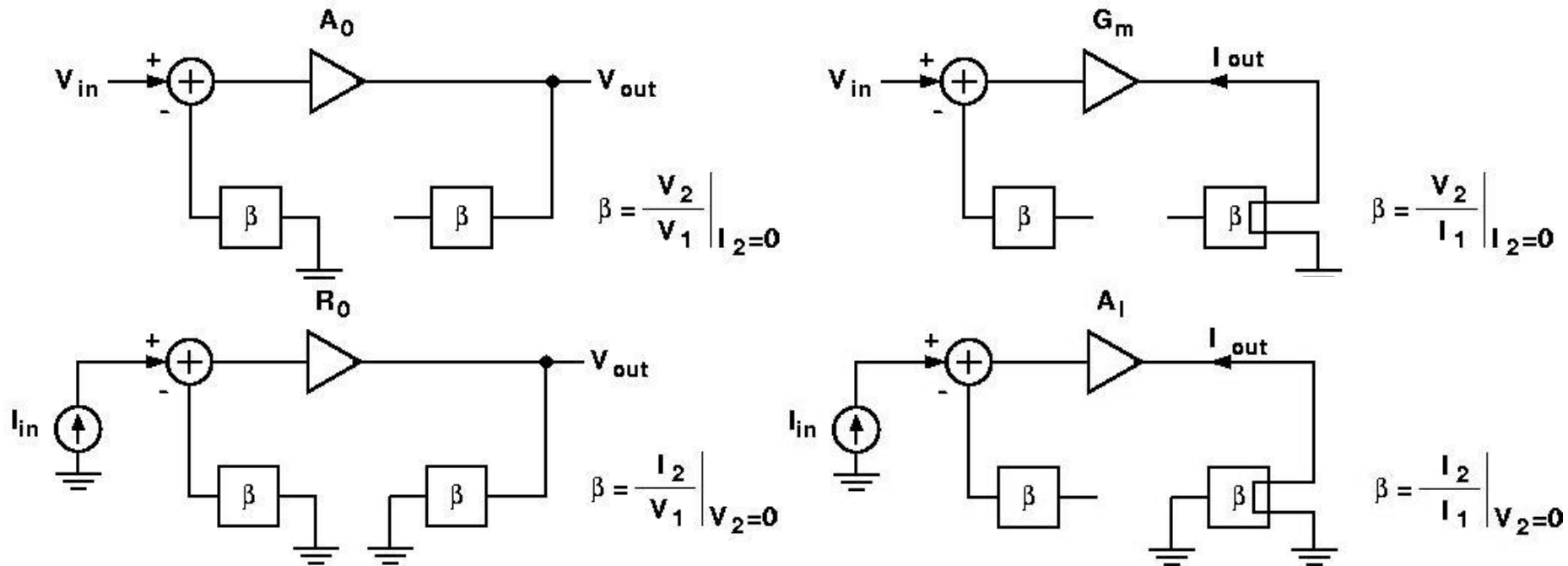- The analysis is carried out in three steps
 - Open the loop with proper loading and calculate the open-loop gain A_{OL} , and the open-loop input and output impedances.
 - Determine the feedback ratio β and hence the loop gain βA_{OL} .
 - Calculate the closed-loop gain and input and output impedances by scaling the open loop values by a factor of $1 + \beta A_{OL}$.





Outline

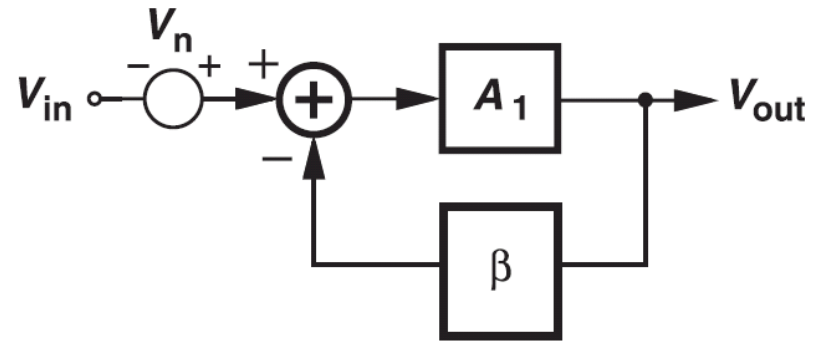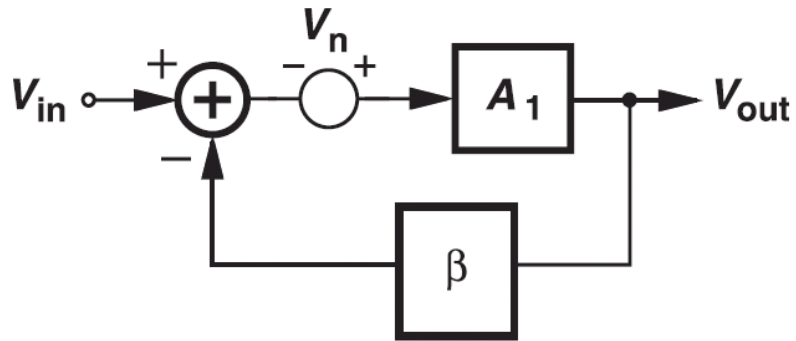1. General Consideration
2. Feedback Topologies
3. Effect of Loading
- 4. Effect of Feedback on Noise**

Effect of Feedback on Noise


- Feedback does not improve the noise performance of circuits.
- Assume the open-loop voltage amplifier A_1 is characterized by only an input-referred noise voltage and the feedback network is noiseless.



$$(V_{in} - \beta V_{out} + V_n)A_1 = V_{out} \quad V_{out} = (V_{in} + V_n) \frac{A_1}{1 + \beta A_1}$$

- In practice, the feedback network itself may contain resistors or transistors, degrading the overall noise performance.

Effect of Feedback on Noise

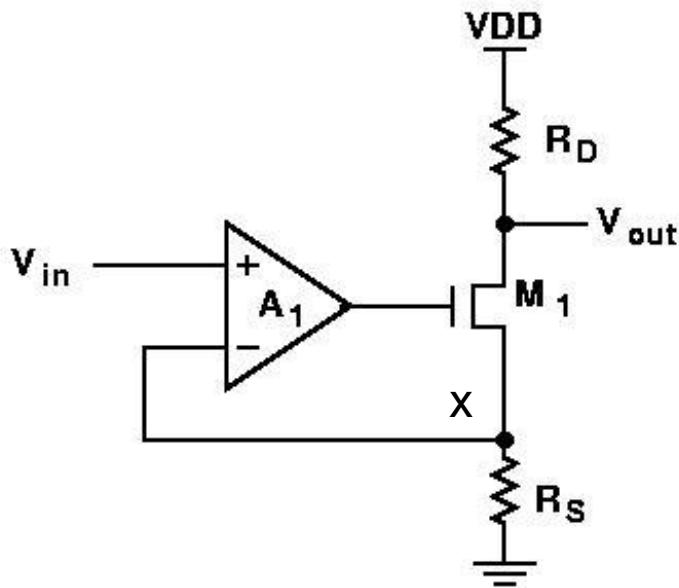

$$\left[(V_{in} - V_x) A_1 - V_x \right] \cdot g_m = \frac{V_x}{R_S}$$

$$V_x = \frac{g_m A_1 V_{in}}{\frac{1}{R_S} + g_m (1 + A_1)}, \quad V_o = -\frac{R_D}{R_S} V_x$$

$$\left. \frac{V_o}{V_{in}} \right|_{closed} = -\frac{g_m R_D A_1}{1 + g_m R_S (1 + A_1)}, \quad |V_{n,in,closed}| = \frac{|V_{n,R_D}|}{A_1 R_D} \left[\frac{1}{g_m} + (1 + A_1) R_S \right]$$

$$\left. \frac{V_o}{V_{in}} \right|_{open} = -\frac{g_m R_D A_1}{1 + g_m R_S}, \quad |V_{n,in,open}| = \frac{|V_{n,R_D}|}{A_1 R_D} \left[\frac{1}{g_m} + R_S \right]$$

- As

$$A_1 \rightarrow \infty, \quad |V_{n,in,closed}| \rightarrow |V_{n,R_D}| \frac{R_S}{R_D} \quad \text{whereas} \quad |V_{n,in,open}| \rightarrow 0$$