

1. Use composer and hspice to simulate the capacitance characteristic of pMOS as shown in Fig. 1 with body connected to vdd=1.8V. (30%) (*hint*: .probe DC ctot=par("lx18(MN)"))
  - (a) Assume the  $W/L = 5 \times 10 \mu\text{m} / 0.5 \mu\text{m}$ ,  $V_G = 0\text{V} \sim 3.6\text{V}$ . (use CIC 0.18 $\mu\text{m}$  hspice model). (10%)
  - (b) Modify the  $W/L = 50 \mu\text{m} / 0.5 \mu\text{m}$ , redo the simulation and plot, comments the capacitance difference compared to (a). (10%)
  - (c) Modify the  $W/L = 5 \mu\text{m} / 5 \mu\text{m}$ , redo the simulation and plot, comments the capacitance difference compared to (a) and (b). (10%)

 


Fig. 1.

2. A common source as shown in Fig. 2 has  $V_{DD} = 1.8\text{V}$ , Output DC voltage=0.9V, and  $R=10\text{k}\Omega$ . (50%)
  - (a) Choose the size ( $m=1$ ) and the input DC voltage of  $M_1$ . Use function “.tf v(out) vin” to find the AC gain >5. (5%)
  - (b) Find the linear range (1. Definition: 10% gain deviation. 2. Range of both input and output) and gain of this common source with voltage transfer curve  $V_{in}$  vs.  $V_{out}$  only. (10%)
  - (c) Use the same width and length with  $m=20$  to find input DC voltage again. And redo the (b). (15%)
  - (d) Comment on what makes the difference of gain and linear range between (b) and (c). (20%)

 


Fig. 2.

3. Choose two nMOSs (1.8V devices) with  $W/L = 3\mu\text{m}/0.3\mu\text{m}$  and  $W/L = 3\mu\text{m}/3\mu\text{m}$ . Use HSPICE DC sweep analysis to show the  $I_D$ - $V_{DS}$  characteristic waveforms with  $V_{GS} = 0, 0.3, 0.6, 0.9, 1.2, 1.5$  and  $1.8\text{V}$  as shown in Fig. 3. Comment the characteristics difference between long-channel and short-channel devices. (20%)

 


Fig. 3.

- ✧ *The following should be included in your report (a) schematic (b) HSPICE netlist & simulation file (c) waveform with cursor values (d) comments.*