



# Hspice Tutorial

2008

---

**Professor: Jin-Fu Li**

**TAs:**

**陳詠孝 & 陳亭如**



**ARES LAB**

*Y.-S. Chen*


# Contents

---

- **Introduction**
- Simulation Input and Controls
- Waveform Instructions
- Simulation Output
- Appendix

# Introduction(1/2)

---

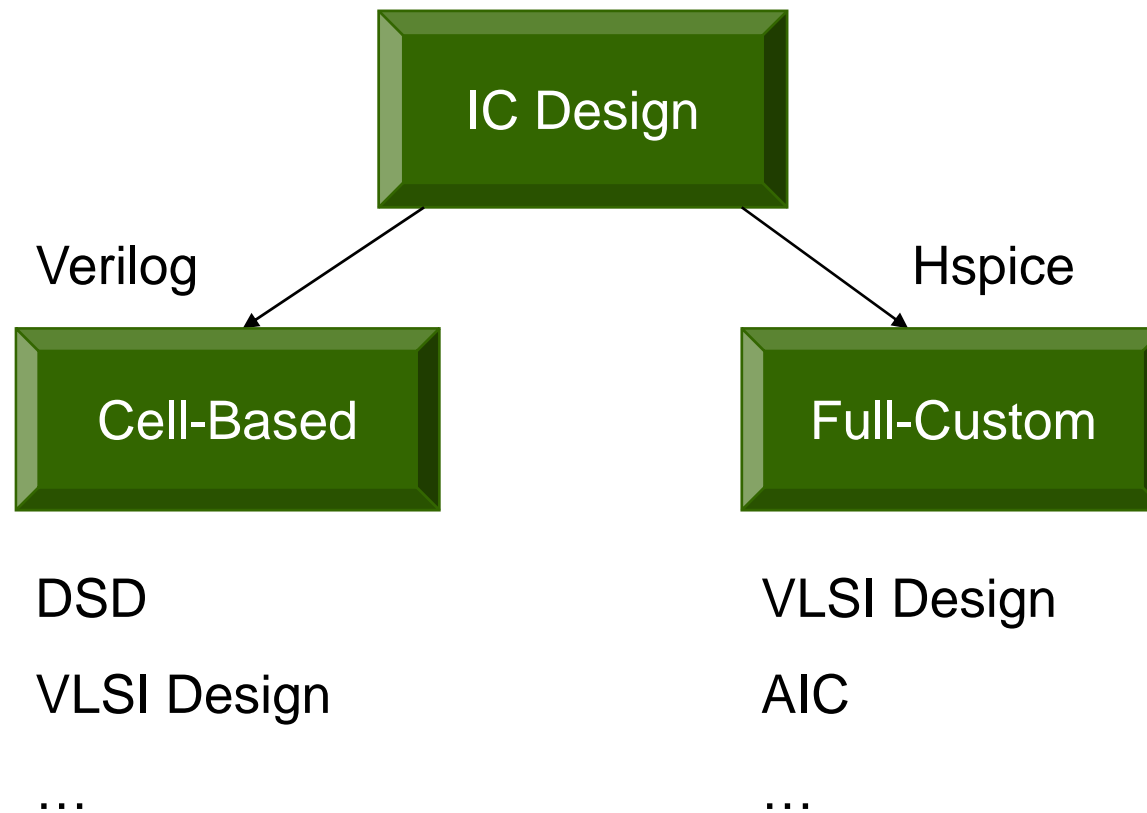

# Introduction(2/2)


---

- **SPICE :**

**Simulation Program with Integrated Circuit Emphasis**

- Hspice 是一個電路模擬軟體，用來模擬所設計電路的行為及功能特性。
- Hspice 係以電晶體、二極體、電阻及電容等各種元件模型為基礎，透過數值方法來計算電路各節點的電壓、電流變化。
- 對於非線性的電路系統，Hspice 是在計算近似解，所得結果的正確性和元件模型、演算法則有密切關係。
- Hspice 主要提供穩態、暫態及小信號頻率響應模擬，使用者需依所設計的電路種類自行規劃分析的指令及相關的輸入。

# Basic Flow for SPICE

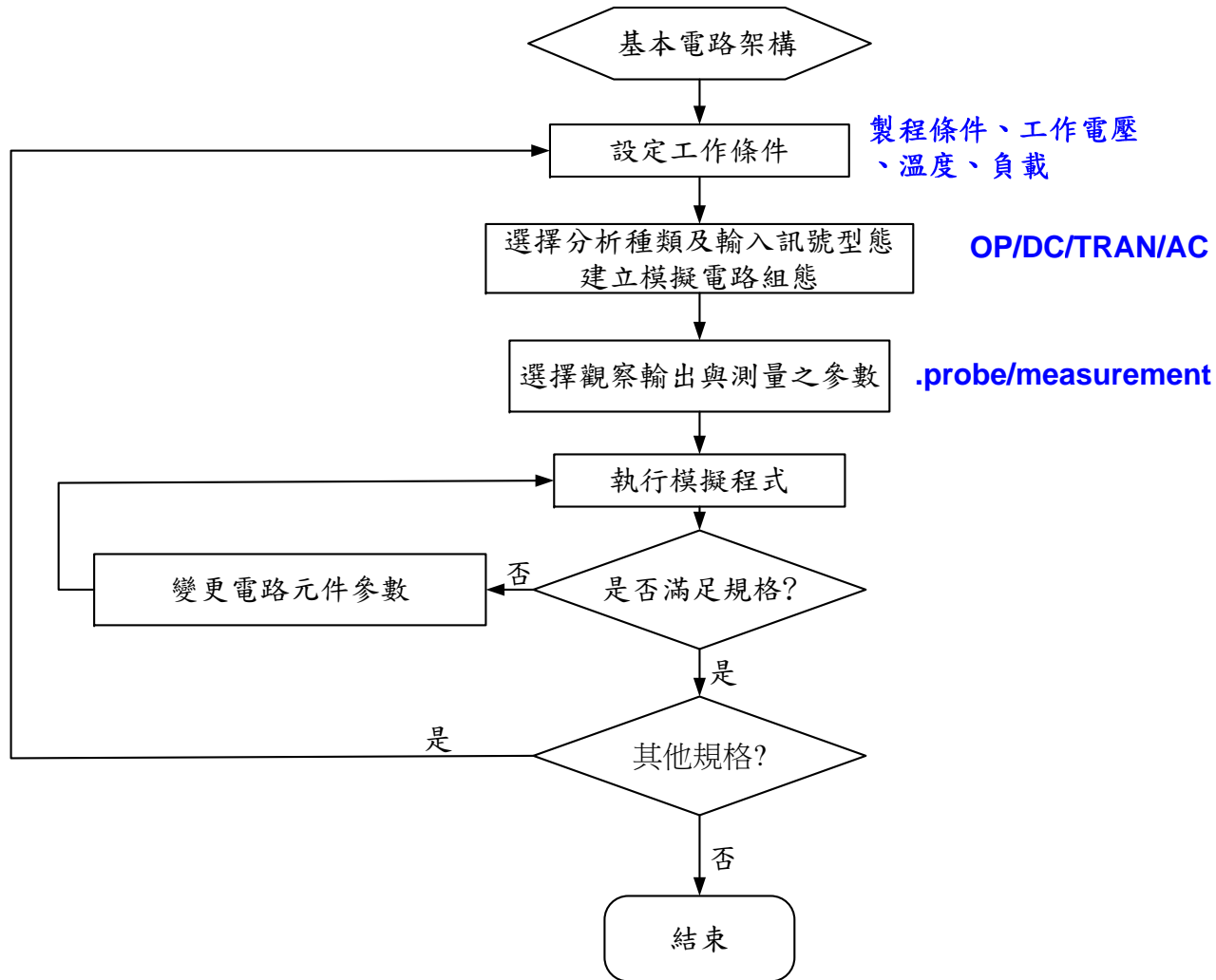

# Basics for Using SPICE Tools

---

## SPICE 之外所需的基本概念

- 了解元件的基本特性
- 熟悉所設計電路的功能
- 了解電路的輸入信號特性
- 了解電路各項規格的相依性及優先程度
- 了解需要驗證的電路規格及對應的模擬種類及電路組態
- 了解電路元件參數與架構對各項電路特性的相關性，以利模擬結果的改進

# Contents

---

- Introduction
- **Simulation Input and Controls**
- Waveform Instructions
- Simulation Output
- Appendix

# Instance and Element Names

---

	C	Capacitor
	I	Current
	L	Inductor
★	M	MOSFET
	R	Resistor
	V	Voltage Source
	X	Subcircuit Call



# Unit and Scale Factor

---

- Units:

**R** Ohm (e.g. R1 node1 node2 1K)

**L** Henry (e.g. L1 node1 node2 1n)

**C** Farad (e.g. C1 node1 node2 1p)

- Scale Factors:

**F** 1e-15

**T** 1e12

**P** 1e-12

**K** 1e3

**N** 1e-9

**Meg** 1e6

**U** 1e-6

**G** 1e9

**M** 1e-3

**DB**  $20\log_{10}$

**Examples:**

1pF

1nH


10Meg Hz

vdb(v3)
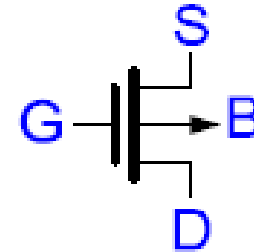
# Instance and Element Descriptions

---


Mname D G S B N/PMOS W=?u L=?u  
Mp out in vdd vdd pch W=3u L=1u



R1 A B 1K



C1 out gnd 1p

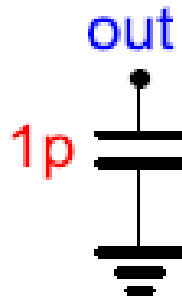

# Subcircuit

---

**.SUBCKT** <Subname> <node1> <node2>.....

次電路區塊描述

**.ENDS** <Subname>

```
.subckt inv out in Wn=0.22u Wp=0.22u Lmin=0.18u  
mp0 out in vdd vdd pch w=Wp l=Lmin  
mn0 out in vss vss nch w=Wn l=Lmin  
.ends inv
```

如果要在SPICE檔案中呼叫次電路時，格式如下：


**Xname** <node1> <node2>..... <Subname>

```
xinv dout0 d0 inv Wn=0.22u Wp=0.22u Lmin=0.18u
```

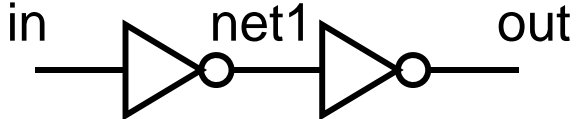
# Example

```


***** inv *****
.global vdd vss
.subckt inv in out
MM0 out in vdd vdd pch w=3u l=350n
MM1 out in vss vss nch w=1u l=350n
.ENDS
x1 in net1 inv
x2 net1 out inv
    
```



x1	in	1	inv
x2	1	out	inv

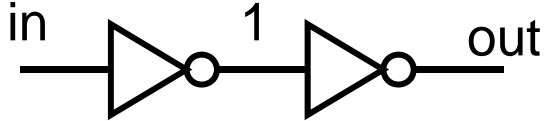

x1	in	0	inv
x2	0	out	inv

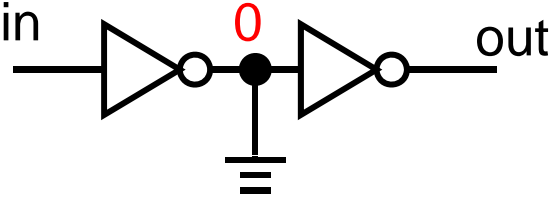

# Input Control Statement

---

- **GLOBAL**

- ALL nodes are assumed to be local
- Node names can across all subcircuits by **.GLOBAL**

```
.GLOBAL VDD VSS
```

# Netlist Structure

---

Title	→	<pre>.Title inv .GLOBAL gnd! + vdd!</pre>
Model	→	<pre>.protect .lib 'C:\VLSI\mm0355v.l' TT .unprotect</pre>
Controls	→	<pre>.op .options post .tran 0.05n 25n .temp 25</pre>
Sources	→	<pre>v1 vdd! 0 3.3v v2 gnd! 0 0v v3 Vin 0 pulse( 0v 3.3v 0.1n 0.1n 0.1n 0.5n 1.2n)</pre>
Components	→	<pre>MM1 Vout Vin vdd! vdd! Pch W=3u L=350.00n MM0 Vout Vin gnd! gnd! Nch W=1u L=350.00n</pre>
END file	→	<pre>.end</pre>

# Control Statements

---

<b>.AC</b>	電路之交流分析(頻率響應)
<b>.DC</b>	電路之直流分析
<b>.OP</b>	靜態點分析
<b>.NOISE</b>	雜訊分析
★ <b>.TRAN</b>	暫態分析
<b>.SUBCKT</b>	定義次電路
<b>.ENDS</b>	次電路之結束
<b>.OPTIONS</b>	可設定參數及其他功能
<b>.PRINT</b>	指定輸出的內容
<b>.PLOT</b>	圖形式輸出
<b>.TEMP</b>	指定模擬環境的溫度
<b>.END</b>	檔案結束

# Example

## Inverter

```
.prot
.lib      'mm0355v.l' tt
.unprot
.options  captab probe accurate
.temp    25
.global   VDD!    VSS!
Vdd       VDD!    0      dc      3.3
Vss       VSS!    0      dc      0

.op
.tran     50p     100n
.probe    v(in) v(out)

Mp        out     in      VDD!    VDD!    pch     l= 0.35u  w= 20u
Mn        out     in      VSS!    VSS!    nch     l= 0.35u  w= 4u

.end
```



# Example

---

## Inverter

Title. To note what circuit is described in this file.  
It will be skipped when SPICE is running.

**.prot**


**.lib'mm0355v.l' tt**

**.unprot**


**.options captab probe accurate**

**.temp 25**


Simulation  
temperature



Display the node  
capacitance in  
the .lis file.



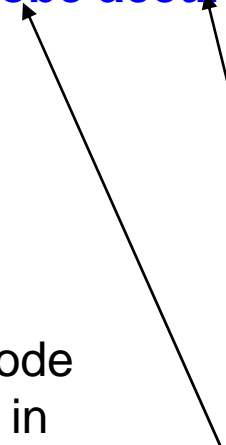
Only the node or element specified  
with .probe command will be displayed  
in the output file.



The content between **.prot** and **.unprot** will not display in the .lis file. Usually, it was used when you have some circuit secrets or you don't want the useless information, such as the library, show up in the list file.

**.lib** command is used to specify the location of the technology library and the corner used in this simulation.

Increase the simulation accuracy  
and the simulation time as well.



# Example

```
.global      VDD!  VSS!
Vdd         VDD!  0    dc    3.3
Vss         VSS!  0    dc    0
```

**.global**: Specify the global argument. All nodes with the same name will be treated as the same one.

Global ground.

**.op**: DC operating point analysis.

```
.op
.tran      50p    100n
.probe    v(in) v(out)
```

**.tran**: transient analysis. Time step is 50ps and stop time is 100ns

**.probe**: Record the node waveform while the option 'probe' is added in the .opstions statement.

```
Mp      out    in    VDD!  VDD!  pch    l= 0.35u  w= 20u
Mn      out    in    VSS!  VSS!  nch    l= 0.35u  w= 4u
```

Describe a PMOS and an NMOS.

```
.end
```

**.end**: EOF.



Y.-S. Chen

Additional space is need. Or the .end statement will be ignored.

# .dc Statement

## Inverter

```

.proton
.lib 'mm0355v.l' tt
.unproton
.options captab probe accurate
.temp 25
.global VDD! VSS!
Vdd VDD! 0 dc 3.3
Vss VSS! 0 dc 0

.op
.dc sweep vin 0 3.3 0.1
.probe v(out)

Vin in 0 dc 1.65
Mp out in VDD! VDD! pch l= 0.35u w= 20u
Mn out in VSS! VSS! nch l= 0.35u w= 4u
.end

```

**.dc**: dc voltage sweep.

The voltage source Vin will change its voltage from 0V to 3.3V with a step of 0.1V.

You must specify a certain dc value for the voltage source while performing dc sweep.

# .ac Statement

## Inverter

```

.proton
.lib 'mm0355v.l' tt
.unproton
.options captab probe accurate
.temp 25
.global VDD! VSS!
Vdd VDD! 0 dc 3.3
Vss VSS! 0 dc 0

.op
.ac dec 100 1 100Meg
.probe vdb(out) vp(out)

```

↑  
Display the node voltage in dB.

← Display the node phase.

```

Vin in 0 dc 1.65 ac 1
Mp out in VDD! VDD! pch l= 0.35u w= 20u
Mn out in VSS! VSS! nch l= 0.35u w= 4u
.end

```

**.ac**: ac frequency sweep.  
 Simulate 100 times/decade  
 from 1Hz to 100MHz. The  
 'dec' statement can be  
 replaced by 'lin' for linear  
 scale.

An ac voltage source is  
 needed for ac simulation.  
 If the amplitude of the ac  
 voltage is 1, the output  
 voltage will equals to the  
 voltage gain.

# Contents

---

- Introduction
- Simulation Input and Controls
- **Waveform Instructions**
- Simulation Output
- Appendix


# Transient Sources

---

- ★ Pulse (**PULSE** Function)
- ★ Sinusoidal (**SIN** Function)
- Exponential (**EXP** Function)
- ★ Piecewise Linear (**PWL** Function)
- Single-Frequency FM (**SFFM** Function)
- Single-Frequency AM (**AM** Function)
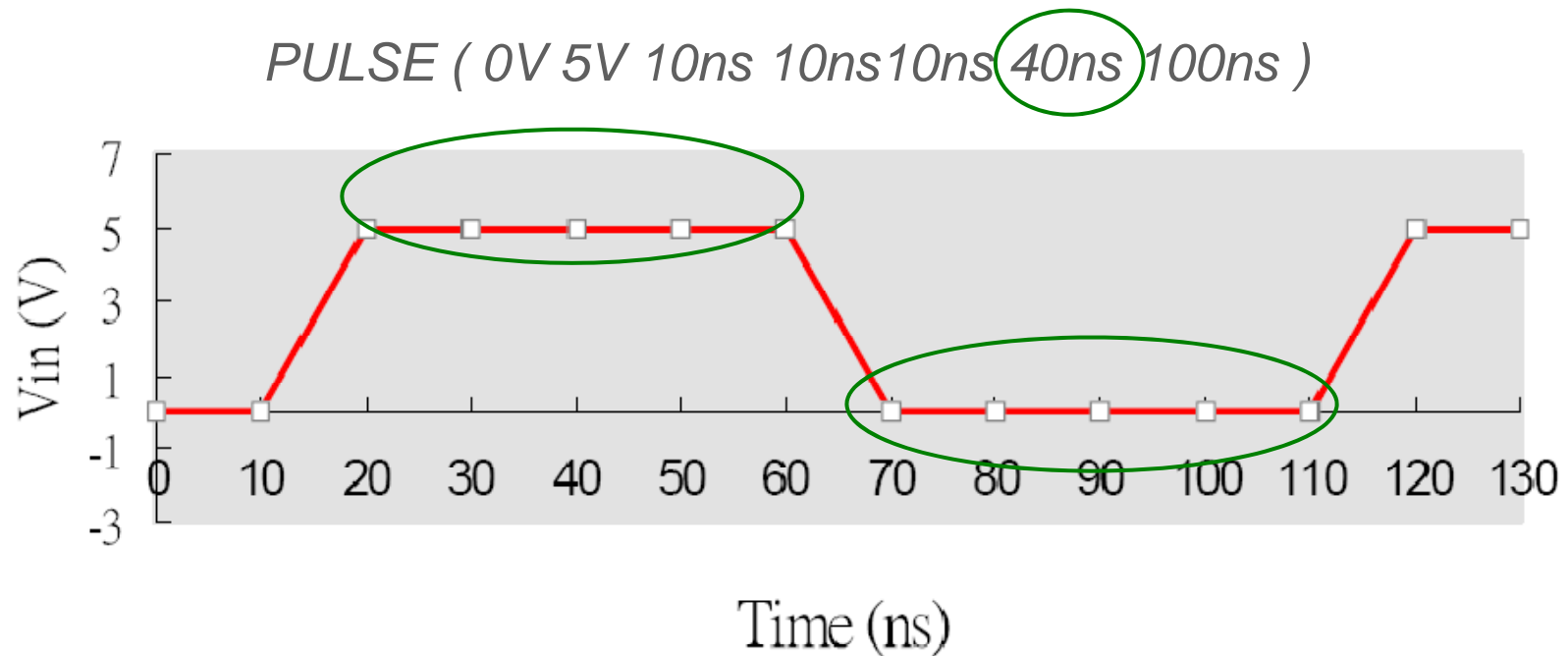
# PULSE

- **PULSE** (Periodic Waveform)  
***PULSE ( V1 V2 td tr tf pw per )***




# PWL

- **PWL** (Piece Wise Linear Waveform)

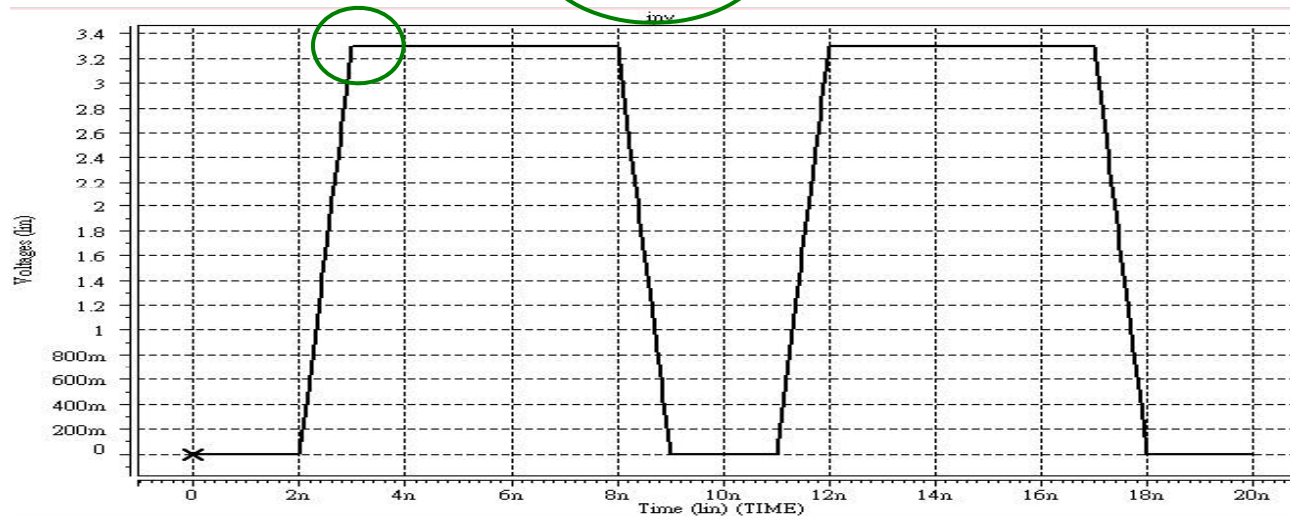***PWL ( t1 V1 t2 V2 t3 V3 ... R )***

*PWL (1n 0v 2n 0v 3n 3.3v 8n 3.3v 9n 0v R 0)*






# SIN

- **SIN** (Sinusoidal Waveform)

***SIN ( Voffset Vacmag < Freq Tdelay Dfactor > )***

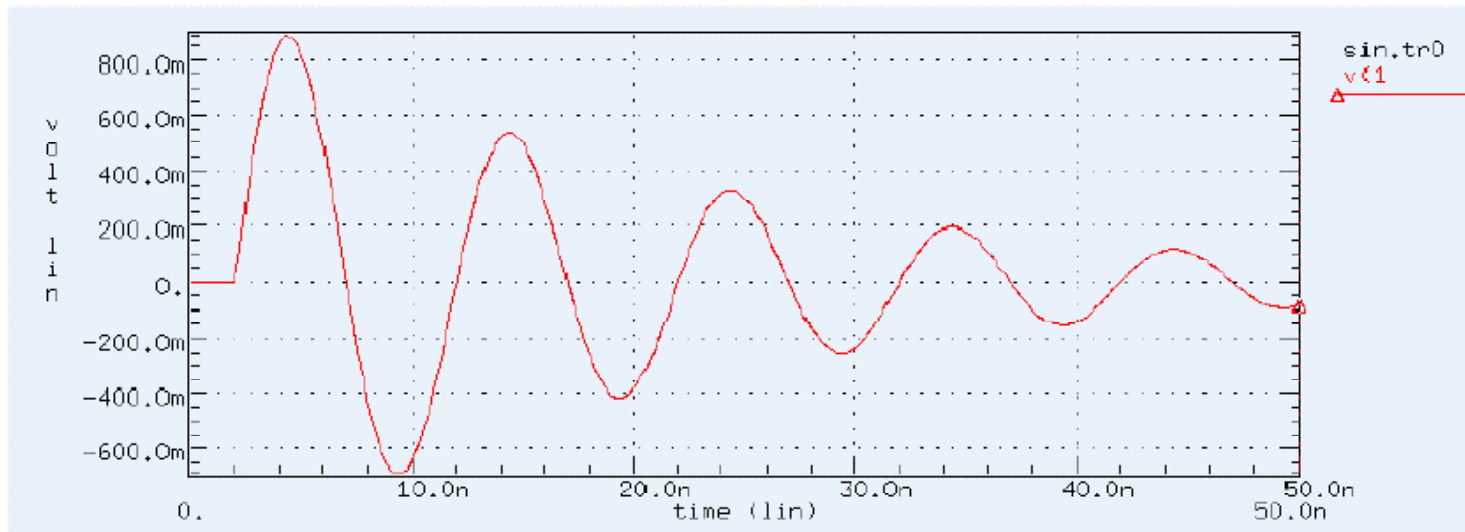***Vin 3 0 SIN ( 0V 1V 100Meg 2ns 5e7 )***




# Contents

---

- Introduction
- Simulation Input and Controls
- Waveform Instructions
- **Simulation Output**
- Appendix
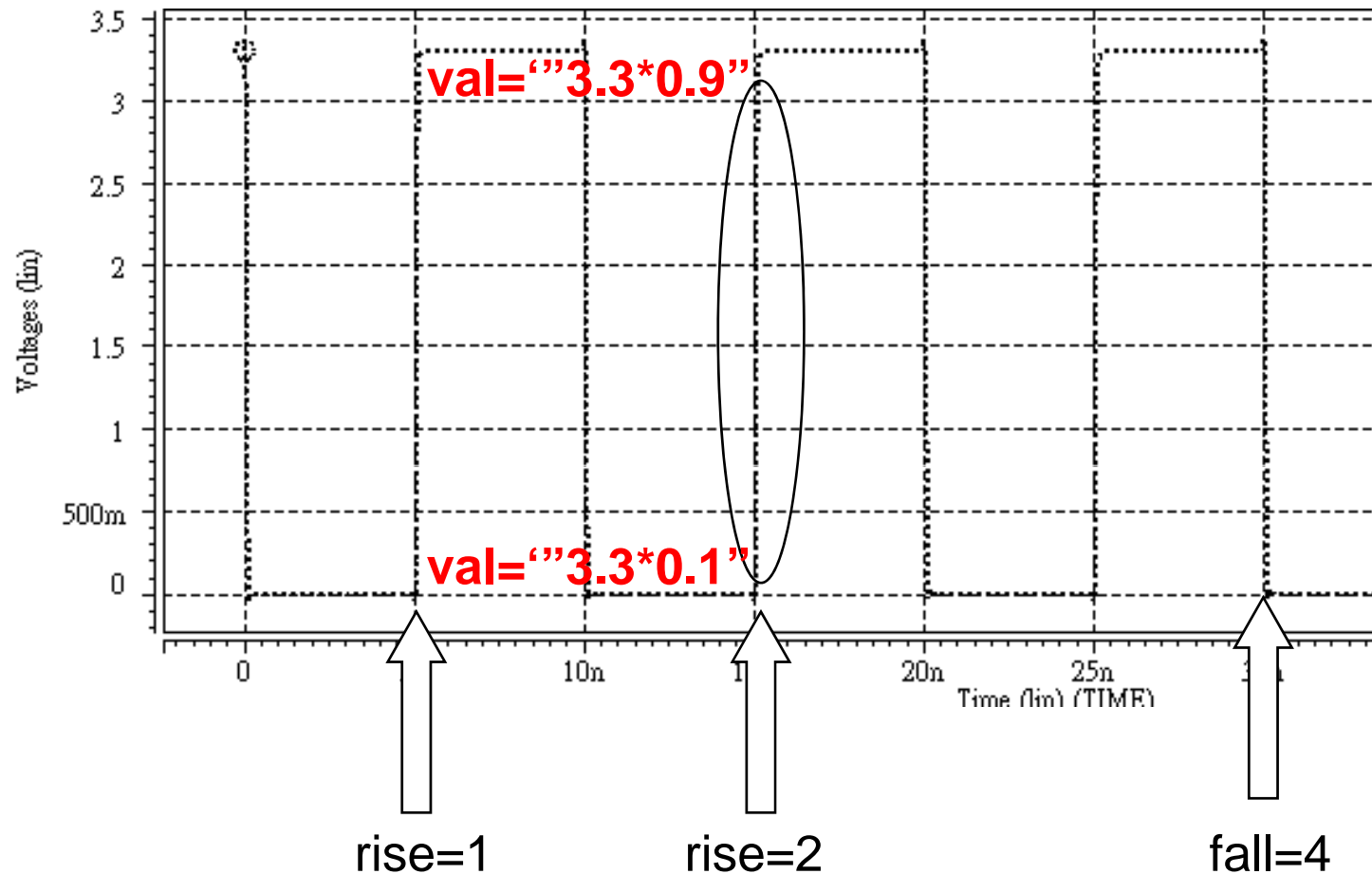
# Timing Measurement

```
.meas tran Tr trig v(out) val="3.3*0.1" rise=2 targ v(out) val="3.3*0.9" rise=2
```



# Example

SP檔

```
inv - 記事本
檔案(E) 編輯(E) 格式(O) 檢視(V) 說明(H)
***** inv *****
.global vdd vss
.subckt inv in out
MM0 out in vdd vdd pch w=3u l=350n
MM1 out in vss vss nch w=1u l=350n
.ENDS
.protect
.lib 'mm0355v.1' TT
.unprotect
vdd vdd 0 3.3
vss vss 0 0
vin in 0 pulse(0 3.3 0n .1n .1n 4.9n 10n)
x1 in out inv
.op
.options post
.tran 0.1n 50n
.meas tran Tr trig v(out) val="3.3*0.1" rise=2
+ targ v(out) val="3.3*0.9" rise=2
.end
```

mt0檔

```
inv - 記事本
檔案(E) 編輯(E) 格式(O) 檢視(V) 說明(H)
$DATA1 SOURCE='HSPICE' VERSION='X-2005.09'
.TITLE '***** inv *****'
tr          temper      alter#
6.738e-11   25.0000     1.0000
```

Simulate

Tr=6.738e-11 s

# Power

---

- Command :
- `.meas tran pwr avg power`
  - 在暫態分析中，量測整個電路的平均功率消耗
  - 結果顯示在\*.mt0檔

# Contents

---

- Introduction
- Simulation Input and Controls
- Waveform Instructions
- Simulation Output
- **Appendix**

# Appendix

---

