



1. CS stage

a) It's a typical CS stage amplifier, and we know it very well.

i) $S_{out}(f) = 4kTR_L = 4x(1.38x10^{-23})x300x600 = 9.9E-18 (V^2/Hz)$

ii) $\overline{V_{output,n}^2} = S_{out}(f) \times 1GHz = 9.9 nV^2 = (99u V_{rms})^2$

iii) $\overline{V_{output,n,RL}^2} = \frac{kT}{C} = 41.4 nV^2 = (0.2m V_{rms})^2$

b)

i) DC analysis

Size : W/L = 8um/0.18um.

Power : 2.3mW

```
***** transient analysis tnom= 25.000 temp= 27.000 *****
total_avg_pwr_uw= 2.2333k from= 0. to= 100.0000n
```

Output DC voltage : 1.05V

| node | =voltage | node | =voltage | node | =voltage |
|--------|----------|-------|-------------|--------|----------|
| +0:vdd | = 1.8000 | 0:vin | = 950.0000m | 0:vout | = 1.0556 |
| +0:vss | = 0. | | | | |


ii) AC analysis

At f=1kHz, gain=2(or 6dB), 3-dB bandwidth = 2.69GHz




iii) Noise analysis

Output noise PSD:

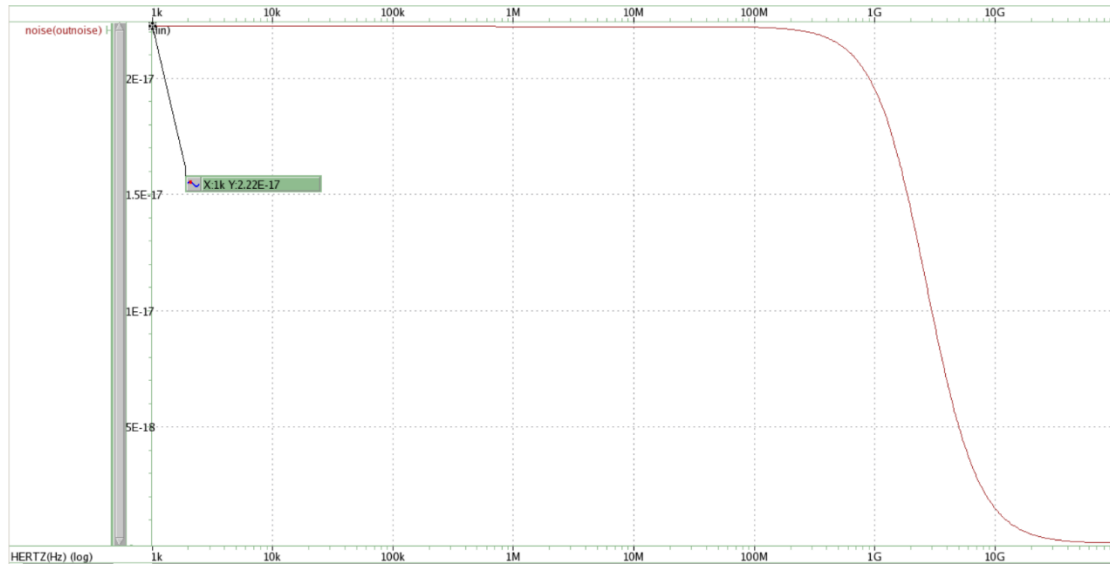

Integral of PSD

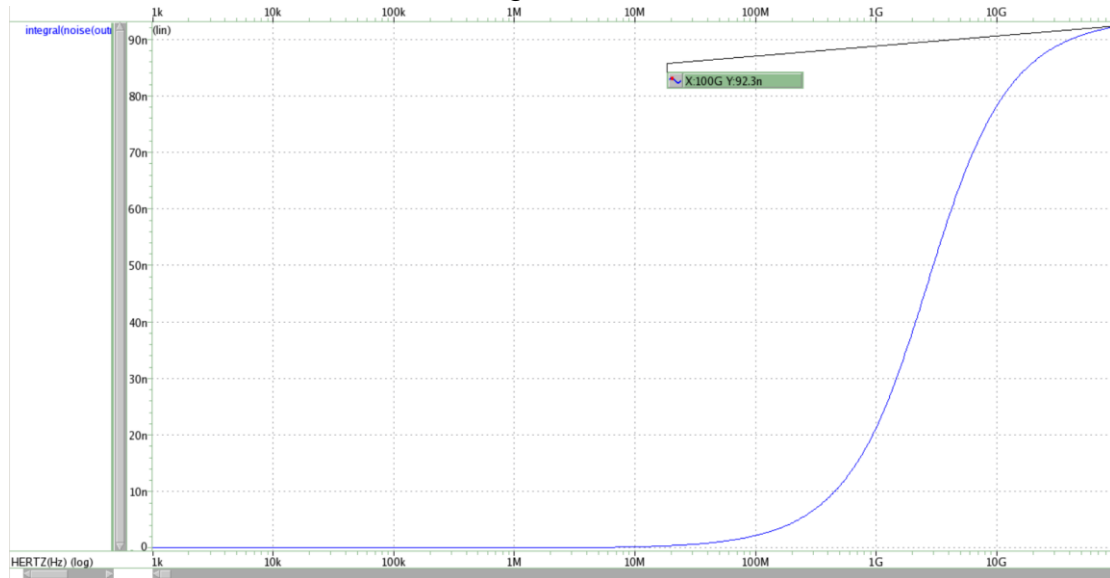

$$\overline{V_{output,n,total}^2} = 93.2 \text{ nV}^2$$

From a-iii, $\overline{V_{output,n,RL}^2} = 41.4 \text{ nV}^2$, the difference comes from the noise of M1.

We can get $\overline{V_{output,n,M1}^2} = (93.2 - 41.4) \text{ nV}^2 = 51.8 \text{ nV}^2 = (0.23 \text{ mV}_{rms})^2$

Lastly, $\overline{V_{input,n,total}^2} = \frac{93.2 \text{ nV}^2}{\text{gain}^2} = \frac{93.2 \text{ nV}^2}{2^2} = 23.3 \text{ nV}^2 = (0.15 \text{ mV}_{rms})^2$

2. CG stage

- a) gain = $g_{m1}R_D$
- b) output swing = $V_{DD} - V_{ov1} - V_{ov2}$
- c) By the textbook:

$$\text{input-referred noise voltage} = \left(\sqrt{4kT\gamma \frac{1}{g_{m1}} + 4kT \frac{1}{g_{m1}^2 R_D}} \right) V/\sqrt{\text{Hz}}^2$$

$$\text{input-referred noise current} = \left(\sqrt{4kT\gamma g_{m2} + 4kT \frac{1}{R_D}} \right) A/\sqrt{\text{Hz}}^2$$

d)

$g_{m1} = \sqrt{2 \mu n C_{ox} \left(\frac{W}{L}\right)_1 I_D} = \sqrt{2 \times 303 \frac{\mu A}{V^2} \cdot \frac{6}{0.18} \cdot 1 \text{mA}} = 4.5 \times 10^{-3}$
 $A_v \geq 3 \Rightarrow g_{m1} R_D \geq 3 \Rightarrow R_D \geq \frac{3}{4.5 \times 10^{-3}} = 667 \text{ (}\Omega\text{)}$
 $V_{ov1} = \sqrt{\frac{I_D}{\frac{1}{2} \mu n C_{ox} \frac{W}{L}}} = \sqrt{\frac{1 \text{mA}}{\frac{1}{2} (303 \frac{\mu A}{V^2}) \cdot \frac{6}{0.18}}} = 0.44 \text{ (V)}$
 $\text{swing} \geq 1.2 \text{ V} \Rightarrow V_{ov1} + V_{ov2} \leq 0.6 \text{ V} \Rightarrow V_{ov2} \leq 0.16 \text{ (V)}$
 $I_{D2} = \frac{1}{2} \mu n C_{ox} \left(\frac{W}{L}\right)_2 V_{ov2}^2 \Rightarrow 1 \text{mA} = \frac{1}{2} \cdot 303 \frac{\mu A}{V^2} \cdot \left(\frac{W}{L}\right)_2 (0.16)^2 \Rightarrow \frac{W}{L} = 258$
 取 $L_2 = 0.18 \mu\text{m} \Rightarrow W = 50 \mu\text{m}$

e)

i)

Gain = 3

**** small-signal transfer characteristics

| | | |
|------------------------------|---|----------|
| v(vout)/vin | = | 3.0332 |
| input resistance at vin | = | 308.5876 |
| output resistance at v(vout) | = | 989.3366 |

DC current through Vin = -5 uA, which is small.

| subckt | 0:vin | 0:vbn1 | 0:vbn2 | 0:vdd | 0:vss |
|---------|-----------|--------|-----------|------------|-----------|
| element | 0:vin | 0:vbn1 | 0:vbn2 | 0:vdd | 0:vss |
| volts | 250.0000m | 1.1700 | 600.0000m | 1.8000 | 0. |
| current | -5.5330u | 0. | 0. | -703.8386u | 709.3716u |
| power | 1.3832u | 0. | 0. | 1.2669m | 0. |

Bias current < 1mA, output swing = 1.8 - (0.387+0.088) = 1.33 V

```

subckt
element 0:m1      0:m2
model   0:n_18.1 0:n_18.1
region  Saturati Saturati
id      703.8386u 709.3716u
ibs     -172.6252a -1.477e-19
ibd     -658.8887a -1.2513f
vgs     920.0000m 600.0000m
vds     705.3936m 250.0000m
vbs     -250.0000m 0.
vth     532.9514m 511.1554m
vdsat   273.0098m 133.2226m
vod     387.0486m 88.8446m
beta    11.6024m 98.4985m
gam_eff 514.0252m 507.4467m
gm      2.5766m 8.5836m

```

ii) Bias point: $V_{bn1}=1.17\text{ V}$, $V_{bn2}=0.6\text{ V}$, $V_{in,DC}=0.25\text{ V}$
Power: 1.3mW

```

***** transient analysis tnom= 25.000 temp= 27.000 *****
total_avg_pwr_uw= 1.2669k from= 0. to= 100.0000n

```

Output DC voltage: 955mV

```

+0:vbn1 = 1.1700 0:vbn2 = 600.0000m 0:vdd = 1.8000
+0:vin  = 250.0000m 0:vout = 955.3936m 0:vss = 0.


```

iii) AC kHz, analysis
(x,y) = (1kHz, 9.64dB)



iv) NOISE analysis

output noise PSD

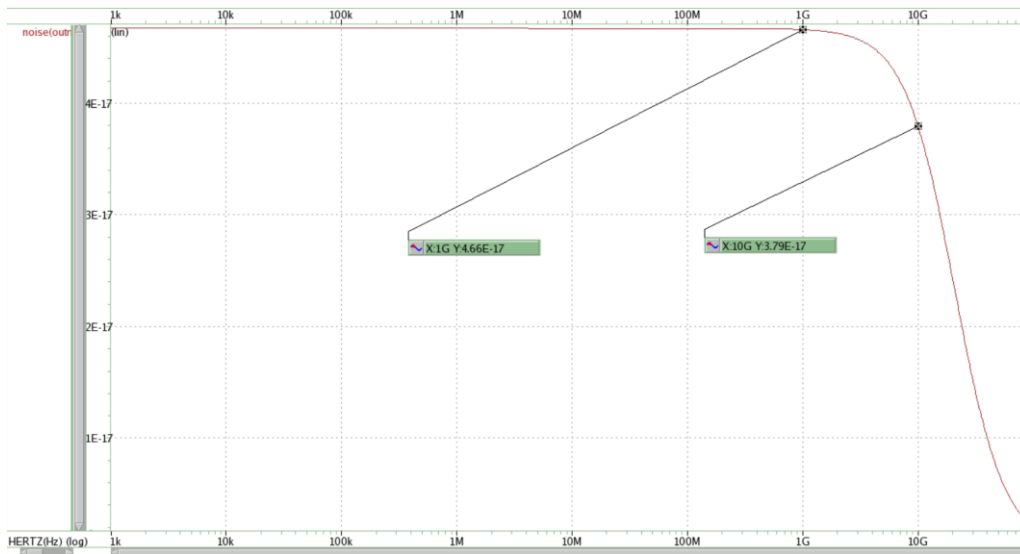

At 1GHz, (x,y)=(1GHz , 4.66E-17); at 10GHz, (x,y)=(10GHz, 3.8E-17)

Input noise PSD



At 1GHz, (x,y)=(1GHz , 5.1E-18); at 10GHz, (x,y)=(10GHz, 5.1E-18)


From 2-d, with $g_{m1}=2.57m$, $R_D=1200$ ohm

$$\overline{V_{input,n,total}^2} = 4kT\gamma \frac{1}{g_{m1}} + 4kT \frac{1}{g_{m1}^2 R_D} = 6.38 \times 10^{-18} V^2$$

The noise derived from 2-d's equation is larger. Discrepancy may come from:

- 1) There is still DC current flowing through V_{in} , so the formula in 2-d cannot entirely represent the noise behavior.
- 2) Second-order effect, such as body effect, causes the error.

計算題:

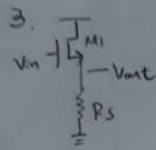

$$A_v = \frac{g_m(R_D \parallel r_o)}{1 + g_m(R_S \parallel r_o)} = \frac{g_m R_S}{1 + g_m R_S} \text{ as } r_o \rightarrow \infty$$


$$\overline{V_{out,RS,n}^2} = \overline{I_{RS,n}^2} \cdot (R_S \parallel 1/g_{m1})^2 = 4kT \frac{1}{R_S} \cdot (R_S \parallel 1/g_{m1})^2$$

$$\overline{V_{in,RS,n}^2} = \frac{1}{A_v^2} \overline{V_{out,RS,n}^2} = \left(\frac{1 + g_m R_S}{g_m R_S} \right)^2 4kT \frac{1}{R_S} \left(\frac{R_S}{1 + g_m R_S} \right)^2 = 4kT \frac{1}{R_S} \frac{1}{g_{m1}^2}$$

$$\therefore \overline{V_{in,total,n}^2} = \overline{V_{in,RS,n}^2} + \overline{V_{in,M1,n}^2}$$

$$= 4kT \frac{1}{R_S} \left(\frac{1}{g_{m1}} \right)^2 + 4kT \gamma \frac{1}{g_{m1}} \Rightarrow \boxed{4kT \frac{1}{g_{m1}} \left(\gamma + \frac{1}{g_{m1} R_S} \right) \left(\frac{1}{\sqrt{\text{Hz}}} \right)}$$

4. (1) w/o. RP
Consider M2

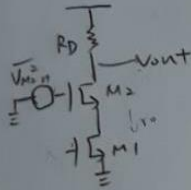

1° M2's input 到 Vout 的 voltage gain gainM2 is

$$| \text{gain } M_2 | = \frac{g_{m2} r_{o2}}{R_2} (R_D \parallel R_2)$$

$$\text{where } R_2 = [1 + g_{m2} r_{o2}] r_{o1} + r_{o2} \approx g_{m2} r_{o1} r_{o2}$$

$$\Rightarrow | \text{gain } M_2 | \approx \frac{g_{m2} r_{o2}}{g_{m2} r_{o1} r_{o2}} (R_D \parallel g_{m2} r_{o1} r_{o2}) = \frac{1}{r_{o1}} (R_D \parallel g_{m2} r_{o1} r_{o2})$$

$$\therefore M_2 \text{ 在 } V_{out} \text{ 造成的 noise } \overline{V_{out,M2,n}^2} = \overline{V_{M2,n}^2} \cdot (\text{gain } M_2)^2$$

此 noise refer 回 M1's input 的 input-refered noise

$$\text{為 } \overline{V_{in,M2,n}^2} = \overline{V_{out,M2,n}^2} \cdot \left(\frac{1}{\text{gain } M_1} \right)^2 = \overline{V_{M2,n}^2} \left(\frac{\text{gain } M_2}{\text{gain } M_1} \right)^2$$

$$(\text{gain } M_1)^2 = (g_{m1} \cdot (R_D \parallel g_{m2} r_{o1} r_{o2}))^2$$

$$\therefore \overline{V_{in,M2,n}^2} = \overline{V_{M2,n}^2} \frac{(R_D \parallel g_{m2} r_{o1} r_{o2})^2 / r_{o2}^2}{g_{m1}^2 \cdot (R_D \parallel g_{m2} r_{o1} r_{o2})^2} = \left(\frac{1}{g_{m1} r_{o1}} \right)^2$$

$$\text{when } r_o \rightarrow \infty, \overline{V_{in,M2,n}^2} \rightarrow 0$$

$$2^\circ R_D \text{ 造成的 noise} = \overline{I_{RD,n}^2} \cdot R_D^2 \Rightarrow \overline{V_{out,RD,n}^2} = 4kT R_D$$


$$3^\circ M_1 \text{ 可直接 refer 至 input} \Rightarrow \overline{V_{in,M1,n}^2} = 4kT \gamma \frac{1}{g_{m1}}$$

$$\therefore \overline{V_{in,total,n}^2} = \overline{V_{in,M1,n}^2} + \overline{V_{in,M2,n}^2} + \overline{V_{in,RD,n}^2}$$

$$= 4kT \gamma \frac{1}{g_{m1}} + 0 + \frac{4kT R_D}{(g_{m1} R_D)^2} \Rightarrow \boxed{4kT \left(\frac{\gamma}{g_{m1}} + \frac{1}{g_{m1}^2 R_D} \right) \left(\frac{1}{\sqrt{\text{Hz}}} \right)}$$

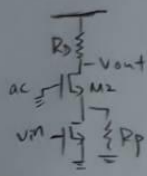2) with R_p .

1° we need to calculate gain M_1 , gain M_2 first.



For gain M_1 , 小信号分析 V_{in} 造成 M_2 current 的 变化 Δ

$$(g_m V_{in}) \frac{R_p}{1/g_{m2} + R_p} = \frac{V_{in} \cdot g_{m1} g_{m2} R_p}{1 + g_{m2} R_p}$$


$$\text{For } V_{out} = R_D \cdot \left(\frac{V_{in} g_{m1} g_{m2} R_p}{1 + g_{m2} R_p} \right) \therefore \text{gain } M_1 = \frac{R_D g_{m1} g_{m2} R_p}{1 + g_{m2} R_p}$$

And $\text{gain } M_2 = \frac{R_D}{1/g_{m2} + R_p}$ (the gain of the CS stage with source degeneration)

$$\Rightarrow \frac{\text{gain } M_2}{\text{gain } M_1} = \frac{R_D / (1/g_{m2} + R_p)}{R_D g_{m1} g_{m2} R_p / (1 + g_{m2} R_p)} = \frac{1}{g_{m1} R_p}$$

$$\therefore \overline{V_{in, M2, n}} = \overline{V_{M2, n}} \left(\frac{\text{gain } M_2}{\text{gain } M_1} \right)^2 = 4kT \gamma \frac{1}{g_{m1} R_p}$$

2° R_p .

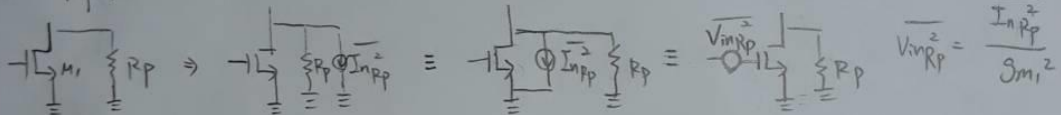


3° R_D

$$\overline{V_{in, RD, n}} = \overline{V_{out, RD, n}} \cdot \left(\frac{1}{\text{gain } M_1} \right)^2 = 4kT R_D \cdot \left(\frac{1 + g_{m2} R_p}{R_D g_{m1} g_{m2} R_p} \right)^2 = 4kT \frac{1}{R_D} \left(\frac{1 + g_{m2} R_p}{g_{m1} g_{m2} R_p} \right)^2$$

$$\therefore \overline{V_{in, total, n}} = \overline{V_{in, M1, n}} + \overline{V_{in, M2, n}} + \overline{V_{in, Rp, n}} + \overline{V_{in, RD, n}}$$

$$\Rightarrow \sqrt{4kT \gamma \frac{1}{g_{m1}} + 4kT \gamma \frac{1}{g_{m2}} \left(\frac{1}{g_{m1} R_p} \right)^2 + 4kT \frac{1}{R_p} \frac{1}{g_{m1}^2} + 4kT \frac{1}{R_D} \left(\frac{1 + g_{m2} R_p}{g_{m1} g_{m2} R_p} \right)^2} \quad (\sqrt{\text{Hz}}) \quad \#$$

5.

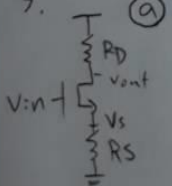

For R_S

$$\overline{V_{out, RS, n}} = \overline{I_{nRS}} \left(\frac{R_S}{R_S + 1/g_{m1}} \right)^2 \cdot R_D^2 = \overline{I_{nRS}} \frac{g_{m1} R_S}{(1 + g_{m1} R_S)^2} R_D^2$$

$$\therefore \overline{V_{in, RS, n}} = \left(\frac{1 + g_{m1} R_S}{g_{m1} R_D} \right)^2 \overline{I_{nRS}} \left(\frac{g_{m1} R_S R_D}{1 + g_{m1} R_S} \right)^2 = \frac{4kT}{P_S} \cdot R_S = 4kT R_S$$

$$\therefore \overline{V_{in, total}} \Rightarrow \sqrt{4kT \gamma \frac{1}{g_{m1}} + 4kT R_S + \frac{4kT R_D}{(g_{m1} R_D)^2} (1 + g_{m1} R_S)^2} \quad (\sqrt{\text{Hz}}) \quad \#$$

(b) If $4kT R_S = 4kT \gamma \frac{1}{g_{m1}} \Rightarrow R_S g_{m1} = \gamma$

$$\frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{ov}^2 = \frac{V_S}{R_S} \Rightarrow \frac{1}{2} g_{m1} V_{ov} = \frac{V_S}{R_S} \quad (\because g_{m1} = \mu_n C_{ox} \frac{W}{L} V_{ov})$$

$$\therefore \frac{V_S}{V_{ov}} = \frac{g_{m1} R_S}{2} = \frac{1}{2} \gamma$$