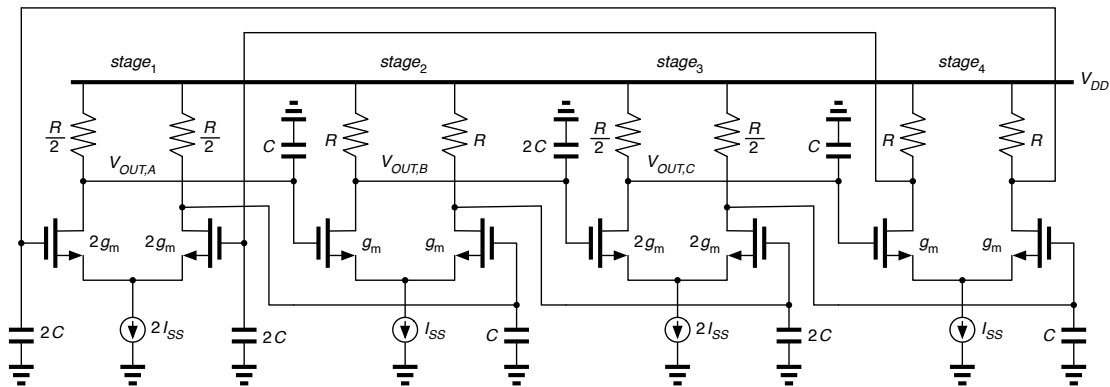


Homework II – due date: 05/22 (Friday) 10AM (No late homework!!!)

- Please submit your report with the correct file name (HW3_105061703.pdf or HW3_105061703.doc) to our course website (iLMS system) by the deadline. **No hardcopy will be accepted this time.**
- Please replace 105061703 with your own student ID.
- Use cic018.l for simulations. Do not change any of the model parameters.

- 1) Neglect other capacitances. In the following circuit, stage₁ and stage₃ are twice “wider” than stage₂ and stage₄. Therefore, compared to stage_{2,4}, a) the differential pairs of stage_{1,3} exhibit twice larger g_m , b) the load resistance is twice smaller, c) the input capacitance is twice larger (as shown in the figure), and d) the tail current is twice larger.



- 1a) Plot the small-signal transfer functions (Bode plot – both magnitude and phase) for stage₁ and stage₂. Indicate the low-frequency values (both magnitude and phase) and the locations of poles.
- 1b) Determine the minimum required low-frequency gain per stage that guarantees oscillation.
- 1c) Calculate the oscillation frequency in terms of R and C . How much additional phase shift do stage₁ and stage₂ contribute at the oscillation frequency?
- 1d) If the circuit is at the edge of oscillation (the swings are quite small), and the oscillation swing of $V_{OUT,A}$ is “ A_0 ”, what is the oscillation swing of $V_{OUT,B}$?
- 2) Following the previous question, use **HSpice** to design the ring oscillator with the following specifications and conduct the necessary simulations.
 $V_{DD}=1.8$ V and common-mode of of 1.0 V for all the oscillation signals. Use ideal current sources of 500 μ A for I_{SS} , (and 1 mA for $2 \times I_{SS}$). Design the oscillator with an operating frequency of 2 GHz (by adding proper values of C and $2C$).

- 2a)** Design each stage with the low-frequency gain of 6 times the value calculated in **1b)**. Report the capacitance added and the transistor sizes used. Plot ac response (Bode plot – both magnitude and phase) for stage₁ and stage₂. Indicate the low-frequency values (both magnitude and phase) and the locations of poles.
- 2b)** Connect all four stages into a ring for oscillation. Perform transient simulations, and make sure that the waveforms settle. Use “.option accurate” in your simulation. Set the time step to less than 1 ps.
- 2c)** Plot all 8 oscillation waveforms into one figure (on the same row) for at least 2 but no more than 3 periods in steady state. Mark the oscillation amplitudes of stage₁ and stage₂. Measure the additional phase shift stage₁ and stage₂ contribute.
- 2d)** Comment (with concrete arguments) on any difference between the simulation results and the prediction from analysis (from previous questions).
- 3)** Design a VCO based on the previous question. But this time, make all stages the same (instead of stage₁ and stage₃ twice “wider” than stage₂ and stage₄).
- Use the same size for all stages.
 - Change the load resistors using PMOS transistors that operate in triode region.
 - Use ideal current sources of 500 μA for I_{SS} .
 - Design the oscillator so that with a control voltage of 0.6 V, the operating frequency is **300 MHz**, and the common mode is 1.4 V for all the oscillation signals. You may need to add additional capacitors for C.
 - Size the NMOS transistors large enough so that the oscillation amplitude is large and the tail current steers fully when oscillating.
- 3a)** Report the transistor sizes (both NMOS and PMOS) and the capacitor size.
- 3b)** Plot VCO frequency vs. V_{ctrl} (for V_{ctrl} from 0 V to 1.0 V with step of 0.1 V). What is the V_{ctrl} value for 500 MHz? Estimate the VCO gain (K_{VCO}) at frequency of **500 MHz**.
- 3c)** Plot all 8 oscillation waveforms (at 500 MHz) into one figure (on the same row) for at least 2 but no more than 3 periods in steady state. Measure the phase difference between stage₄ and stage₁, as well as between stage₁ and stage₂.