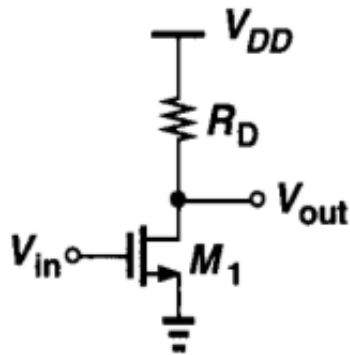

EE4280 Lecture 1: Nonlinearity

Ping-Hsuan Hsieh (謝秉璇)
Delta Building R908
EXT 42590
phsieh@ee.nthu.edu.tw


Nonlinearity

Nonlinear characteristic deviates from a straight line as the input swing increases



Nonlinearity

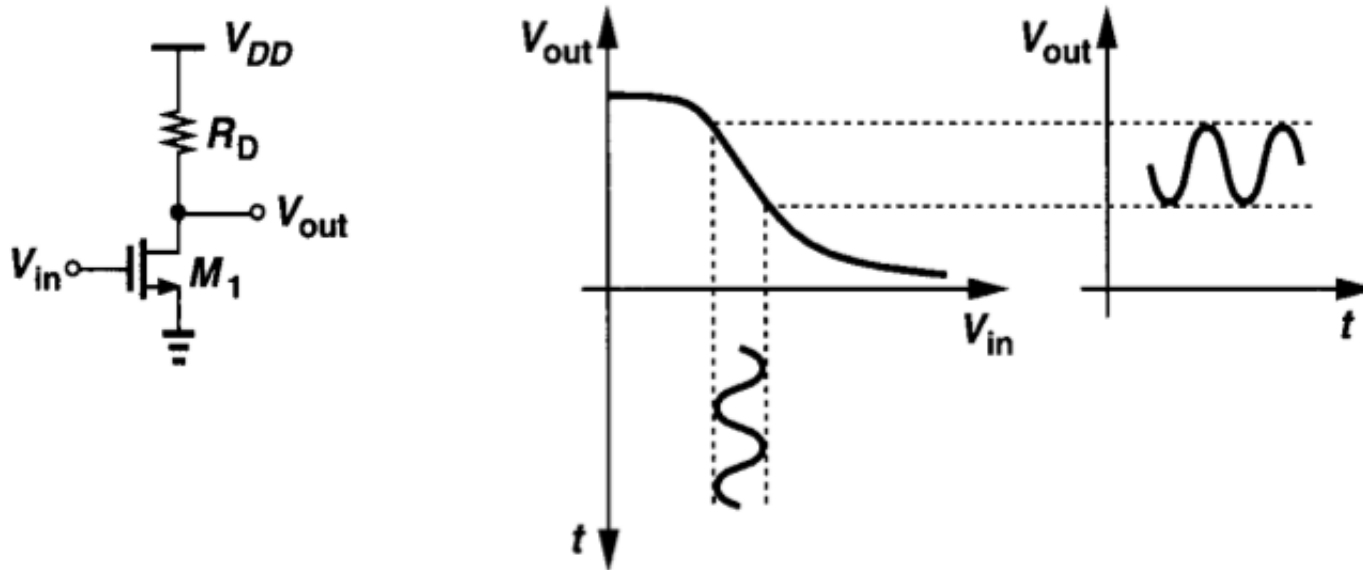
Nonlinear characteristic deviates from a straight line as the input swing increases



- ◆ For small input swing, the output is a reasonable replica of the input
 - Small-signal gain is related to the slope at a given bias point

Nonlinearity

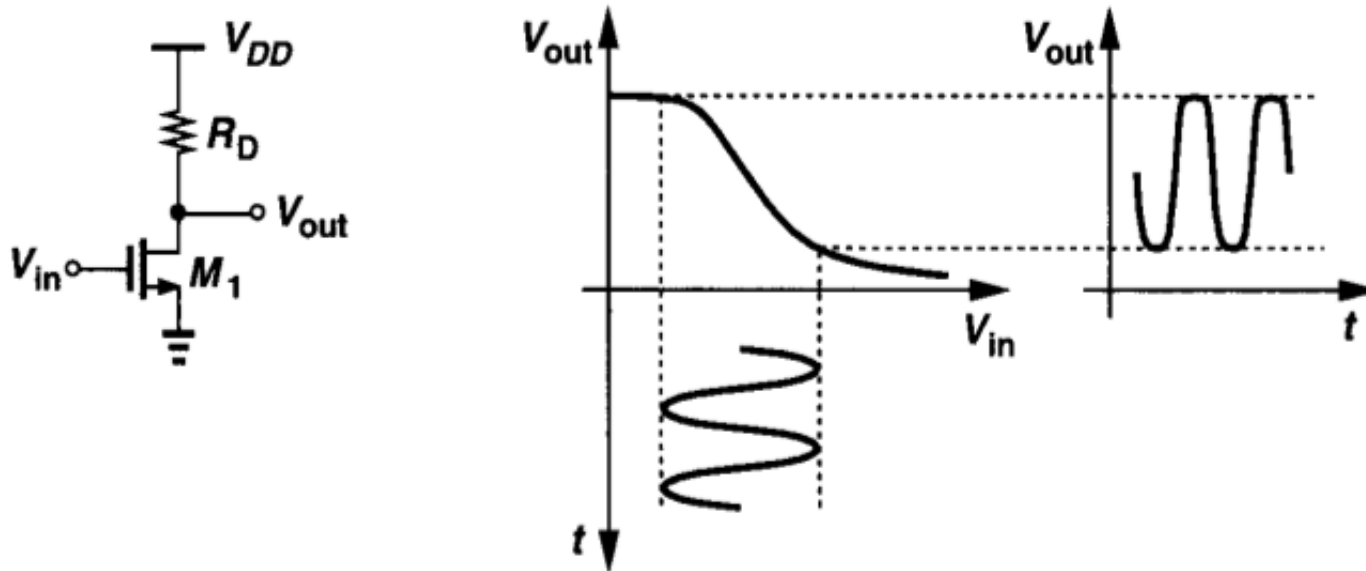
Nonlinear characteristic deviates from a straight line as the input swing increases



- ◆ For small input swing, the output is a reasonable replica of the input
- ◆ For large input swings, most amplifiers experience gain compression (instead of expansion)
 - The output exhibits “saturated” levels due to supply voltage or bias current

Nonlinearity

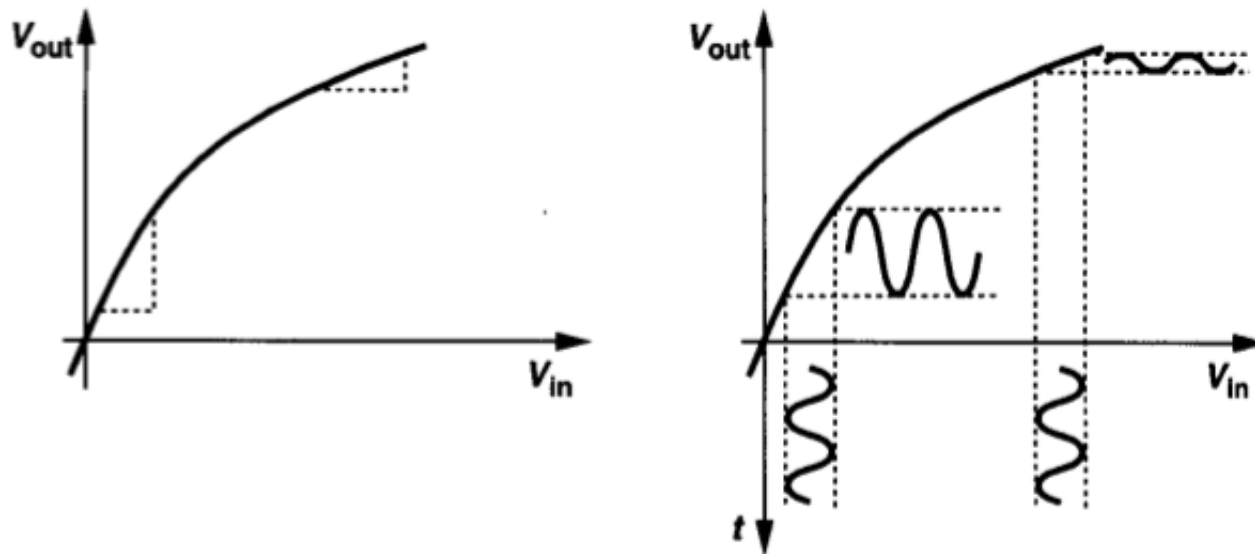Can be viewed as variation of the slope (small-signal gain) with the input level (common-mode)




To Quantify Nonlinearity (I)

- ◆ Taylor Expansion

- ◆ Maximum deviation from an ideal straight line

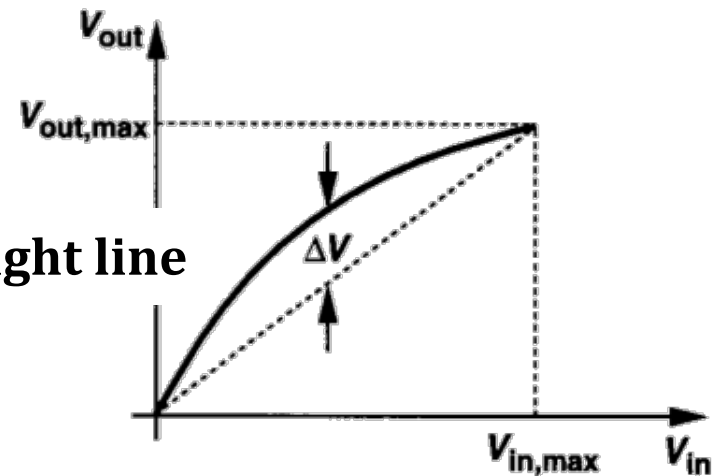$\Delta V / V_{out,max}$ for certain $V_{in,max}$



To Quantify Nonlinearity (II)

- ◆ **A single tone test**

$$\Delta x = A \cos \omega_1 t$$

$$\Delta y = \alpha_1 A \cos \omega_1 t + \alpha_2 A^2 \cos^2 \omega_1 t + \alpha_3 A^3 \cos^3 \omega_1 t + \dots$$

- ◆ **Total harmonic distortion**

$$THD =$$

To Quantify Nonlinearity (III)

- ◆ 1-dB compression point


The signal at ω_1

$$\Delta y = \left(\alpha_1 A + \frac{3}{4} \alpha_3 A^3 \right) \cos \omega_1 t$$

The input level where the gain has dropped by 1dB

Nonlinearity of Differential Circuits (I)

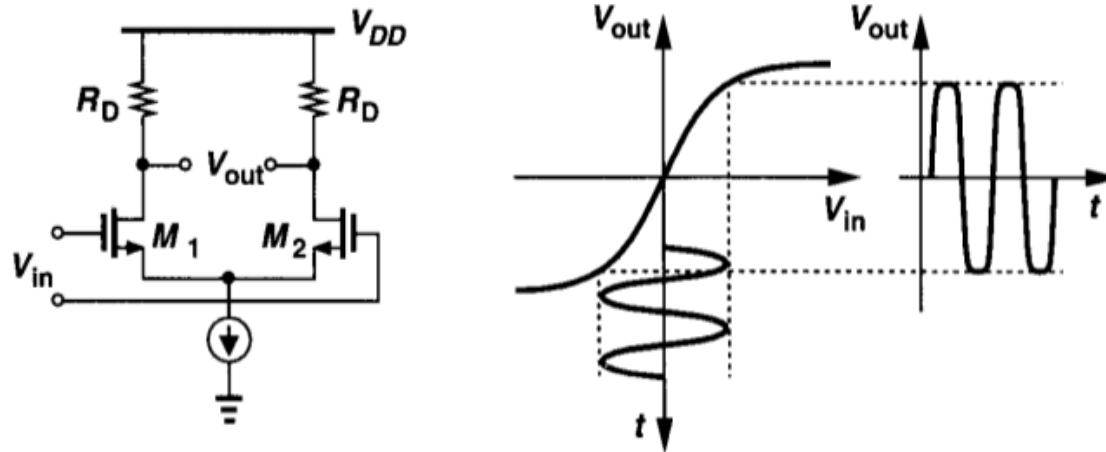- ◆ Differential circuits exhibit an “odd-symmetric” input/output characteristics, i.e., $f(-x) = -f(x)$




- ◆ For the Taylor expansion to be an odd function, all the even-order terms must be zero.

$$\Delta y = \alpha_1 \Delta x + \alpha_3 (\Delta x)^3 + \alpha_5 (\Delta x)^5 + \dots$$

- ◆ **A differential circuit produces no even-order harmonics**

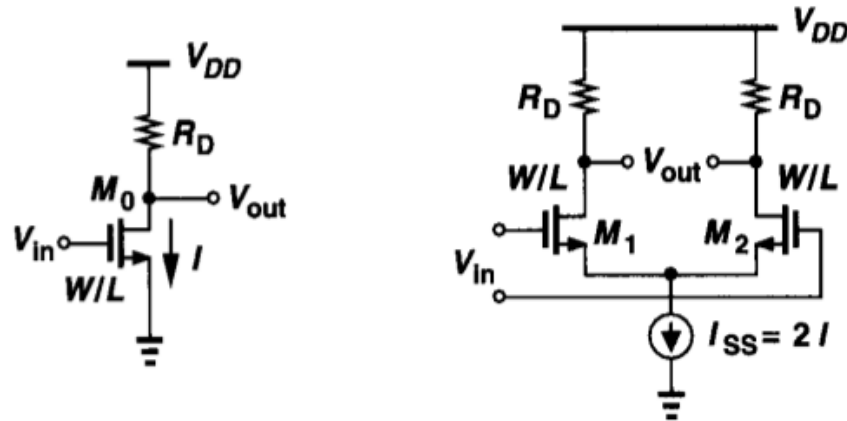Nonlinearity in Differential Circuits (II)



- ◆ Single-ended and differential amplifiers with the same voltage gain

$$|A_v| \approx g_m R_D$$

$$= \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) R_D$$

- ◆ For the single-ended case:

$$V_{DD} - V_{out} = I_D \cdot R_D$$


With $V_{in} = V_{GS} + V_m \cos \omega t$

We have $V_{DD} - V_{out} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} + V_m \cos \omega t - V_{th})^2 R_D$

Nonlinearity for Differential Circuits (III)

- ◆ For the single-ended case:
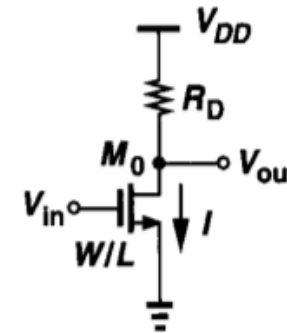
$$V_{DD} - V_{out} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} + V_m \cos \omega t - V_{th})^2 R_D$$



- ◆ The second harmonic distortion:

$$\frac{A_{HD2}}{A_F} =$$


Nonlinearity for Differential Circuits (IV)

- ◆ For the differential amplifier:

$$\Delta V_{out} = (I_{D1} - I_{D2})R_D$$

From Chapter 4:
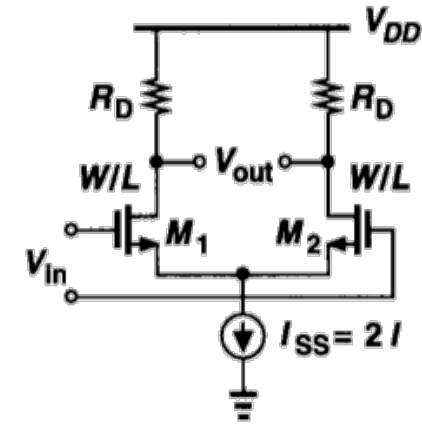
$$= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \Delta V_{in} \sqrt{4(V_{GS} - V_{th})^2 - \Delta V_{in}^2}$$



- ◆ The third harmonic distortion:

$$\frac{A_{HD3}}{A_F} \approx$$


Effect of Negative Feedback on Nonlinearity (I)

- ◆ Negative feedback makes the closed-loop gain relatively independent of the op amp's open-loop gain → **Gain Desensitization**
- ◆ Nonlinearity can be viewed as small-signal gain variation with input level → suppressed by negative feedback as well

- ◆ Consider an open-loop gain of

$$\text{With } x(t) = V_m \cos \omega t$$

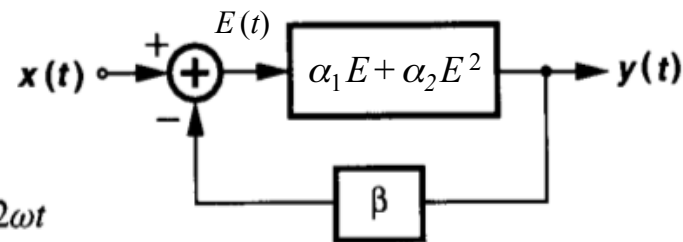and if the output can be approximated as $y \approx a \cos \omega t + b \cos 2\omega t$



$$E(t) =$$

$$y(t) =$$

Effect of Negative Feedback on Nonlinearity (II)

$$\text{With } \begin{cases} a = (\alpha_1 - \alpha_2 \beta b)(V_m - \beta a) \\ b = -\alpha_1 \beta b + \frac{\alpha_2 (V_m - \beta a)^2}{2} \end{cases}$$

◆ **The second harmonic distortion:** $\frac{A_{HD2}}{A_F} = \frac{b}{a} =$


◆ **Compared to the open-loop case:**

With the same input swing:

With the same output swing:

Linearization Technique (I)

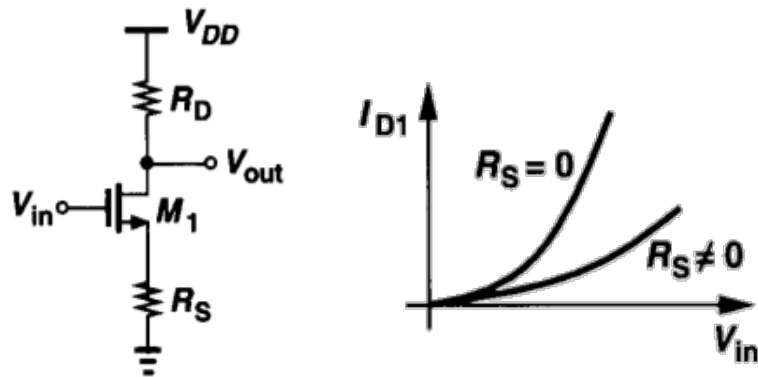- ◆ To reduce the dependence of gain on input level
 - To reduce the dependence of gain on transistor bias current
- ◆ Source degeneration effectively reduce the signal swing on V_{GS}



$$\frac{\Delta I_D}{\Delta V_{in}} =$$


- ◆ Trade-off between linearity, noise, power dissipation, and gain

Linearization Technique (III)

◆ Post correction

- A common-source amplifier is in fact a voltage-to-current converter followed by a current-to-voltage converter
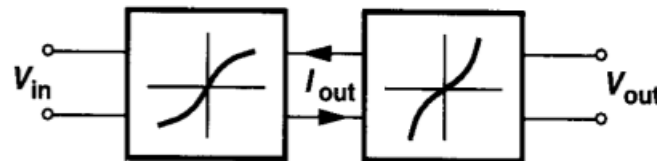
$$\Delta V_{in} \rightarrow \Delta I_D \rightarrow \Delta V_{out}$$




For $\Delta I_D = f(\Delta V_{in})$

If we have $\Delta V_{in} = A \cdot f^{-1}(\Delta I_D)$

Linearization Technique (IV)

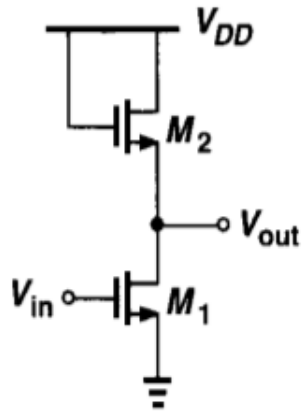- ◆ **Common-source with diode-connected load**



- ◆ **Some of the design considerations include**

- Body-effect that degrades the linearity
- Limited voltage headroom

