

---

# EE4280 Lecture 2: Mismatch


---

**Ping-Hsuan Hsieh (謝秉璇)**  
Delta Building R908  
EXT 42590  
[phsieh@ee.nthu.edu.tw](mailto:phsieh@ee.nthu.edu.tw)
 
# Mismatch (I)

Due to uncertainties in each step of the manufacturing process  
For identical devices, random and microscopic variations lead to

- Mismatches in physical dimension
- Mismatches in threshold voltages



**To study mismatch of devices:**

1. Identify and formulate the mechanisms leading to mismatches
2. Analyze the impact on circuit performance
  - Techniques to suppress the impact from mismatches


## Mismatch (II)

For a transistor operating in saturation region

$$I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{GS} - V_{th})^2$$

All mismatches decreases as the **area** of the transistor  $WL$  increases

 - Random variations experience greater averaging




Can be extended to other device parameters

$$\Delta V_{TH} = \frac{A_{VTH}}{\sqrt{WL}} \quad \Delta \left( \mu C_{ox} \frac{W}{L} \right) = \frac{A_K}{\sqrt{WL}}$$

 
# DC Offset

With perfect symmetry  $V_{out} = 0$  when  $V_{in} = 0$

With mismatches  $V_{OS,out} \neq 0$  when  $V_{in} = 0$




 - May saturate the following stages
- Degrade the precision with which signals can be measured


 
# DC Offset of a differential pair

- ◆ To calculate the input-referred offset



$$V_{out} = 0 \Rightarrow I_D R_D = (I_D + \Delta I_D)(R_D + \Delta R)$$

$$V_{OS,in} = V_{GS1} - V_{GS2}$$

## DC Offset of a differential pair


- ◆ To calculate the input-referred offset

$$V_{OS,in} = \frac{V_{GS} - V_{TH}}{2} \left[ \frac{\Delta R_D}{R_D} + \frac{\Delta(W/L)}{(W/L)} \right] - \Delta V_{TH}$$

- Depends on device mismatches and **bias conditions**
- ◆ **Offset can be viewed as low-frequency noise**
  - Similar to noise, larger  $g_{m1}$  suppresses input-referred offset voltage
- ◆ **Variance:**
  
- ◆ **Consider only transistor mismatch, for  $I_{D1}=I_{D2}$**
 
# Current mismatch in current mirror

- ◆ Consider nominally identical transistors ( $M_1$  and  $M_2$ ) and neglect  $r_o$



$$I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{GS} - V_{th})^2$$
$$= f\left(\mu C_{ox}, \frac{W}{L}, V_{GS}, V_{th}\right)$$


$$\Delta y = \frac{\partial f}{\partial x_1} \Delta x_1 + \frac{\partial f}{\partial x_2} \Delta x_2 + \dots$$

$$\Delta I_D = \frac{\partial I_D}{\partial (W/L)} \Delta \left(\frac{W}{L}\right) + \frac{\partial I_D}{\partial (V_{GS} - V_{TH})} \Delta (V_{GS} - V_{TH})$$


- ◆ From output current point of view
  - Smaller  $g_m$  required to suppress the mismatch
  - The same for noise current
 
# Offset Cancellation Techniques

- ◆ Add two voltage sources in series with  $V_{out}$



 
- ◆ Use output series capacitors  $C_1$  and  $C_2$ 
  - With stored charges that corresponds to  $V_{OS,out}$





 
# Output Offset Storage

- ◆ How to store the required charge on  $C_1$  and  $C_2$ ?


 
# Output Offset Storage

- ◆ A dedicated offset cancellation period required
  - Controlled by signal  $CK$
  - Design of switches  $\rightarrow$  may cause additional mismatch




- ◆  $V_{OS,out}$  may saturate the amplifier, degrading the voltage gain


 
# Input Offset Storage

- ◆ How to store the required charge on  $C_1$  and  $C_2$ ?




$$V_{OS, in} =$$

- ◆ Allows larger  $A_V$
- ◆ Still subject to switches mismatch
- ◆ Additional capacitors in the signal path
 
# Offset Cancellation Techniques


- ◆ To avoid capacitors in the signal path



- ◆ How to generate  $V_1$  for offset cancellation?

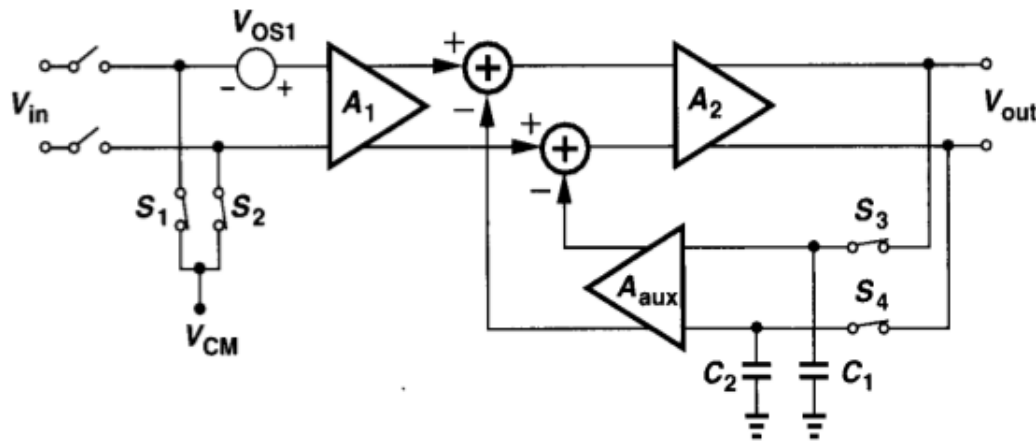
# Offset Cancellation Techniques

- ◆ Add an additional stage  $A_2$  and apply negative feedback


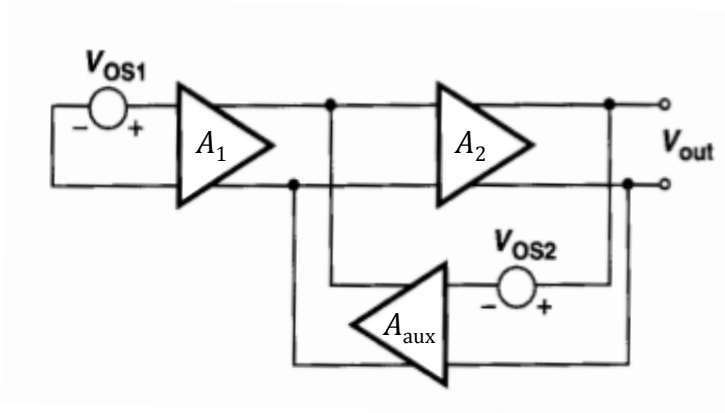
# Offset Cancellation Techniques


- ◆ If we further consider the offset in  $A_{aux}$



- ◆ For mismatch in charge injection when turning  $S_3$  and  $S_4$  OFF
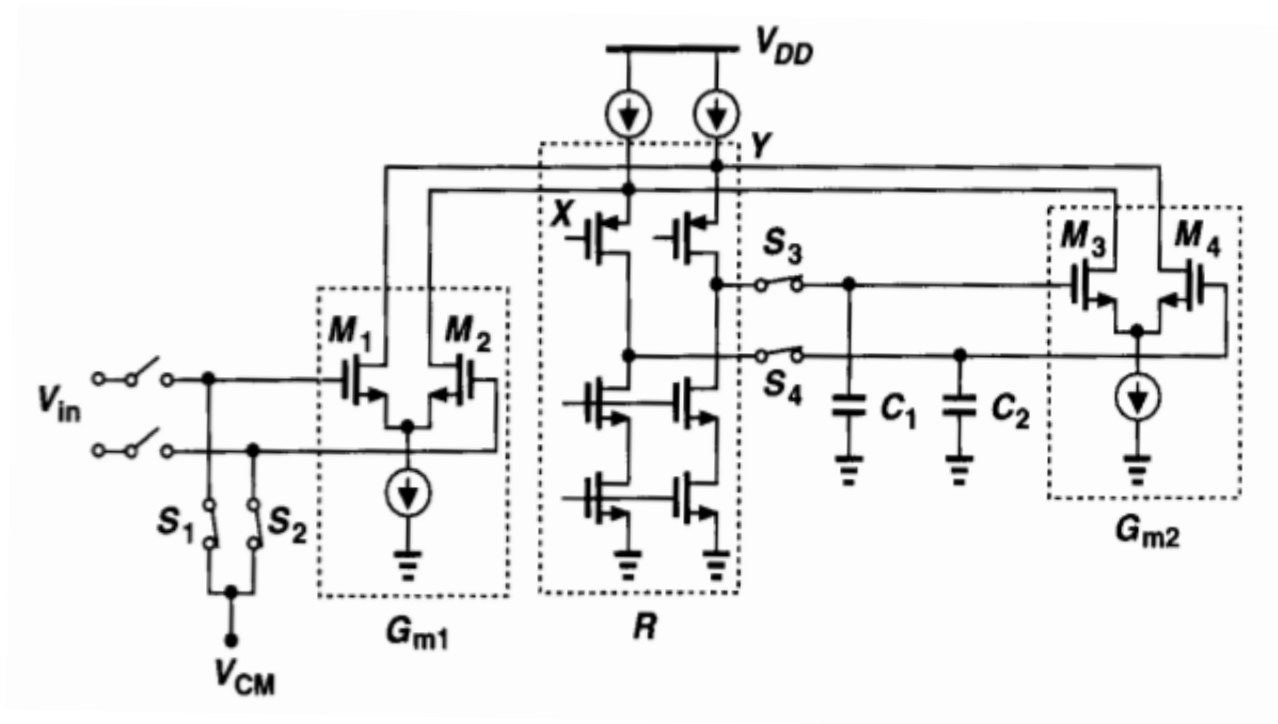
# Offset Cancellation Techniques

- ◆ The additional stage  $A_2$  may not be allowed
- ◆ How to achieve “voltage addition”?





# Reduction of Noise by Offset Cancellation

- ◆ For a cascade of two amplifiers in the front-end of a sampling system
  - Noise/offset of  $A_1$  corrupts  $V_{in}$  directly

