

---


# **EE4280 Lecture 8: Charge-Pump Phase-Locked Loops**

---

**Ping-Hsuan Hsieh (謝秉璇)**  
Delta Building R908  
EXT 42590  
[phsieh@ee.nthu.edu.tw](mailto:phsieh@ee.nthu.edu.tw)

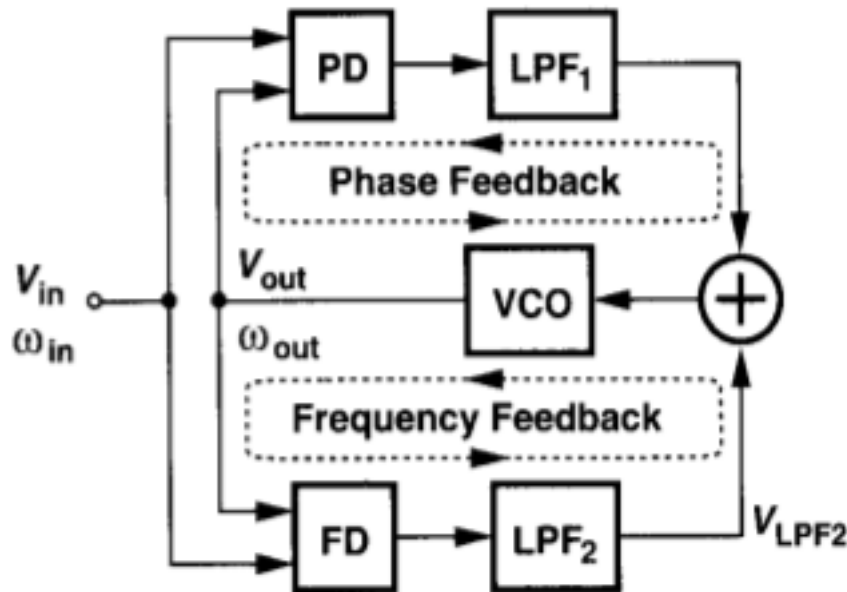
# Issues with Type-I Phase-Locked Loop

- ◆ **Strict trade-offs between response time, stability, steady-state ripple & jitter, and steady-state phase error**
- ◆ **Limited acquisition range**
  - The initial frequency of VCO can be very far from the input frequency
  - The acquisition range is on the order of  $\omega_{LPF}$
  - Difference between  $\omega_{in}$  and  $\omega_{out}$  has to be less than  $\omega_{LPF}$
  - Trade-offs further tightened
  - Possible solution:


 
## Two Inputs with Different Frequencies


- ◆ **An XOR cannot detect frequency error**



- ◆ **Output pulses varies periodically**
  - At beat frequency (the frequency difference of the two)
  - The larger the difference, the faster the output pulse width changes
  - The LPF output stays constant and does not change due to the change of phase difference
- XOR (phase detector) does not detect frequency difference
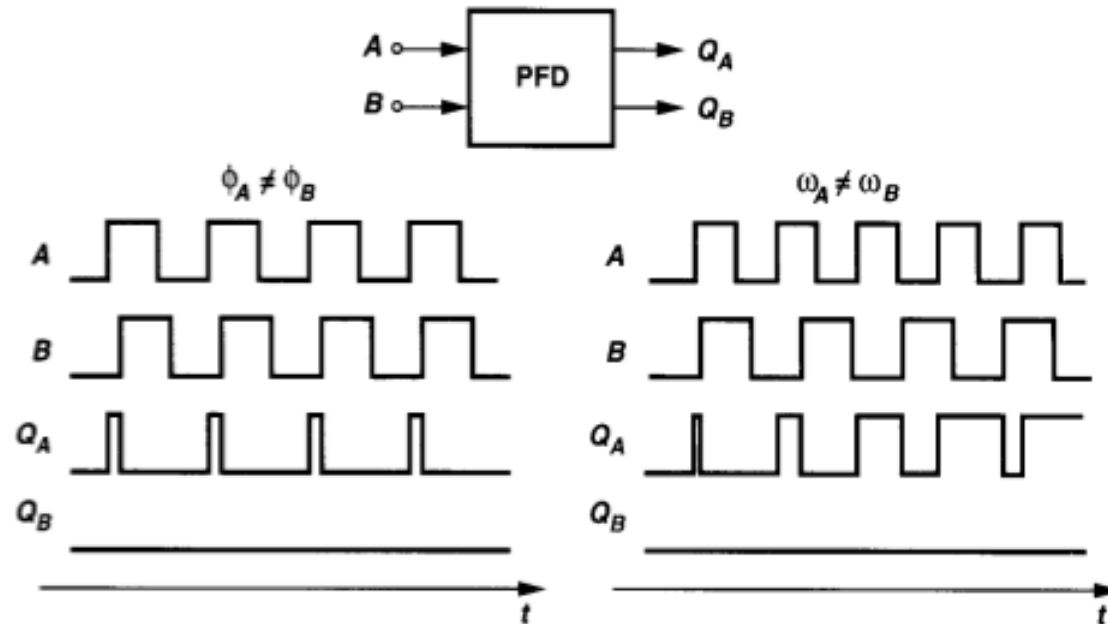
# Phase Frequency Detector


- ◆ Sequential logic of 3 states that responds to input edges



- Reset state:  $Q_A=Q_B=0$  initially
- $Q_A$  responds to rising edge of input  $A$
- does not reset until rising edge of input  $B$
- Two outputs indicate fast and slow in either phase or frequency

# PFD – in Case with Large Frequency Difference


- ◆ For larger frequency difference

 


# The Transfer Function of PFD

- ◆ Consider two outputs of the same frequency

in case where A leads B

 


in case where B leads A

 

# Implementation Example


- ◆ Using resettable flip-flops

 

- ◆  $Q_A$  and  $Q_B$  are simultaneously high for a short period of time
- Reset pulse
 
# Implementation Example

- ◆ Using resettable flip-flops → implemented using SR latch?





## The Problem of Using SR Latch for Resettable FF

- ◆ For two clocks with close phases

## The Problem of Using SR Latch for Resettable FF

- ◆ **For two clocks with close phases**
  - We want the outputs to stay low in this case



- ◆ **How many numbers of stage delay is the reset pulse?**

## To Take the PFD's Outputs to VCO

- ◆ A simple way
  
# Charge Pump



- ◆  $I_1$  and  $I_2$  are nominally identical
- ◆ In case where  $A$  leads  $B$



- ◆ The slope of  $V_{out}$
- ◆ Effect of the reset pulses that appear in both  $Q_A$  and  $Q_B$

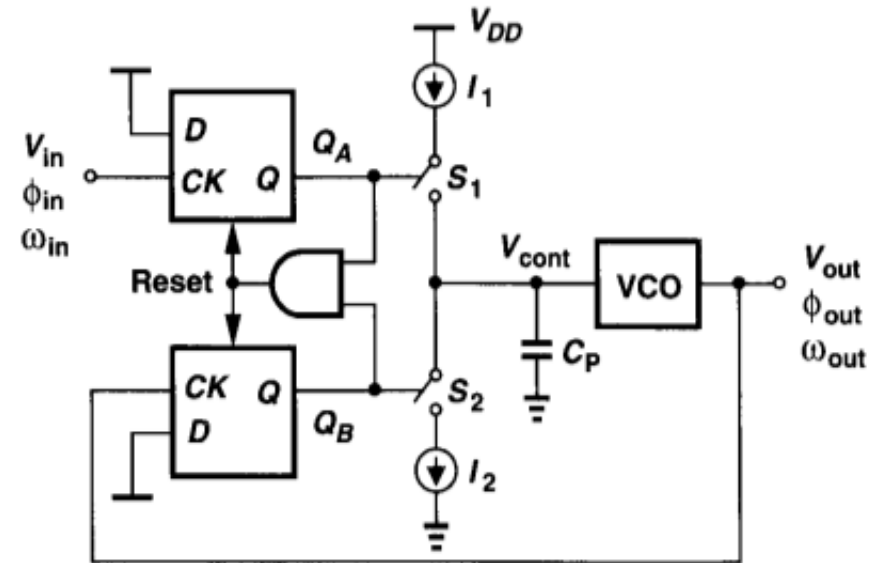
 
# Dynamics of Charge-Pump Phase-Locked Loops

- ◆ When the system is just turned on,  $\omega_{out}$  and  $\omega_{in}$  may be very different
- ◆ As  $\omega_{out}$  approaches  $\omega_{in}$
- ◆ Transfer function of PFD+CP  
In case if  $\Delta\phi_{in}$  doubles


  
# Dynamics of Charge-Pump Phase-Locked Loops


- ◆ When the system is just turned on,  $\omega_{out}$  and  $\omega_{in}$  may be very different
- ◆ As  $\omega_{out}$  approaches  $\omega_{in}$
- ◆ Transfer function of PFD+CP  
In case if  $\Delta\phi_{in}$  doubles



➔ Strictly speaking: not a linear system

# Transfer Function of PFD+CP (I)


- ◆ With a phase step at input

 
 
## Transfer Function of PFD+CP (II)

◆ Average output current with  $\Delta\phi_{in}$


→ The current flows into a capacitor, establishing  $V_{out}$




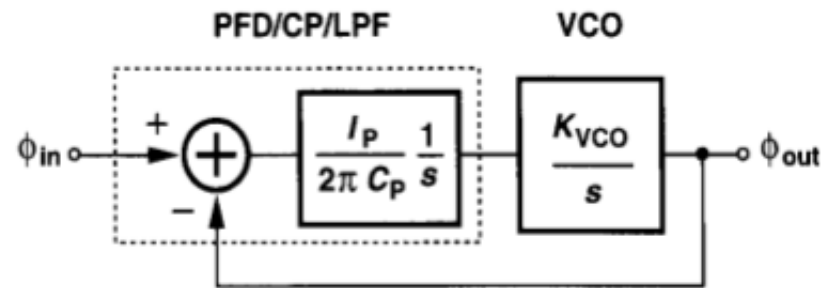
# Loop Dynamics (I)

- ◆ Linear model of the PLL → to derive the response from  $\phi_{in}$  to  $\phi_{out}$




- ◆ Open-loop transfer function (from phase → voltage → voltage → phase)

$$\frac{\Phi_{out}(s)}{\Phi_{in}(s)}|_{open} = \frac{I_P}{2\pi C_P} \frac{K_{VCO}}{s^2}$$

- Two poles at origin → type-II PLL

- ◆ Closed-loop transfer function


 
$$H(s) = \frac{\frac{I_P K_{VCO}}{2\pi C_P}}{s^2 + \frac{I_P K_{VCO}}{2\pi C_P}}$$



## To Stabilize the Loop

- ◆ We need certain phase margin at  $\omega_u$
- A left-plane zero by inserting a resistor
- The charge pump sees R in series with C


$$\frac{\Phi_{out}}{\Phi_{in}}(s)|_{open} = \frac{I_P}{2\pi} \left( R_P + \frac{1}{C_P s} \right) \frac{K_{VCO}}{s}$$

 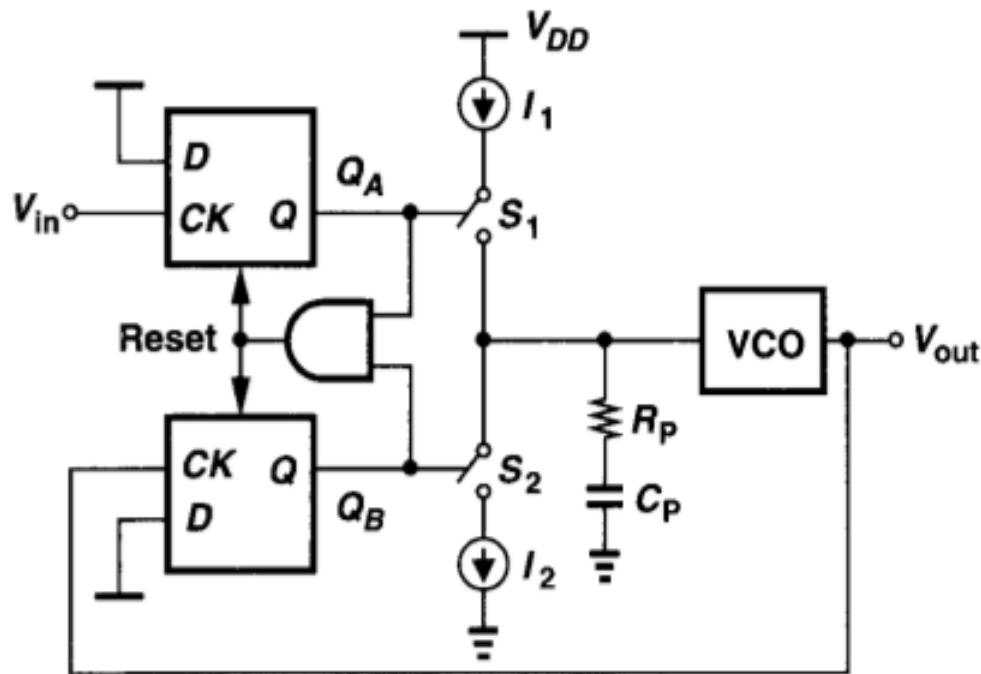

## Loop Dynamics (II)
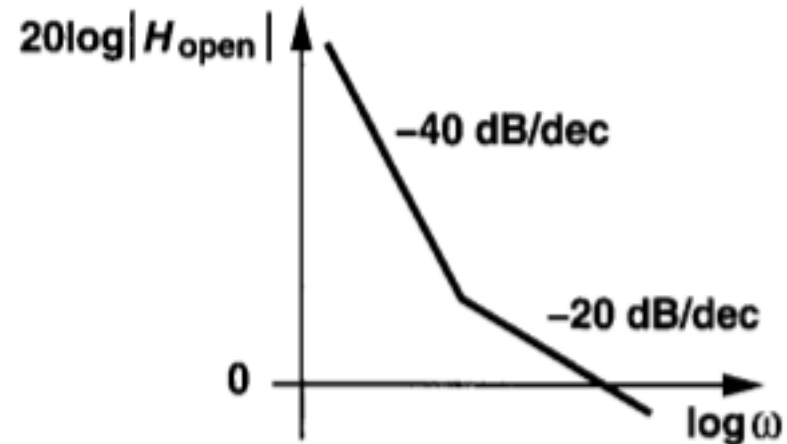
### ◆ Closed-loop transfer function

$$H(s) = \frac{\frac{I_P K_{VCO}}{2\pi C_P} (R_P C_P s + 1)}{s^2 + \frac{I_P}{2\pi} K_{VCO} R_P s + \frac{I_P}{2\pi C_P} K_{VCO}}$$




- Low-frequency gain of unity
- Output tracks the input **phase** well if input phase varies slowly
- For input phase step, output phase eventually catches up
- The same applies to **frequency** as well

### ◆ Second-order system $\omega_n = \sqrt{\frac{I_P K_{VCO}}{2\pi C_P}}$ $\zeta = \frac{R_P}{2} \sqrt{\frac{I_P C_P K_{VCO}}{2\pi}}$ .

- To stabilize the system by increasing the damping factor
- To speed up the loop response
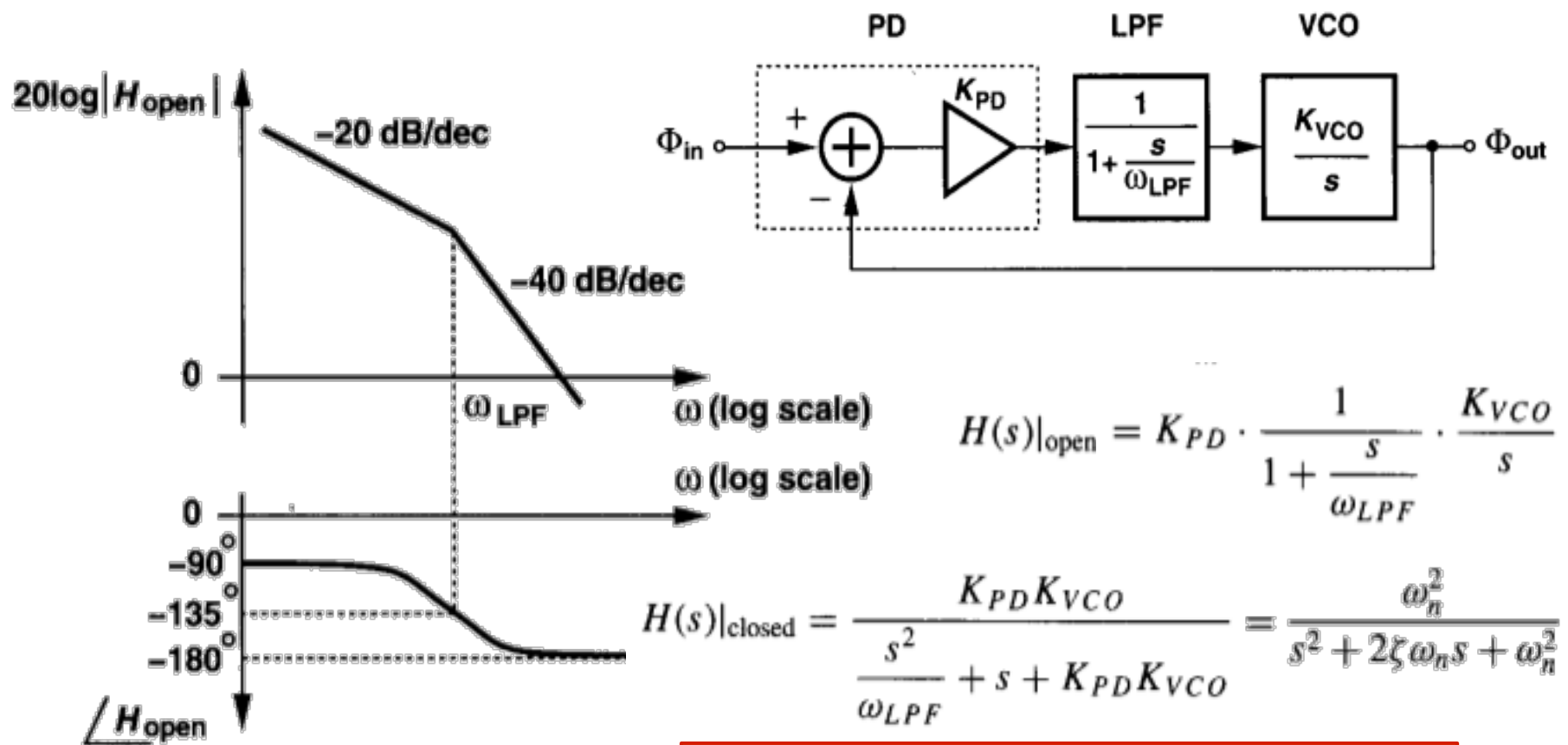
# Loop Dynamics of Basic PLL


- ◆ From Bode plot of open-loop transfer function



$$\omega_n = \sqrt{\omega_{LPF} K_{PD} K_{VCO}} \quad \zeta = \frac{1}{2} \sqrt{\frac{\omega_{LPF}}{K_{PD} K_{VCO}}}$$
 
# The Third-Order Capacitor

- ◆ Transient in  $V_{ctrl}$  with series R+C





- ◆ Add a capacitor  $C_2$  in parallel with R+C to smooth  $V_{ctrl}$

$$H(s)|_{open}$$
  
# The Third-Order Capacitor

- ◆ Transient in  $V_{ctrl}$  with series R+C



- ◆ Add a capacitor  $C_2$  in parallel with R+C to smooth  $V_{ctrl}$

$$H(s)|_{open}$$

# Discrete-Time Nature of Phase-Locked Loops (I)


- ◆ **Continuous-time and linear approximation**
  - Yield reasonably accurate results when input frequency/phase varies slowly (compared to the reference frequency)
  - For example, with the operating frequency of 1 GHz and the input frequency varying with 1 MHz
  - Very dense sampling → close to continuous-time operation

## Discrete-Time Nature of Phase-Locked Loops (II)

- ◆ When the frequency (that the signal frequency/phase is varying at) becomes comparable to the reference frequency
  - For example, if  $\omega_m = 0.25\omega_{REF}$
  
- ◆ Nonlinear operation
- ◆ Sampling delay results in additional phase shift → degrade stability
- ◆ Typically  $\omega_n$  is kept to be  $1/20 \sim 1/10 \omega_{REF}$



# Frequency Divider

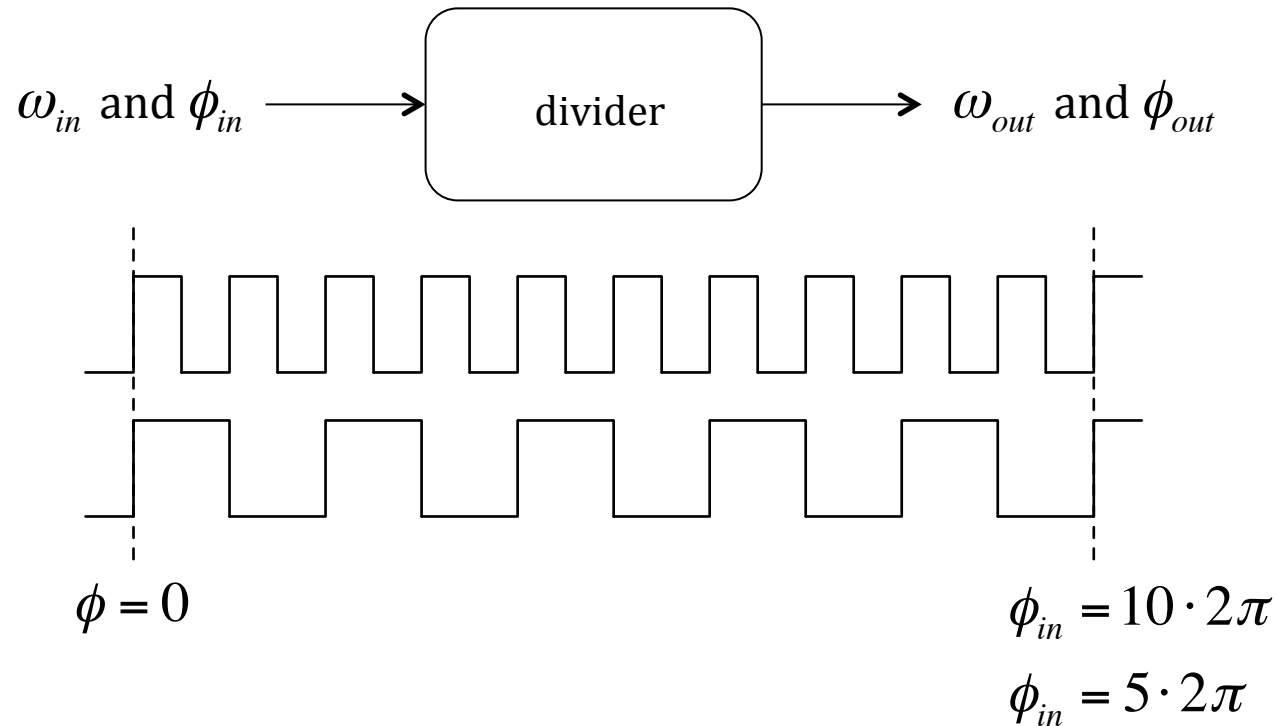

- ◆ Usually implemented using digital circuits
- ◆ Both frequency and phase are divided by N

## With Frequency Divider in the Loop

- ◆ **Input frequency can be different from output frequency**

## With Frequency Divider in the Loop

- ◆ Input frequency can be different from output frequency

- ◆ The transfer function: 
$$\frac{\phi_{out}}{\phi_{in}} = \frac{\frac{I_{CP}}{2\pi} \left( R + \frac{1}{sC_P} \right) K_{VCO}}{1 + \frac{I_{CP}}{2\pi} \left( R + \frac{1}{sC_P} \right) \frac{K_{VCO}}{M}} = \frac{\frac{I_{CP} K_{VCO}}{2\pi C_P} (1 + sRC_P)}{s^2 + \frac{I_{CP} K_{VCO}}{2\pi M} RS + \frac{I_{CP} K_{VCO}}{2\pi C_P M}}$$


$$\omega_n = \sqrt{\frac{I_{CP} K_{VCO}}{2\pi M}} \quad \text{and} \quad \xi = \frac{R}{2} \sqrt{\frac{I_{CP} C_P K_{VCO}}{2\pi M}}$$

- ◆ Can be used for frequency synthesis
- Frequency adjustment set by reference

# Nonidealities in Phase-Locked Loops (I)

- ◆ Design considerations of PFD+CP

 
1) Reset pulse width: in case with no pulse or very narrow pulse



# Nonidealities in Phase-Locked Loops (I)

## ◆ Design considerations of PFD+CP

 1) Reset pulse width: in case with no pulse or very narrow pulse




→ CP switches may not even get turned on

→ CP current may not settle in the short duration


# Nonidealities in Phase-Locked Loops (I)

## ◆ Design considerations of PFD+CP

 1) Reset pulse width: in case with no pulse or very narrow pulse



 
- CP switches may not even get turned on
- CP current may not settle in the short duration
- For very small phase error, PFD+CP fail to produce proportional outputs


 
## Nonidealities in Phase-Locked Loops (II)


- ◆ **Effect of dead zone**

→ negative feedback is broken with small phase error



- ◆ **Sufficiently wide reset pulse allows PFD+CP to settle**


→ Ready for small phase error

 
 
## Nonidealities in Phase-Locked Loops (II)


- ◆ **Effect of dead zone**

→ negative feedback is broken with small phase error



- ◆ **Sufficiently wide reset pulse allows PFD+CP to settle**

→ Ready for small phase error

 





## Nonidealities in Phase-Locked Loops (III)

- ◆ Design considerations of PFD+CP

  - 2) Skew in  $Q_A$  and  $Q_B$  pulses

- As the upper part of circuit is usually implemented using PMOS




## Nonidealities in Phase-Locked Loops (IV)

### ◆ Design considerations of PFD+CP
 
#### 3) Mismatch between up and down currents

- Even with perfect pulse alignment, for example, if  $I_{up} > I_{down}$




## Nonidealities in Phase-Locked Loops (IV)

- ◆ Design considerations of PFD+CP

 - 3) Mismatch between up and down currents

- Even with perfect pulse alignment, for example, if  $I_{up} > I_{down}$




## Nonidealities in Phase-Locked Loops (IV)

- ◆ Design considerations of PFD+CP

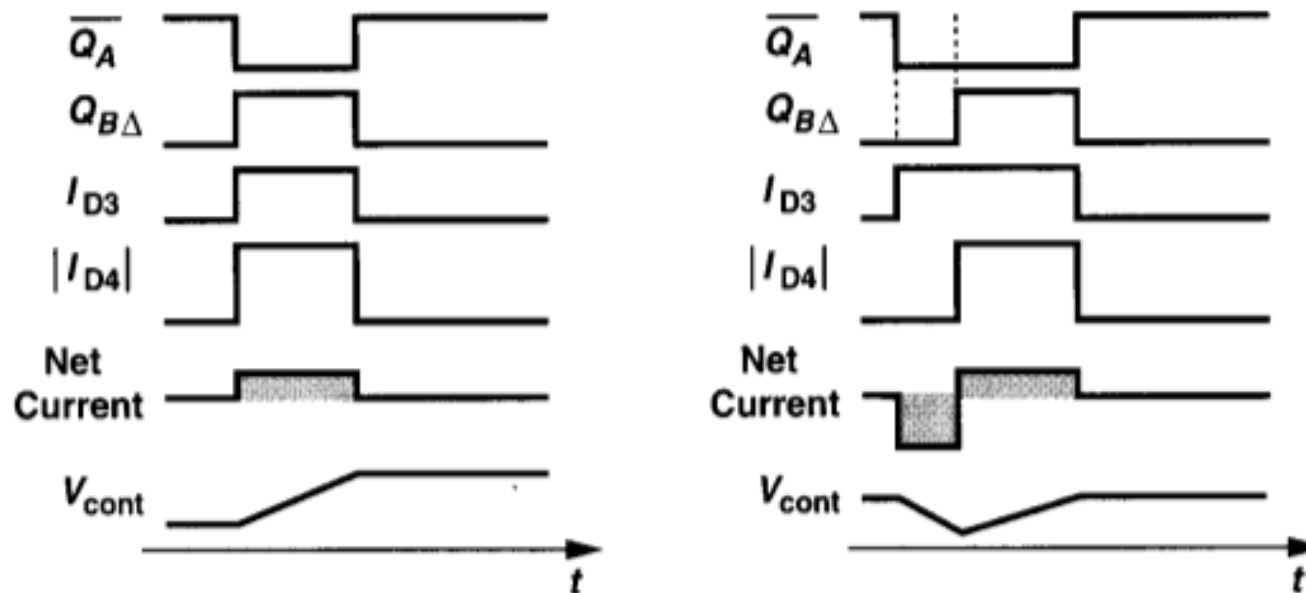- 3) Mismatch between up and down currents


- Even with perfect pulse alignment, for example, if  $I_{up} > I_{down}$



- Resulting in static phase error and  $V_{ctrl}$  ripple
- Difficult to maintain perfect match between  $I_{up}$  and  $I_{down}$  due to  $r_o$  of transistors  $\rightarrow$  worse for advanced technology
 
# Phase Noise and Jitter in Phase-Locked Loops (I)


- ◆ Total phase of a clean clock vs. a jittery clock



- ◆ Different ways to characterize and quantify jitter
  - Cycle jitter, cycle-to-cycle jitter, long-term or absolute jitter

## Phase Noise and Jitter in Phase-Locked Loops (II)

- ◆ The rate at which the phase varies

 

- ◆ Two sources of jitter that are of most interest

- Jitter of the reference input


$$\frac{\Phi_{out}}{\Phi_{in}}(s) = \frac{\frac{I_P K_{VCO}}{2\pi C_P} (R_P C_P s + 1)}{s^2 + \frac{I_P}{2\pi} K_{VCO} R_P s + \frac{I_P}{2\pi C_P} K_{VCO}}$$

- Jitter generated from the VCO

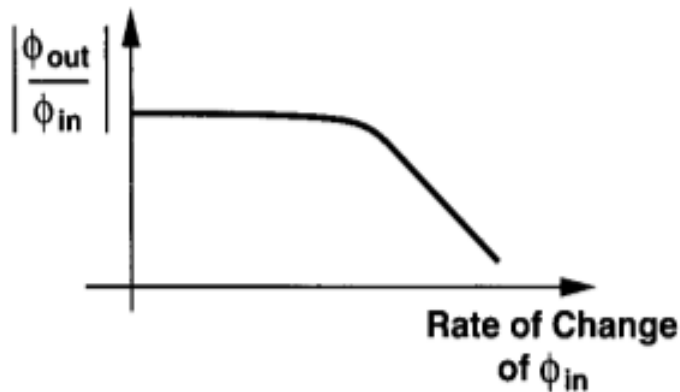
# Phase Noise and Jitter in Phase-Locked Loops (III)

- ◆ Jitter from VCO

$$\frac{\Phi_{out}}{\Phi_{in}}(s) = \frac{\frac{I_P K_{VCO}}{2\pi C_P} (R_P C_P s + 1)}{s^2 + \frac{I_P}{2\pi} K_{VCO} R_{PS} + \frac{I_P}{2\pi C_P} K_{VCO}}$$


 
$$\frac{\Phi_{out}}{\Phi_{VCO}}(s) = \frac{s^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$



- ◆ Trade-off between noise contributions from different sources