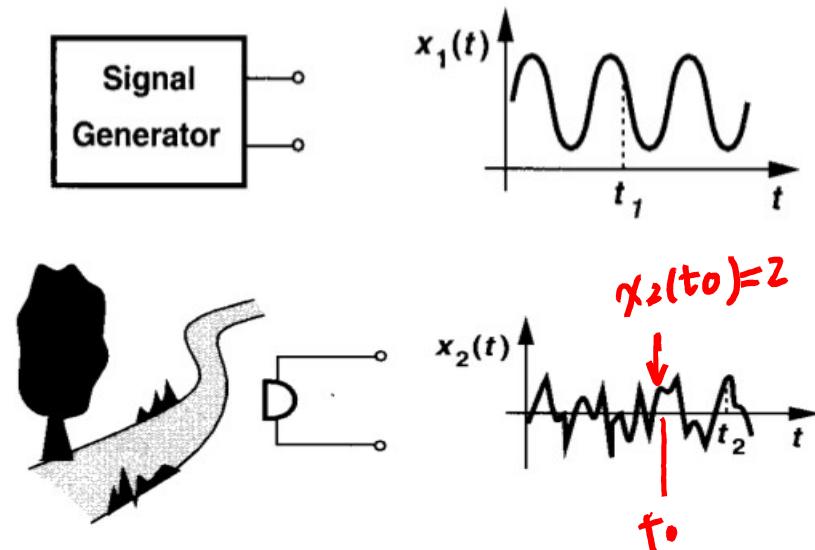

EE4280 Lecture 9: Noise

Ping-Hsuan Hsieh (謝秉璇)
Delta Building R908
EXT 42590
phsieh@ee.nthu.edu.tw

What is Noise?



Noise is a random process. We consider a phenomenon random because we do not know everything about it, or simply because we do not need to know everything about it.




Since the instantaneous noise amplitude is not known, we resort to 'statistical' models, i.e., some properties that can be predicted.

Statistical Characterization

1. Mean and Average Power

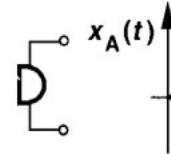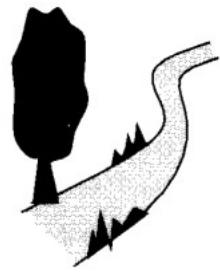

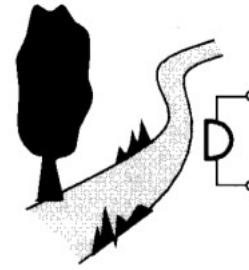
$$\lim_{T \rightarrow \infty} \frac{1}{T} \int_T x_A(t) dt = \bar{x}_A = 0$$



$$\begin{aligned} \lim_{T \rightarrow \infty} \frac{1}{T} \int_T x_B^2(t) dt &= \bar{x}_B^2 = 25 \text{ mV}^2 \\ &= (5 \text{ mV}_{\text{rms}})^2 \end{aligned}$$

$$\bar{x}_B^2 = (1.5 \text{ mV})^2$$

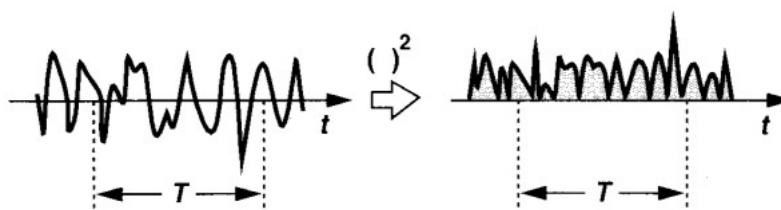
Larger fluctuations mean that the noise is 'stronger'



Statistical Characterization

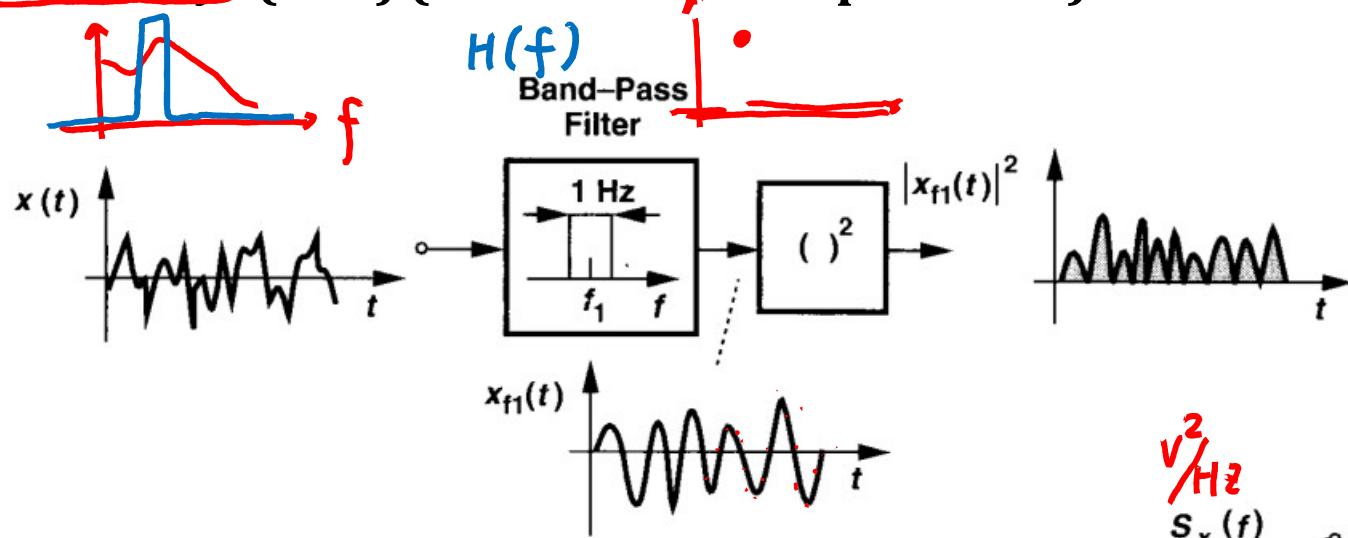
2. Frequency Domain

For random signals, the concept of Fourier transform cannot be directly applied. But we still know that men carry less high-frequency components in their voice than women do. We define the "power spectral density" (PSD) (also called the "spectrum") as:



The PSD thus indicates how much power the signal carries in a small bandwidth around each frequency.
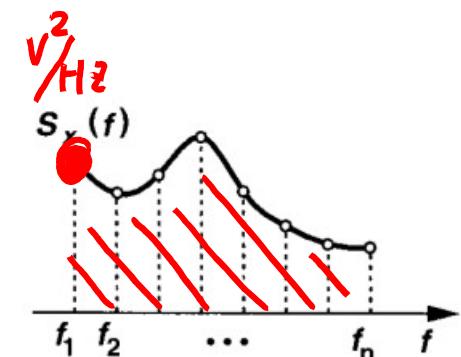
$$P_{av} = \lim_{T \rightarrow \infty} \frac{1}{T} \int_T x^2(\tau) d\tau = \int S_x(f) df$$




Statistical Characterization


- What is the unit of $S_n(f)$?
- What is the total noise power?

A flat spectrum is called 'white'

- Is the total noise power infinite?

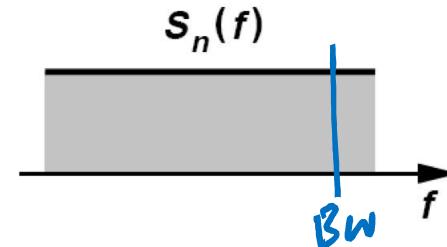

Important Theorem

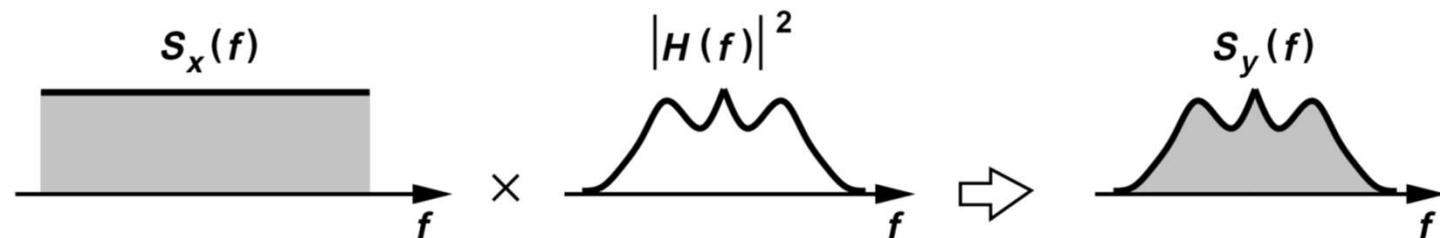


If a signal with spectrum $S_x(f)$ is applied to a linear time-invariant system with transfer function $H(s)$, the output spectrum is given by

$$S_Y(f) = S_X(f)|H(f)|^2$$

Statistical Characterization

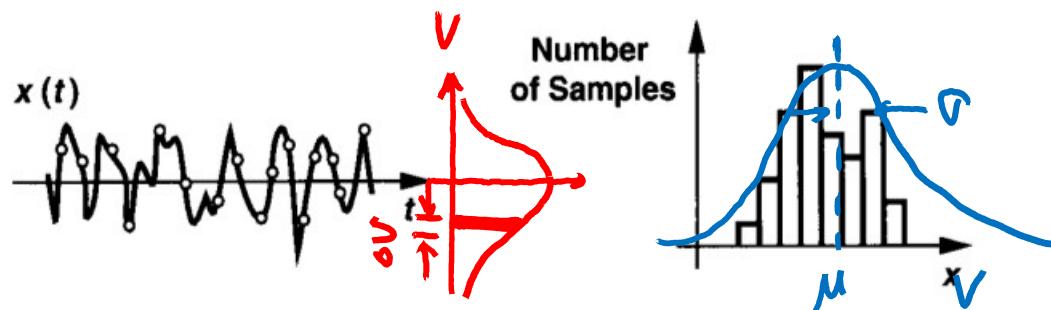3. Amplitude Distribution

By sampling the time-domain waveform for a long time, we can construct a “probability density function (PDF). The PDF in essence indicates “how often” the amplitude is between certain limits.



For example, a Gaussian distribution is defined by a mean and a standard deviation. We say the noise amplitude rarely exceeds 4σ .

Note: Generally PDF and PSD bear no relationship.

Thermal Noise: Gaussian, white

Flicker Noise: Gaussian, not white

Correlated and Uncorrelated Sources


Can we use superposition for average noise power from a few noise components?

$$P_{av} = \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{+T/2} [x_1(t) + x_2(t)]^2 dt$$
$$= \lim_{T \rightarrow \infty} \frac{1}{T} \int (x_1^2(t) + 2x_1(t)x_2(t) + x_2^2(t)) dt$$

$$\lim_{T \rightarrow \infty} \frac{1}{T} \int_T x(t) dt = \lim_{T \rightarrow \infty} \frac{1}{T} \int_T (x_1(t) + x_2(t)) dt = P_{av1} + P_{av2}$$

$$\bar{x}(t) = \bar{x_1}(t) + \bar{x_2}(t) = \emptyset \quad \bar{x_1^2}(t) = (3mV_{rms})^2 + \cancel{\frac{2x_1(t)x_2(t)}{2}} \rightarrow \emptyset$$
$$\bar{x_2^2}(t) = (4mV_{rms})^2 \quad \text{if } x_1(t) \text{ and } x_2(t)$$

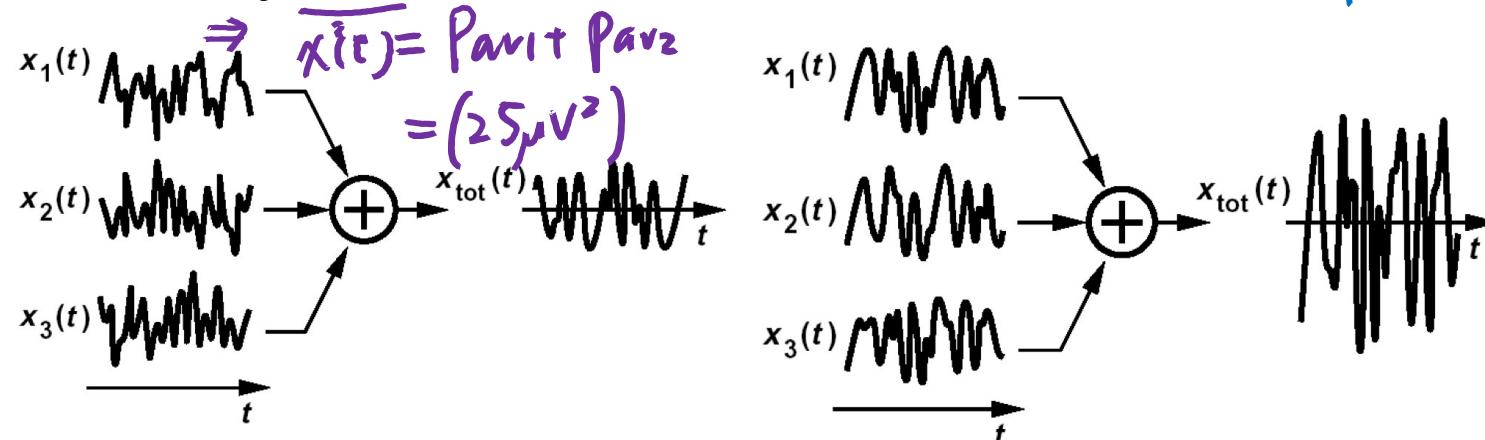We occasionally encounter correlated sources: are independent to E.O.








Types of Noise

1. Thermal Noise in Resistors

Random movement of charge carriers in a resistor causes fluctuations in the current. The PDF is Gaussian because there are so many carriers. The PSD is given by:

$$i_R \downarrow \begin{array}{c} \text{---} \\ \text{---} \\ R \\ \text{---} \\ \text{---} \end{array} \quad \begin{array}{c} + \\ \text{---} \\ \text{---} \\ - \\ \text{---} \end{array} \quad v_R$$

$$v_R = i_R \cdot R$$

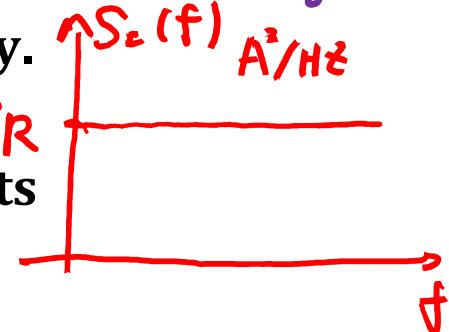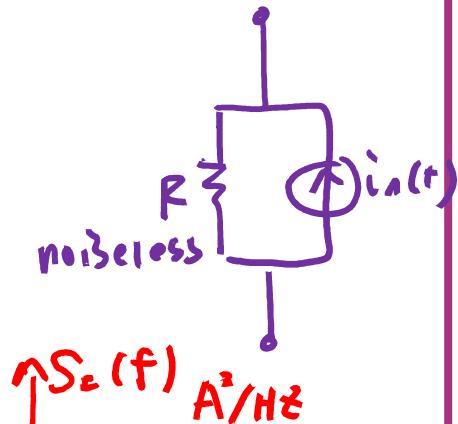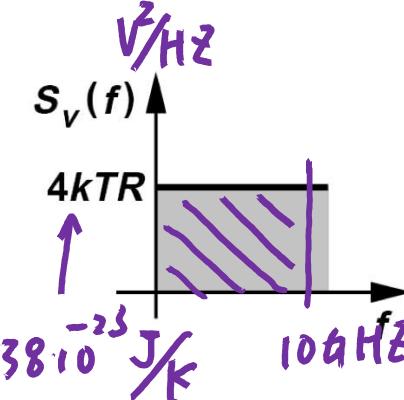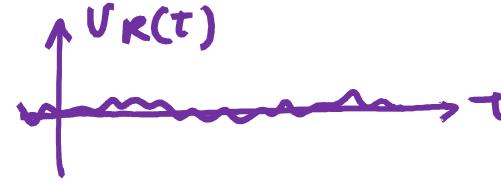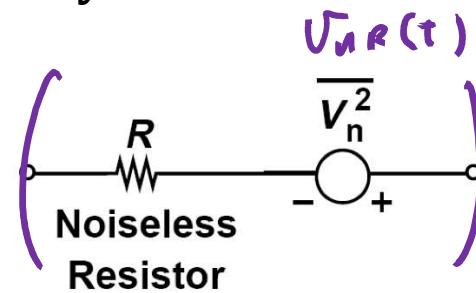

Note that the polarity of the voltage source is arbitrary.


Example: A $50\text{-}\Omega$ resistor at room temperature exhibits

$$S_v(f) = 4 \cdot k \cdot T \cdot 50 = (91 \text{ nV})^2/\text{Hz}$$

If the resistor is used in a system with 10-GHz bandwidth, then it contributes a total rms voltage of

$$(91 \text{ nV})^2/\text{Hz} \cdot 10 \text{ GHz} = (91 \text{ nV}_{\text{rms}})^2$$


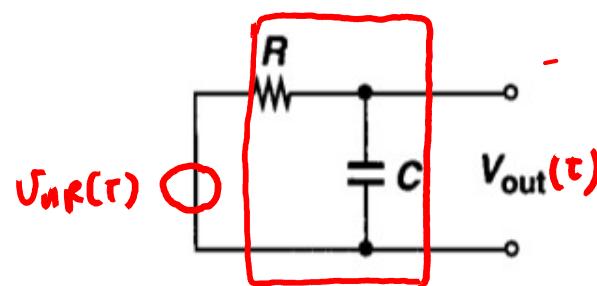
Example: Noise Spectrum and Total Noise Power



$$\frac{V_{out}(s)}{V_R} = \frac{1}{1 + sRC}$$

$$S_{out}(f) = S_{in}(f) \left| \frac{1}{1 + sRC} \right|^2 = \frac{4kTR}{1 + (\omega RC)^2}$$
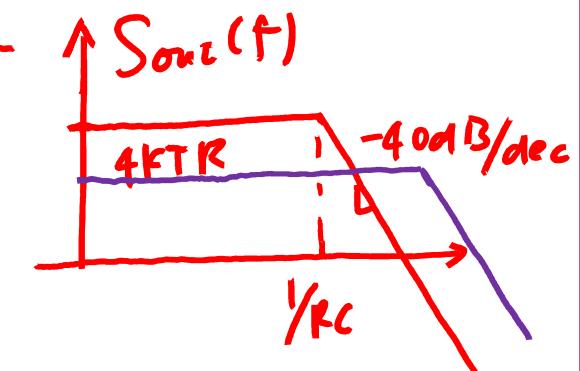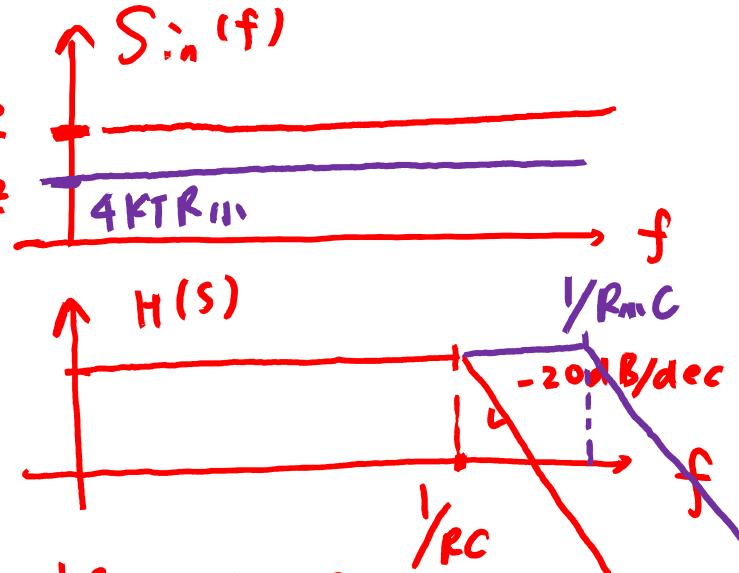
$$P_{n,out} = \int S_{out}(f) df = \frac{K_T}{C}$$



For $R=50 \Omega$ and $C=1 \text{ pF}$:

$$= (6.25 \text{ mV}_{\text{rms}})^2$$

Trade-offs between noise, area, speed, and power

Types of Noise


2. Thermal Noise in Transistors

Triode region

$$R_{on} = \frac{1}{\mu C_{ox} \frac{W}{L} (V_{GS} - V_{th})}$$

$$\overline{I_n^2} = 4kT\gamma g_m \quad S_{in}(f) = \frac{4kT}{R_{on}} A^2/\text{Hz}$$


$$= 4kT \mu C_{ox} \frac{W}{L} V_{GS}$$

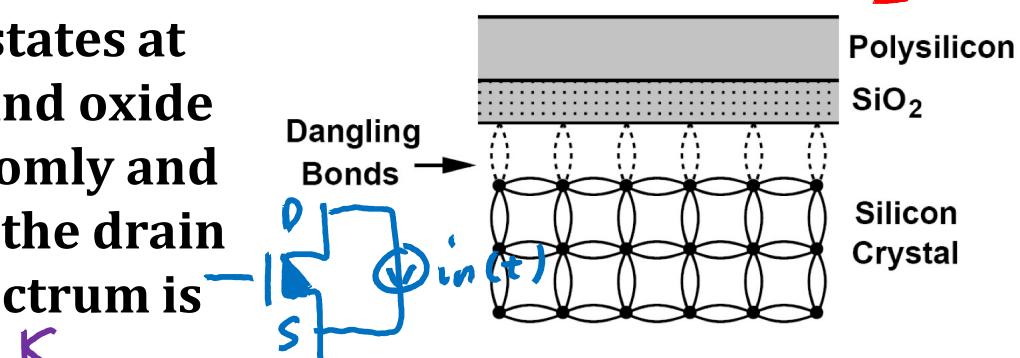

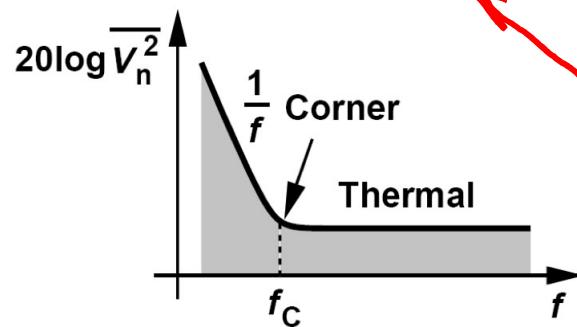
3. Flicker Noise in Transistors

In MOSFETs, the extra energy states at the interface between silicon and oxide trap and release carriers randomly and at different rates. The noise in the drain current is Gaussian, but its spectrum is given by:

$$S_{inf}(f) = \frac{k}{C_{ox} \cdot W \cdot L \cdot f}$$



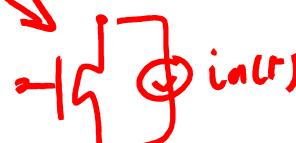Where k is a constant and its value
vily depends on how 'clean' the
We often characterize the
noise by considering
frequency.





$$S_{inf}(f) \propto 4kT V_{GS} \quad A^2/\text{Hz}$$

$$= 4kT \mu C_{ox} \frac{W}{L} V_{GS} g_m$$

$$S_{inf}(f) = \frac{k g_m^2}{C_{ox} W L f} A^2/\text{Hz}$$

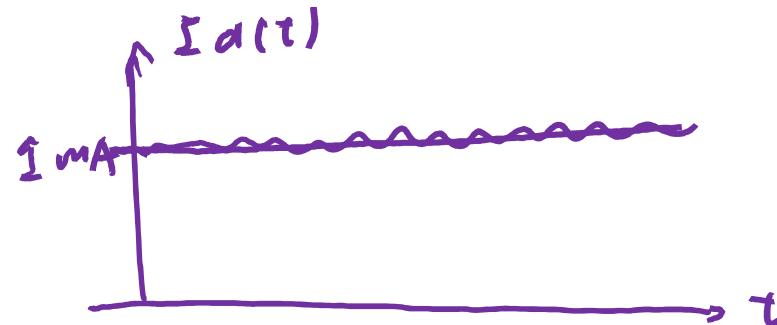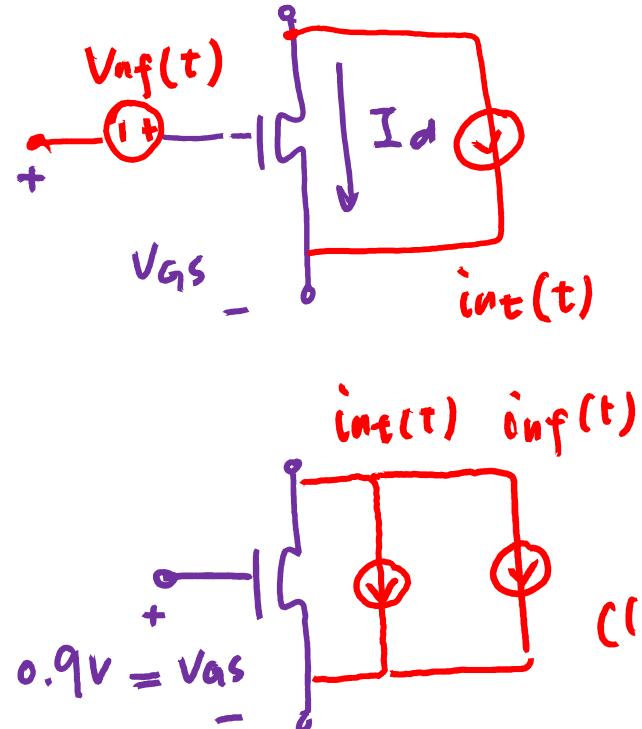
Example: A Current Source


Total noise in the drain current for a band from 1 kHz to 1 MHz



$$i_d(t) = 1\text{ mA} + \underline{i_{n1}(t)} + \underline{i_{n2}(t)}$$

$$i_n(t) = i_{n1}(t) + i_{n2}(t)$$

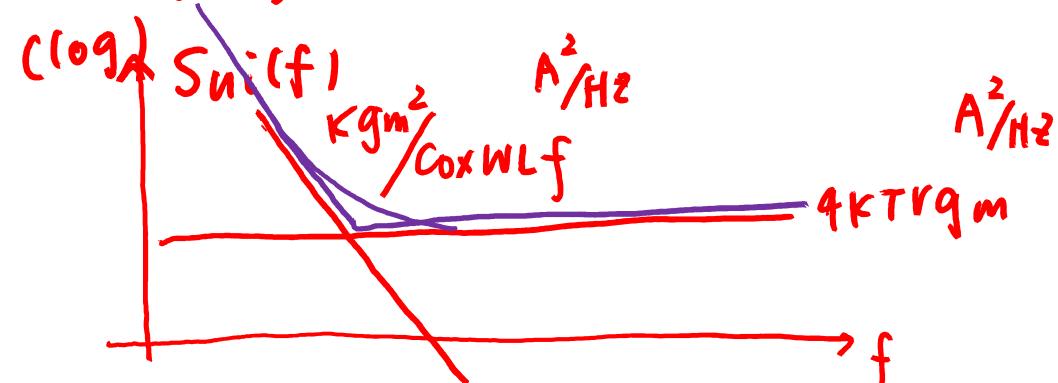

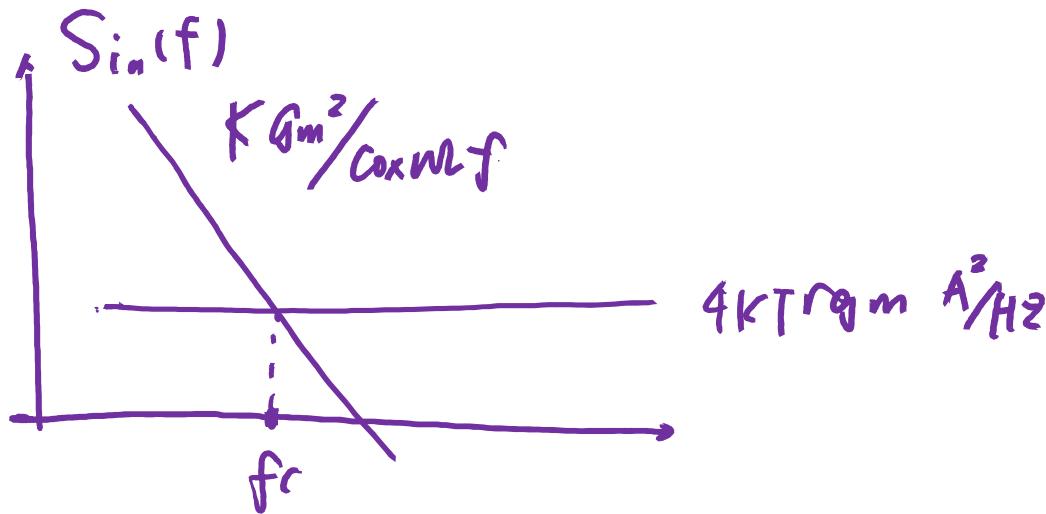

find out f_c such that $\frac{k g_m^2}{C_{ox} W L f_c} = 4 k T r g_m$


$$f_c = \frac{k}{C_{ox} W L} g_m \frac{1}{4 k T r}$$

from 1 kHz to 1 MHz

$10 \text{ kHz} \sim 10 \text{ MHz}$

$$\overline{I_{n,Tot}^2} = \int_{1K}^{1M} S_{in}(f) df = 4 k T r g_m (10^6 - 10^3) + \frac{k g_m^2}{C_{ox} W L} (10^6 - 10^3)$$




Common-Source Stage

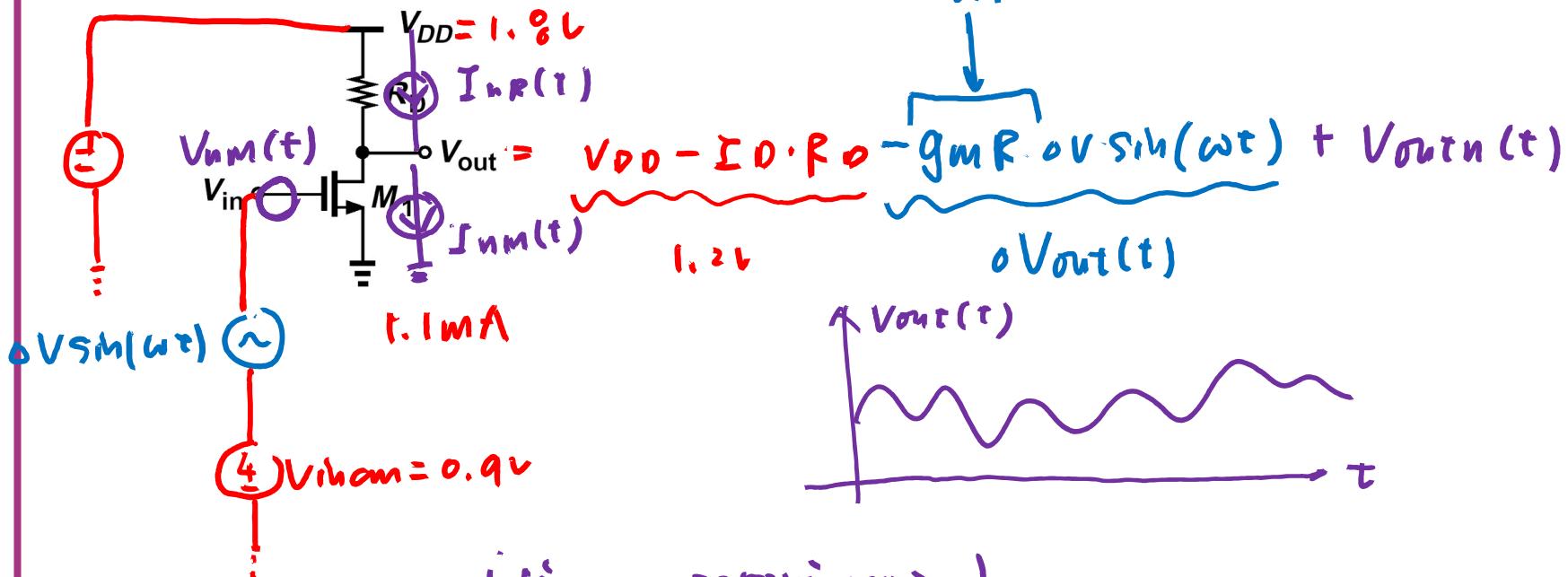


We are applying small-signal analysis with superposition for all the sources, including $\text{o}V_{in}$, I_{inR} , I_{inM} , ...

$$V_{outn}(t) = V_{NM}(t) \cdot g_m R - I_{inR}(t) \cdot R + I_{inM}(t) \cdot R$$
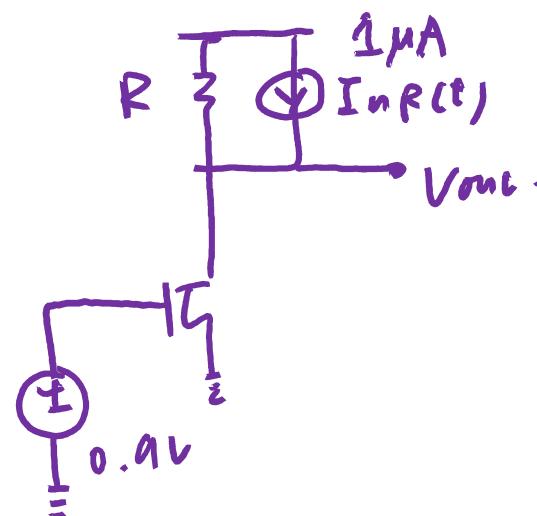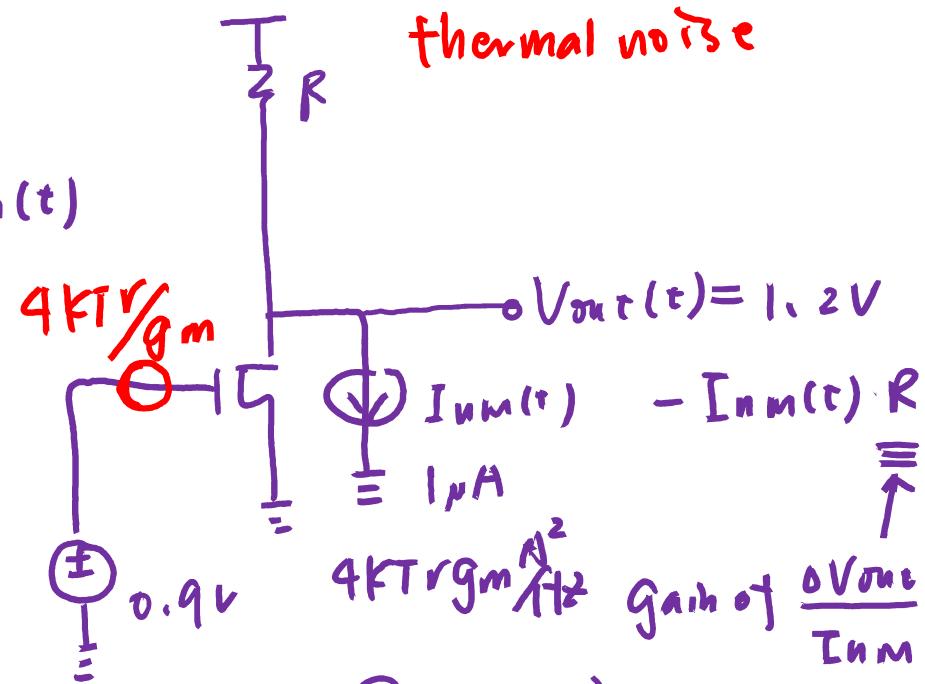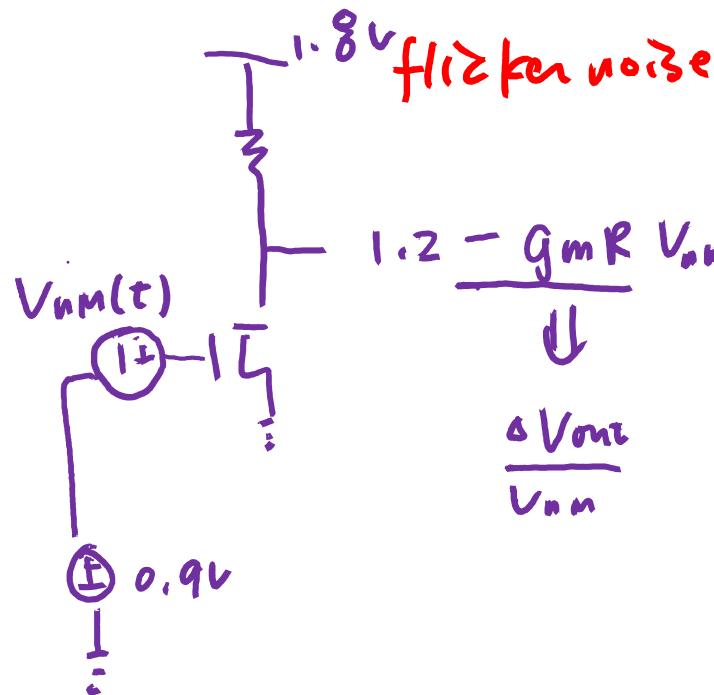
$$S_{Voutn}(f) = S_{VNM}(f) \cdot (g_m R)^2 + S_{IinR}(f) R^2 + S_{IinM}(f) \cdot R^2$$



$$S_{V_{out}(f)} = 4KTR g_m (g_m R)^2$$


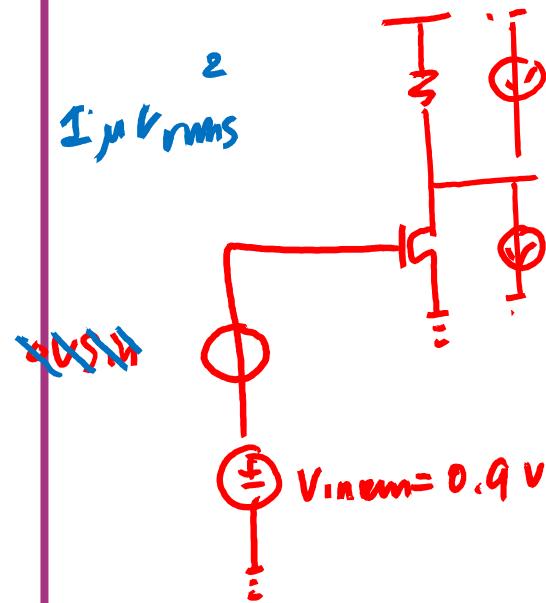


for noise



$$S_{Vout}(f) = S_{inm}(f) \cdot R^2 + S_{nR}(f) \cdot R^2$$

$$= 4kT r g_m R^2 + 4kT / R \cdot R^2 \frac{V^2}{Hz}$$

$S_{inm} V_{rms}^2$

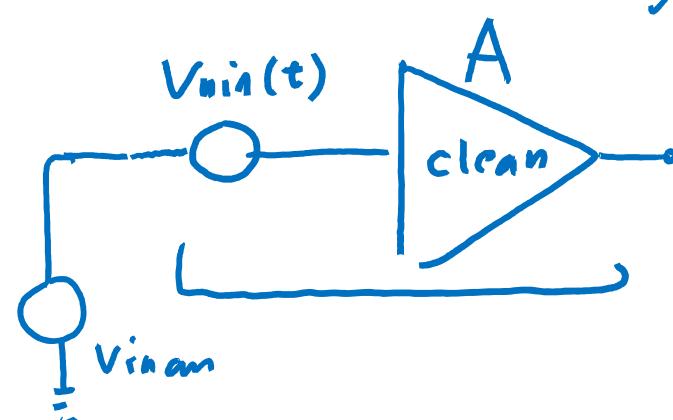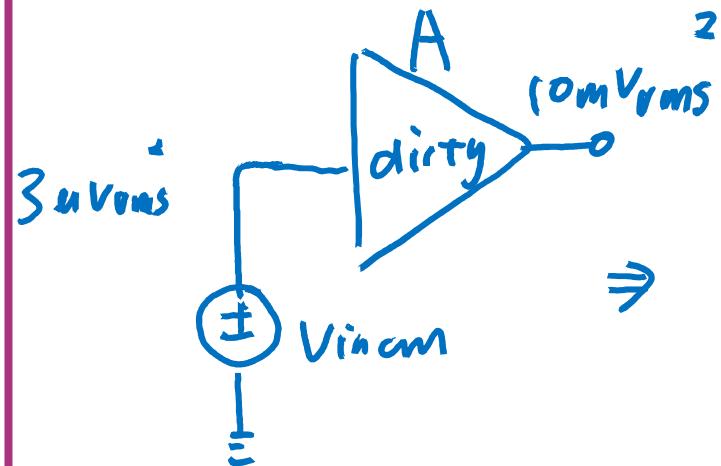


Common-Source Stage

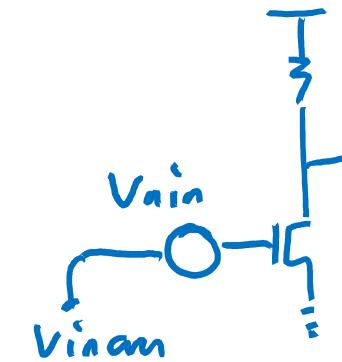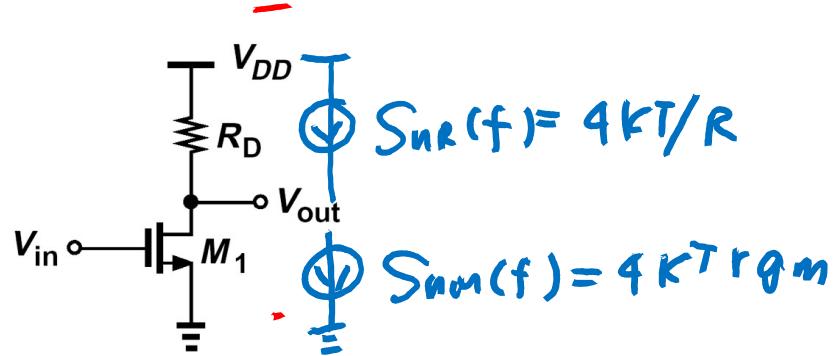

$$\underline{S_{V_{n,out}^2}(f)} = \underline{4kT \cdot R + 4kT r g_m R^2}$$

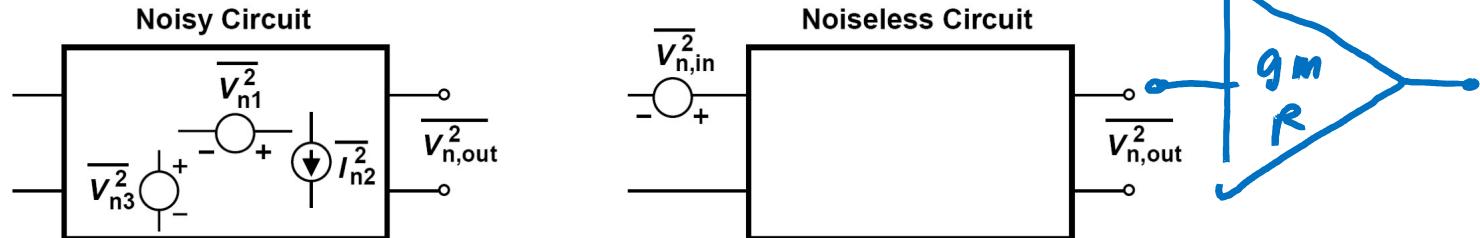Input-Referred Noise is the noise voltage or current that, when applied to the input of the noiseless circuit, generates the same output noise as the actual circuit does.



$$\underline{S_{V_{n,in}^2}(f)} = \frac{4kTR}{(gmR)^2} + \frac{4kTr}{gm}$$

Common-Source Stage

$$\overline{V_{n,in}^2} = 4kT \left(\frac{2}{3g_m} + \frac{1}{g_m^2 R_D} \right) + \frac{K}{C_{ox}WL} \frac{1}{f}$$

Why does the noise decrease as R_D increases?

With a current-source load:

$$S_{V_{n,out}^2(f)} = (4kT r g_{m1} + 4kT r g_{m2}) |H(f)|$$

$$\overline{V_{n,in}^2} = \frac{4kT r}{g_{m1}} + \frac{4kT r g_{m2}}{g_{m1}^2} \left| \frac{R_{out}}{1 + S_C R_{out}} \right|^2$$

Consider BW limitation from C_L and a low-frequency signal V_m at input:


$$\overline{V_{n,out}^2} = P_{n,out} = r(g_{m1} + g_{m2})(r_{d1} // r_{d2}) \frac{\frac{kT}{C_L} \frac{(r_{d1} // r_{d2})^2}{1 + \omega^2 C_L^2 (r_{d1} // r_{d2})^2}}{V_{rms}^2} df$$



$$\text{SNR}_{out} =$$

$$V_m \sin(\omega t) \rightarrow \sigma V_m = V_m \cdot g_m \cdot (r_{d1} // r_{d2}) \cdot \sin(\omega t)$$

How to reduce the noise?

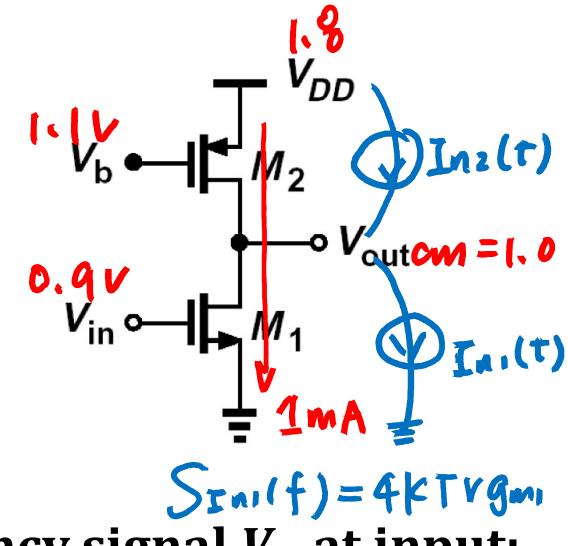
Trade-offs between speed, power, and voltage headroom



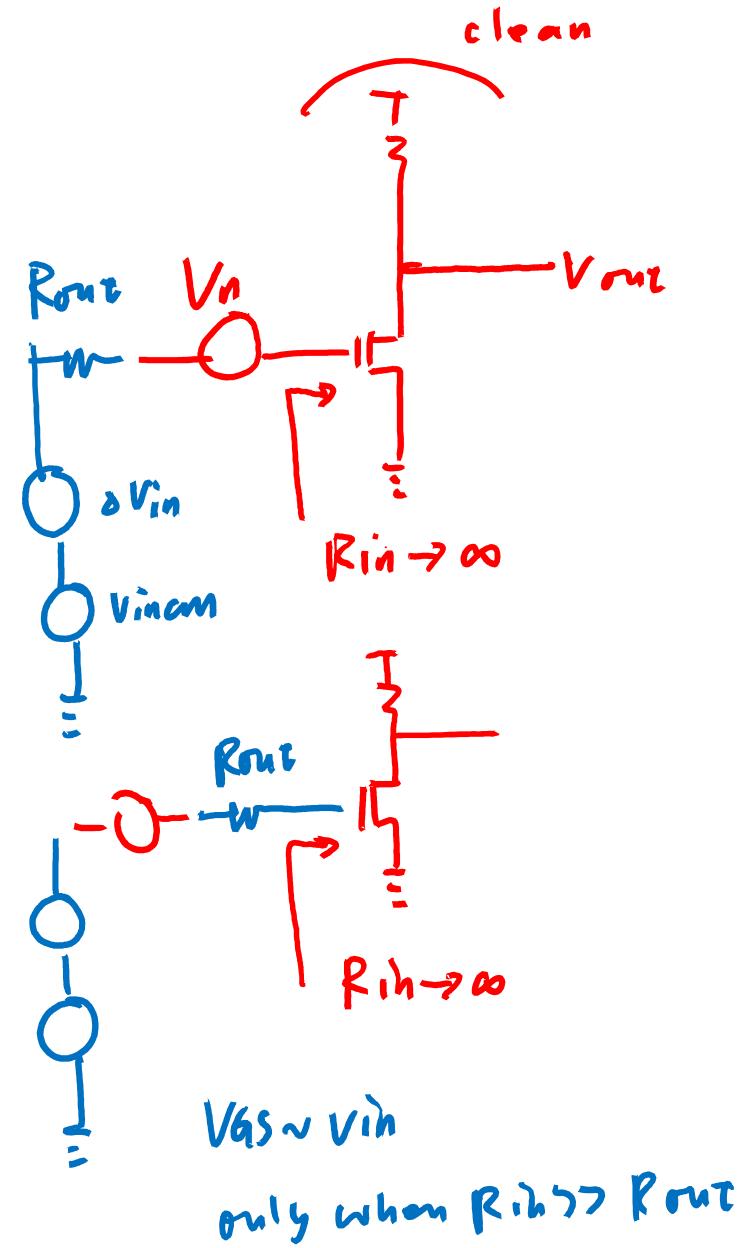
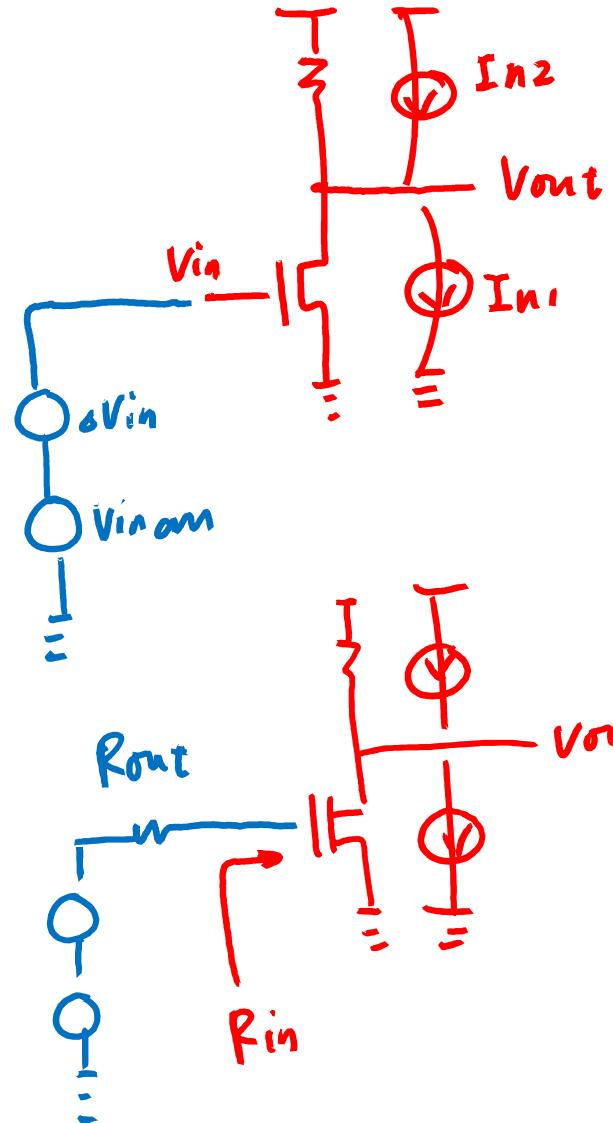


Input-Referred Noise

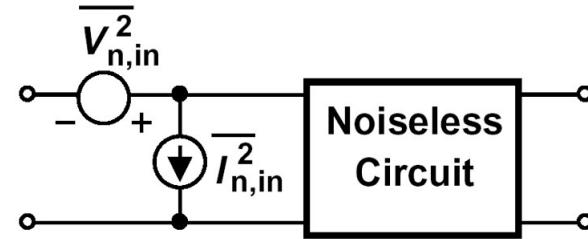In general, we need both a voltage source and a current source at the input to model the circuit noise.




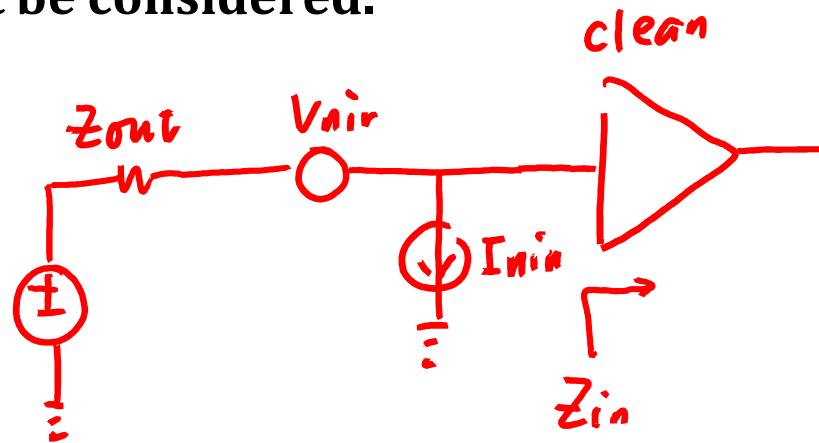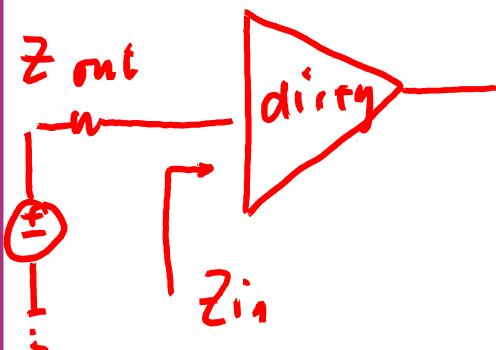If the source impedance is high with respect to the input impedance of the circuit, then both must be considered.




How To Calculate Input-Referred Noise?


With $Z_S=0$:

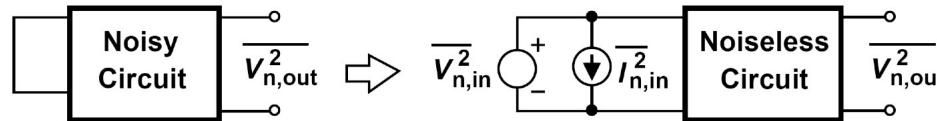

With $Z_S=\infty$:

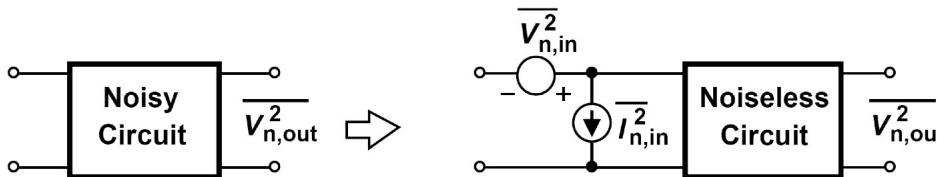

Example:

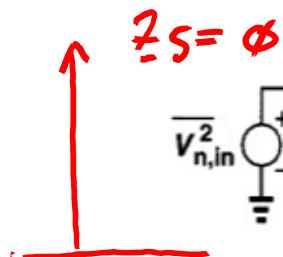


$$S_{nout}(f) = 4kT r g_m R_o + f k T R_o$$

$$\overline{V_{n,in}^2}(f) \cdot (g_m, R_o)^2 = S_{nout}(f)$$

~~$\overline{V_{n,out}^2}$~~

$Z_S \rightarrow \infty$

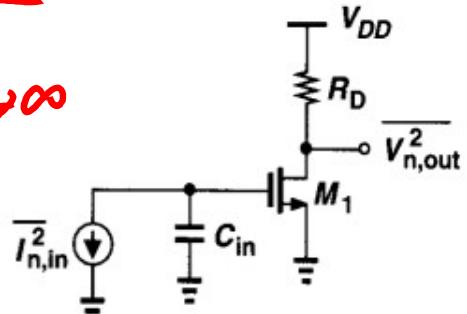

~~$\overline{V_{n,out}^2}$~~

$$\overline{I_{n,in}^2}(f) \cdot \left(\frac{1}{\omega C_{in}} \right)^2 \cdot (g_m, R_o)^2 = S_{nout}(f)$$

Common-Gate Stage

Basic operation

