

---

# **EE4280 Lecture 1:**



# **Nonlinearity**

---

**Ping-Hsuan Hsieh (謝秉璇)**  
Delta Building R908  
EXT 42590  
**[phsieh@ee.nthu.edu.tw](mailto:phsieh@ee.nthu.edu.tw)**
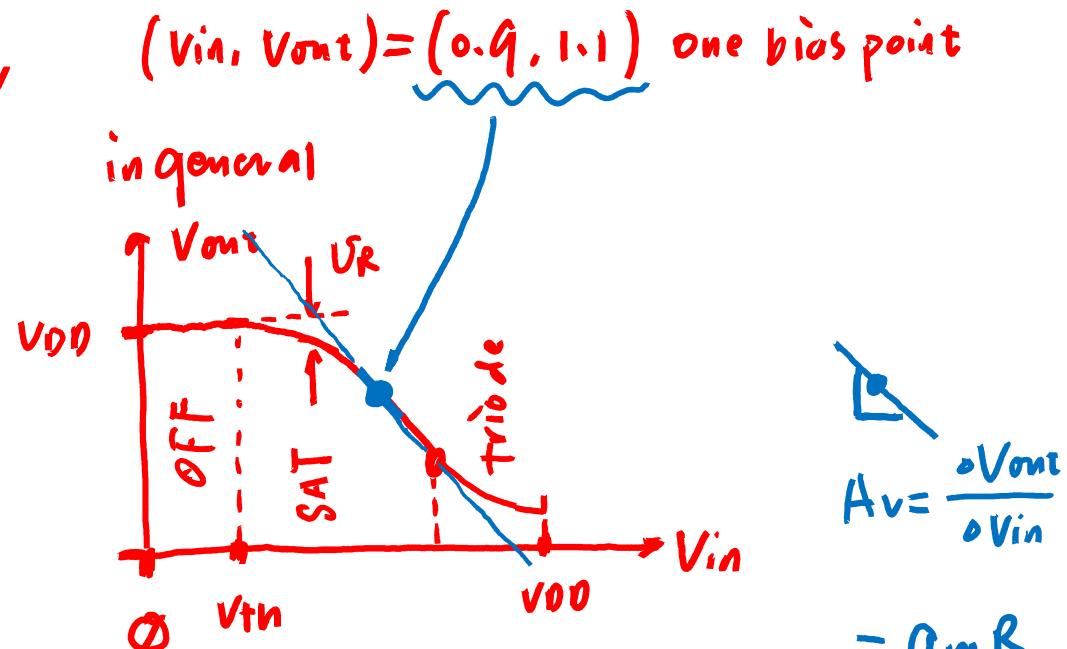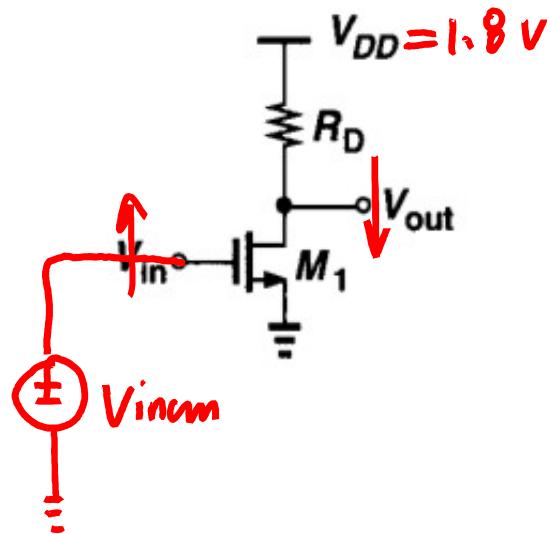
# Nonlinearity

Nonlinear characteristic deviates from a straight line as the input swing increases



$$= g_m R \\ = f(V_{in})$$

Gain being a function of  $V_{in}$   
(bias point)



Shows that the original curve is nonlinear

# Nonlinearity

$$y = f(x) \text{ expand @ } x=0.9$$

Nonlinear characteristic deviates from a straight line as the input swing increases

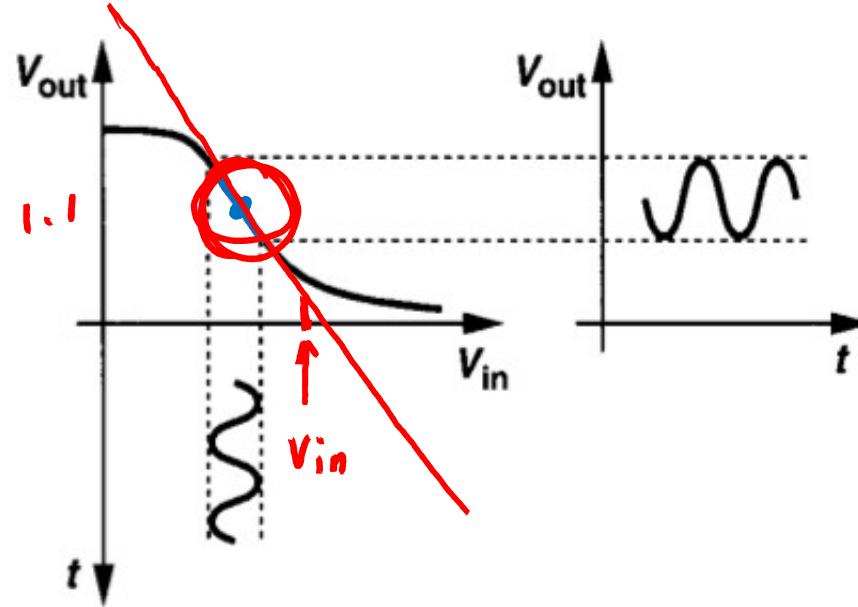
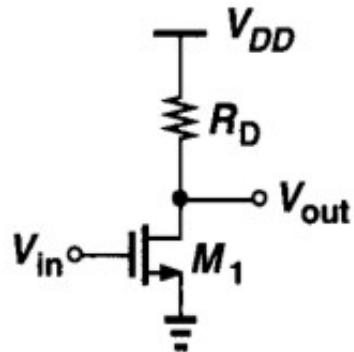
$$\rightarrow y = 1.1 + (A_v) \cdot (x - 0.9)$$



- ♦ For small input swing, the output is a reasonable replica of the input
  - Small-signal gain is related to the slope at a given bias point
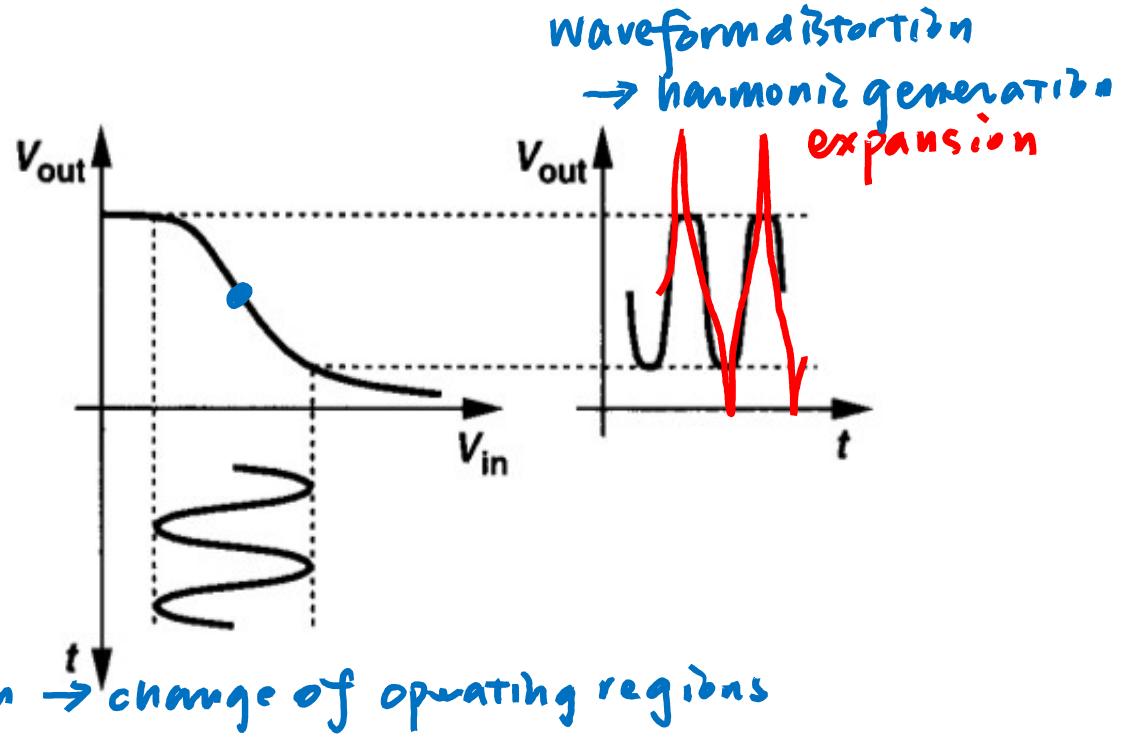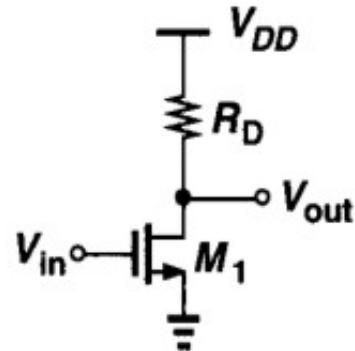
# Nonlinearity



Nonlinear characteristic deviates from a straight line as the input swing increases



- ♦ For small input swing, the output is a reasonable replica of the input
- ♦ For large input swings, most amplifiers experience gain compression (instead of expansion)
  - The output exhibits “saturated” levels due to supply voltage or bias current
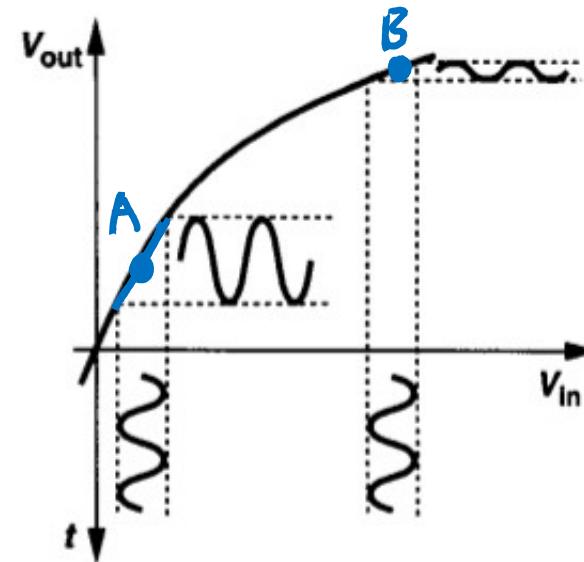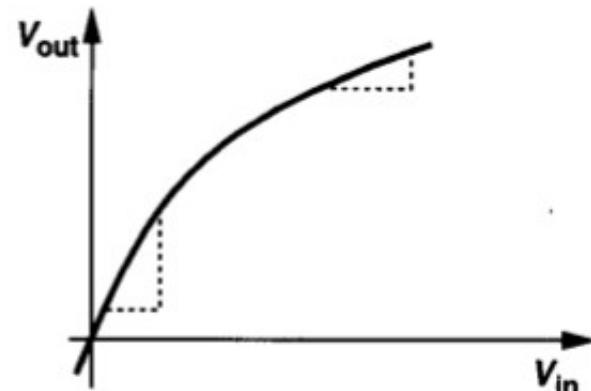
# Nonlinearity

Can be viewed as variation of the slope (small-signal gain) with the input level (common-mode)



# To Quantify Nonlinearity (I)

- ◆ Taylor Expansion

$$y = f(x) = \underline{f(x_0)} + \frac{f'(x_0)}{1!}(x - x_0) + \frac{f''(x_0)}{2!}(x - x_0)^2 + \dots$$

@  $x = x_0$

$$y - f(x_0) = \alpha_1(x - x_0) + \alpha_2(x - x_0)^2 + \alpha_3(x - x_0)^3 + \dots$$

$$\underline{\delta y} = \alpha_1 \delta x + \alpha_2 \delta x^2 + \alpha_3 \delta x^3 + \dots$$

( $-g_m R$ )

linear approximation OK when

$\alpha_2, \alpha_3, \dots$  are small  
or when  $\delta x$  is small

$$\frac{\delta V}{V_{in,range}} \text{ or } \frac{\delta V}{V_{out,range}}$$


#1

Maximum deviation from an ideal straight line

$\Delta V/V_{out,max}$  for certain  $V_{in,max}$

#2 gain variation as well

$A_{v,max}, A_{v,min}, \delta V_{range}$

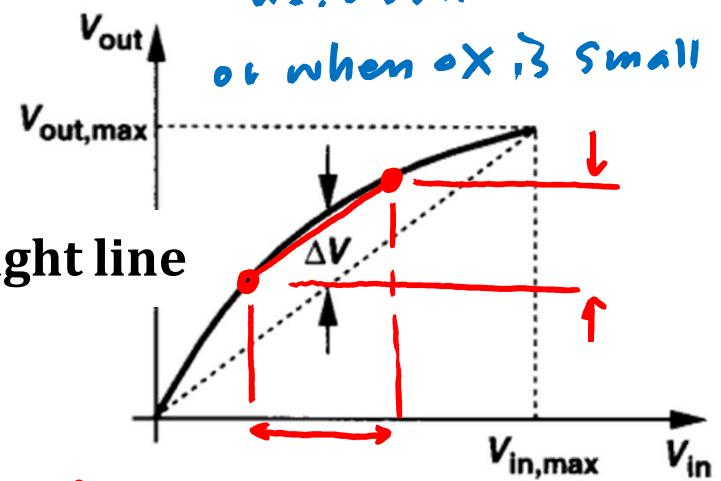

## To Quantify Nonlinearity (II)

- ◆ A single tone test

$$\Delta x = A \cos \omega_1 t \quad x(t) = x_0 + A \cos \omega_1 t$$

$$\Delta y = \alpha_1 A \cos \omega_1 t + \underbrace{\alpha_2 A^2 \cos^2 \omega_1 t}_{\frac{\alpha_2 \cdot A^2}{2} (1 + \cos 2\omega_1 t)} + \underbrace{\alpha_3 A^3 \cos^3 \omega_1 t}_{\alpha_3 A^3 (\frac{3}{4} \cos \omega_1 t + \frac{1}{4} \cos 3\omega_1 t)} + \dots$$

$$= (\alpha_1 A + \frac{3}{4} \alpha_3 A^3) \cos \omega_1 t$$

$$+ \left( \frac{\alpha_2 A^2}{2} \right) \cos 2\omega_1 t$$

$$+ \frac{1}{4} \alpha_3 A^3 \cos 3\omega_1 t + \dots$$

$$\propto \frac{\alpha_2}{\alpha_1} A^2$$

- ◆ Total harmonic distortion

$$THD = \frac{\left( \frac{\alpha_2 A^2}{2} \right)^2 + \left( \frac{1}{4} \alpha_3 A^3 \right)^2}{\left( \alpha_1 A + \frac{3}{4} \alpha_3 A^3 \right)^2}$$

## To Quantify Nonlinearity (III)

- 1-dB compression point

The signal at  $\omega_1$

$$\Delta y = \left( \alpha_1 A + \frac{3}{4} \alpha_3 A^3 \right) \cos \omega_1 t$$

output amplitude


$$20 \log \left( \frac{\alpha_1 A + \frac{3}{4} \alpha_3 A^3}{\alpha_1 A_{1dB}} \right) = 1 \text{ dB}$$

input amplitude of A

$$\alpha_1 A_{1dB} + \frac{3}{4} \alpha_3 A_{1dB}^3$$




$$\Rightarrow A_{1dB} = \sqrt{0.11 \cdot \frac{3}{4} \frac{\alpha_1}{\alpha_3}}$$

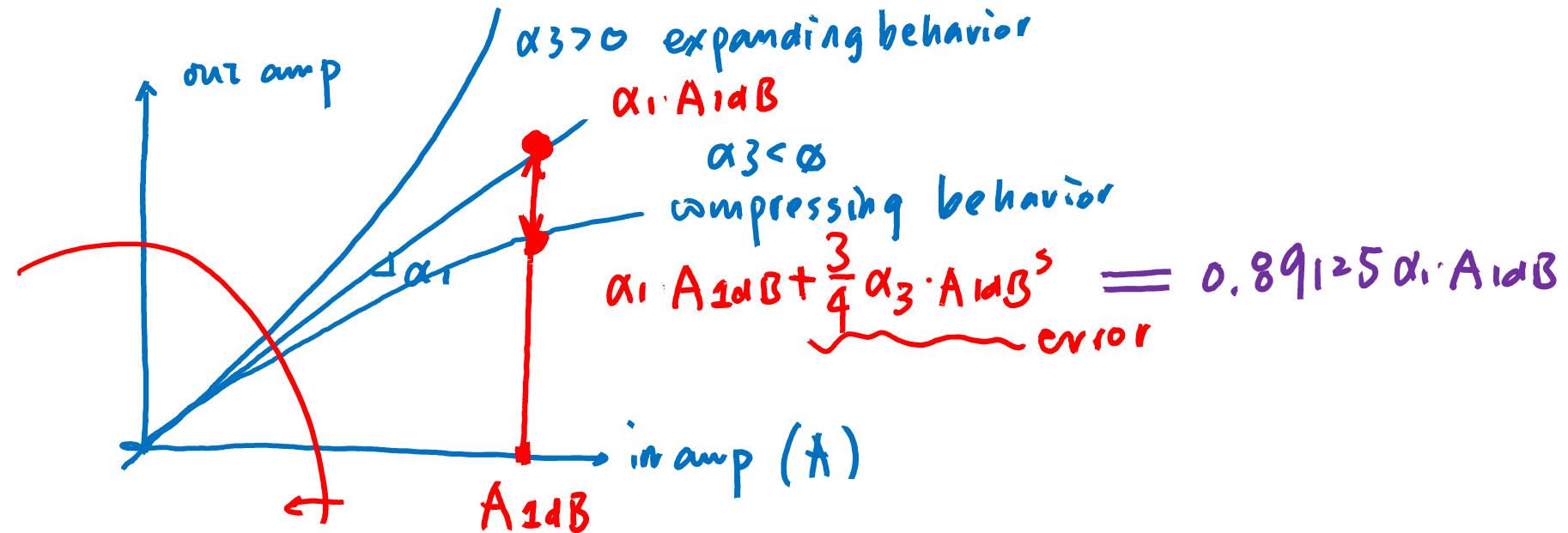The input level where the gain has dropped by 1dB



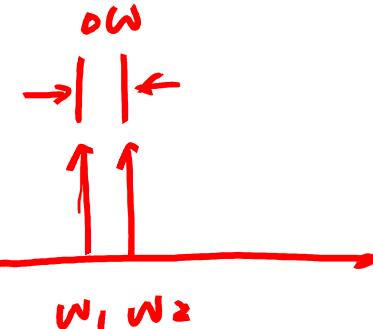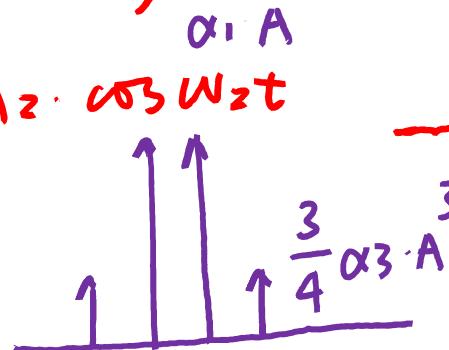
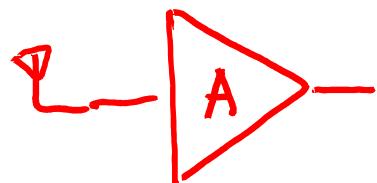
## two-tone test (RF application)

$$x(t) = A_1 \cdot \cos(\omega_1 t) + A_2 \cdot \cos(\omega_2 t)$$



$$y(t) = \alpha_1 \cdot x(t) + \alpha_2 \cdot x^2(t) + \alpha_3 \cdot x^3(t) + \dots$$

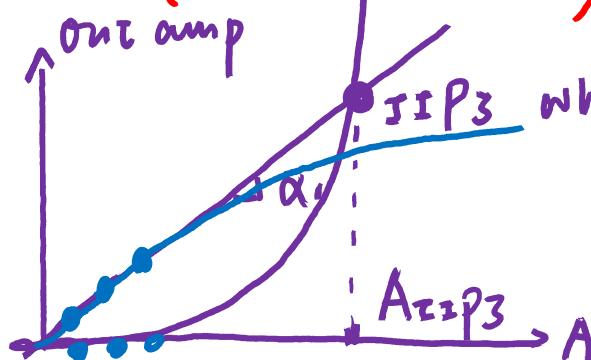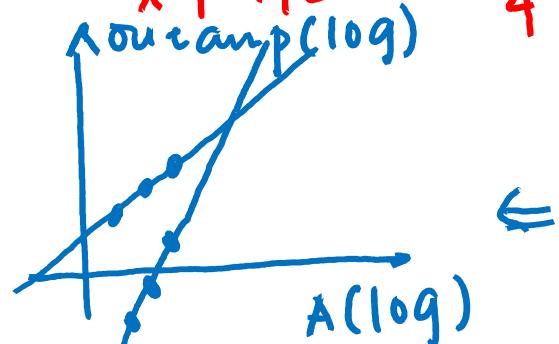其中會產生  $\frac{3 \cdot \alpha_3 \cdot A_1^2 \cdot A_2}{4} (\cos(2\omega_1 - \omega_2)t) + \frac{3}{4} \alpha_3 A_1 A_2 \cos(2\omega_2 - \omega_1)t$




when  $\alpha_1 \cdot A_{IIP3} = \frac{3}{4} \alpha_3 \cdot A_{ZIP3}$

$$\Rightarrow A_{IIP3} = \sqrt{\frac{4 |\alpha_1|}{3 |\alpha_3|}}$$

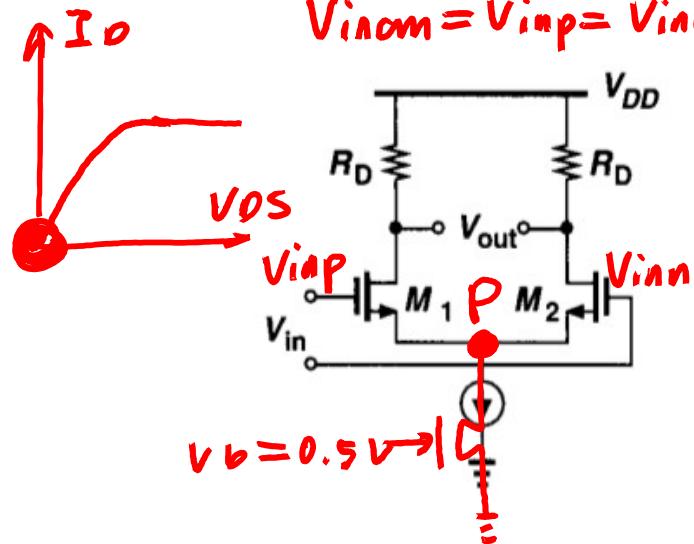
# Nonlinearity of Differential Circuits (I)

- Differential circuits exhibit an “odd-symmetric” input/output characteristics, i.e.,  $f(-x) = -f(x)$



$$V_{inom} = V_{inP} = V_{inn} = 1/2 V$$
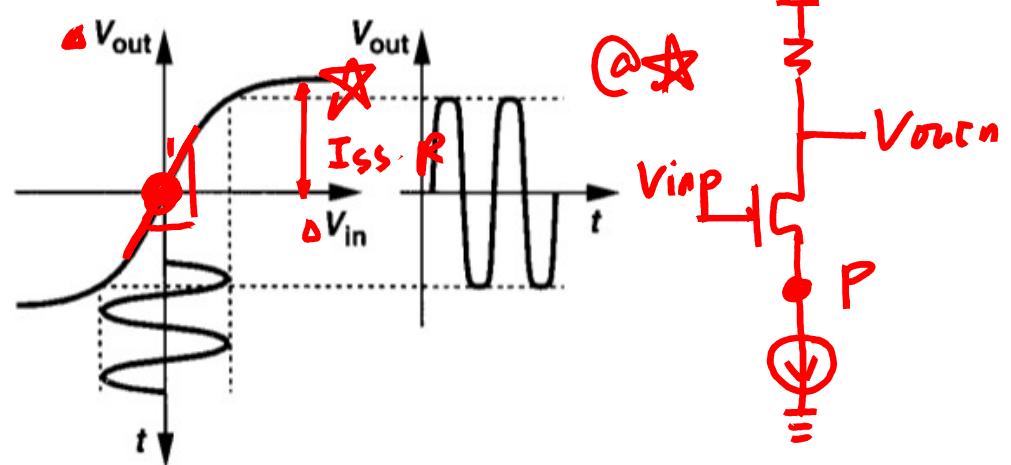
$$A_v = \frac{\Delta V_{out}}{\Delta V_{in}} = g_m R$$



$$\Delta V_{out} = f(\Delta V_{in})$$

$$y = f(x)$$



differential operation:  $f(-x) = -f(x)$

- For the Taylor expansion to be an odd function, all the even-order terms must be zero.

$$\Delta y = \alpha_1 \Delta x + \alpha_3 (\Delta x)^3 + \alpha_5 (\Delta x)^5 + \dots$$

- A differential circuit produces no even-order harmonics
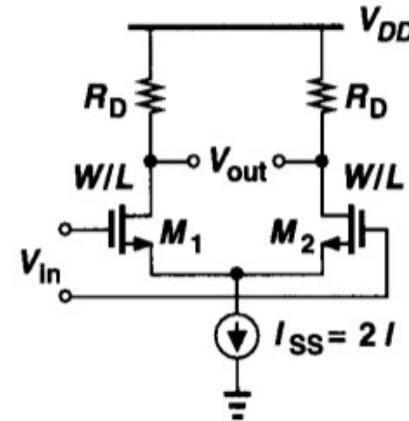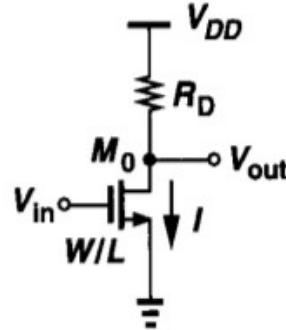
## Nonlinearity in Differential Circuits (II)



- Single-ended and differential amplifiers with the same voltage gain

$$|A_v| \approx g_m R_D = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) R_D$$

$V_{GS} \approx V_m \cdot \cos \omega t$

- For the single-ended case:
- $$V_{DD} - V_{out}(t) = R_D \left( \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in}(t) - V_{th})^2 \right) = f(V_{in})$$

$$V_{DD} - V_{out} = I_D \cdot R_D$$

With

$$V_{in} = V_{GS} + V_m \cos \omega t$$

We have  $V_{DD} - V_{out} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} + V_m \cos \omega t - V_{th})^2 R_D$

## Nonlinearity for Differential Circuits (III)

- For the single-ended case:

$$V_{DD} - V_{out} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} + V_m \cos \omega t - V_{th})^2 R_D$$

$$V_{out} = f(V_{in})$$

$$= f(V_{GS\theta}) + \frac{f'(V_{GS\theta})}{1!} (V_{in} - V_{GS\theta}) + \frac{f''(V_{GS\theta})}{2!} (V_{in} - V_{GS\theta})^2$$

$$= 1.1V + f'(V_{GS\theta}) \cdot V_m \cos \omega t + \frac{1}{2} f''(V_{GS\theta}) (V_m \cos \omega t)^2$$


$$N C_{ox} \frac{W}{L} (V_{in} - V_{th}) R_D$$

$$@ \omega_0: N C_{ox} \frac{W}{L} (V_{GS\theta} - V_{th}) R_D \cdot V_m$$

$$@ 2 \cdot \omega_0: \frac{1}{4} N C_{ox} \frac{W}{L} R_D \cdot V_m^2$$

- The second harmonic distortion: with  $V_m$  of  $20\% \cdot V_{DD}$
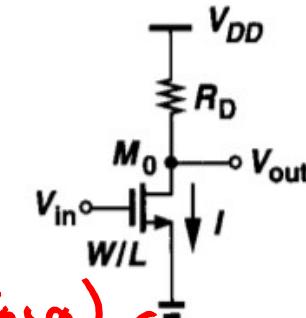
$$\frac{A_{HD2}}{A_F} = \frac{V_m}{4(V_{GS\theta} - V_{th})} \uparrow = 5\%$$



$$\begin{aligned} & \frac{1}{2} \mu C_{ox} \frac{W}{L} R_D \left( V_m^2 \cos^2 \omega t \right) \\ & \frac{1}{2} (1 + \cos^2 \omega t) \end{aligned}$$

# Nonlinearity for Differential Circuits (IV)

- For the differential amplifier:

$$\Delta V_{out} = (I_{D1} - I_{D2}) R_D$$

*@ around equilibrium point*

$$= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \Delta V_{in} \sqrt{4(V_{GS} - V_{th})^2 - \Delta V_{in}^2}$$

*From Chapter 4:*

$$\delta V_{out} = f(\delta V_{in})$$

$$= R \frac{1}{2} \mu C_{ox} \frac{W}{L} \delta V_{in} \cdot 2(V_{GS} - V_{in}) \left( 1 - \frac{\delta V_{in}^2}{4(V_{ov})^2} \right)^{\frac{1}{2}} \stackrel{=} {(1+\alpha)^\alpha}$$


$$\stackrel{=} {R \mu C_{ox} \frac{W}{L} \delta V_{in} \cdot V_{ov} \left( 1 - \frac{1}{8} \frac{\delta V_{in}^2}{V_{ov}^2} \right)} \stackrel{=} {1 + \alpha \alpha}$$

$$= R \mu C_{ox} \frac{W}{L} \cdot V_{ov} \cdot \delta V_{in} - \frac{1}{8} R \mu C_{ox} \frac{W}{L} \frac{1}{V_{ov}} \cdot \delta V_{in}^3$$

*Single-Tone test:  $\delta V_{in} = V_m \cos \omega_0 t$       @  $\omega_0 \mu C_{ox} \frac{W}{L} V_{ov} \cdot R \cdot V_m$*

- The third harmonic distortion:      @  $3\omega_0 \cdot \frac{1}{32} \mu C_{ox} \frac{W}{L} \frac{R}{V_{ov}} \cdot V_m^3$
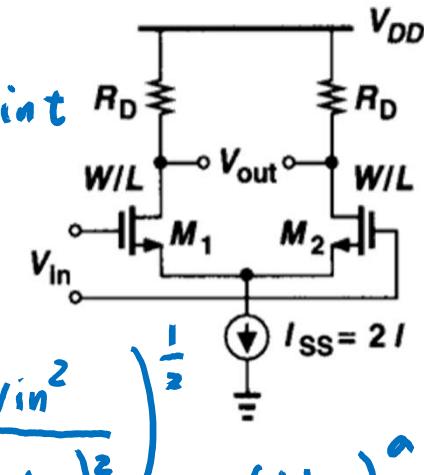
$$\frac{A_{HD3}}{A_F} \approx \frac{1}{32} \frac{V_m^2}{V_{ov}^2} = 0.125\%$$




# Effect of Negative Feedback on Nonlinearity (I)

- ♦ Negative feedback makes the closed-loop gain relatively independent of the op amp's open-loop gain → **Gain Desensitization**
- ♦ Nonlinearity can be viewed as small-signal gain variation with input level → suppressed by negative feedback as well
- ♦ Consider an open-loop gain of

With  $x(t) = V_m \cos \omega t$

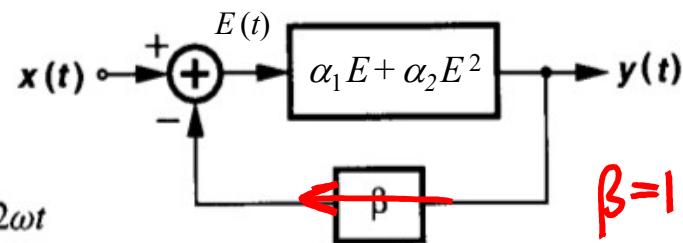and if the output can be approximated as  $y \approx a \cos \omega t + b \cos 2\omega t$



*Find a and b as a function of  $V_m, \alpha_1, \alpha_2$ .*

$$E(t) = x(t) - y(t) = V_m \cos \omega t - a \cos \omega t - b \cos(2\omega t)$$

$$y(t) = @ \omega_0: \alpha_1(V_m - a) - \alpha_2(V_m - a)b = a$$

$$= \alpha_1 E + \alpha_2 E^2 @ 2\omega_0: \left( -\alpha_1 b + \frac{\alpha_2(V_m - a)^2}{2} \right) = b$$