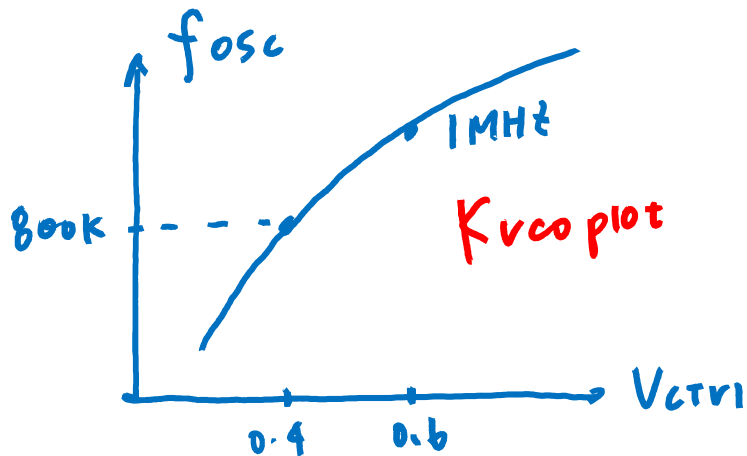


EE4280 Lecture 4:

Voltage-Controlled Oscillator



Ping-Hsuan Hsieh (謝秉璇)
 Delta Building R908
 EXT 42590
 phsieh@ee.nthu.edu.tw


Voltage-Controlled Oscillator

- ◆ To tune the operating frequency

- With a control voltage
- With ideally linear function


$$\omega_{out} = \omega_0 + K_{VCO} \cdot \Delta V_{ctrl}$$



K_{VCO} sensitivity, (VCO) gain

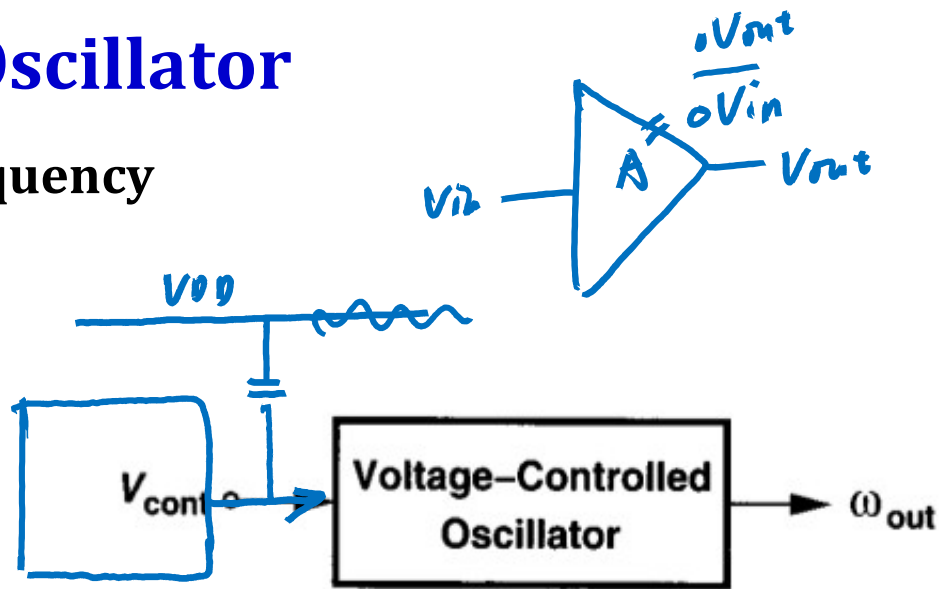


- Center frequency
- Tuning range
- Linearity of transfer function

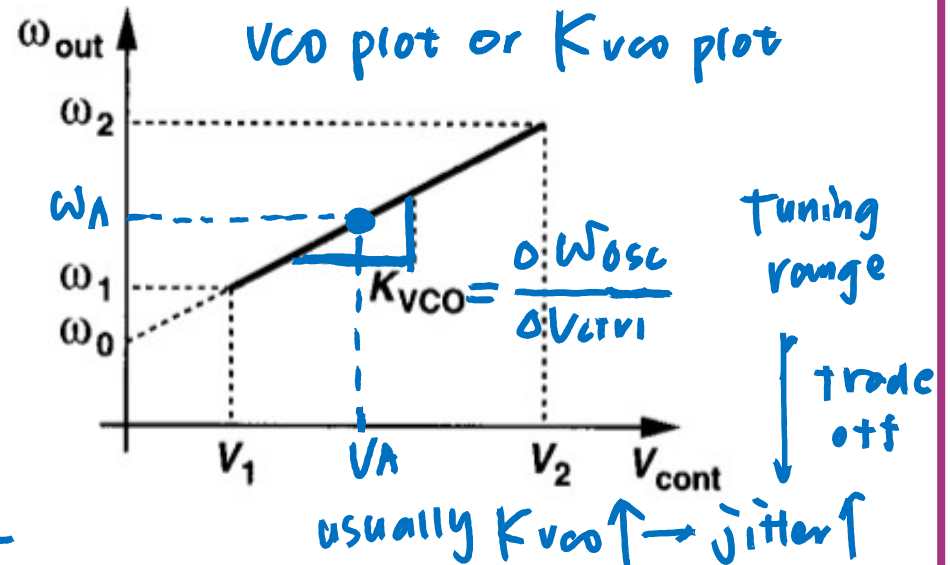- Output signal quality
 - Output amplitude
 - Frequency purity
 - Supply and common-mode rejection
- Power dissipation



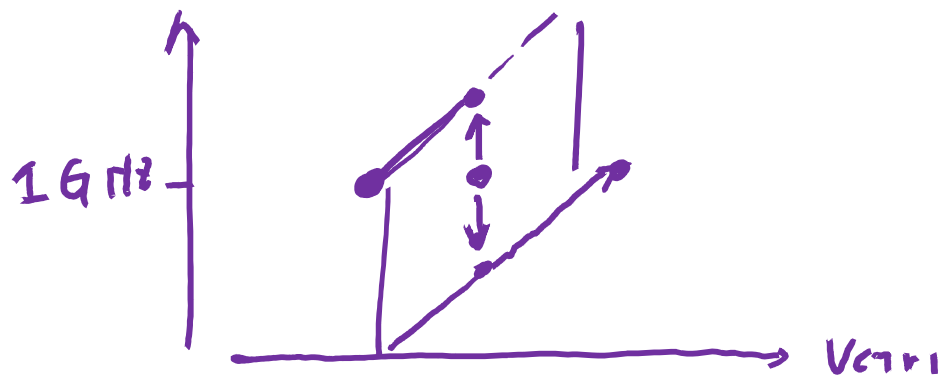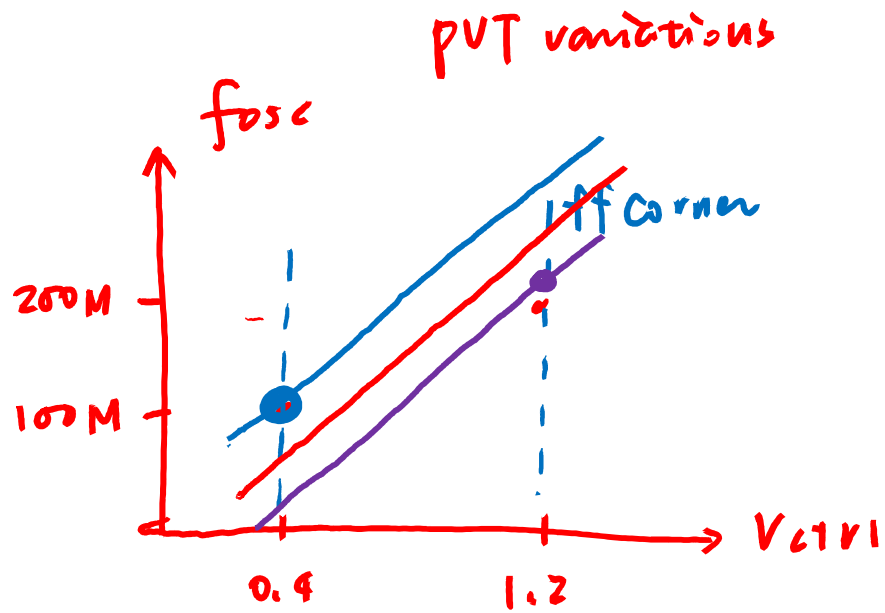

Tuning in Ring Oscillators

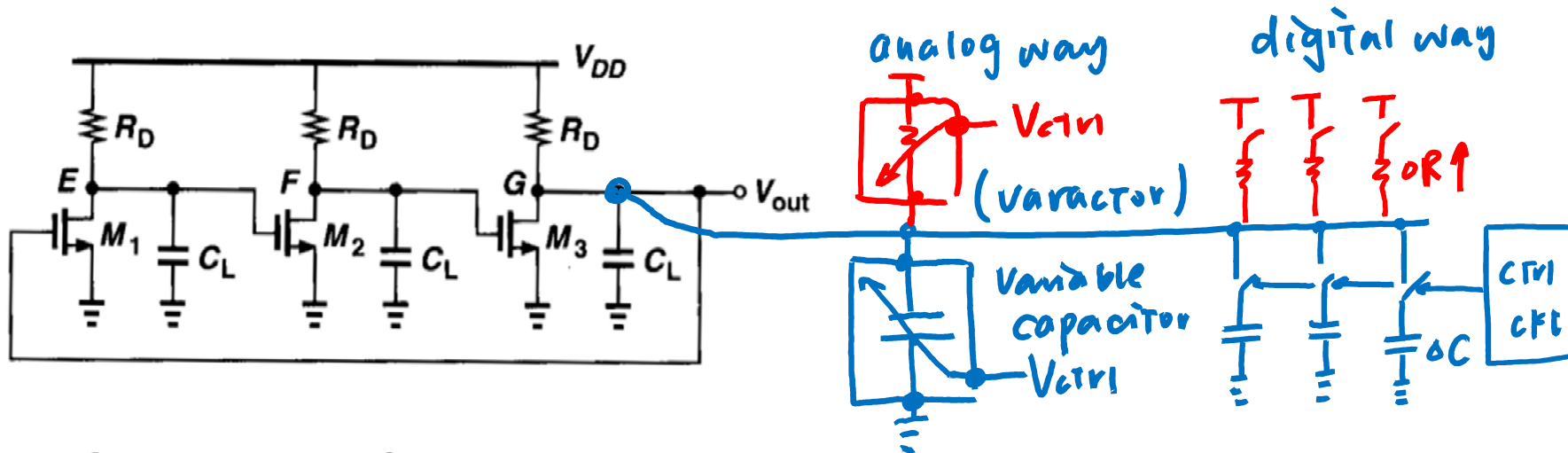


◆ **The operating frequency**


- $\sqrt{3}/2\pi RC$ for small-signal operation
- $1/6T_D$ for large-signal, nonlinear operation

→ Can be tuned by adjusting the R and C values



combining analog/digital method

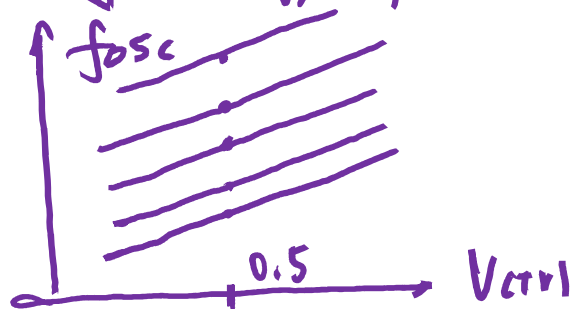

$T \propto R_{eff} \cdot C_{eff}$


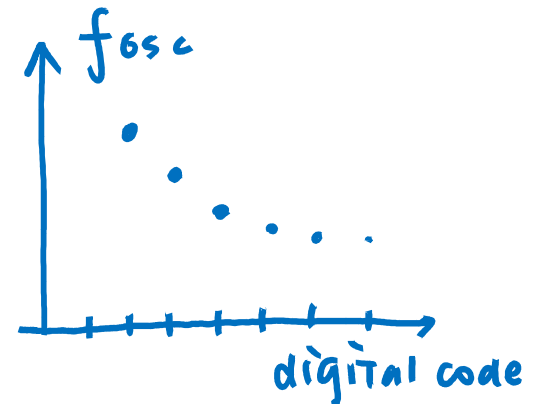


$$R_{eff} = \frac{V_{AB}}{I_{AB}}$$

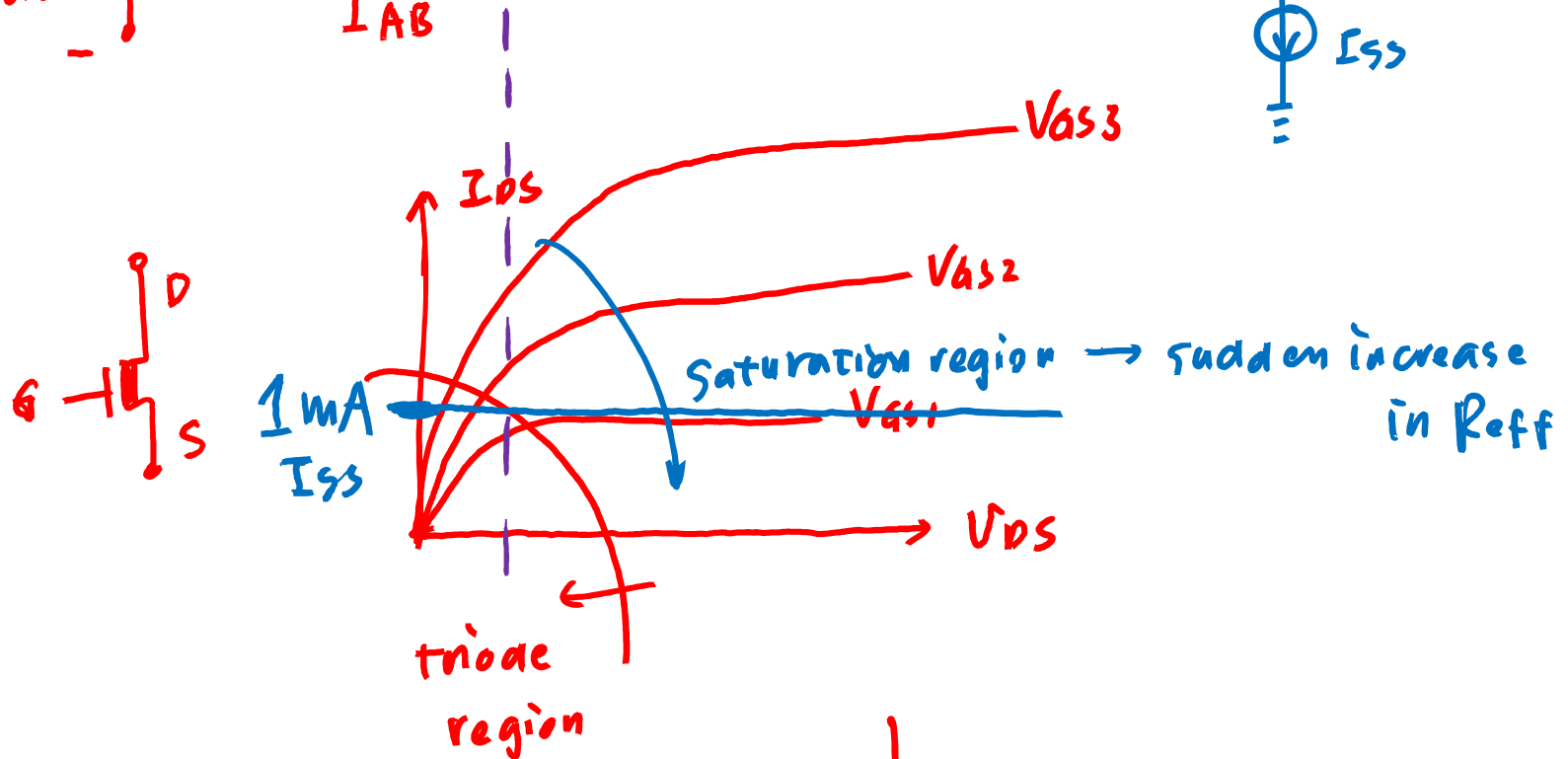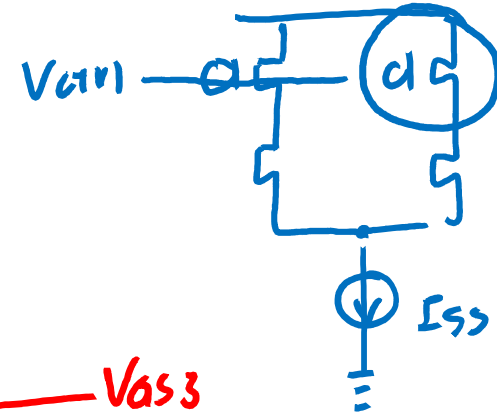

$$R_{on} = \frac{\partial V_{DS}}{\partial I_{DS}} = \frac{1}{\frac{\partial I_{DS}}{\partial V_{DS}}} = \frac{1}{\mu C_{ox} \frac{W}{L} (V_{GS} - V_{th})}$$

Tuning in Ring Oscillators

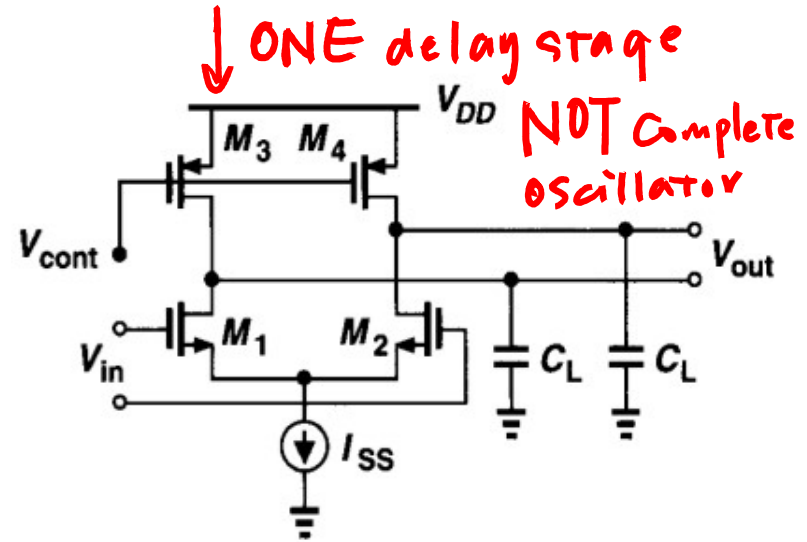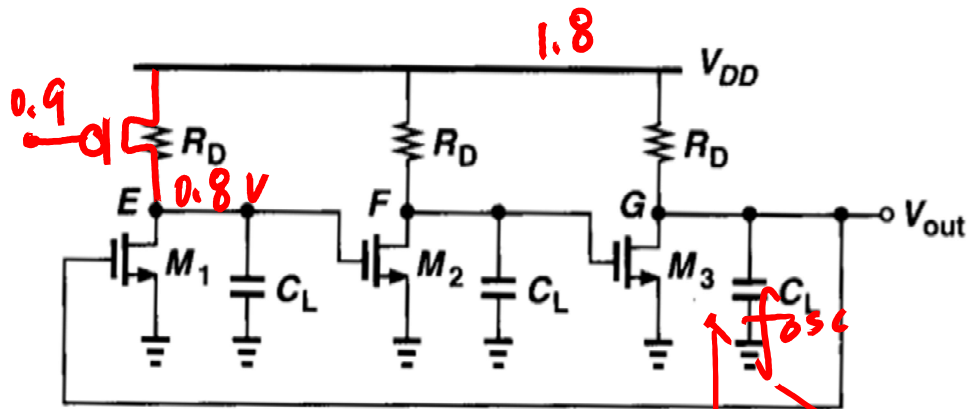

◆ Operating frequency

- $\sqrt{3}/2\pi RC$ for small-signal operation
- $1/6T_D$ for large-signal, nonlinear operation $\propto I_{DRV}/C_L V_{swing}$

→ Can be tuned by adjusting the R and C values

- Resistive load implemented with PMOS operating in triode region

$$R_{on3,4} = 1 / \mu_p C_{ox} \left(\frac{W}{L} \right)_{3,4} (V_{DD} - V_{cont} - |V_{THP}|)$$

$$T_{osc} \propto RC \quad f_{osc} \propto \frac{1}{R} \propto \left(\frac{W}{L} \right) (V_{DD} - V_{cont} - |V_{thp}|)$$

① wider PMOS



② $V_{cont} \downarrow$

Resistive Load with PMOS in Triode Region


◆ Oscillation amplitude varies with operating frequency

• Assume large swing with complete switching

→ Differential swing of

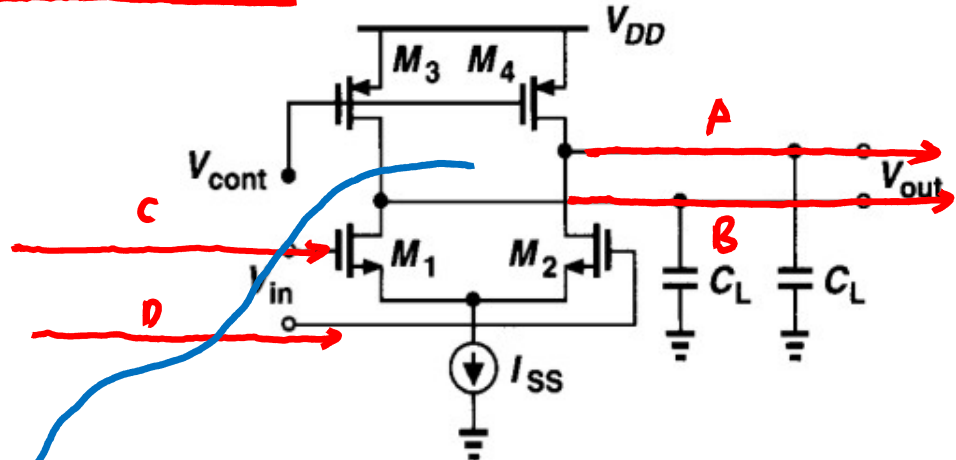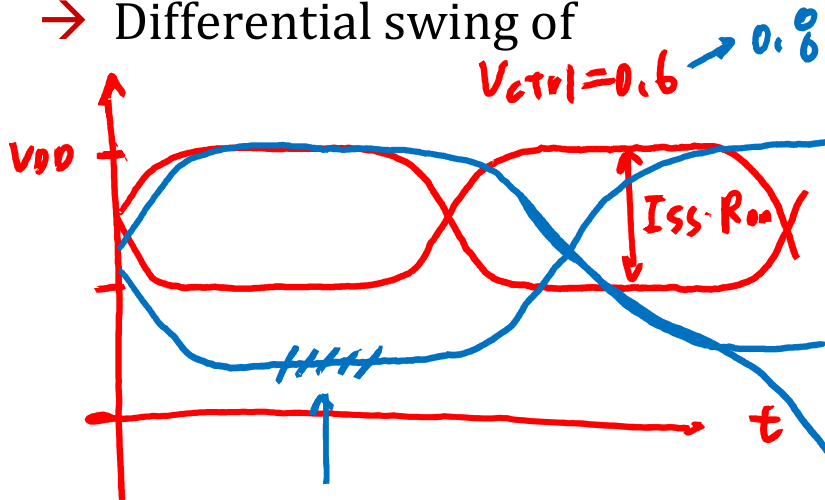

PMOS is likely to enter saturation

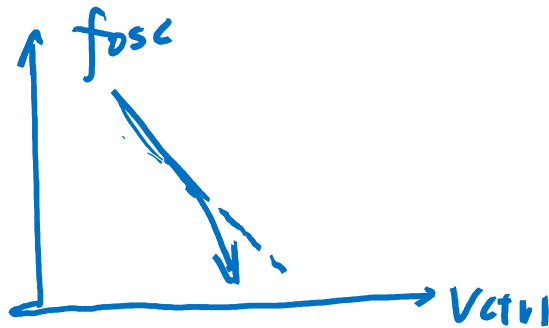


→ Adjust tail current along with operating frequency

- ⑥ With fixed I_{tail}
- as $V_{ctrl} \uparrow$, $R_{on} \uparrow$, $f_{osc} \downarrow$
- $V_{swing} \uparrow$, $\min(V) \downarrow$
- driving PMOS into Sat.
- sudden change in R_{eff}
- K_{VCO} plot not well controlled
- stability issue in PLL

Adjust Tail Current with Operating Frequency (I)

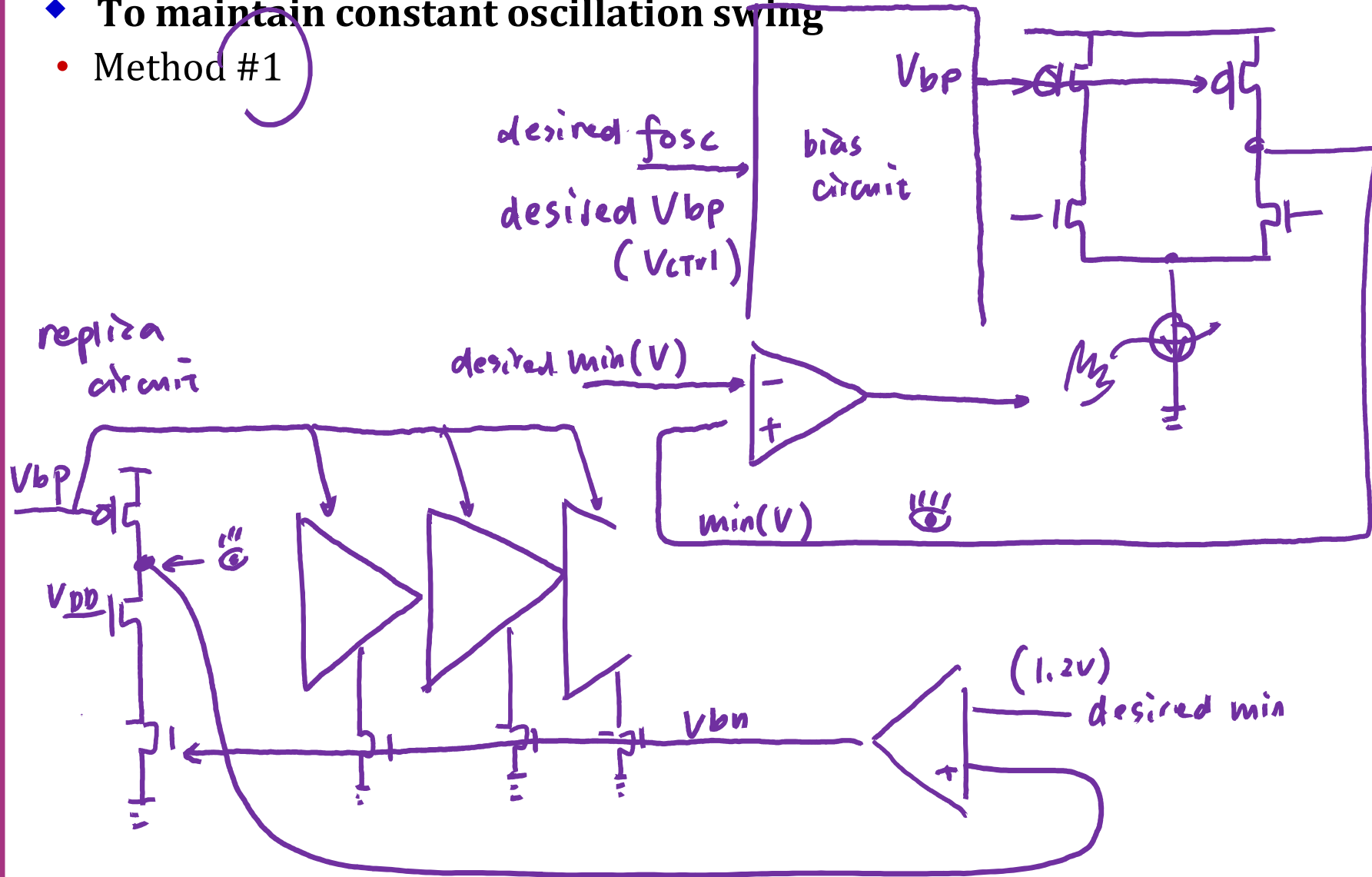- ◆ To maintain constant oscillation swing
 - Method #1





Adjust Tail Current with Operating Frequency (II)

- ◆ **To maintain constant oscillation swing**
 - Method #2

Delay Adjustment through Interpolation - based Method

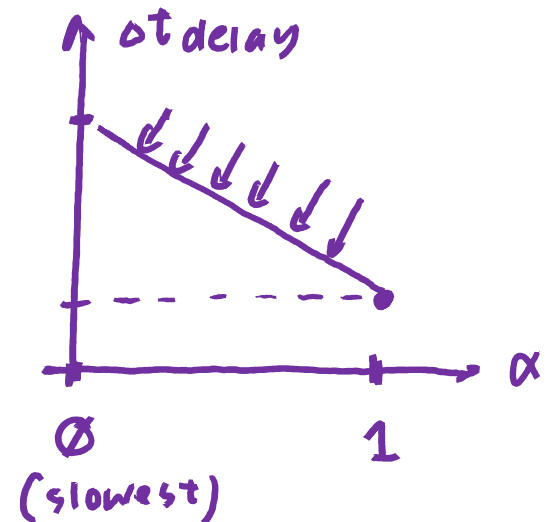
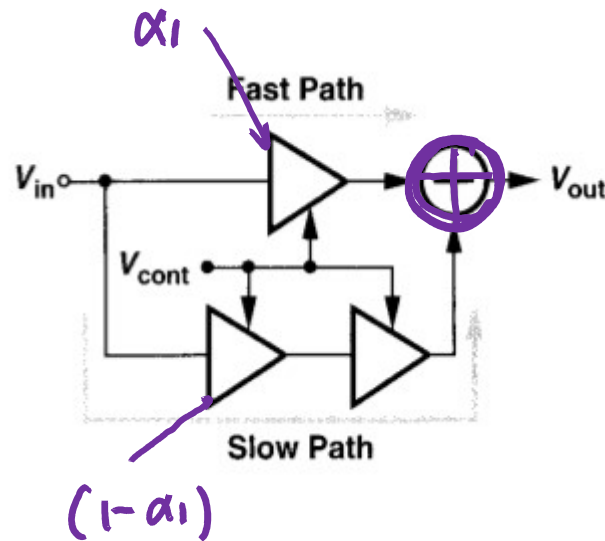
- ◆ V_{cont} changes weighting of two paths with different delays



- Two paths with different delays
 - Multiple stages or different RC time constant
- Addition of two signals
 - In voltage or current domain
- To change weighting of two

A Possible Implementation of Interpolation

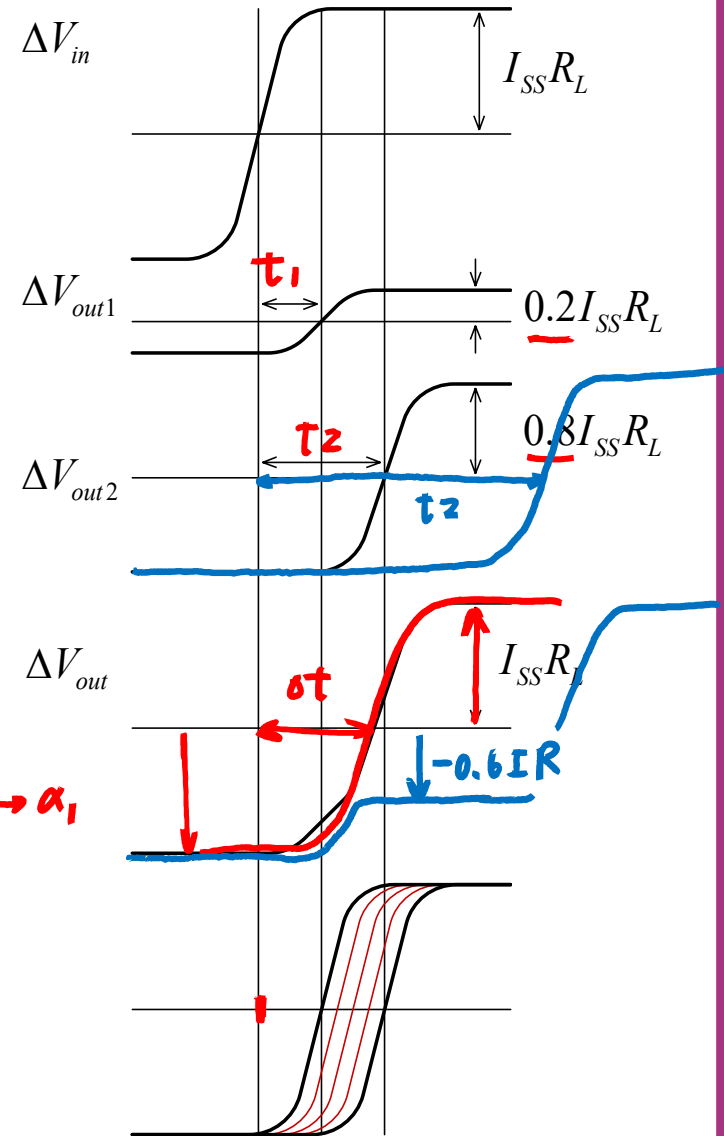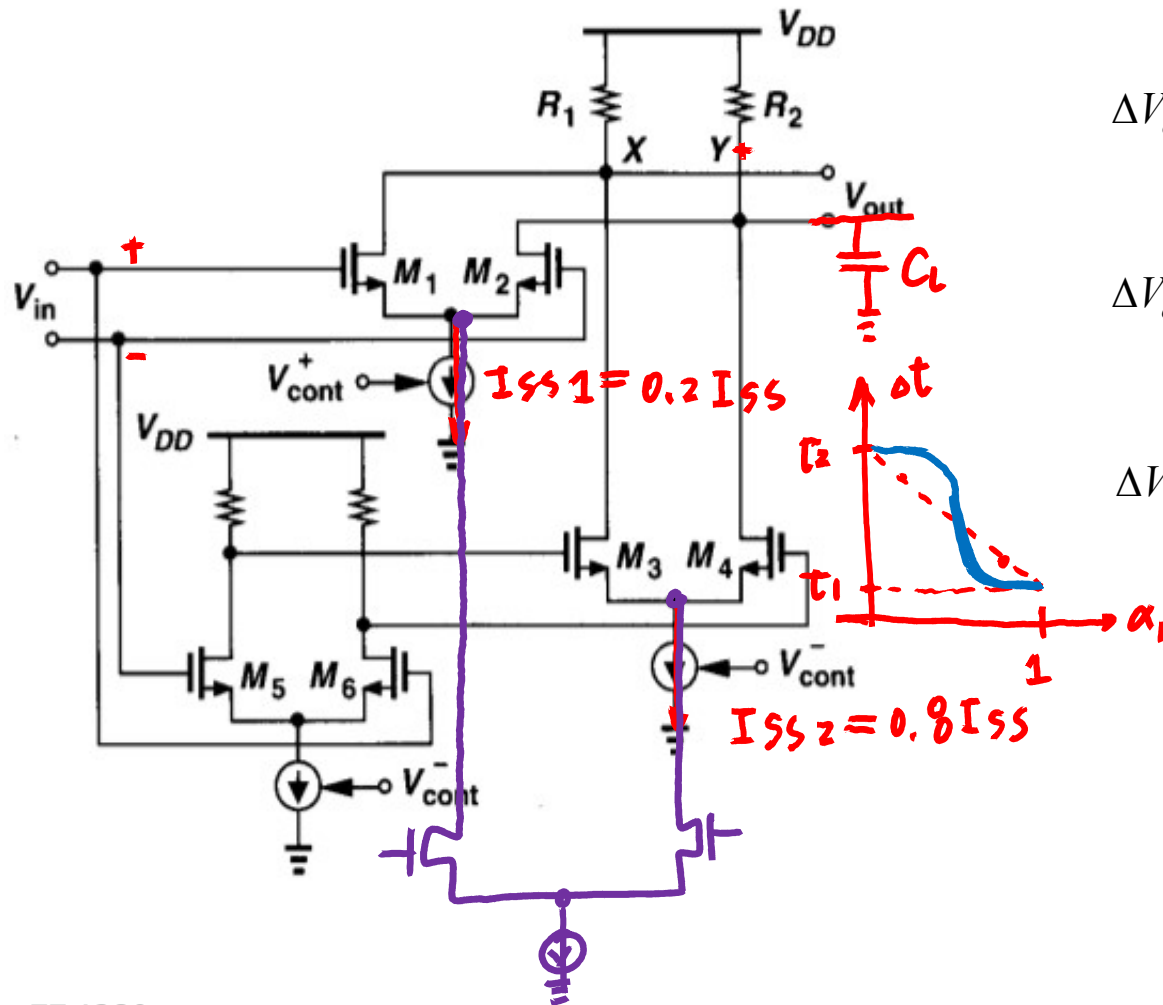- ◆ Summation in current domain
- ◆ Weighting adjusted through tail current



Tail Current Adjustment with Constant Swing

- ◆ Folded structure to save voltage headroom

