

---

# EE4280 Lecture 5: LC Oscillators

---

**Ping-Hsuan Hsieh (謝秉璇)**


Delta Building R908

EXT 42590

[phsieh@ee.nthu.edu.tw](mailto:phsieh@ee.nthu.edu.tw)
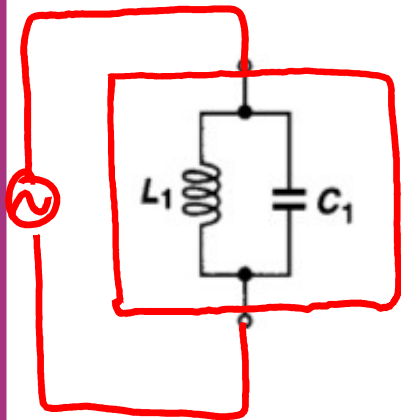
# Starting from LC Tank ...

- ◆ **At resonant frequency of  $\omega_{res} = 1/\sqrt{L_1 C_1}$** 
  - The inductor and the capacitor impedance are **equal** and **opposite**
- ◆ **Ideally without any loss, the impedance goes to infinity  $\rightarrow$  infinite  $Q$** 
  - Inductive when  $\omega < \omega_{res}$ , voltage leads current by  $90^\circ$
  - Capacitive when  $\omega > \omega_{res}$ , current leads voltage by  $90^\circ$



$$V \sin\left(2\pi \frac{1}{\sqrt{LC}} t\right)$$


$$Z_{\text{tank}} = Z_L \parallel Z_C = \frac{sL \cdot \frac{1}{sC}}{sL + \frac{1}{sC}} = \frac{sL}{1 + s^2 LC}$$

$$= \frac{j\omega L}{1 - \omega^2 LC}$$


@ LF  $Z_{\text{tank}} \sim j\omega L$

@ HF  $Z_{\text{tank}} \sim 1/sC$


@  $\omega_{res} = \frac{1}{\sqrt{LC}}$  when  $|Z_L| = |Z_C|$   $\omega L = \frac{1}{\omega C}$   $Z_{\text{tank}} \rightarrow \infty$  (open)

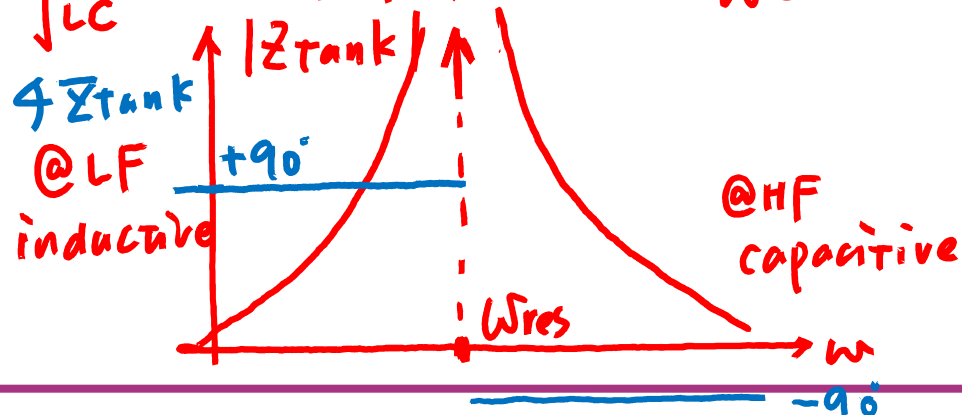

# Capacitor and Inductor $|I| \uparrow$ with $\omega \uparrow, C \uparrow$

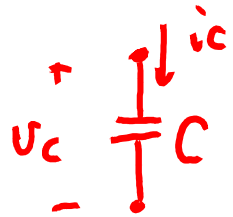


$$i_c = C \cdot \frac{dv_c}{dt}$$

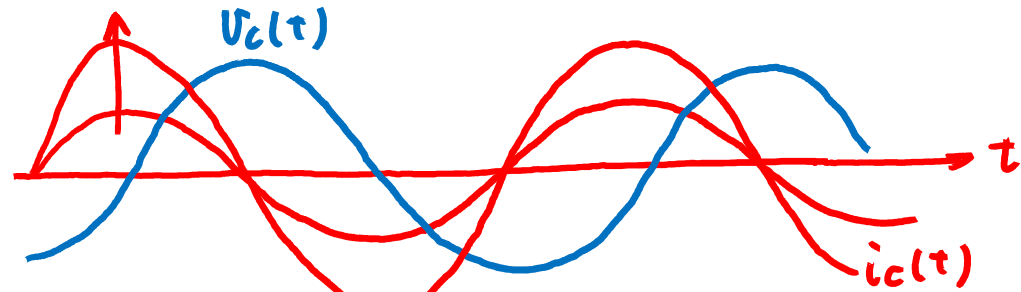


$$Z_c = \frac{1}{sC} = \frac{1}{j\omega C} = \frac{V_c}{I_c}$$

$$\angle V_c - \angle I_c = -90^\circ$$

$$\frac{|V_c|}{|I_c|} = \frac{1}{\omega C}$$

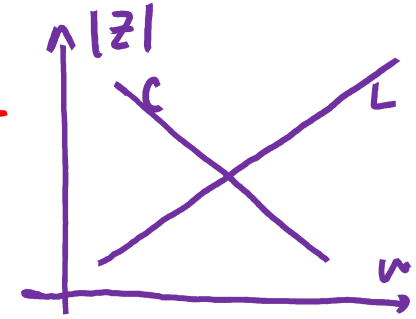

$$v_L = L \cdot \frac{di_L}{dt}$$

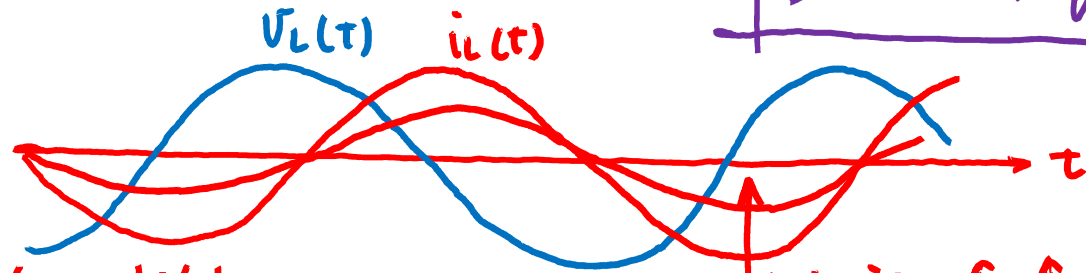


$$Z_L = sL = j\omega L = \frac{V_L}{I_L} \quad \frac{|V_L|}{|I_L|} = \omega L$$

$|I|$  with  $\omega \uparrow, L \uparrow$
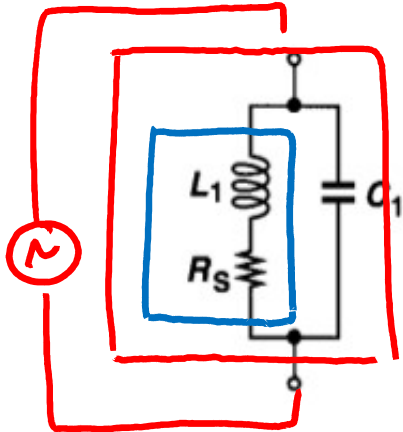
# Consider Loss in the Tank

- ◆ In practice, devices suffer from resistive components


- Series resistance of the metal wire can be modeled as:



$$= (SLT R_S) \parallel \frac{1}{SC}$$

$$Z_{eq}(s) = \frac{(R_S + L_1 s)}{1 + L_1 C_1 s^2 + R_S C_1 s}$$

$$|Z_{eq}(s = j\omega)|^2 = \frac{R_S^2 + L_1^2 \omega^2}{(1 - L_1 C_1 \omega^2)^2 + R_S^2 C_1^2 \omega^2}$$

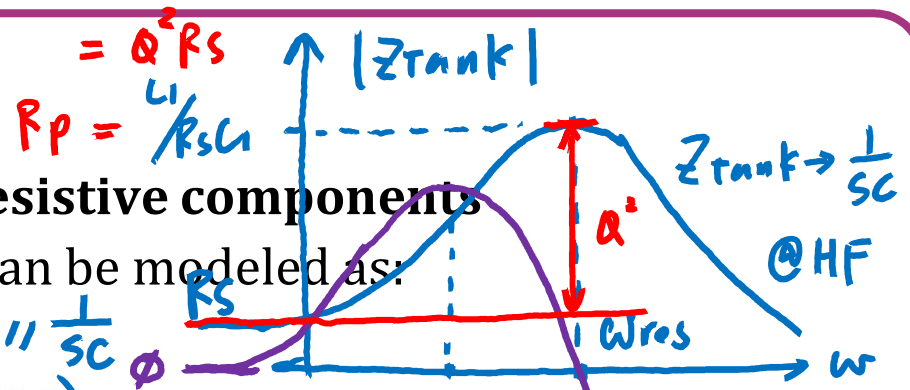


$Q$  of the inductor =  $\omega L_1 / R_S$

$$\approx \frac{SLI}{SRC_1} = \frac{L_1}{RC_1} @ \omega = \frac{1}{\sqrt{LC}}$$

with  $\omega L \gg R_S$  sufficient  $Q$

- The impedance does not go to infinity  $\rightarrow$  this circuit has a finite  $Q$
- $\rightarrow$  The impedance peaked in the vicinity of  $\omega = 1/\sqrt{L_1 C_1}$

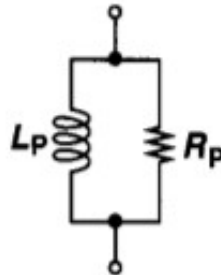- For easy analysis and to provide intuition:




$$L_1 s + R_S = \frac{R_P L_P s}{R_P + L_P s}$$

$$\rightarrow L_P = L_1 \left(1 + \frac{R_S^2}{L_1^2 \omega^2}\right) = L_1 \left(1 + \frac{1}{Q^2}\right) \approx L_1$$

for  $Q \gg 1$
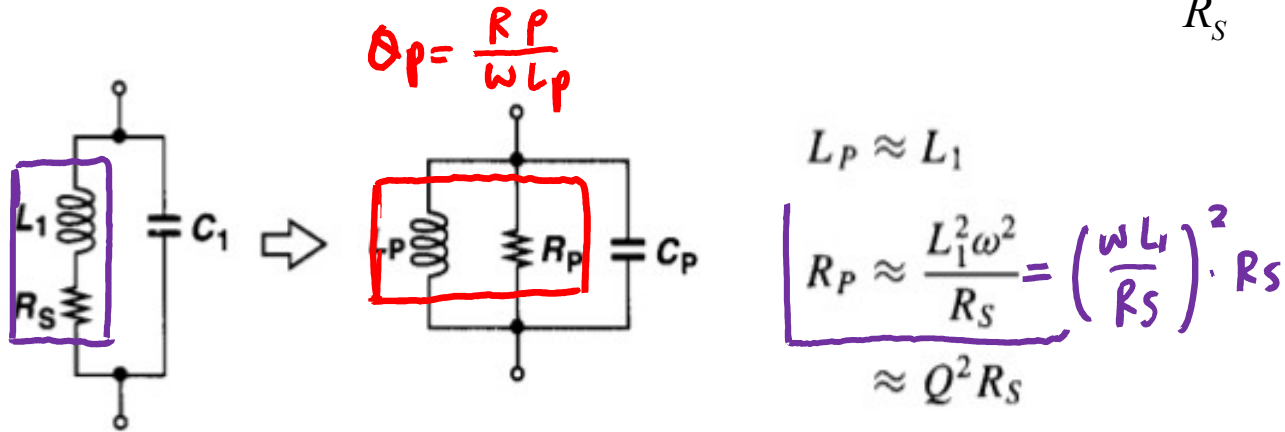
# RLC Tank

- As the operating frequency is high enough and  $Q_L = \frac{\omega L_1}{R_S} \gg 1$



- At  $\omega = 1/\sqrt{L_1 C_1}$ , the tank reduces to a simple resistor

$$Z_{\text{tank}} = \frac{L_1}{R_S C_1} = Q^2 R_S$$

# Common-Source Stage with LC Tank Load (I)





◆ With a single stage

• At low-frequencies

@DC:




• At resonant frequency  $\frac{\Delta V_{out}}{\Delta V_{in}} = -g_{m1} R_P$

So  $V_{mcm} \approx V_{DD}$

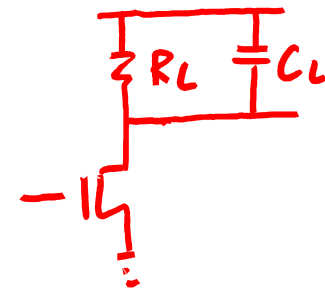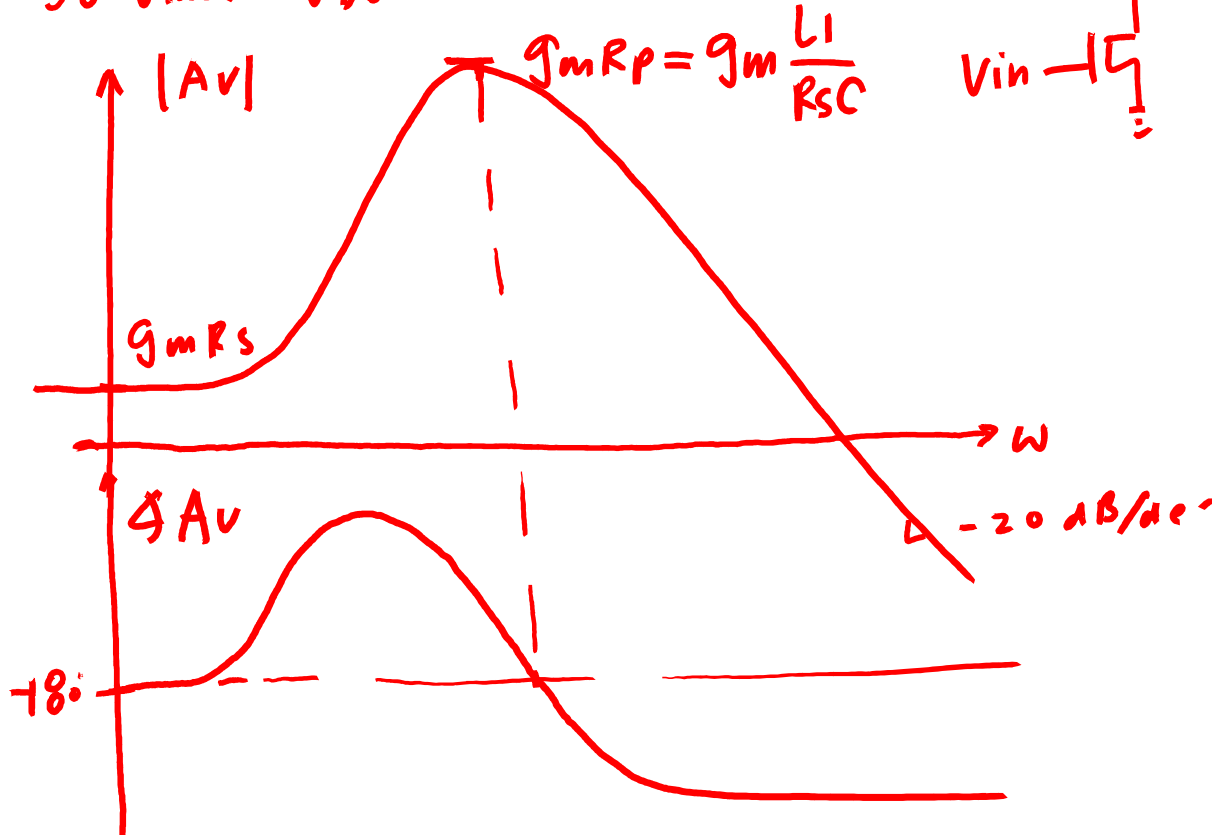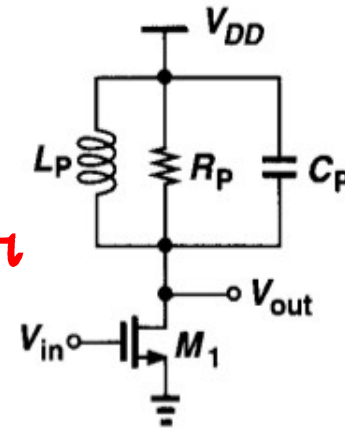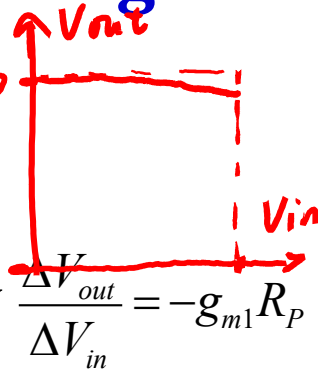

# Common-Source Stage with LC Tank Load (II)

@  $\omega = \frac{1}{\sqrt{LC}}$





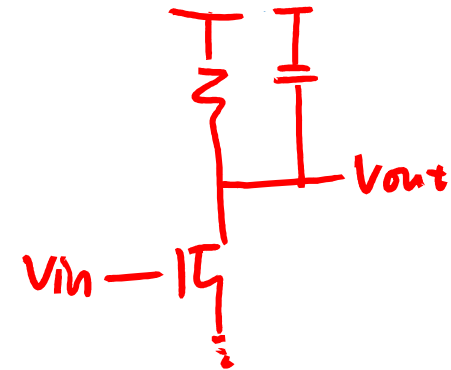
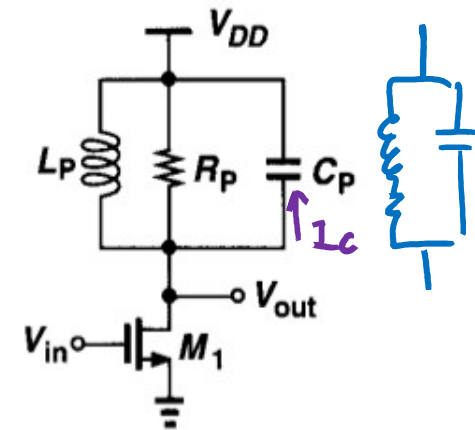
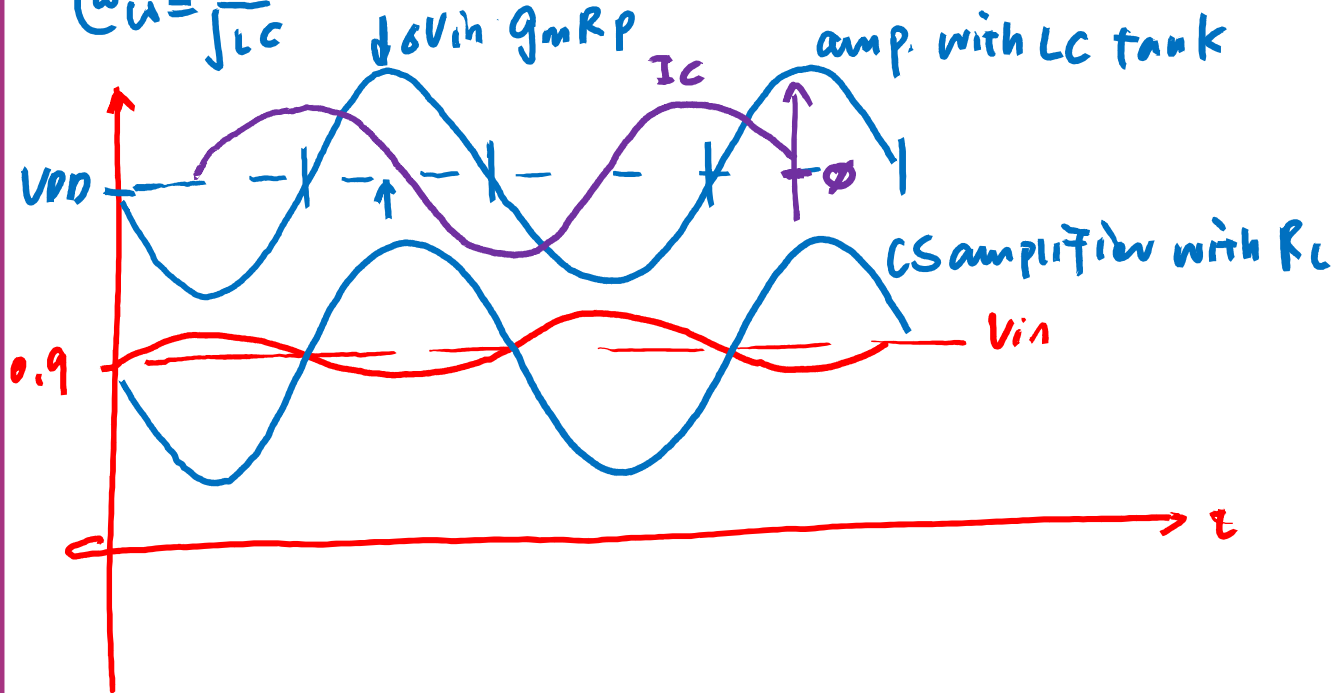


- \*  $V_{out}$  can be "momentarily" higher than  $V_{DD}$
- \*  $L_P // C_P$  behaves like open
- \* current of  $M_1$  flows into  $R_S$   
there are 'reactive current' between  $L_P$  &  $C_P$

# Two-Stage CS with LC Tank Load

## Cross-coupled oscillator

regulator

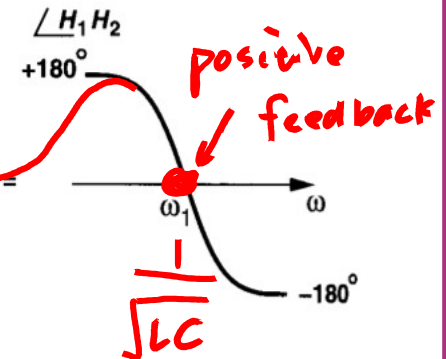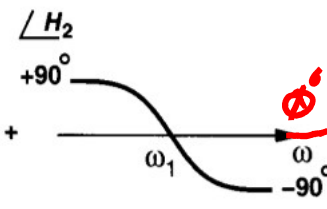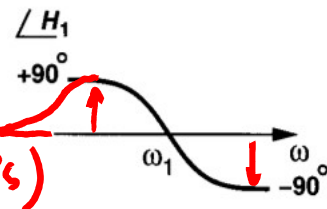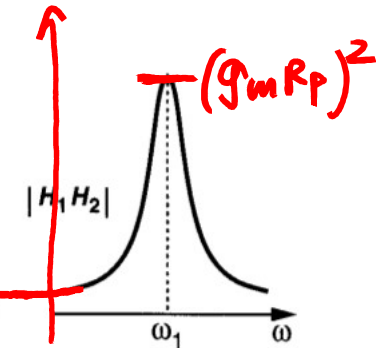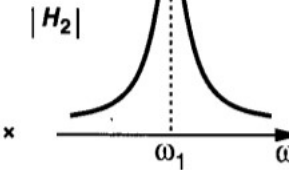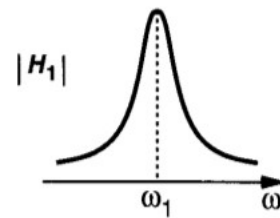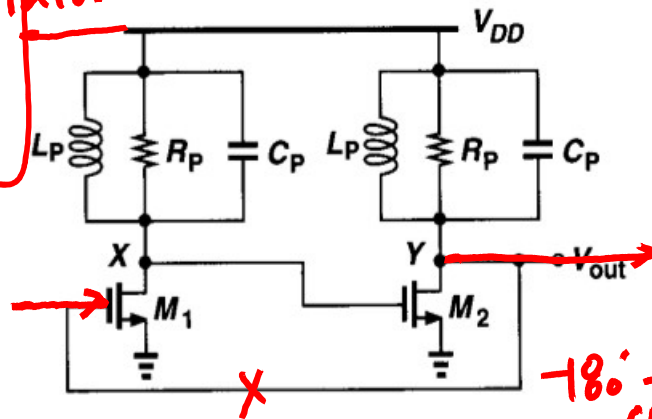

### Two frequencies with 360° phase shift

- Does not latch up at low-frequencies
- Provide zero *additional* phase shift at resonant frequency

### Gain requirement





- $g_{m1} R_P g_{m2} R_P \geq 1$   $g_m = \mu_n \frac{W}{L} (V_{DD} - V_{th})$
- If the inductor dominates the quality factor
- larger inductor is preferred to save power
- The drain current (bias condition) and output swing depend on  $V_{DD}$

$$R_P \approx \frac{L_1^2 \omega^2}{R_S} = \frac{L_1}{C_1 R_S} \text{ at } \omega = \frac{1}{\sqrt{L_1 C_1}}$$



# Cross-Coupled Oscillator (I)

- ◆ With tail current  $I_{SS}$

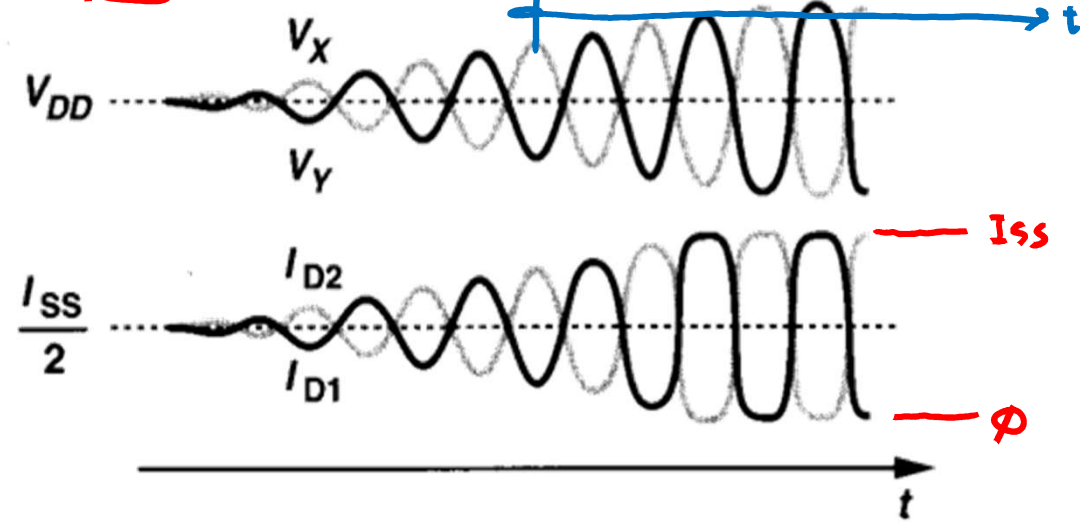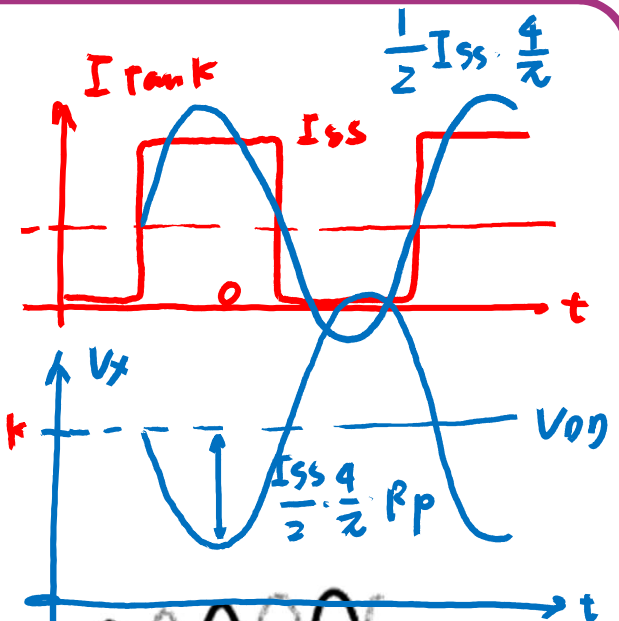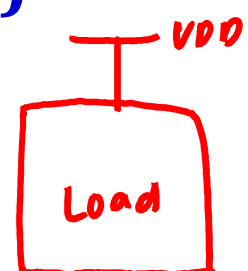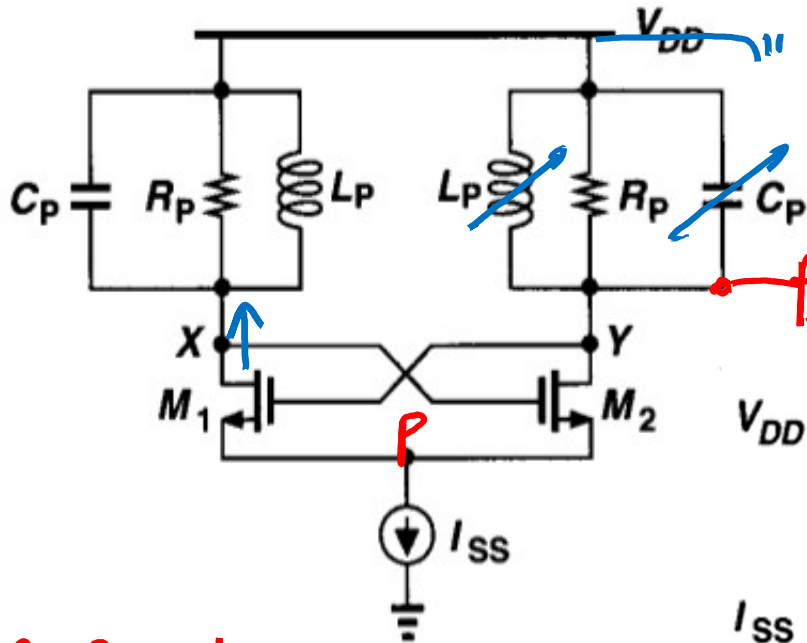


$g_m R_p \gg 1$

$$g_m = \sqrt{2 \cdot \mu \cdot C_{ox} \cdot \frac{W}{L} I_{SS}}$$


- ◆ Common mode at  $\sim V_{DD}$
- ◆  $I_{SS}$  and  $R_p$  determine oscillation amplitude

# Negative Resistance (I)

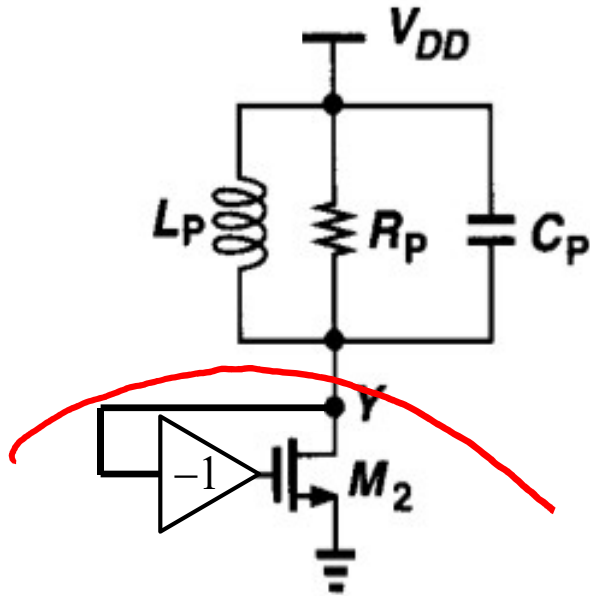
## ◆ Half-circuit of the cross-coupled oscillator



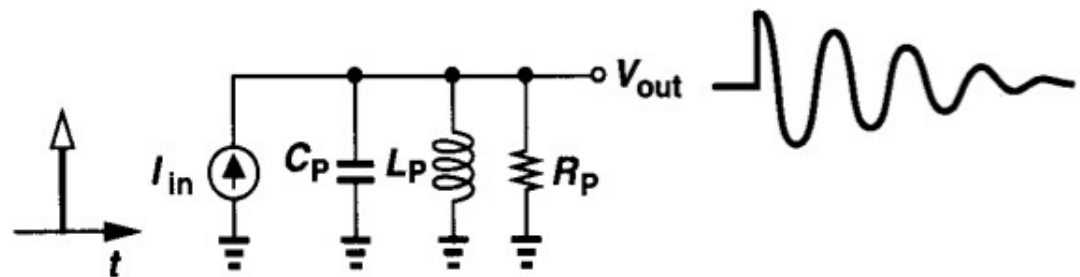- Without bottom part of the circuit  
– only the RLC tank (lossy tank)



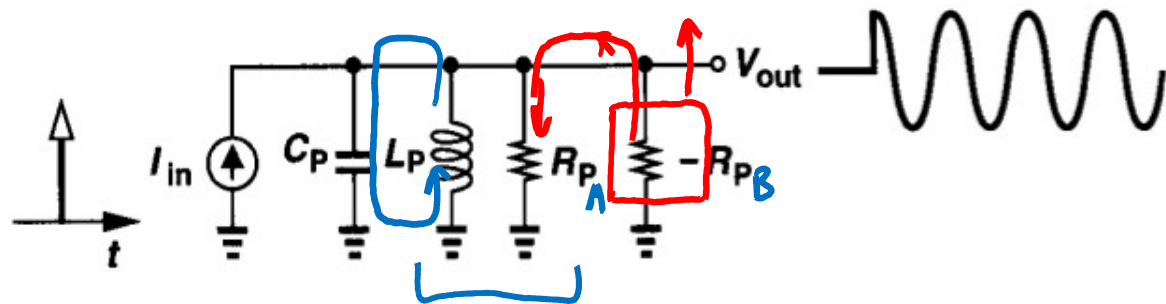- Oscillation can be sustained with **negative** resistance




## Negative Resistance (II)

- ◆ The negative resistance has to be strong enough to sustain oscillation

$$R_{PA} \parallel (-R_{PB}) = \frac{-R_{PA} \cdot R_{PB}}{R_{PA} - R_{PB}} < \infty \Rightarrow R_{PB} < R_{PA}$$

So that the negative res  
is "strong"  
enough

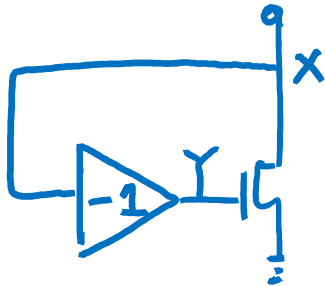- ◆ A positive feedback structure may create negative resistance



$$\text{open-loop } R_{out} = r_o$$

$$\text{closed-loop } R_{out} = \frac{r_o}{1 - g_m r_o} \rightarrow -\frac{1}{g_m}$$

with  $g_m r_o \gg 1$


$$\Rightarrow \frac{1}{g_m} < R_p \xrightarrow{\text{oscillation requirement}} g_m R_p > 1$$

# LC Voltage-Controlled Oscillator

- ◆ **The resonant frequency**

- Little dependence on bias current and transistor transconductance
- Voltage-controlled capacitor → varactor

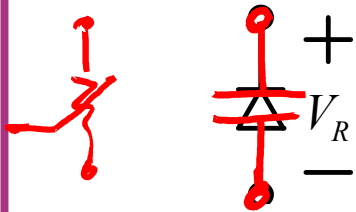- For example: a reversed-biased pn junction



$$C_{var} = \frac{C_0}{\left(1 + \frac{V_R}{\phi_B}\right)^m} \cong 0.3 - 0.9$$

$$\phi_B \cong 0.7V$$

$$V_{Rmin} = 0V \quad C_{eff} = C_0$$

$$V_{Rmax} = V_{DD} = 2V \quad C_{eff} \cong 0.62 C_0$$


$$f_{min} = \frac{1}{\sqrt{LC_0}}$$

$$f_{max} = \frac{1}{\sqrt{L \cdot 0.62^2 C_0}} \cong 1.27 \frac{1}{\sqrt{LC_0}}$$

- Limited range of  $V_R$  results in limited capacitance range.
- Furthermore, to increase the operating frequency,  $C_0$  is minimized.
- Trade-off between operating frequency and tuning range
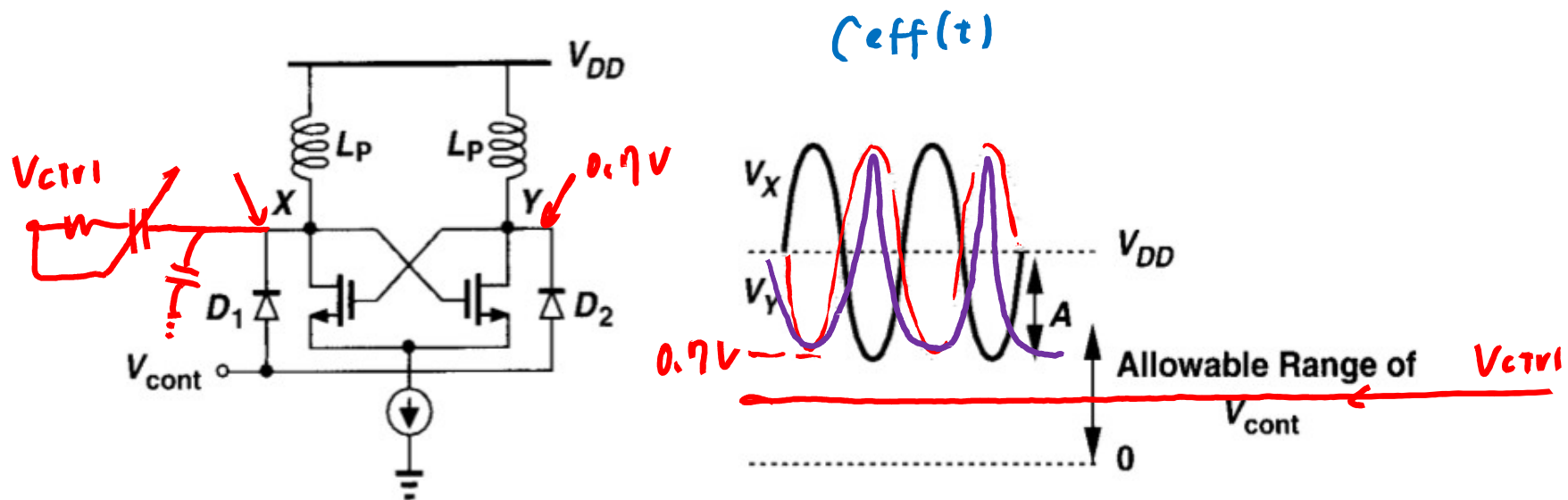
# Adding Varactors to Cross-Coupled Oscillator



- ◆ To avoid forward biasing the two diodes
  - Trade-off between signal swing and tuning range




- ◆ Capacitance depends on signal level and varies over time
  - Average value (depending on  $V_{cont}$ ) determines operating frequency
  - Oscillation waveform is distorted slightly

# Varactor Diode in CMOS Technology

## ◆ PN junction

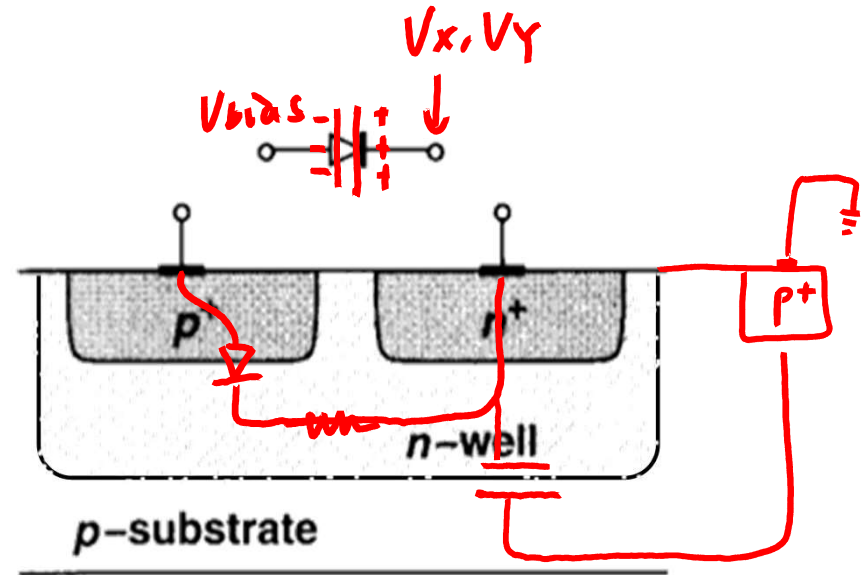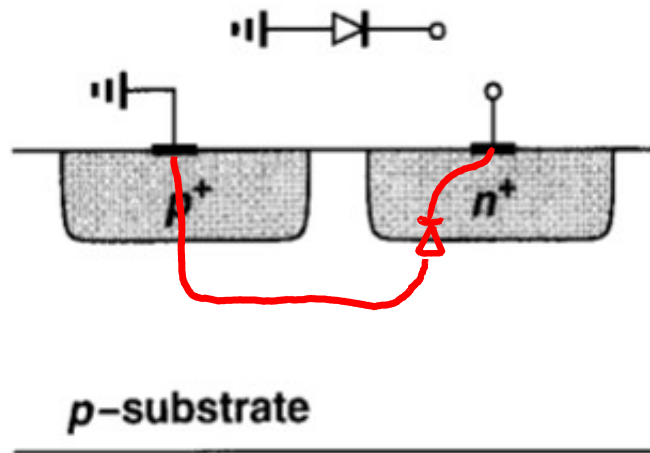

- Anode has to be grounded
- Not tunable

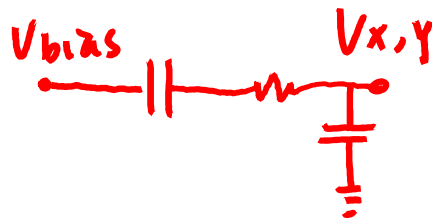

- High resistivity in n-well
- High capacitance between n-well and ground
- Fixed capacitance on signal nodes
- Degrading tuning range

$$C_{total} = C_{var} + C_{fixed}$$