
EE4280 Lecture 6: Phase-Locked Loops

Ping-Hsuan Hsieh (謝秉璇)


Delta Building R908

EXT 42590

phsieh@ee.nthu.edu.tw



Mathematical Model of VCO

$$\phi(t) = \omega_0 t$$

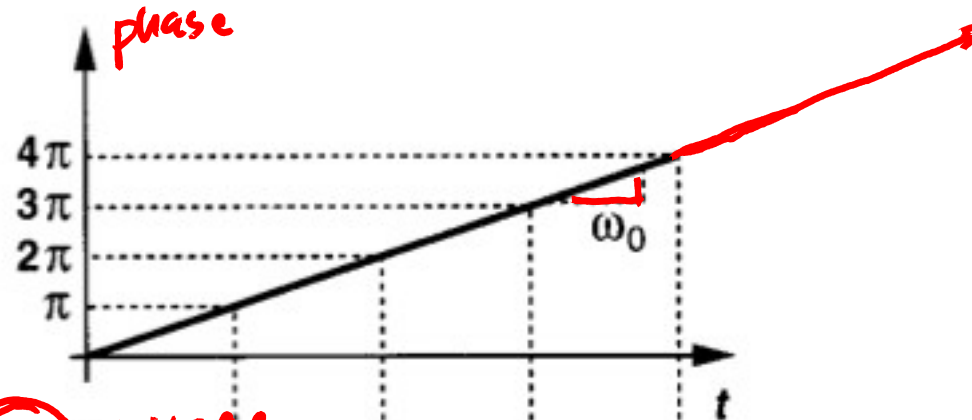

$$V_0(t) = V_m \sin(\omega_0 t)$$

voltage

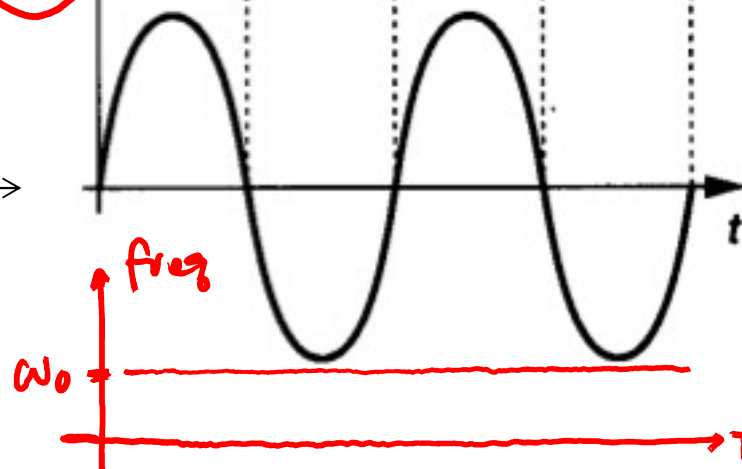
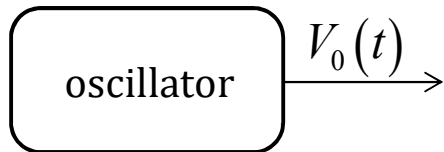


- ◆ Oscillator's output phase is accumulated over time

Mathematical Model of VCO

total phase $\phi(t) = \omega_0 t$

$V_0(t) = V_m \sin \omega_0 t$

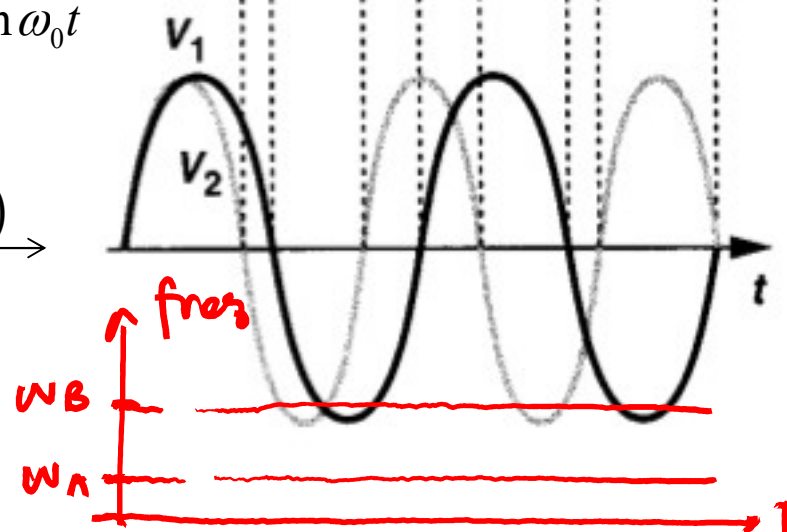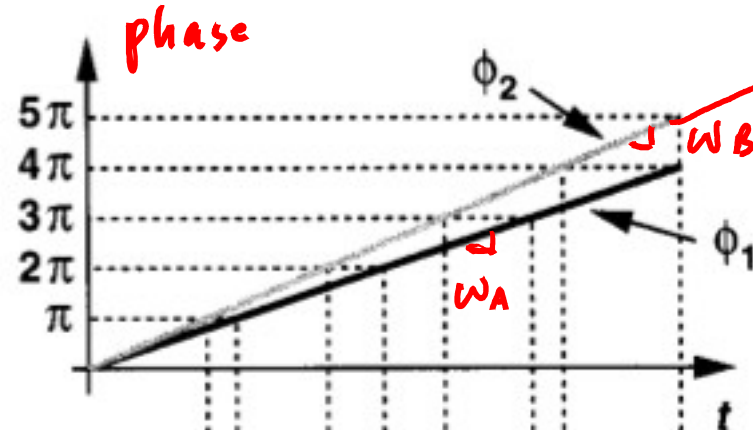


- ◆ Oscillator's output phase is accumulated over time
- ◆ Faster frequency results in faster phase accumulation

From V_{ctrl} to Output Frequency and Phase

- Usually a change in V_{ctrl} immediately results in a change in ω_{out}

→ Memoryless

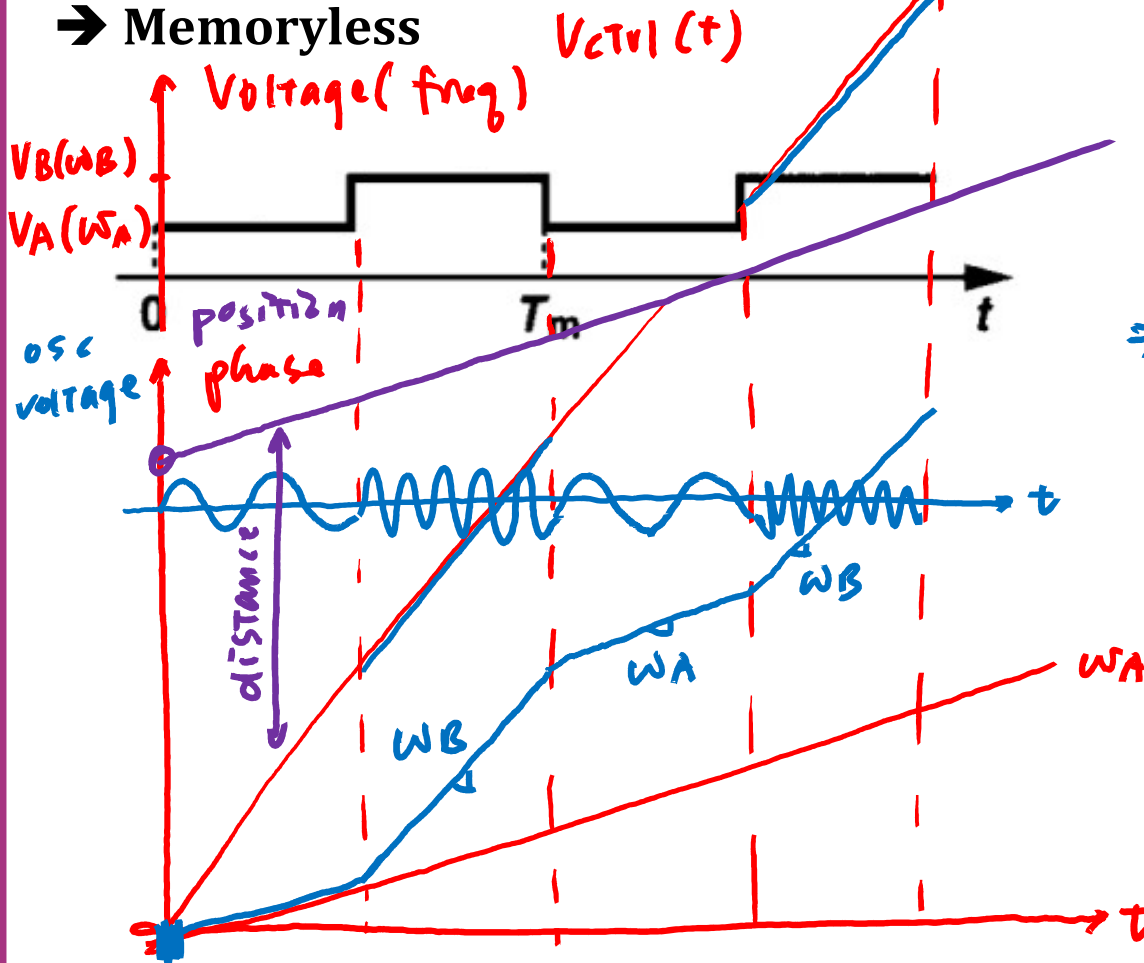

If $V_{ctrl}(t) \rightarrow \omega(t)$



$$\Rightarrow \phi(t) \neq \omega(t) \cdot t$$

$$\Rightarrow \phi(t) = \int \omega(t) dt + \phi_0$$

$\phi_0 = \emptyset$

- If the frequency is a known function of time

Excessive Phase and Transfer Function

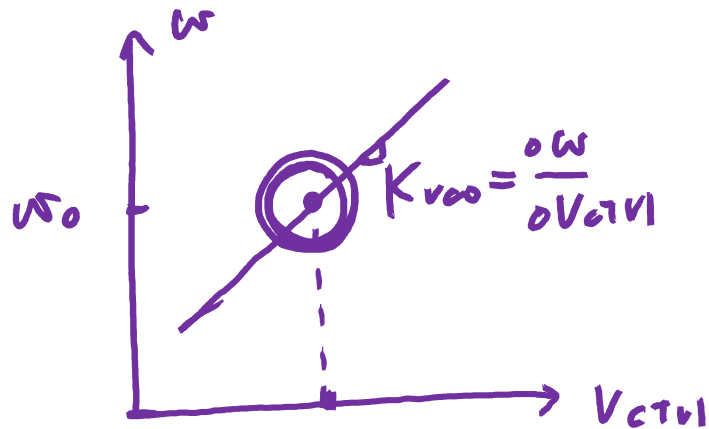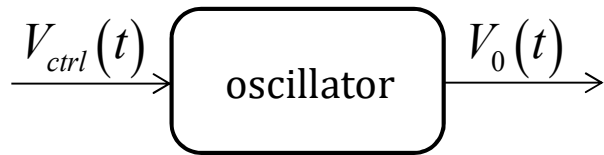

$$\therefore \omega(t) = \omega_0 + K_{vco} \cdot \Delta V_{ctrl}(t)$$

total phase

$$\phi(t) = \int \omega(\tau) \cdot d\tau + \phi_0 \quad \text{excessive phase}$$

$$= \underbrace{\omega_0 t + \int K_{vco} \cdot \Delta V_{ctrl}(\tau) \cdot d\tau}_{\phi_{ex}(t)} + \underbrace{\phi_0}_{\phi}$$

$$V_{out}(t) = A_0 \cdot \cos\left(\omega_0 t + \int K_{vco} \cdot \Delta V_{ctrl}(\tau) \cdot d\tau + \phi_0\right)$$

from $V_{ctrl}(\tau)$ to $\phi_{ex}(t)$

- Often times, the excessive phase is of interest $\phi_{ex}(t) = K_{vco} \int V_{ctrl}(t) dt$


→ Transfer function:

from

$$\frac{\phi_{ex}(s)}{V_{ctrl}(s)} = \frac{K_{vco}}{s} \quad \#$$


Frequency Modulated Signal Example

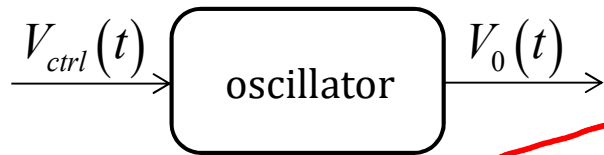- ◆ With a small sinusoidal control voltage




$$\omega(t) = \omega_0 + K_{VCO} \cdot V_m \cos \omega_m t$$

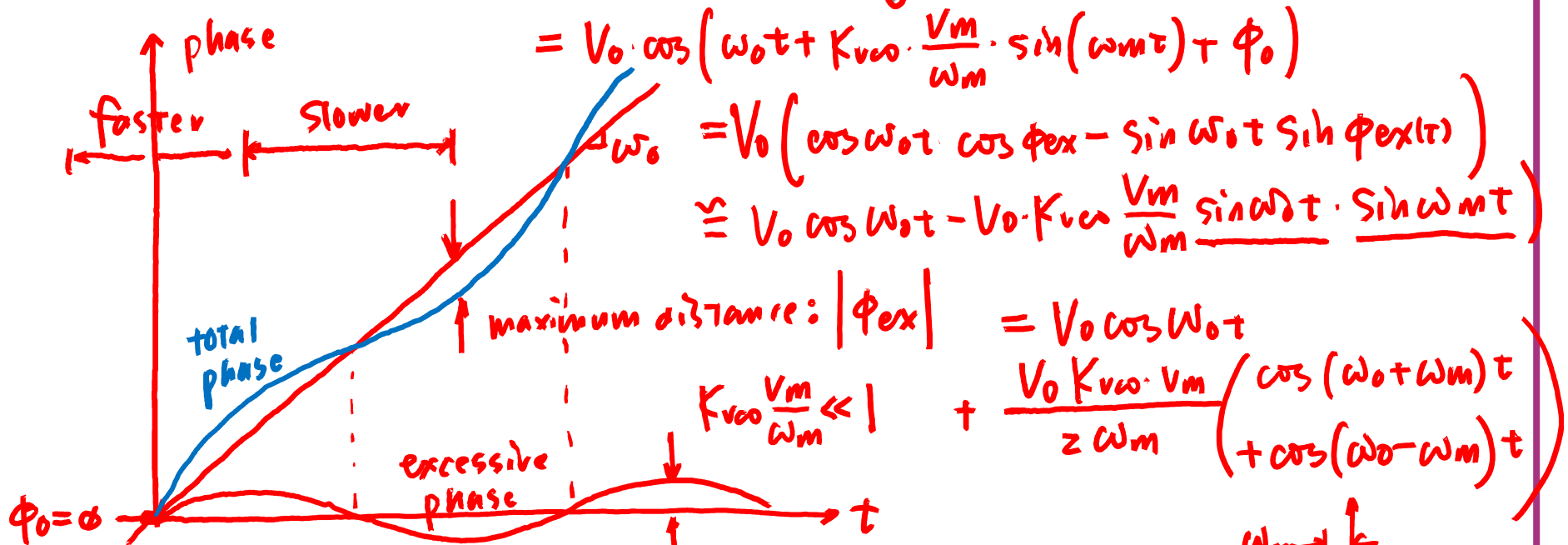$V_{ctrl}(t) = V_m \cos \omega_m t \rightarrow V_{out}(t) = V_0 \cos(\omega_0 t + K_{VCO} \int V_{ctrl} dt)$




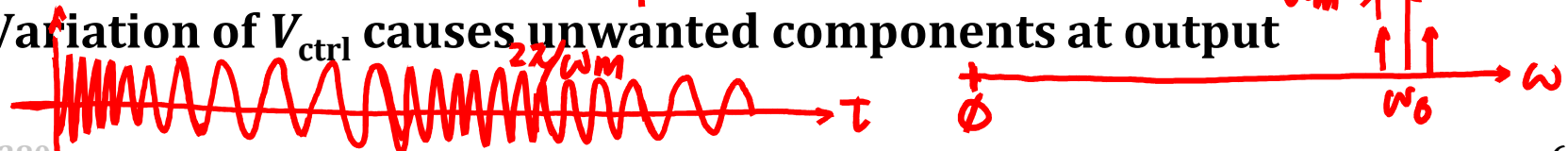- ◆ Variation of V_{ctrl} causes unwanted components at output




Phase-Locked Loops (I)

- ◆ **Phase-locked loops are used to generate a well-defined clock from a reference source**
- ◆ **Wide range of applications**
 - Clock generation and frequency synthesis
 - Generating a 10GHz clock from a 100MHz reference clock
 - Modulation/demodulation in wireless systems
 - Clock-and-data recovery
 - Extract clock frequency and optimum phase from incoming data stream
 - Skew cancellation
 - Phase aligning an internal clock to an I/O clock

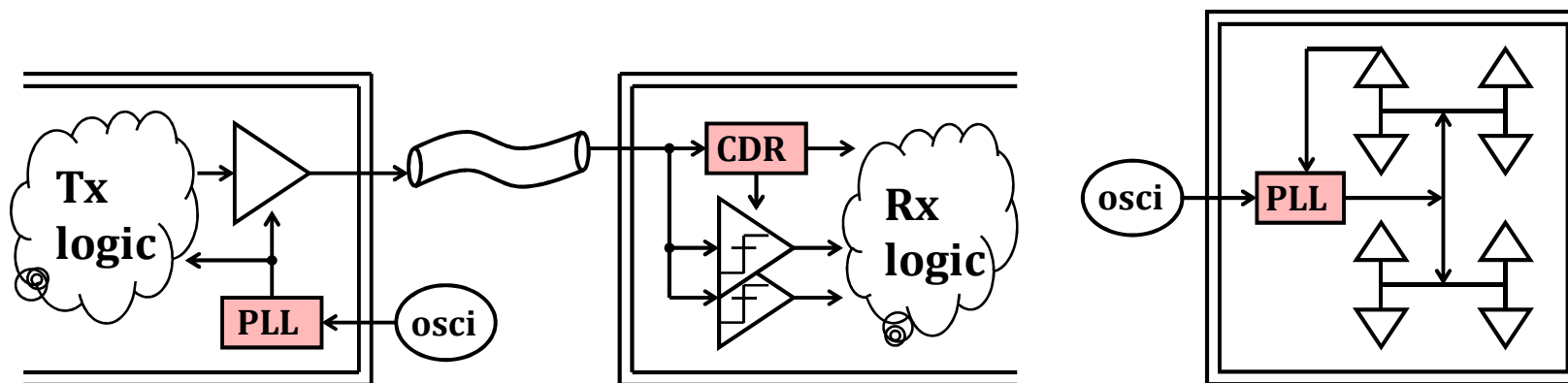


Phase-Locked Loops (II)

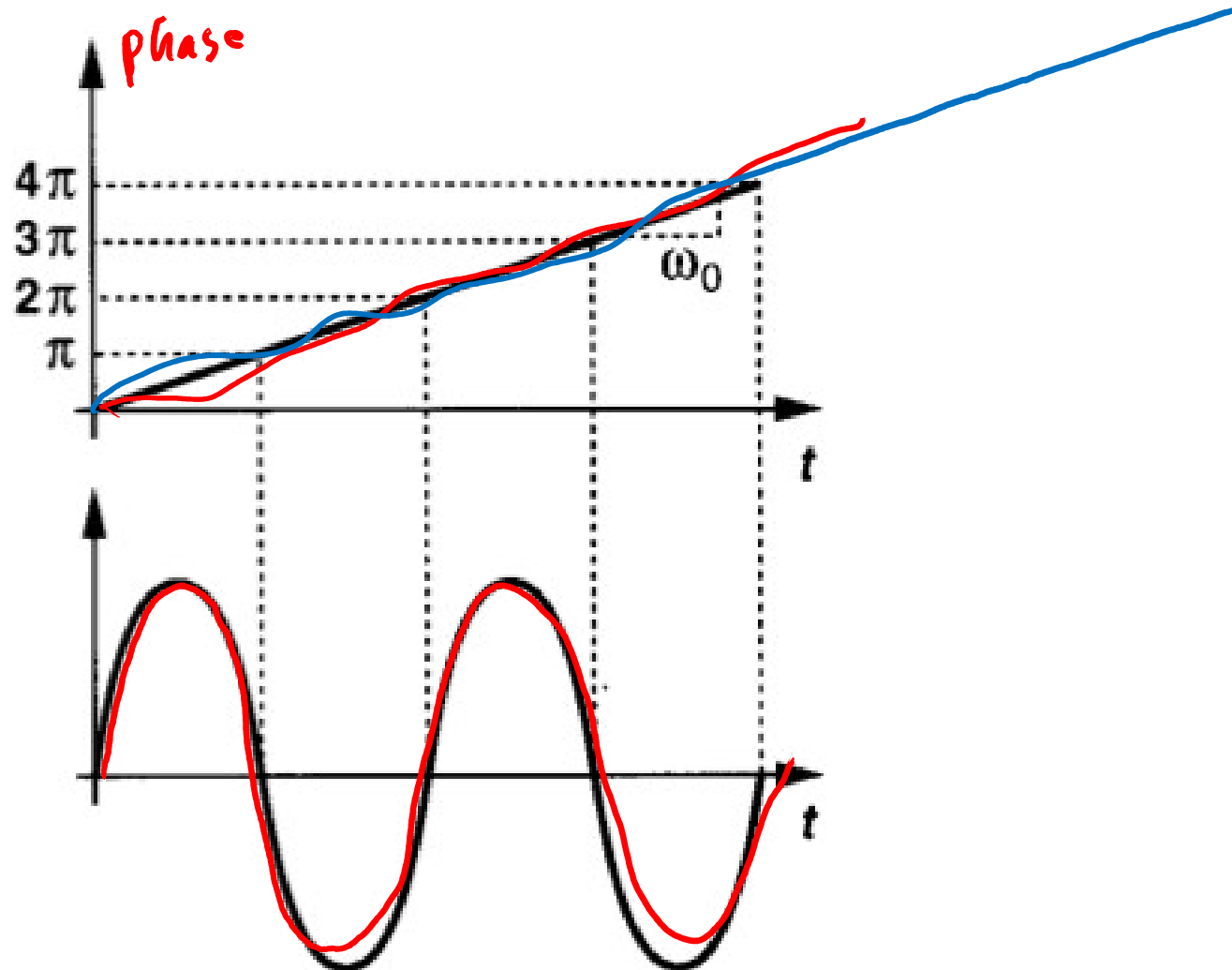- ◆ A **negative feedback system** that compares and adjusts the output phase with the input phase




In Order to Achieve Phase Lock

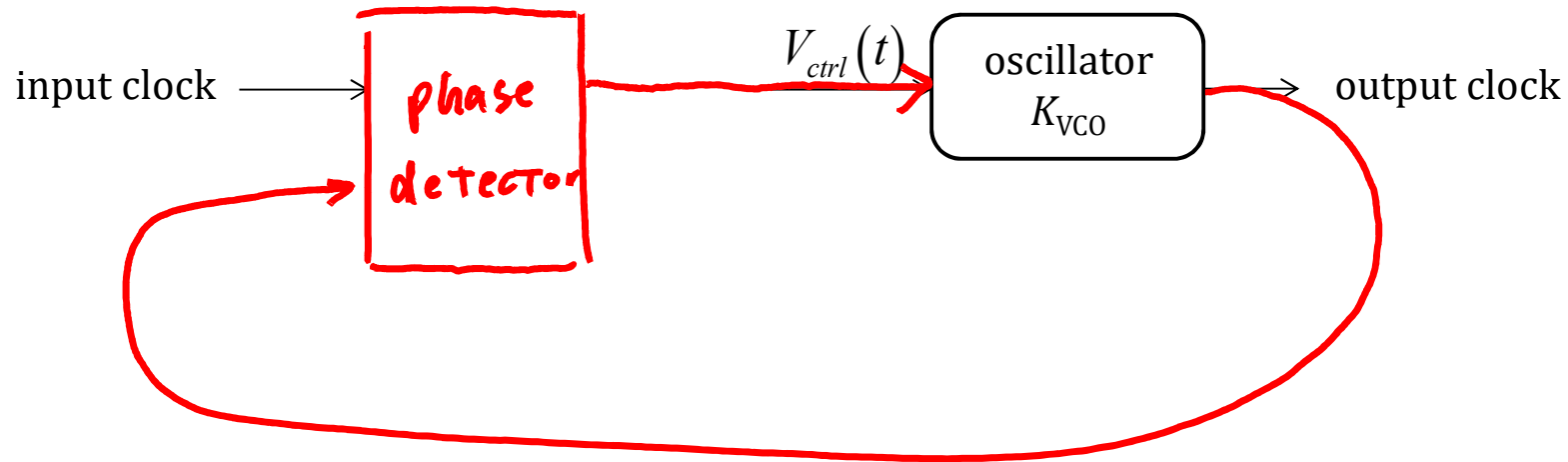

◆ Need to measure the phase difference between the two clocks

→ **Phase detector**

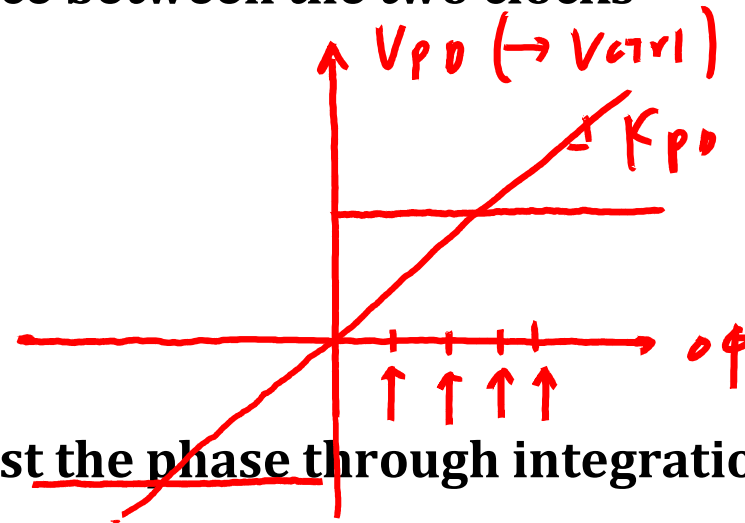A circuit whose average output is linearly proportional to the phase difference between the two inputs




→ We must vary the **frequency** to adjust the phase through integration

Phase Detector Example - XOR Gate (I)

digital gate





A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

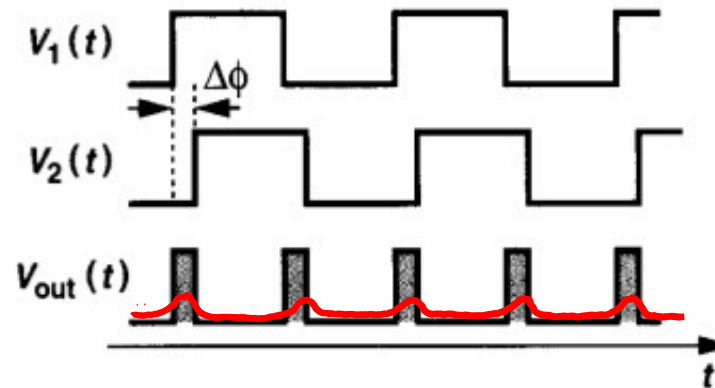

- ◆ Respond to both (rising and falling) edges
- ◆ As the phase difference keeps increasing ...


Phase Detector Example - XOR Gate (II)

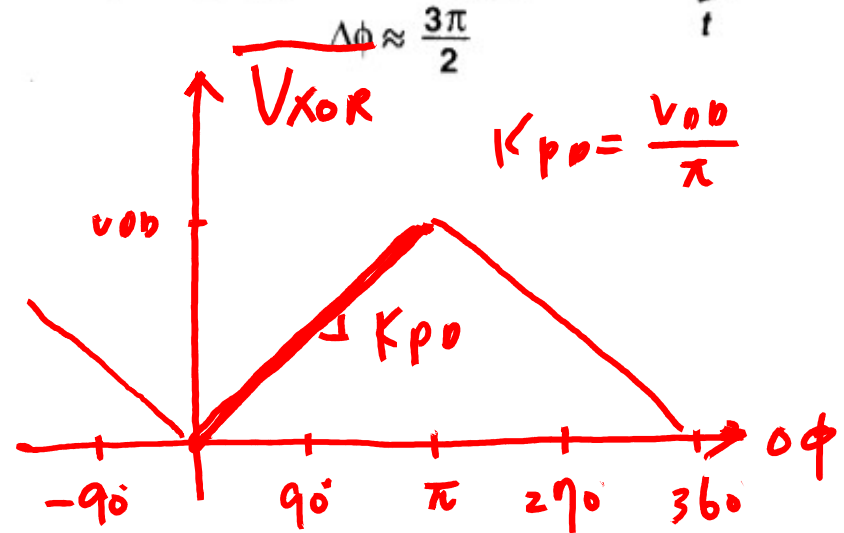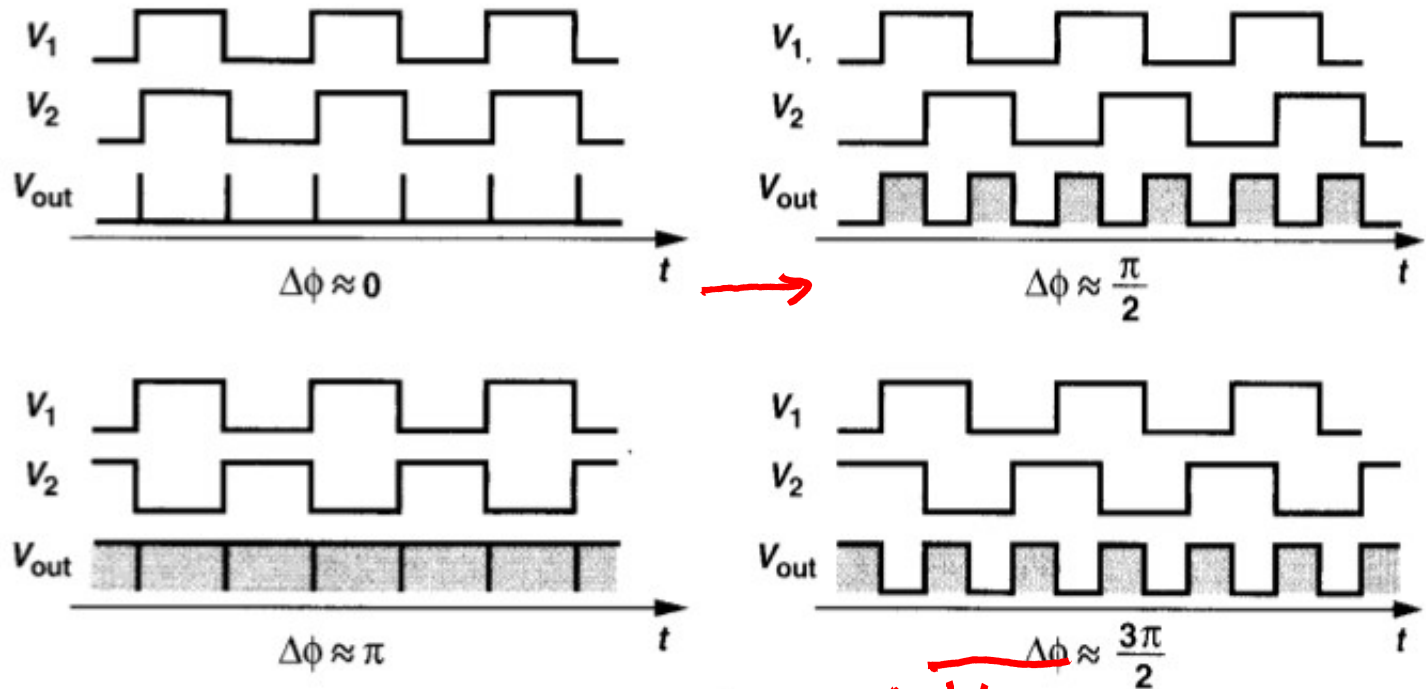


- ◆ The phase detector gain K_{PD} of

Basic PLL Topology

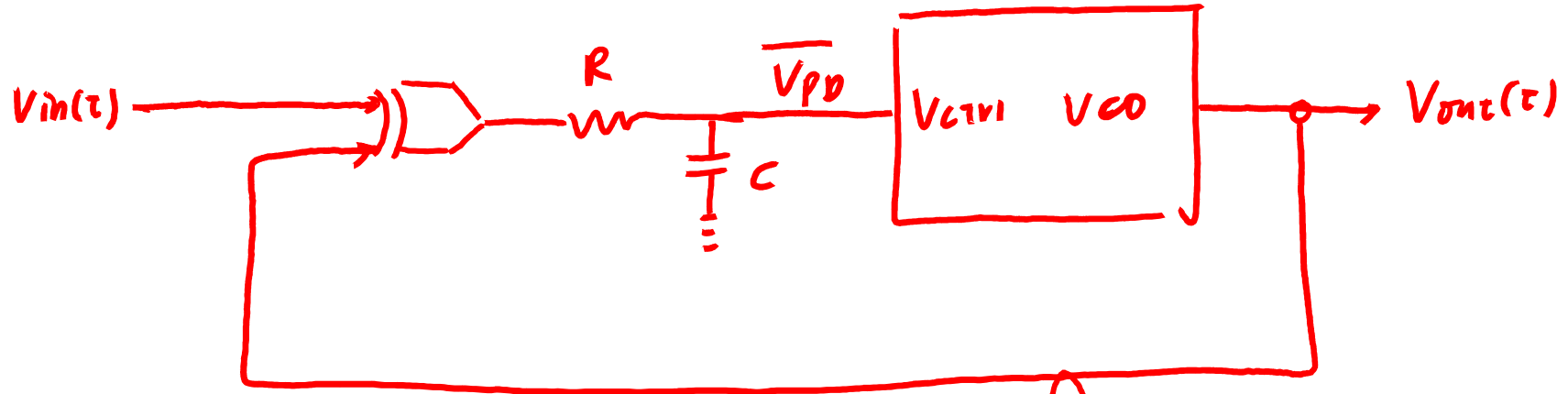- ◆ A low-pass filter is used after the phase detector to extract the average PD output





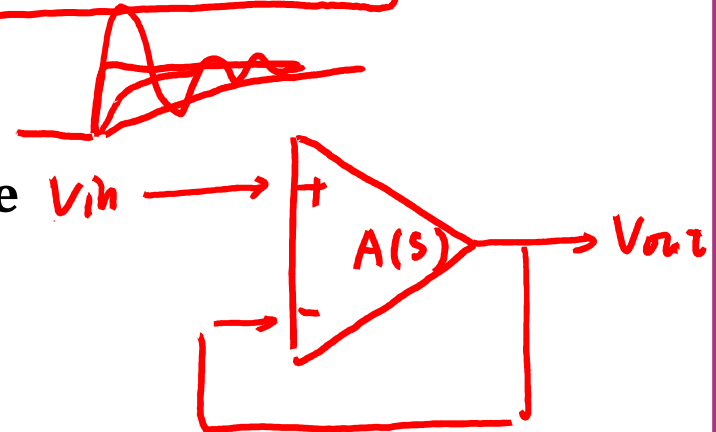
- ◆ In steady state *static phase error*
- ➔ The **phase** difference settles to small value
- ➔ The two **frequency** becomes the same



Phase-Locked Loops in Steady State (I)

loop-filter
low-pass filter

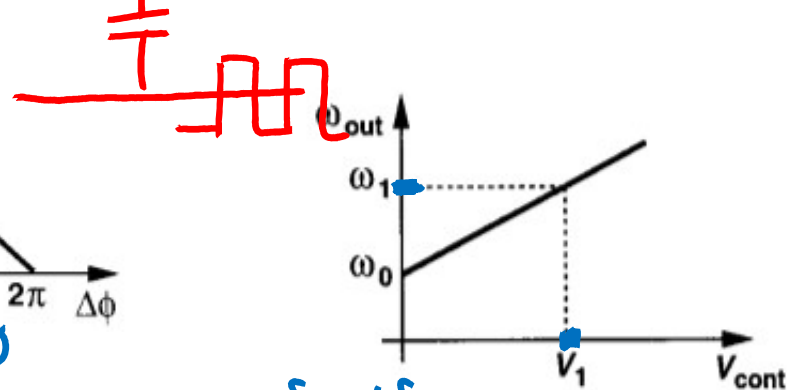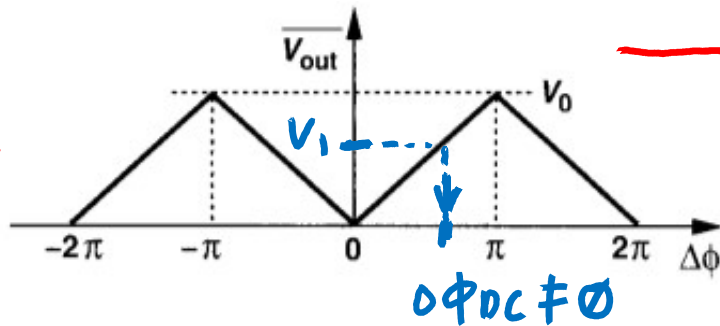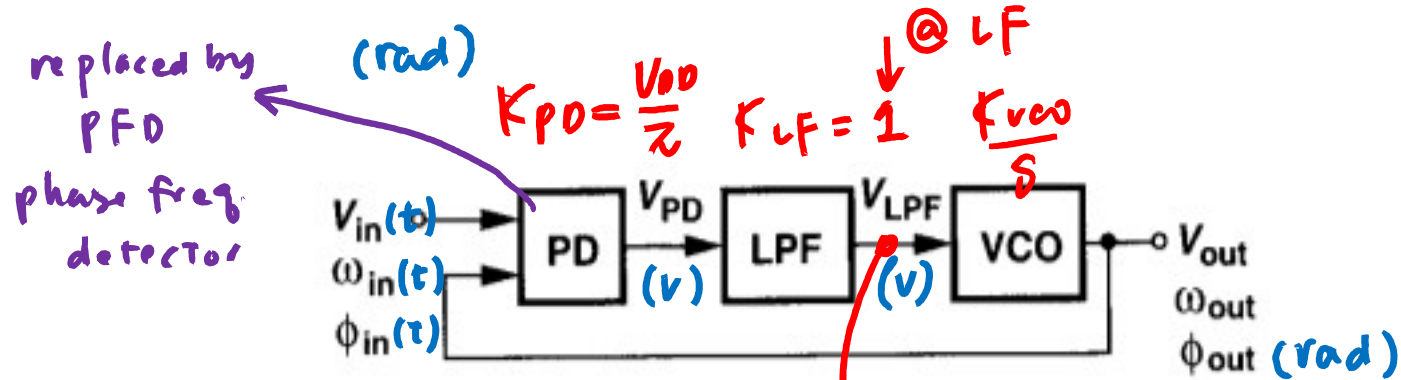- Transfer functions of each building block




in order to run @ ω_1 $V_{cont} = V_1 = \frac{\omega_1 - \omega_0}{K_{vco}}$

so does \bar{V}_{pd} (needs to settle to V_1) $\Rightarrow \frac{V_1}{\Delta\phi_{DC}} = K_{PD} \Rightarrow \Delta\phi_{DC} = \frac{V_1}{K_{PD}}$

$\Rightarrow \Delta\phi_{DC} = \frac{\omega_1 - \omega_0}{K_{vco} \cdot K_{PD}}$


Phase-Locked Loops in Steady State (II)

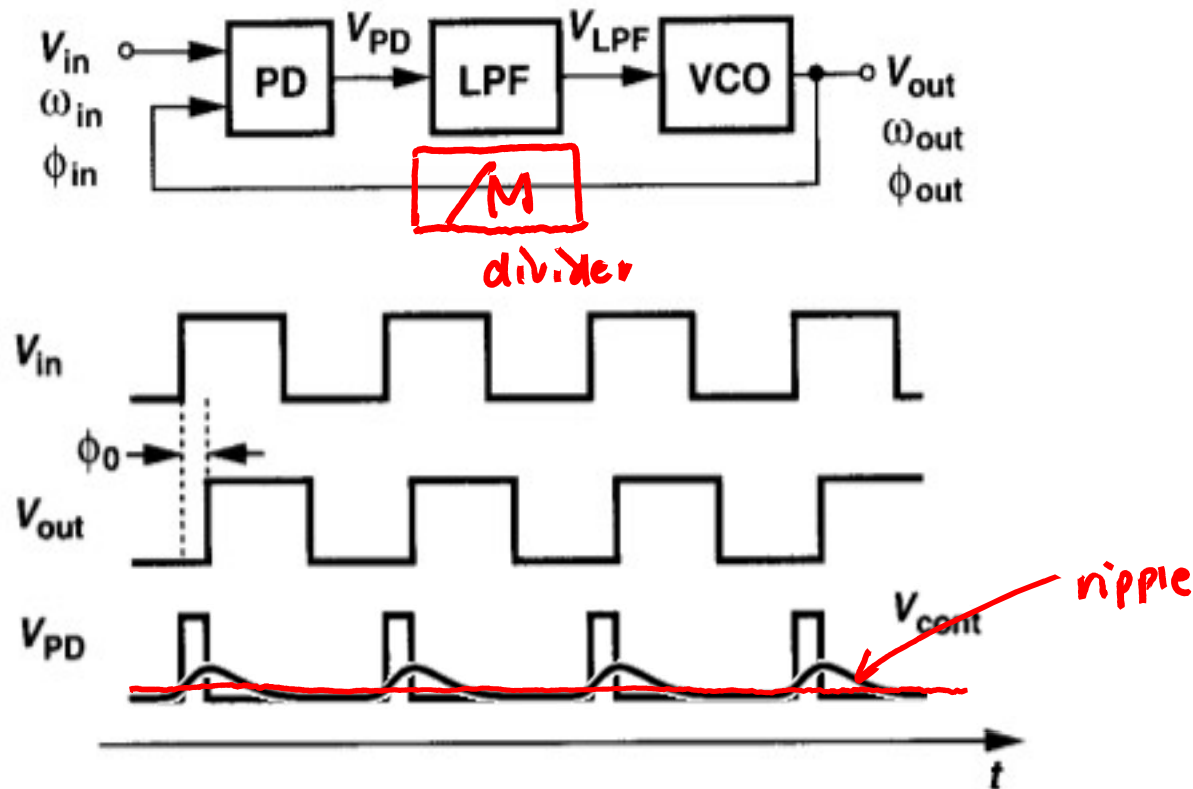

- ◆ The resulting phase error depends on the operating frequency
- ◆ To minimize phase error $\rightarrow K_{PD}K_{VCO}$ needs to be maximized
- ◆ About operating frequency...


In Case with a Phase Jump

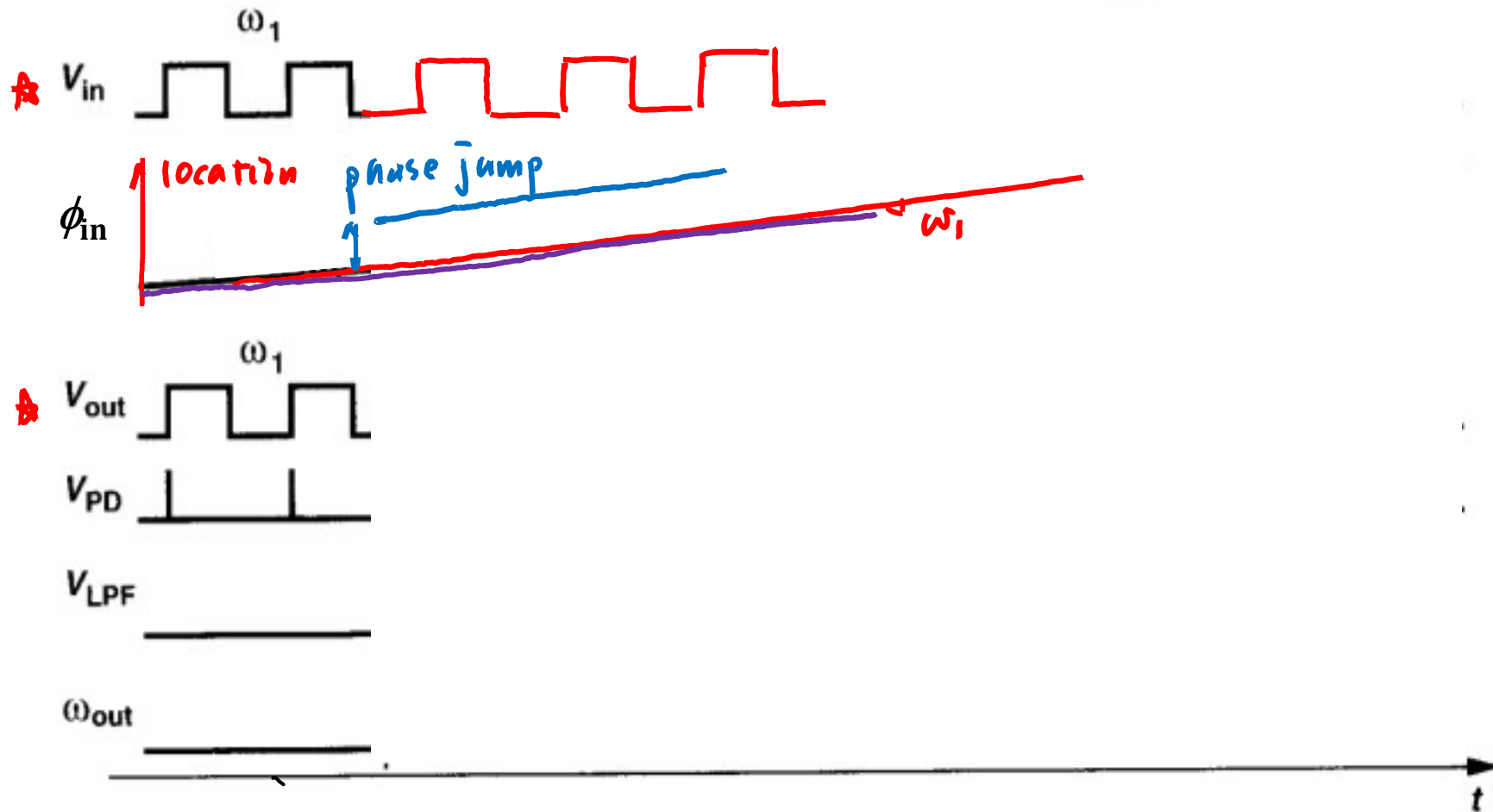- ◆ How does it look like for a **phase** jump?




In Case with a Phase Jump

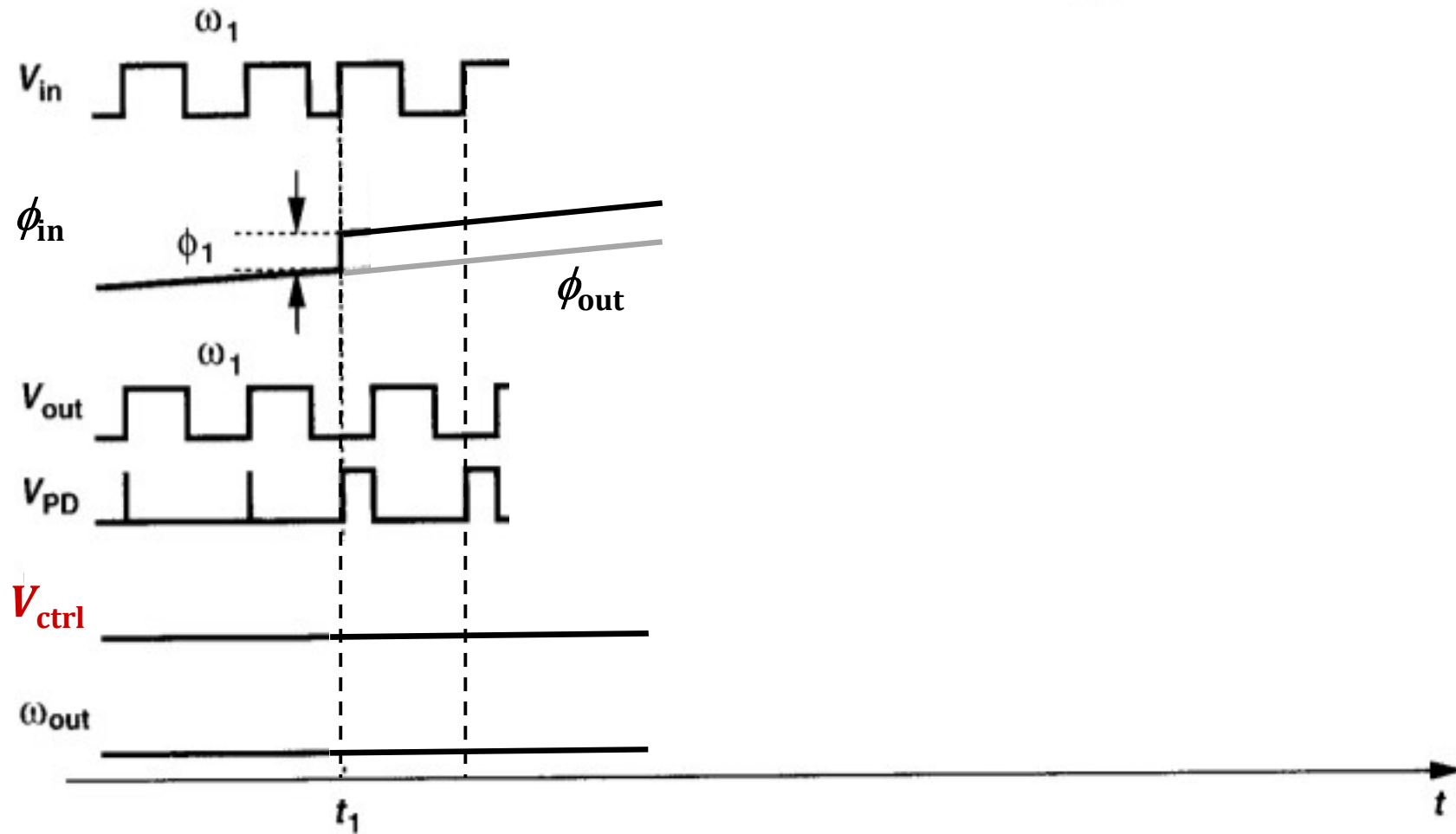- ◆ How does it look like for a phase jump?
- ◆ @ t_1 if open-loop




In Case with a Phase Jump

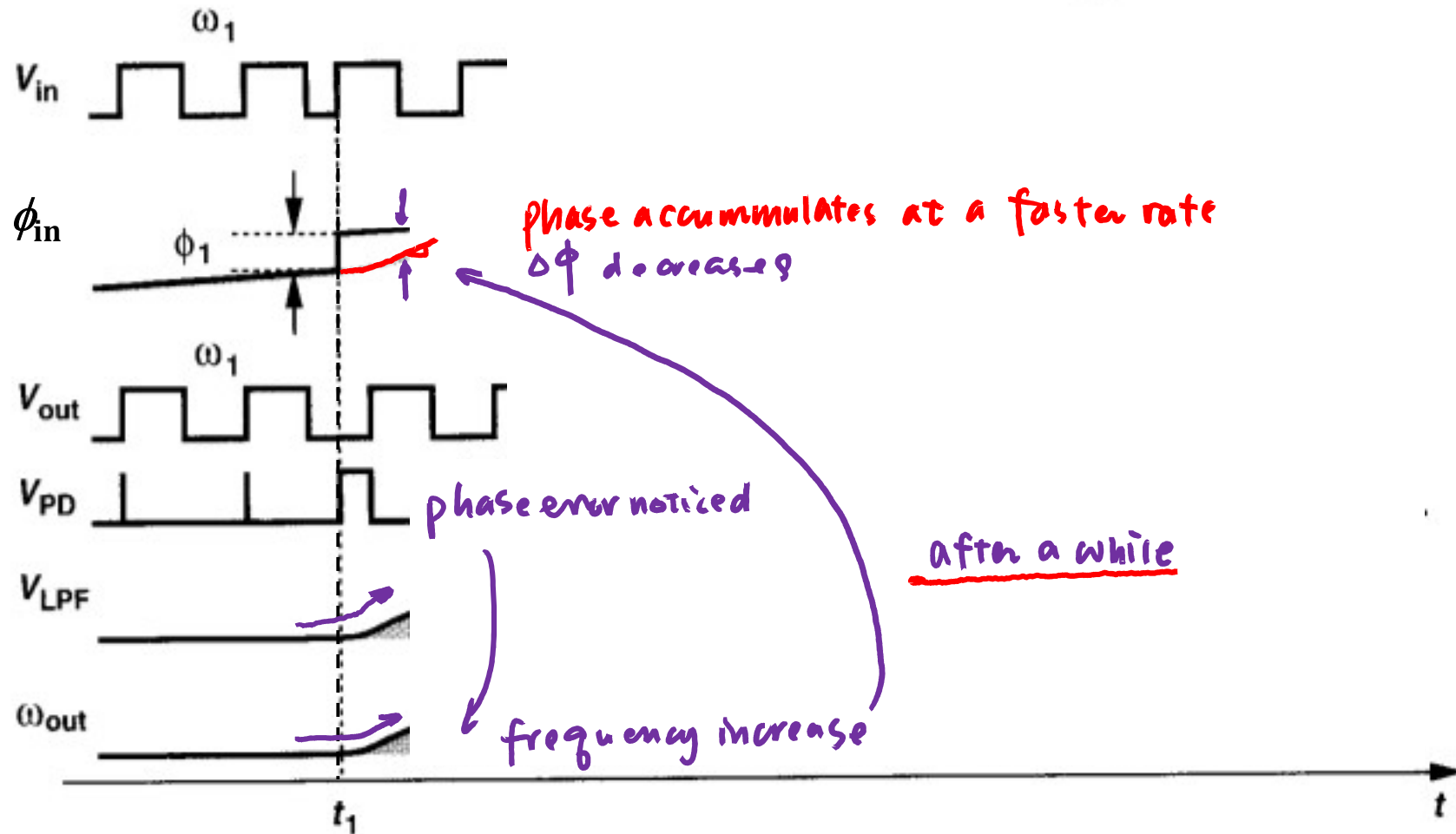- ◆ How does it look like for a phase jump?
- ◆ @ t_1 with feedback loop




In Case with a Phase Jump

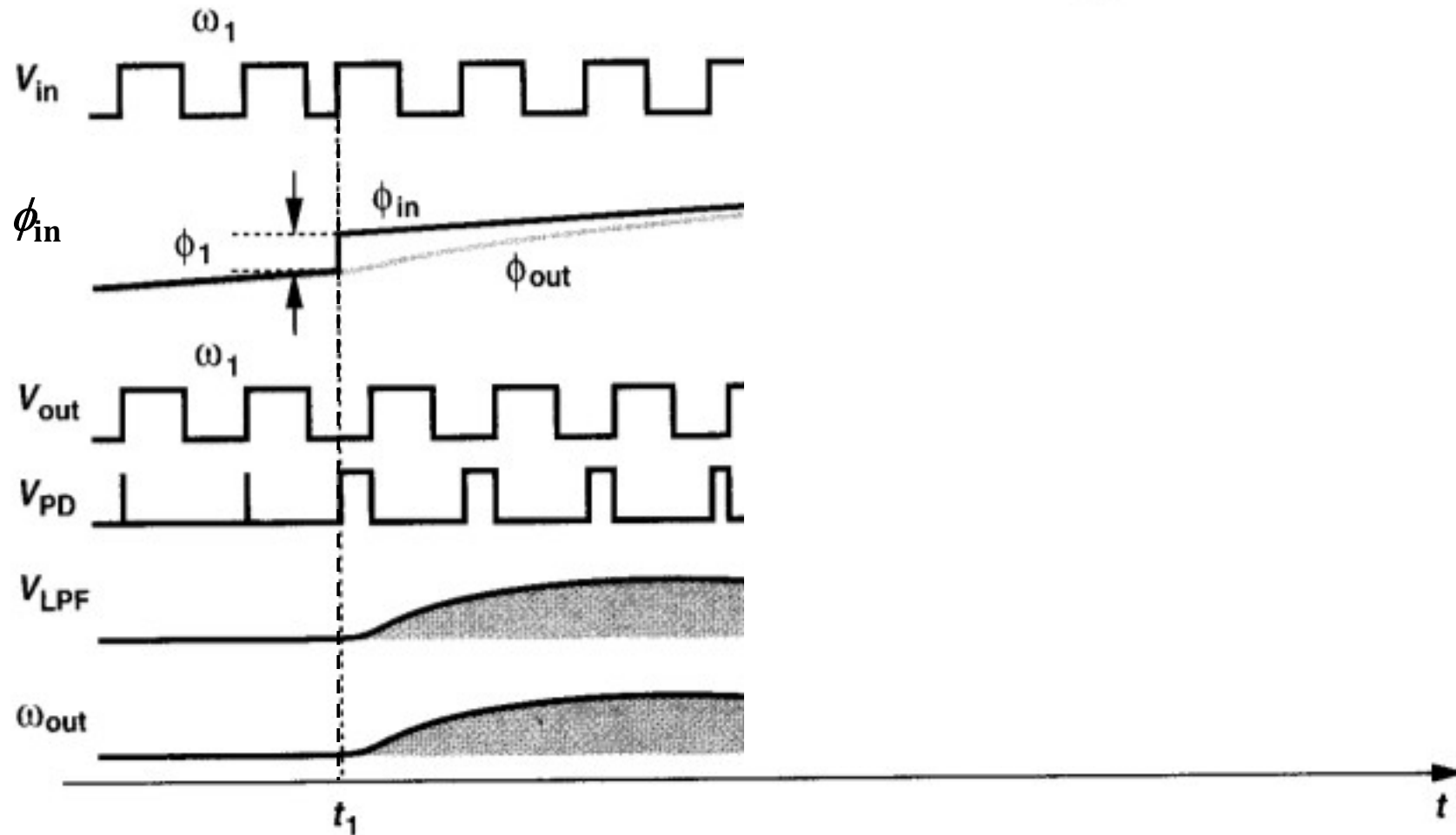- ◆ How does it look like for a phase jump?
- ◆ **With feedback loop**



In Case with a Phase Jump

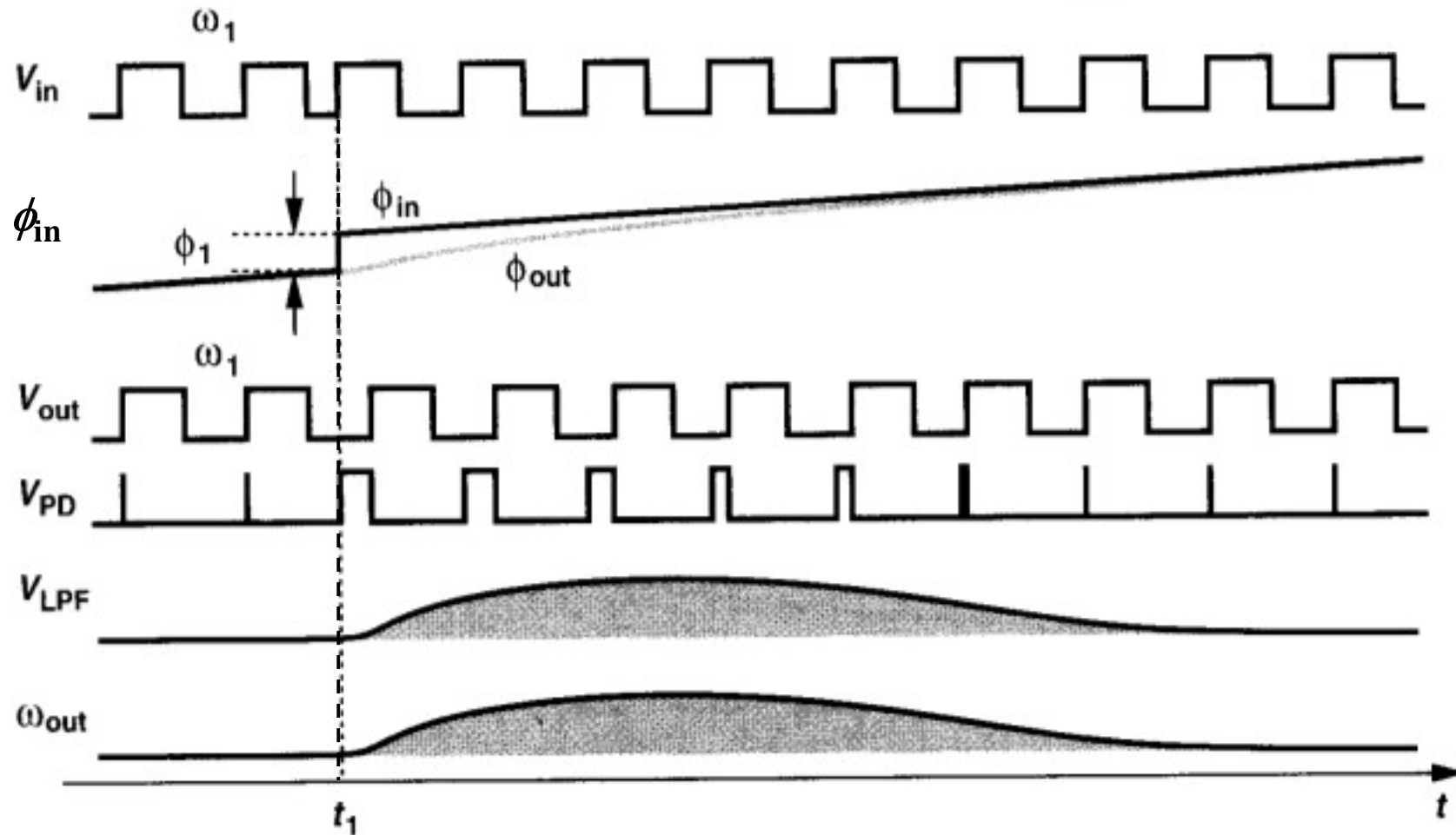
- ◆ How does it look like for a phase jump?
- ◆ **With feedback loop**




In Case with a Phase Jump

- ◆ How does it look like for a phase jump?
- ◆ **With feedback loop**
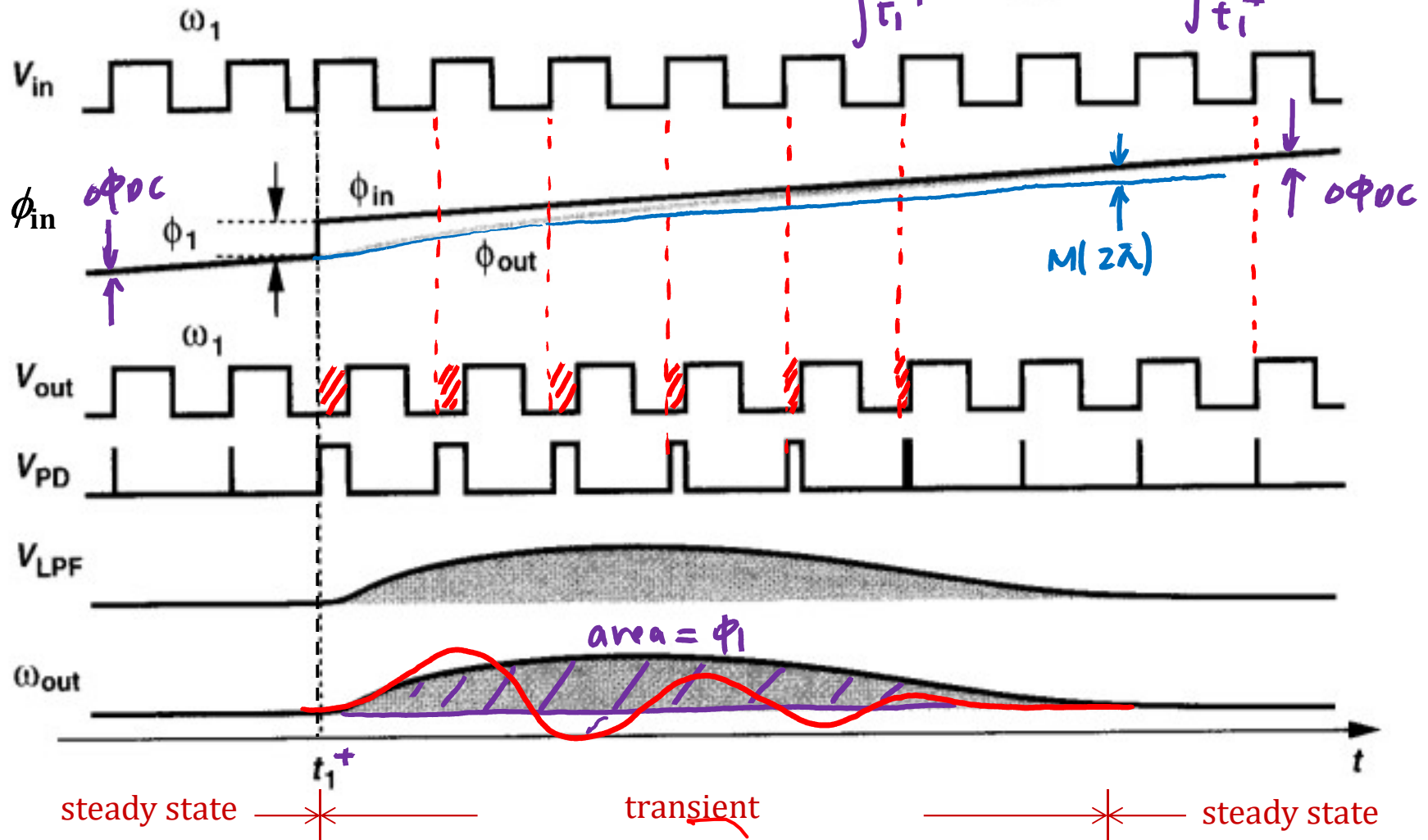
$$\int_{t_1^+}^t (\omega_{out}(\tau) - \omega_i) dt = \int_{t_1^+}^t \omega_{out}(\tau) dt - \int_{t_1^+}^t \omega_i dt$$



Underdamped Response to Phase Step

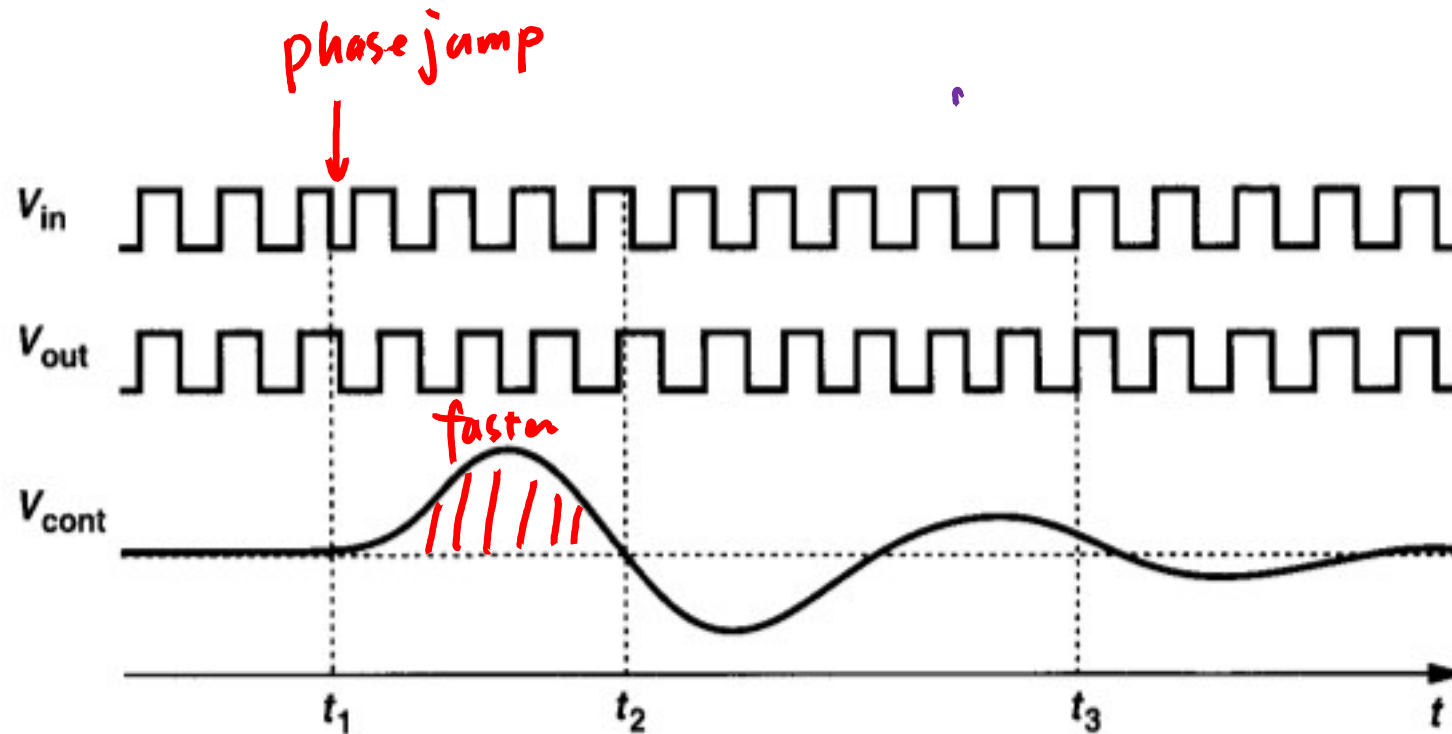


- ◆ @ t_1 the phase jump happens
- ◆ @ t_2 the frequencies are the same, but large phase error
- ◆ @ t_3 the phase is the same, but frequency is not

In Case with a Frequency Jump

- ◆ How does it look like for a **frequency** jump?

If open-loop

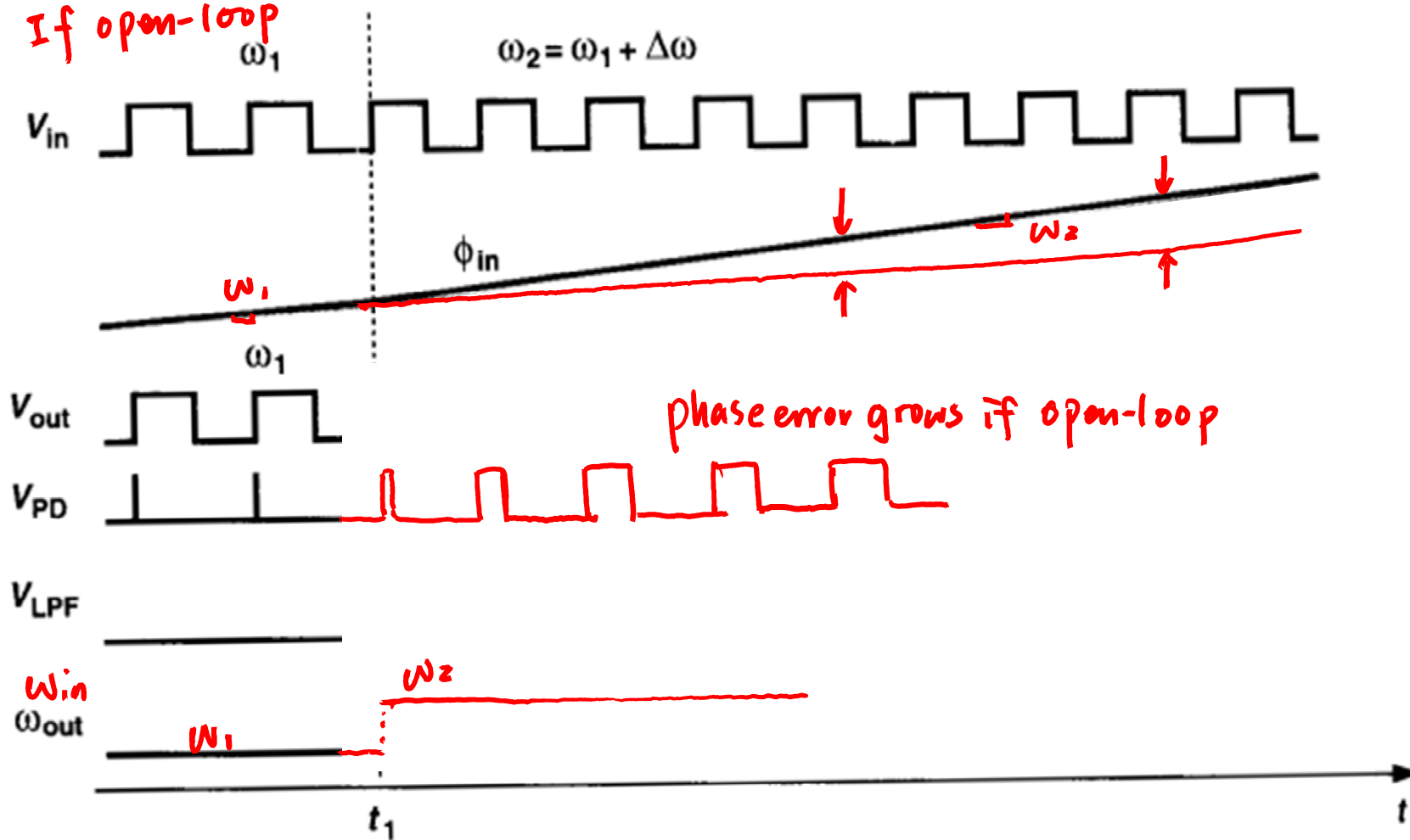

phase error grows if open-loop

In Case with a Frequency Jump


- How does it look like for a **frequency** jump?

throughout the settling behavior

$$\int_{t_1^+}^{t \rightarrow \infty} (\omega_{out}(t) - \omega_{in}(t)) dt$$

$$= (\phi_{out}(\infty) - \phi_{in}(\infty))$$
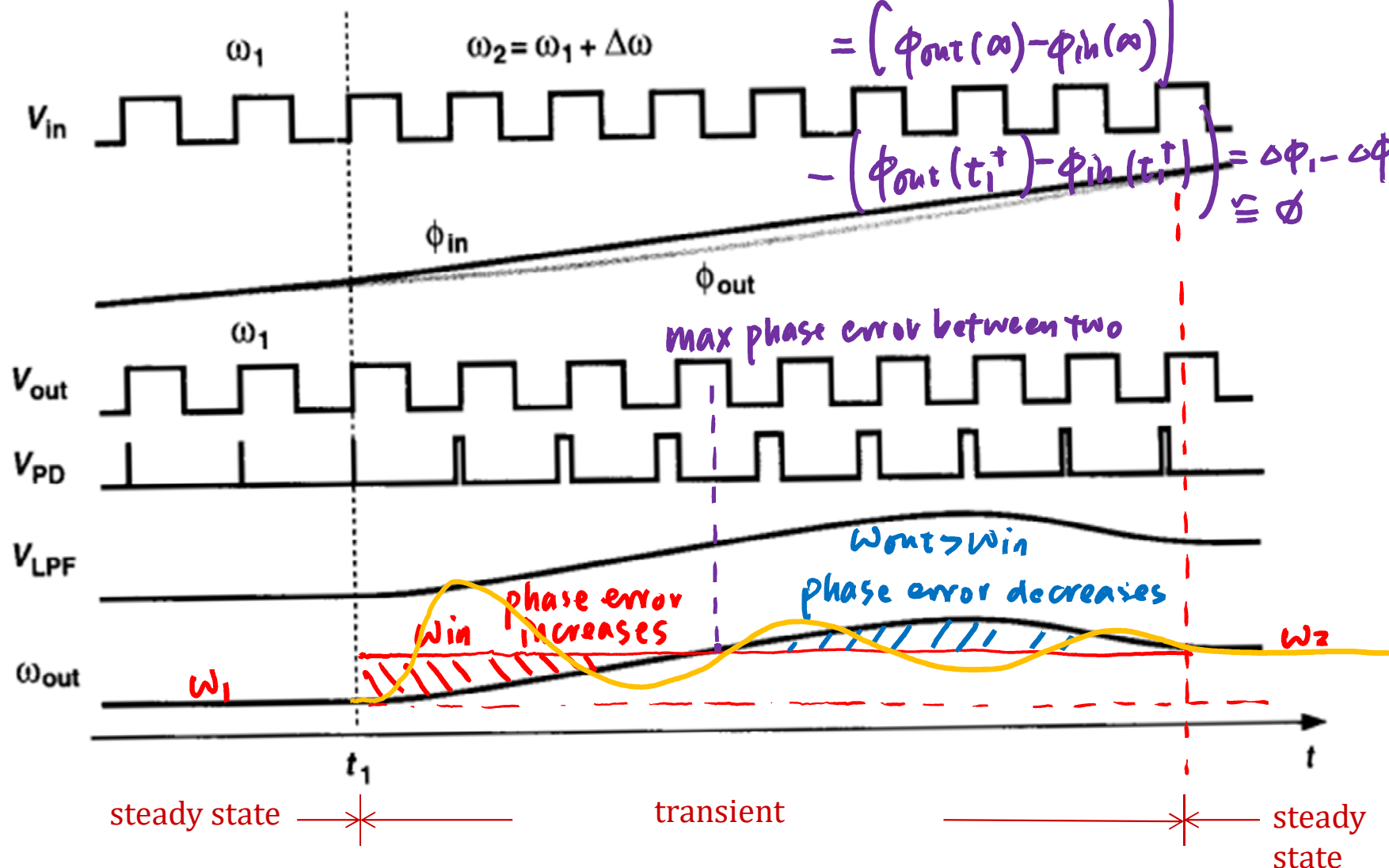
$$- (\phi_{out}(t_1^+) - \phi_{in}(t_1^+)) = \Delta\phi_1 - \Delta\phi_2 \cong \phi$$




Loop Dynamics (I)

- From previous examples, how fast the loop responses depends on the design of the low-pass filter

$$\omega_{LPF} = \frac{1}{RC}$$

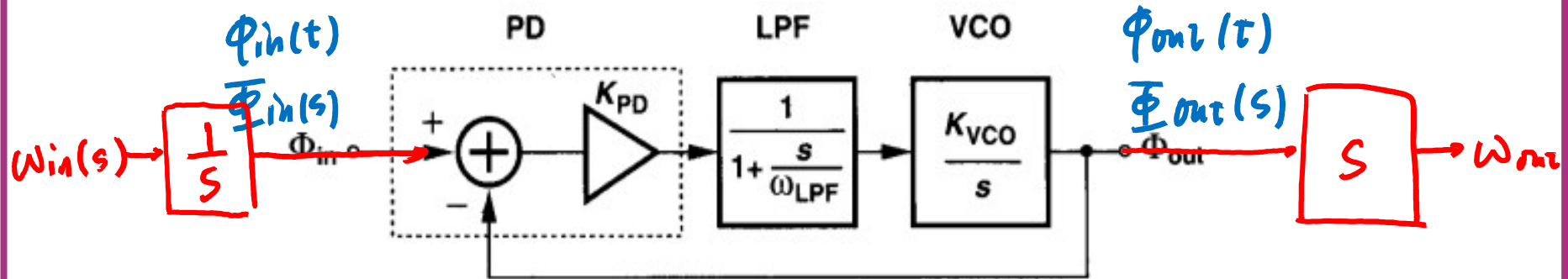- Linear model of the PLL \rightarrow to derive the response from $\phi_{ex,in}$ to $\phi_{ex,out}$



- Open-loop transfer function (from phase \rightarrow voltage \rightarrow voltage \rightarrow phase)

$$H(s)|_{open} = K_{PD} \cdot \frac{1}{1 + \frac{s}{\omega_{LPF}}} \cdot \frac{K_{VCO}}{s}$$

2 poles (one @ DC, one @ $\frac{1}{RC}$)

- Low-frequency gain approaches infinity $|H(s)|_{open} \rightarrow \infty$ as $s \rightarrow 0$

Loop Dynamics (II)

- ◆ Closed-loop transfer function

$$H(s)|_{\text{closed}} = \frac{K_{PD}K_{VCO}}{\frac{s^2}{\omega_{LPF}} + s + K_{PD}K_{VCO}} = \frac{H_{\text{open}}}{1 + H_{\text{open}}} = \frac{\Phi_{\text{out}}(s)}{\Phi_{\text{in}}(s)}$$

- Low-frequency gain of unity **1**
- Output tracks the input **phase** well if input phase varies slowly
- For input phase step, output phase eventually catches up

- ◆ In fact $\frac{\omega_{\text{out}}}{\omega_{\text{in}}}(s) = \frac{K_{PD}K_{VCO}}{\frac{s^2}{\omega_{LPF}} + s + K_{PD}K_{VCO}}$ *the same transfer function*


- Low-frequency gain of unity **1**
- Output tracks the input **frequency** well if input frequency varies slowly
- For input frequency step, output frequency eventually catches up

Loop Dynamics (III)

◆ Second-order transfer function

$$H(s)|_{\text{closed}} = \frac{K_{PD}K_{VCO}}{\frac{s^2}{\omega_{LPF}} + s + K_{PD}K_{VCO}} = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$
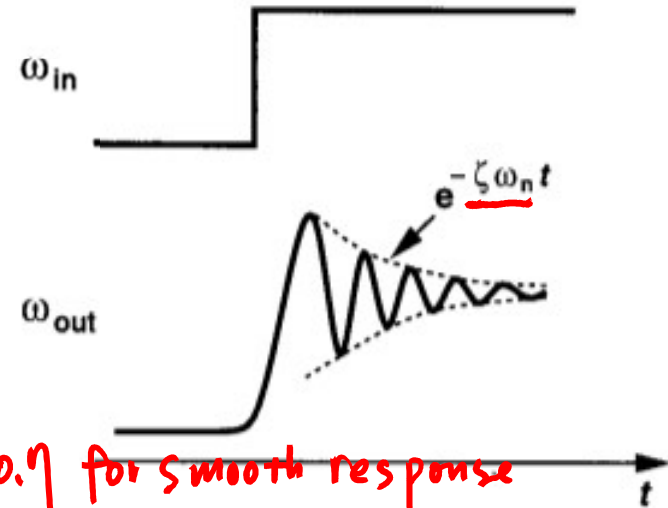
$$\omega_n = \sqrt{\omega_{LPF}K_{PD}K_{VCO}} \quad \zeta = \frac{1}{2} \sqrt{\frac{\omega_{LPF}}{K_{PD}K_{VCO}}}$$



we like to set ζ to 0.6~0.7 for smooth response

- If $\zeta > 1$, both poles are real \rightarrow the system is over damped
- If $\zeta < 1$, both poles are complex \rightarrow the step response can be written as

$$s_{1,2} = -\zeta\omega_n \pm \sqrt{(\zeta^2 - 1)\omega_n^2}$$


$$\omega_{out}(t) = [1 - \frac{1}{\sqrt{1 - \zeta^2}} e^{-\zeta\omega_n t} \sin(\omega_n \sqrt{1 - \zeta^2} t + \theta)] \Delta\omega_{in}(t)$$

(the same behavior for response to phase step)

- Settling speed $\rightarrow \zeta\omega_n$ needs to be maximized

Loop Dynamics (IV)

◆ Damping factor ζ

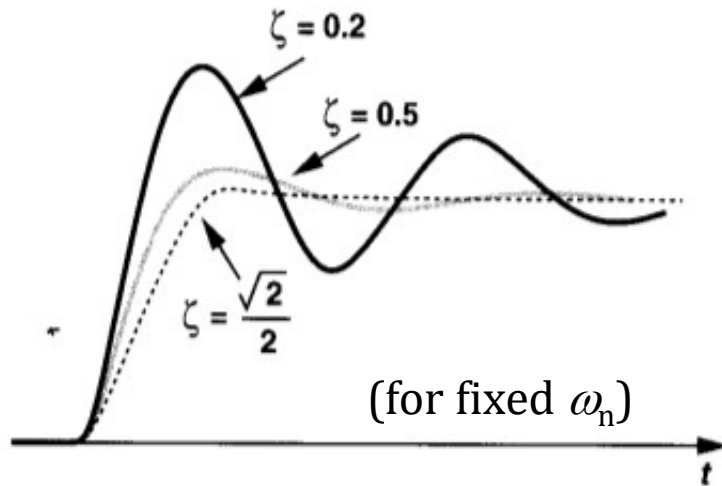

$$\omega_n = \sqrt{\omega_{LPF} K_{PD} K_{VCO}}$$

$$\zeta = \frac{1}{2} \sqrt{\frac{\omega_{LPF}}{K_{PD} K_{VCO}}}$$

$$\zeta \omega_n = \frac{1}{2} \omega_{LPF}$$

◆ For a preferred $\zeta \rightarrow \omega_n$ should be maximized for faster response

→ ω_{LPF} and $K_{PD} K_{VCO}$ should be increased at the same time

→ Strict trade-offs between response time, stability, steady-state ripple & jitter, and steady-state phase error

$\omega \uparrow$


$KK \uparrow$

@ V_{ctrl}

reference spur

Loop Dynamics (V)

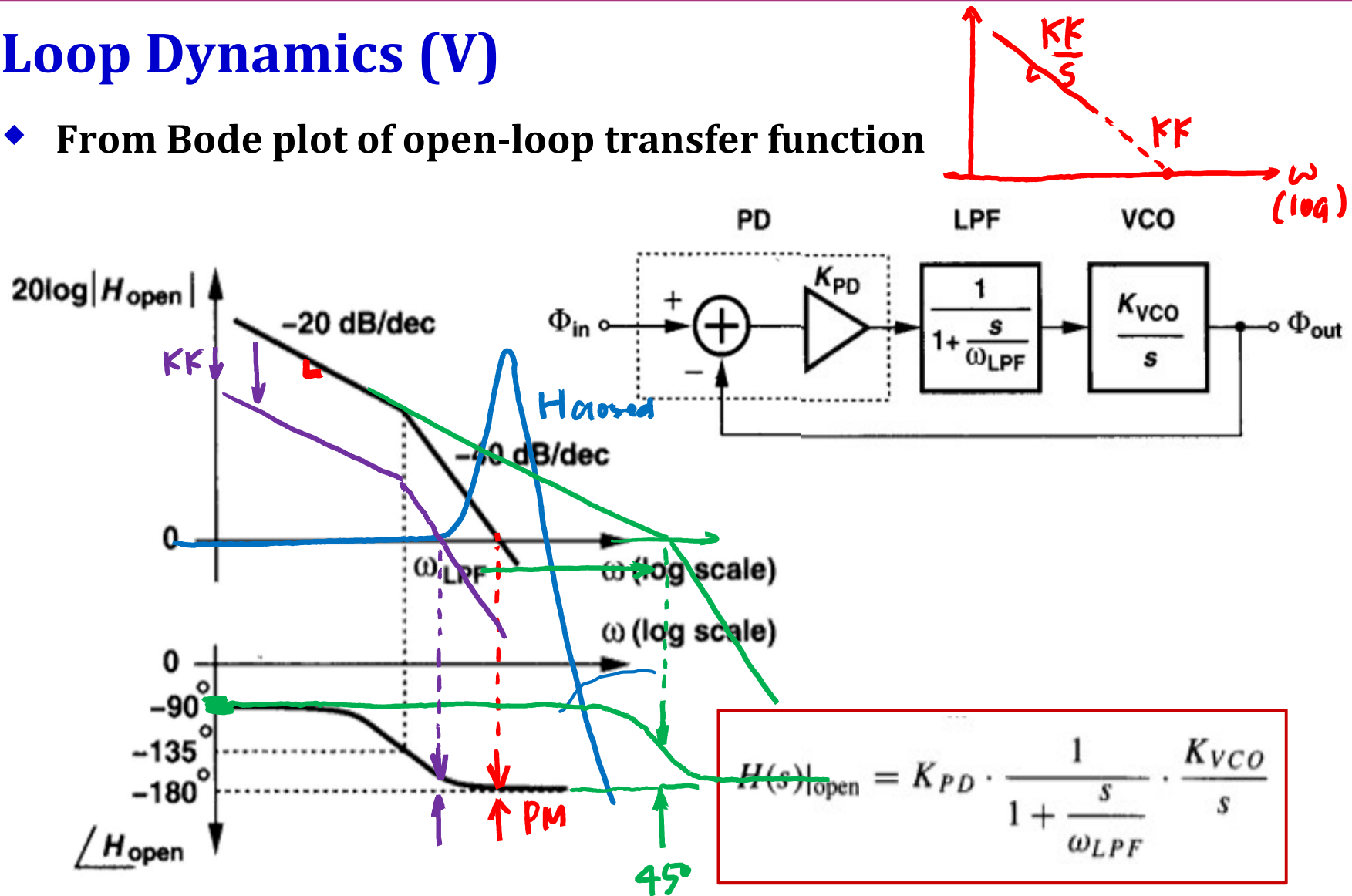- ◆ From Bode plot of open-loop transfer function



- ◆ The loop becomes less stable if ...