

---

# **EE4280 Lecture 8:**

# **Charge-Pump Phase-Locked Loops**

---

**Ping-Hsuan Hsieh (謝秉璇)**

**Delta Building R908**


**EXT 42590**

**[phsieh@ee.nthu.edu.tw](mailto:phsieh@ee.nthu.edu.tw)**
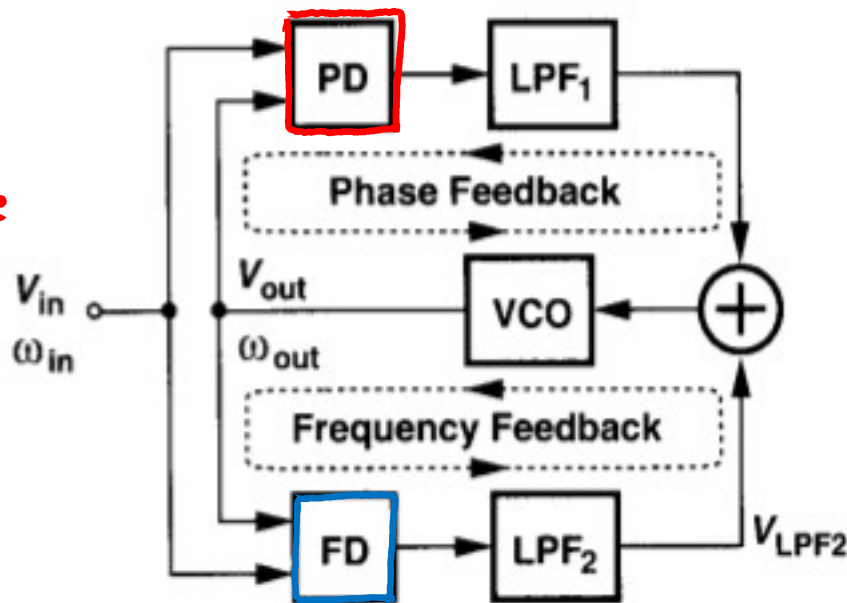
# Issues with Type-I Phase-Locked Loop


- ◆ **Strict trade-offs between response time, stability, steady-state ripple & jitter, and steady-state phase error**
- ◆ **Limited acquisition range**
  - The initial frequency of VCO can be very far from the input frequency
  - The acquisition range is on the order of  $\omega_{LPF}$
- Difference between  $\omega_{in}$  and  $\omega_{out}$  has to be less than  $\omega_{LPF}$
- Trade-offs further tightened
- Possible solution:

*Between steady state behavior and dynamic behavior*




## Two Inputs with Different Frequencies

- ◆ An XOR cannot detect frequency error

 

- ◆ **Output pulses varies periodically**
  - At beat frequency (the frequency difference of the two)
  - The larger the difference, the faster the output pulse width changes
  - The LPF output stays constant and does not change due to the change of phase difference
- XOR (phase detector) does not detect frequency difference


Combinational nature of PD (XOR)

 

# Phase Frequency Detector

- ◆ Sequential logic of 3 states that responds to input edges

digital circuit

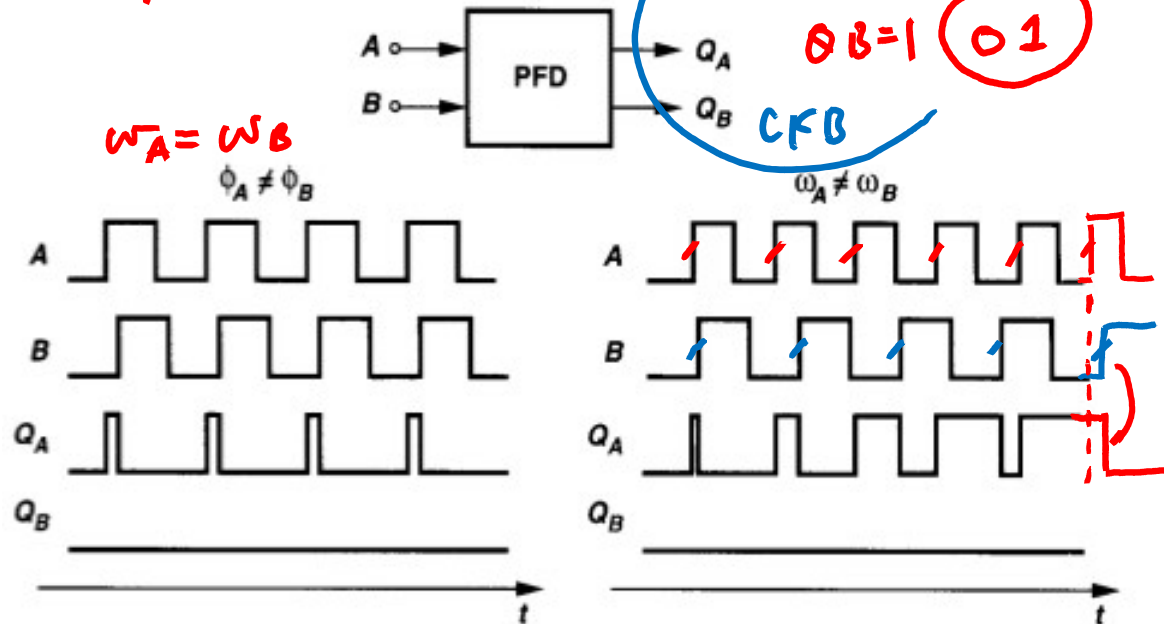

Reset

00

QA=0

QB=0

QB=0  
QA=1

10


CKB

\* QA stays high more when  $f_A > f_B$

- Reset state:  $Q_A=Q_B=0$  initially
- $Q_A$  responds to rising edge of input A
- does not reset until rising edge of input B
- Two outputs indicate fast and slow in either phase or frequency

# PFD – in Case with Large Frequency Difference

- ◆ For larger frequency difference

 

# The Transfer Function of PFD




$\omega_1 = \omega_2$

the module behaves like a PD

- Consider two outputs of the same frequency


in case where A leads B

in case where B leads A

   

# Implementation Example

- ◆ Using resettable flip-flops

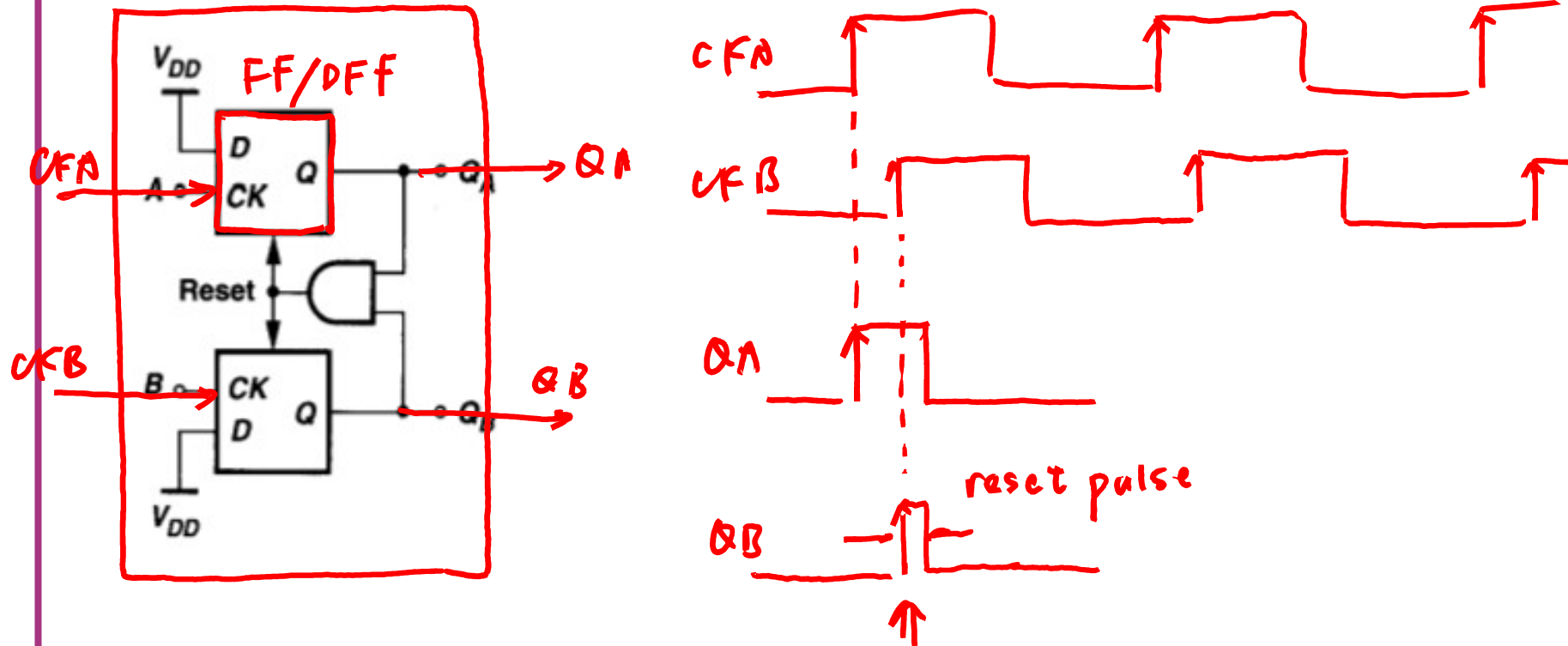


- ◆ QA and QB are simultaneously high for a short period of time  
→ Reset pulse



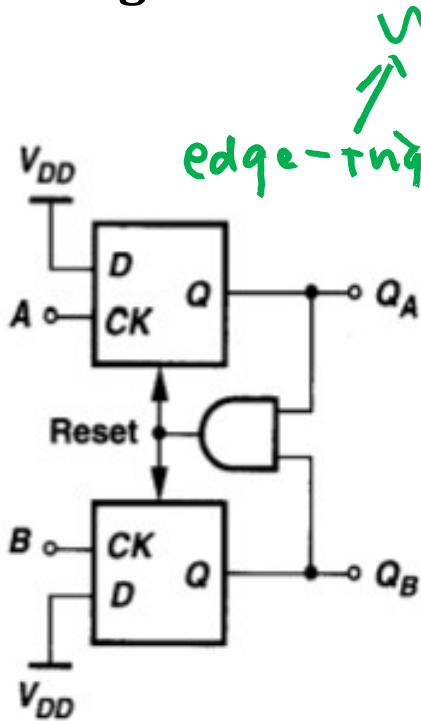
# Implementation Example



- Using resettable flip-flops → implemented using SR latch?



edge-triggered

 


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

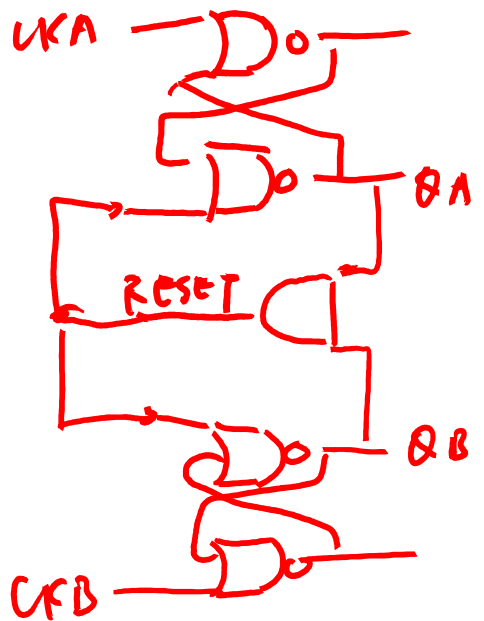 


level-sensitive

# The Problem of Using SR Latch for Resettable FF


- ◆ For two clocks with close phases




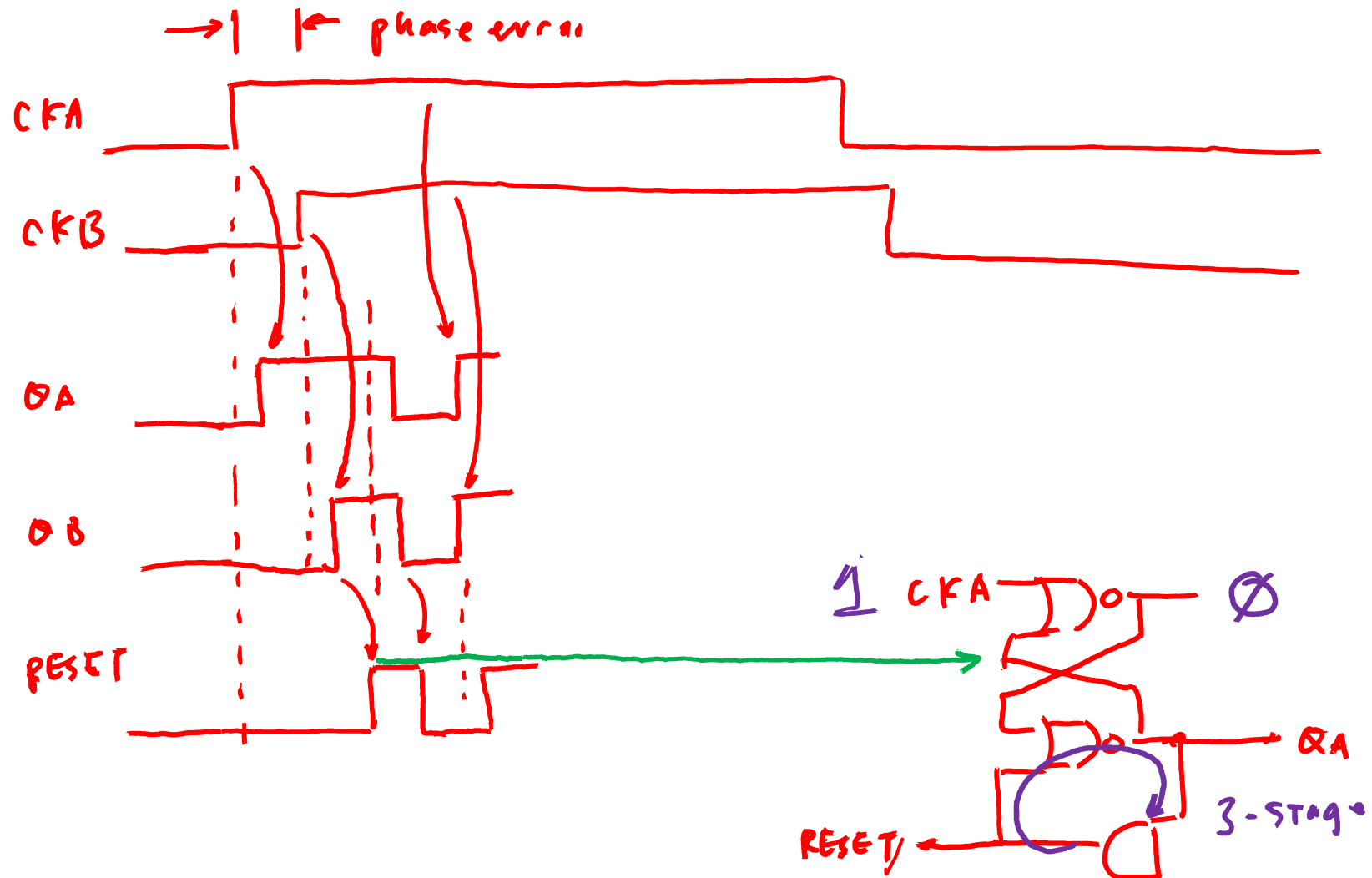


 

assuming Q<sub>B</sub> is high already


RESET pulse is 5Δt

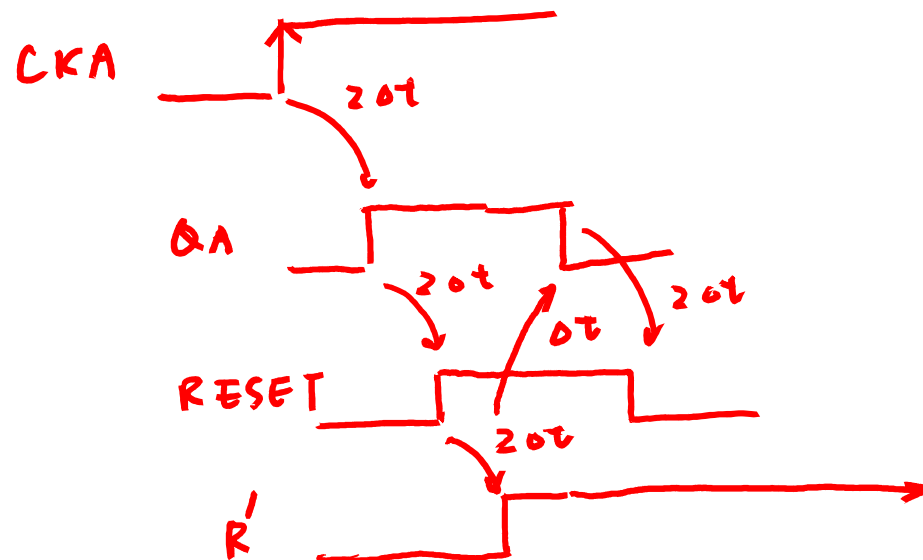

   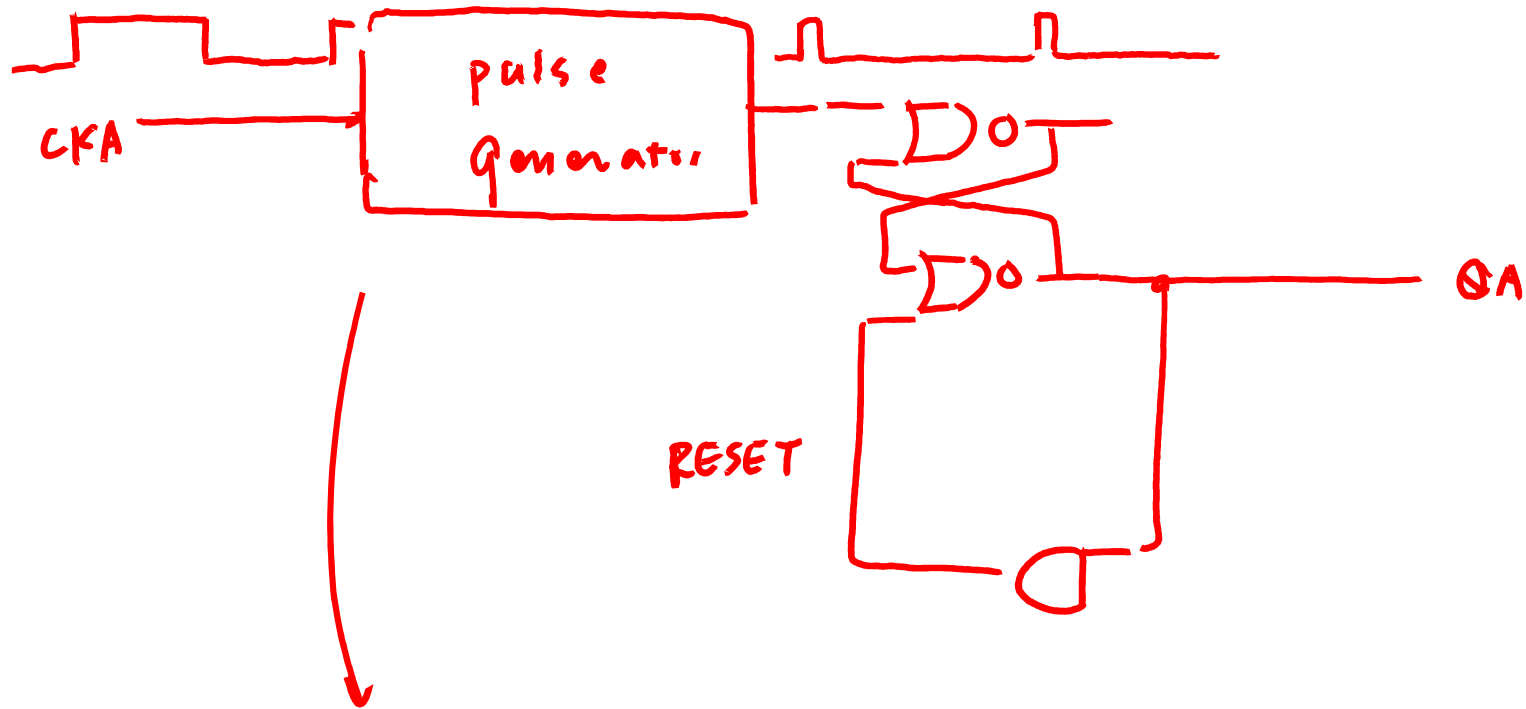
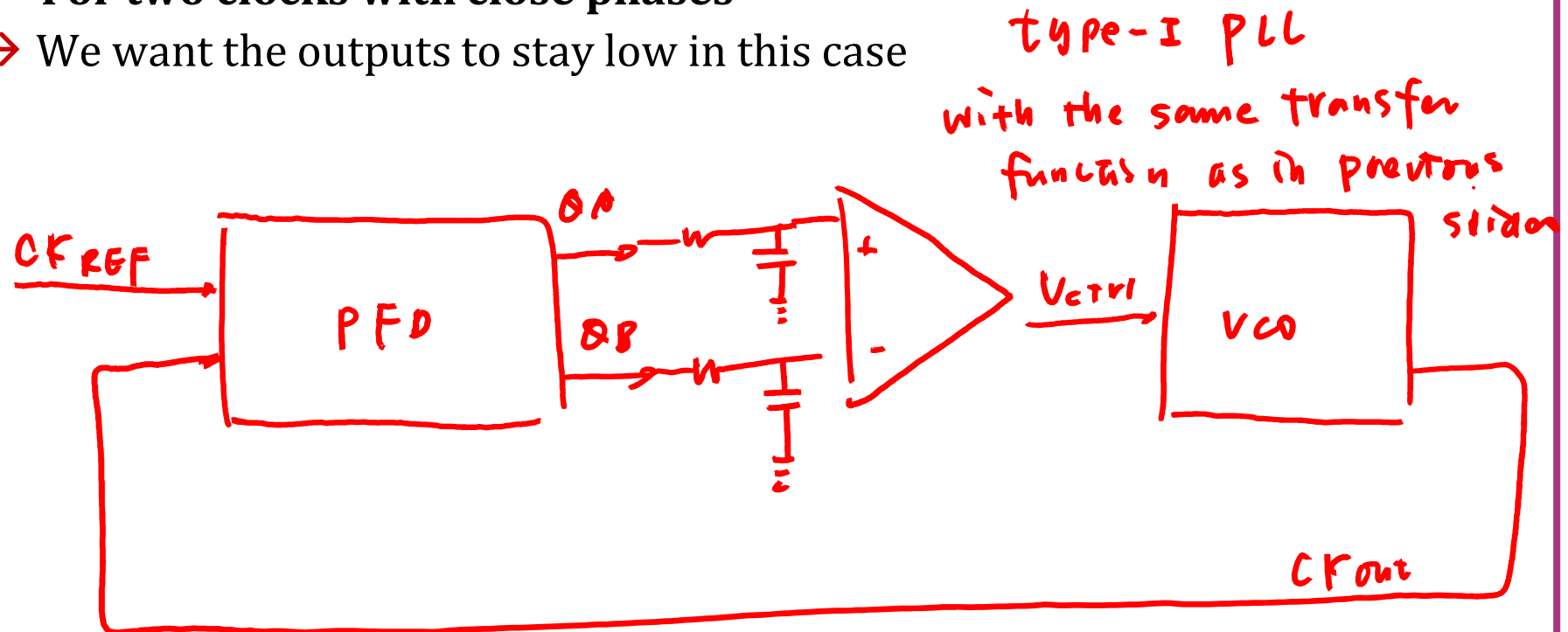
# The Problem of Using SR Latch for Resettable FF

- ◆ For two clocks with close phases
  - We want the outputs to stay low in this case



- ◆ How many numbers of stage delay is the reset pulse?


1

## To Take the PFD's Outputs to VCO


- ◆ A simple way
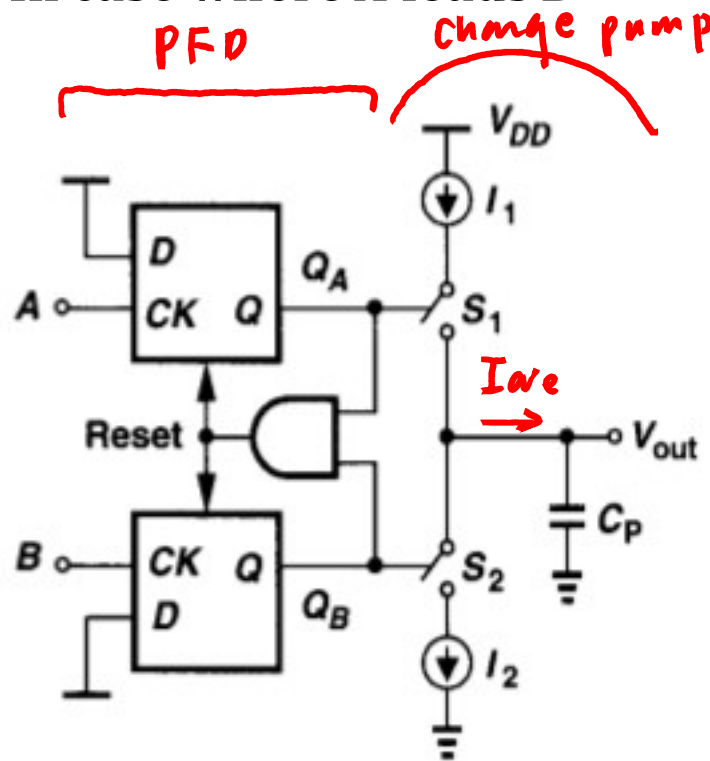
# Charge Pump

- ◆  $I_1$  and  $I_2$  are nominally identical
- ◆ In case where  $A$  leads  $B$




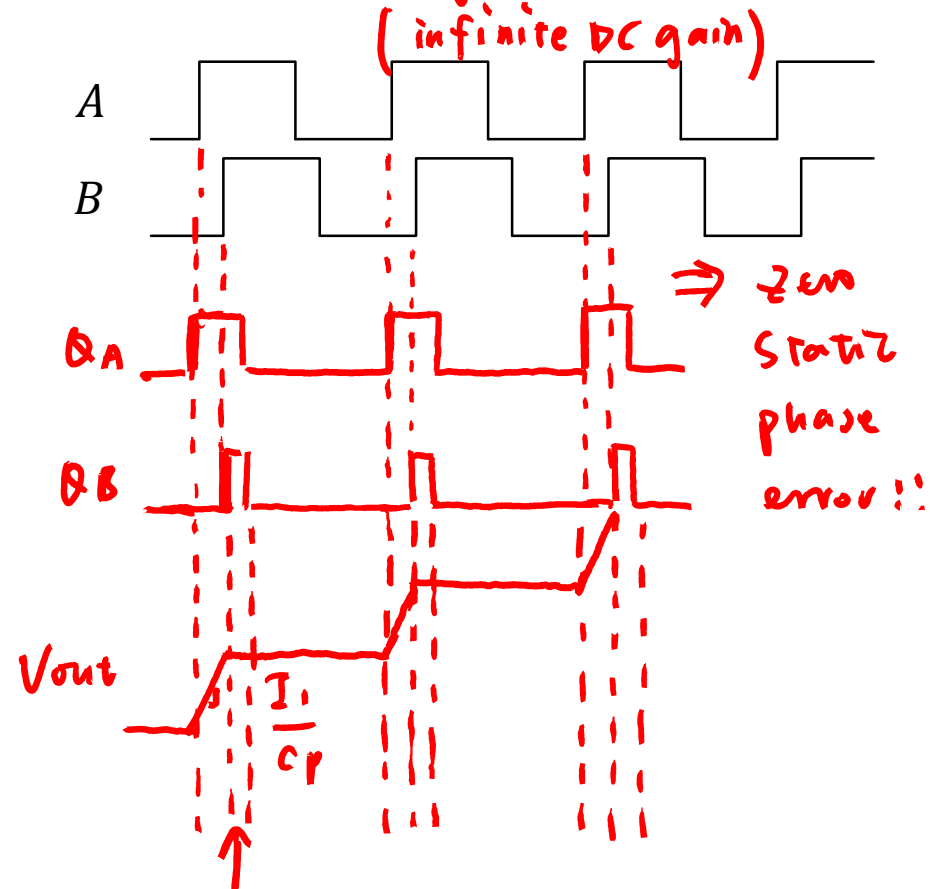
with fixed input (DC input  
DC phase error)  
we get increasing  $V_{out}$  → integrative of  $C$



- ◆ The slope of  $V_{out}$
- ◆ Effect of the reset pulses that appear in both  $Q_A$  and  $Q_B$   $V_{out}$  stays constant
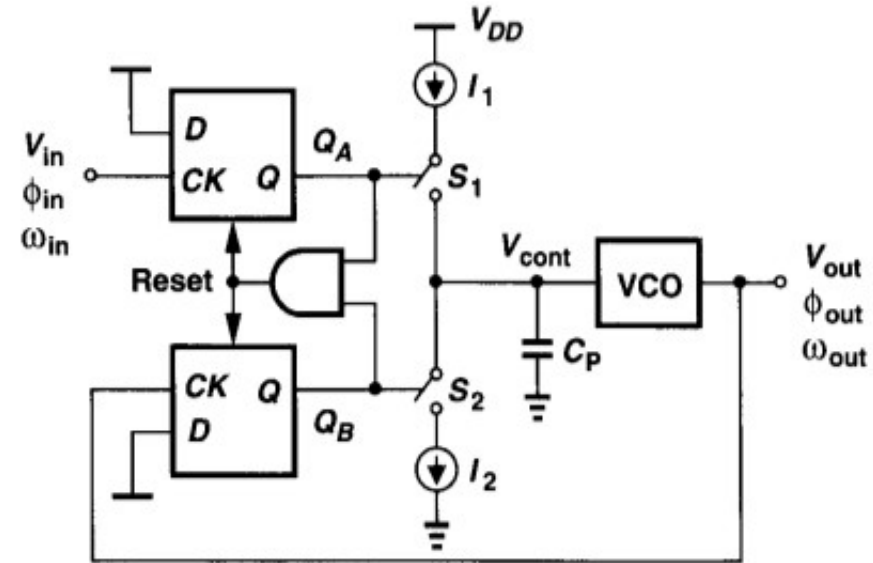 
# Dynamics of Charge-Pump Phase-Locked Loops


- ◆ When the system is just turned on,  $\omega_{out}$  and  $\omega_{in}$  may be very different
- ◆ As  $\omega_{out}$  approaches  $\omega_{in}$
- ◆ Transfer function of PFD+CP  
In case if  $\Delta\phi_{in}$  doubles





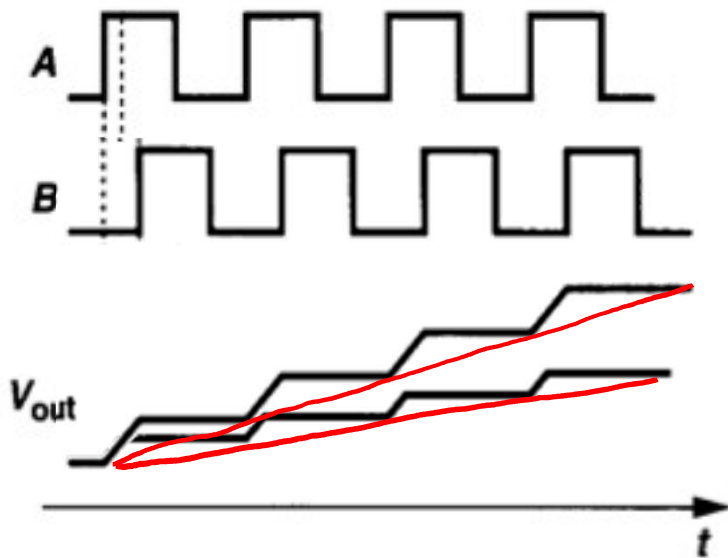
# Dynamics of Charge-Pump Phase-Locked Loops

- ◆ When the system is just turned on,  $\omega_{out}$  and  $\omega_{in}$  may be very different
- ◆ As  $\omega_{out}$  approaches  $\omega_{in}$
- ◆ Transfer function of PFD+CP  
In case if  $\Delta\phi_{in}$  doubles




➔ Strictly speaking: not a linear system

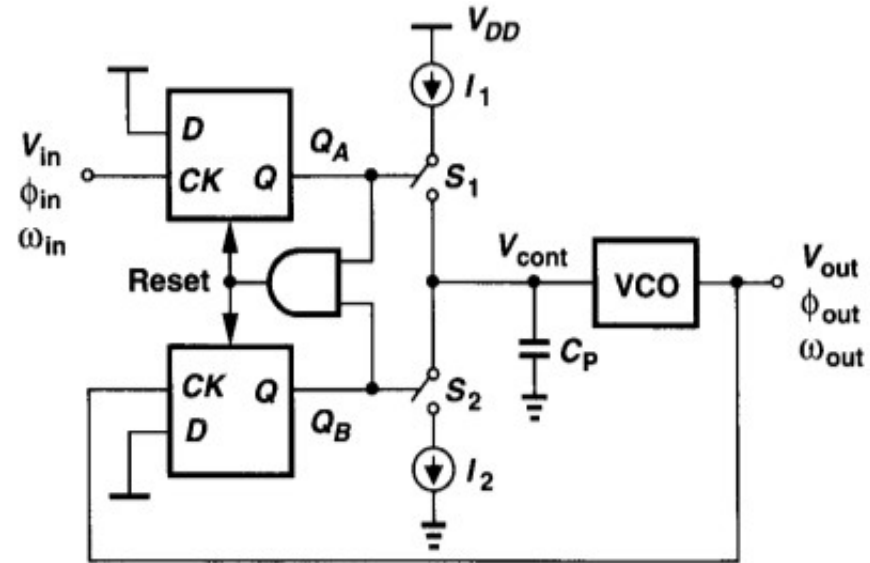

# Transfer Function of PFD+CP (I)

- ◆ With a phase step at input

 

with  $\phi_{in}(t) = \phi_0 \cdot u(t)$

step response

$$V_{out}(t) = \frac{I}{C_P} \cdot \frac{\phi_0}{2\pi} \cdot t \cdot u(t)$$

impulse response

$$h(t) = \frac{I}{C_P} \cdot \frac{\phi_0}{2\pi} \cdot u(t)$$

⇒ transfer function

$$\frac{V_{out}}{\Phi_{in}}(s) = \frac{I}{C_P} \cdot \frac{1}{2\pi} \cdot \frac{1}{s}$$


$\frac{I_P}{C_P}$  for the duration of  $\phi_0$   
average slope

$$\frac{I}{C_P} \cdot \frac{\phi_0}{2\pi}$$
 
# Transfer Function of PFD+CP (II)

◆ Average output current with  $\Delta\phi_{in}$   $\xrightarrow{\quad}$   $I_{ave}$   $\xrightarrow{\frac{1}{sC}}$   $V_{out}$

→ The current flows into a capacitor, establishing  $V_{out}$




$$\frac{\overline{V_{out}}}{\overline{\phi_{in}}}(s) = \frac{I}{2\lambda} \frac{1}{sC}$$

$$I_{ave} = I \frac{\phi_0}{2\lambda} \quad \Rightarrow$$

$$V_{out} = I_{ave} \frac{1}{sC} = I \frac{\phi_0}{2\lambda} \frac{1}{sC}$$
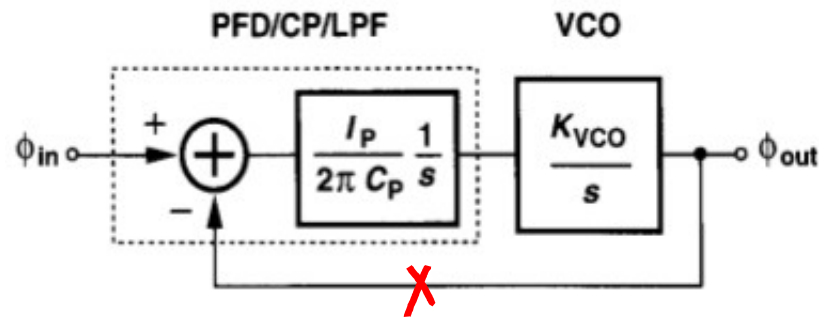
# Loop Dynamics (I)

- ◆ Linear model of the PLL → to derive the response from  $\phi_{in}$  to  $\phi_{out}$



- ◆ Open-loop transfer function (from phase → voltage → voltage → phase)

$$\frac{\Phi_{out}(s)}{\Phi_{in}(s)}|_{open} = \frac{I_P}{2\pi C_P} \frac{K_{VCO}}{s^2}$$


- Two poles at origin → type-II PLL

- ◆ Closed-loop transfer function  $H(s)$

$$H(s) = \frac{\frac{I_P K_{VCO}}{2\pi C_P}}{s^2 + \frac{I_P K_{VCO}}{2\pi C_P}}$$

two imaginary poles
 
$$s_{1,2} = \pm j \sqrt{\frac{I_P K_{VCO}}{2\pi C_P}}$$





# To Stabilize the Loop

- ◆ We need certain phase margin at  $\omega_u$
- A left-plane zero by inserting a resistor
- The charge pump sees R in series with C

$$\frac{\Phi_{out}}{\Phi_{in}}(s)|_{open} = \frac{I_P}{2\pi} \left( R_P + \frac{1}{C_{PS}} \right) \frac{K_{VCO}}{s} = \frac{I_P}{2\pi} \left( \frac{1+sRC}{sC} \right) \frac{K_{VCO}}{s}$$

*Leave ZLF*

 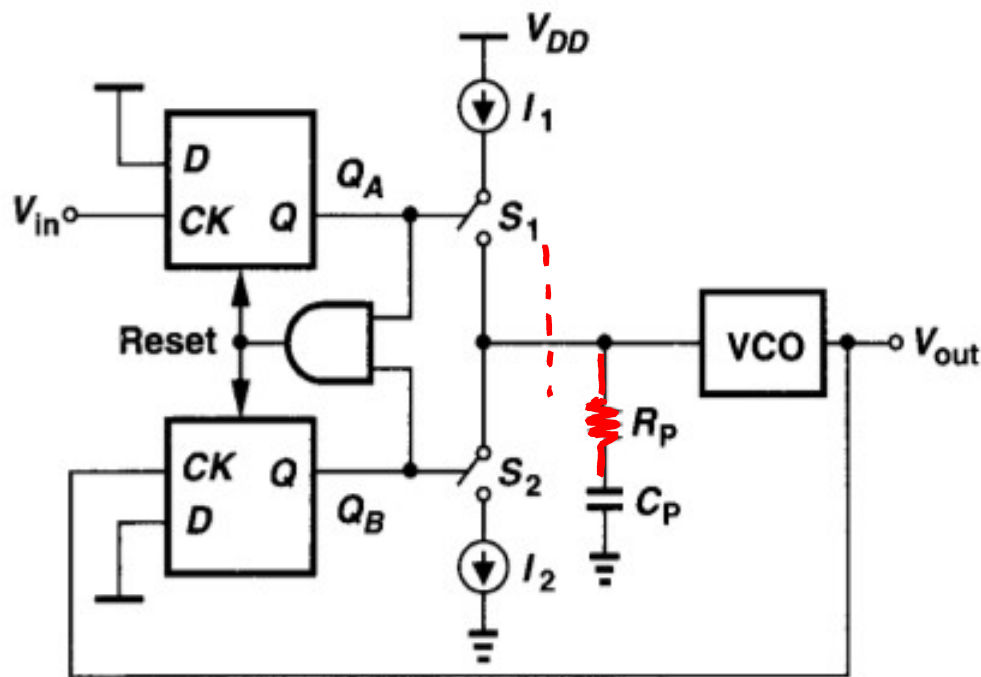


# Loop Dynamics (II)
 
## ◆ Closed-loop transfer function

$$H(s) = \frac{\frac{I_P K_{VCO}}{2\pi C_P} (R_P C_P s + 1)}{s^2 + \frac{I_P}{2\pi} K_{VCO} R_P s + \frac{I_P}{2\pi C_P} K_{VCO}}$$

$= \frac{W_{out}}{W_{in}}(s)$   
 $= \frac{\phi_{out}}{\phi_{in}}(s)$




- Low-frequency gain of unity
- Output tracks the input **phase** well if input phase varies slowly
- For input phase step, output phase eventually catches up
- The same applies to **frequency** as well

## ◆ Second-order system





$$\omega_n = \sqrt{\frac{I_P K_{VCO}}{2\pi C_P}} \quad \zeta = \frac{R_P}{2} \sqrt{\frac{I_P C_P K_{VCO}}{2\pi}} = \frac{R_C}{2} \sqrt{\frac{I_C K_{VCO}}{2\pi C_P}}$$

- To stabilize the system by increasing the damping factor

 - To speed up the loop response (loop BW)  $\uparrow \zeta$   
 $\uparrow \frac{1}{2} \frac{\omega_n}{\omega_z}$  (and  $\omega_z$ )



   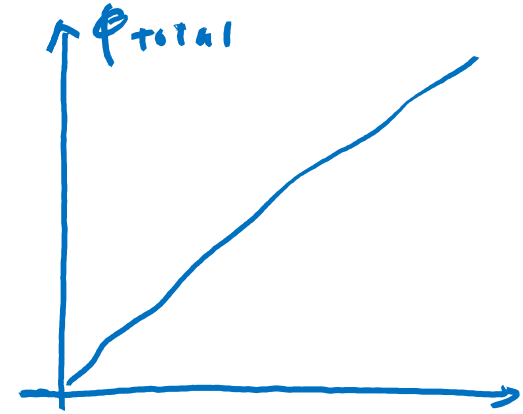
$$\frac{V_{out}}{V_{in}}(s) = A(s) = \frac{\gamma\gamma\delta}{s^2 + xxxs + \gamma\gamma\delta}$$



$$\frac{\phi_{out}}{\phi_{in}}(s) = \frac{\gamma\gamma\delta}{s^2 + xxxs + \gamma\gamma\delta}$$
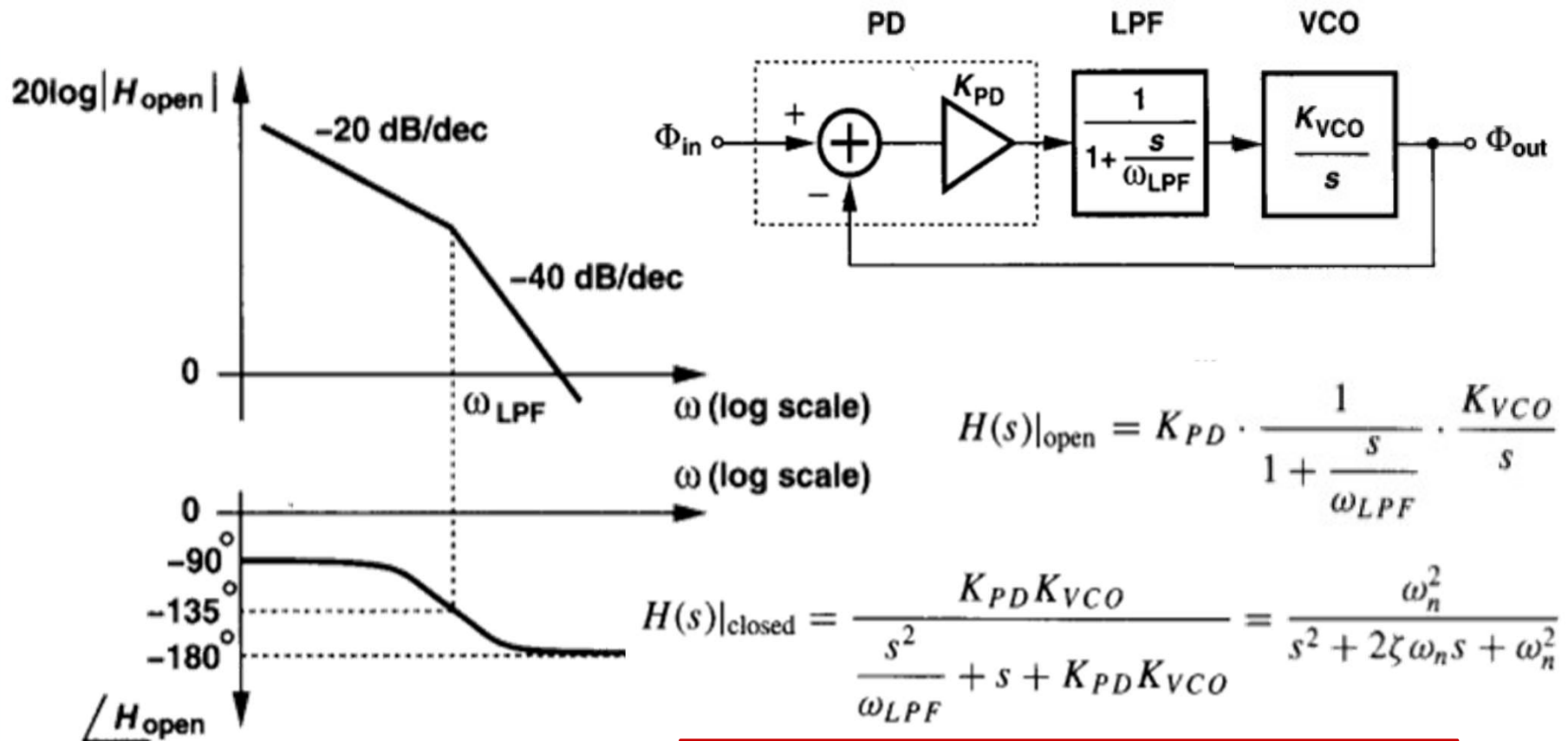
# Loop Dynamics of Basic PLL

- ◆ From Bode plot of open-loop transfer function





$$\omega_n = \sqrt{\omega_{LPF}K_{PD}K_{VCO}} \quad \zeta = \frac{1}{2} \sqrt{\frac{\omega_{LPF}}{K_{PD}K_{VCO}}}$$


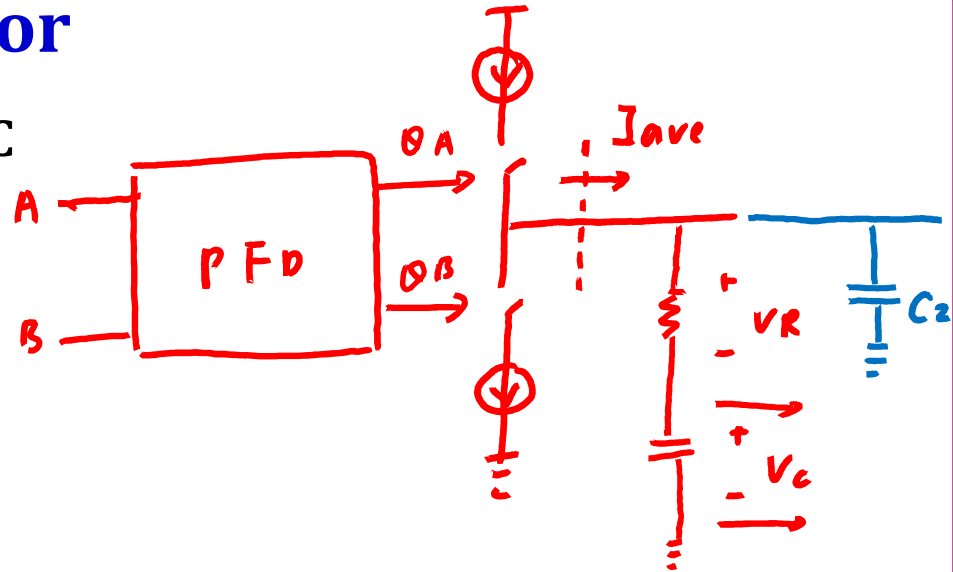 
# The Third-Order Capacitor

- Transient in  $V_{ctrl}$  with series R+C



proportional control

integral control

$$Z_{LF} = \left( R + \frac{1}{sC_1} \right) \parallel \frac{1}{sC_2}$$

additional pole @  $f \frac{C_1 C_2}{C_1 + C_2} \approx \frac{1}{RC_2}$



3-rd order capacitor

- Add a capacitor  $C_2$  in parallel with R+C to smooth  $V_{ctrl}$

$$H(s)|_{open} \approx \frac{I_{up}}{2R} \cdot \frac{K_{vco}}{s} \cdot \frac{1+sRC_1}{sC_1} \cdot \frac{1}{1+sR \frac{C_1 C_2}{C_1 + C_2}}$$
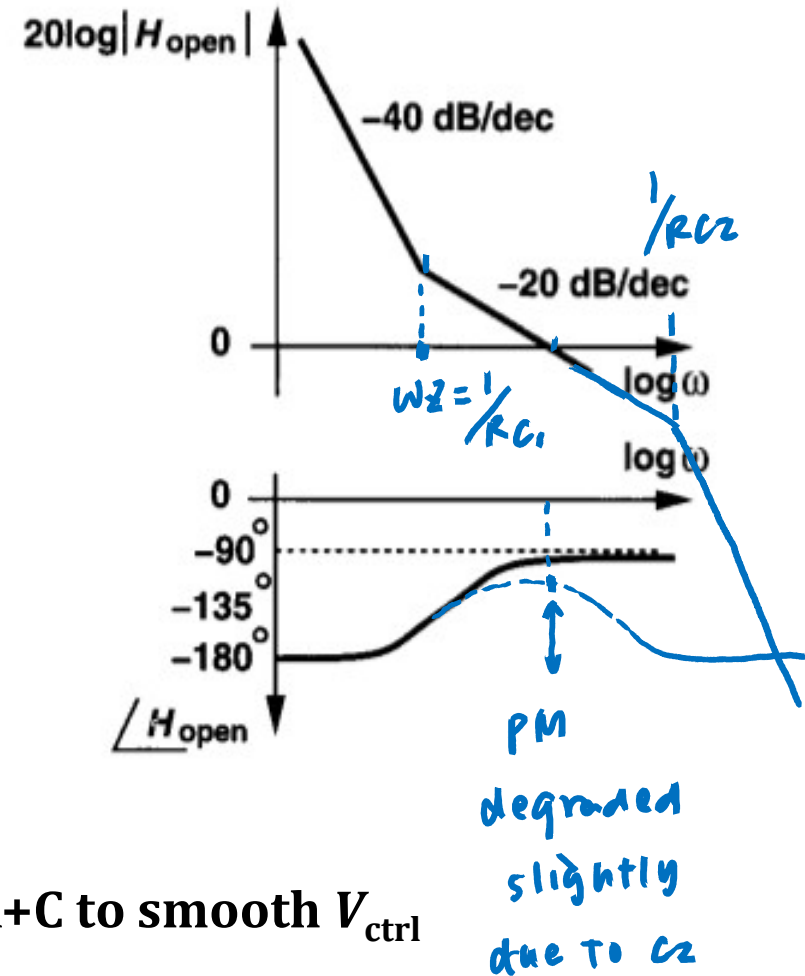 
# The Third-Order Capacitor

- ◆ Transient in  $V_{ctrl}$  with series R+C



- ◆ Add a capacitor  $C_2$  in parallel with R+C to smooth  $V_{ctrl}$

$$H(s)|_{open}$$



# Discrete-Time Nature of Phase-Locked Loops (I)

- ◆ **Continuous-time and linear approximation**
  - Yield reasonably accurate results when input frequency/phase varies slowly (compared to the reference frequency)
  - For example, with the operating frequency of 1 GHz and the input frequency varying with 1 MHz
  - Very dense sampling → close to continuous-time operation

## Discrete-Time Nature of Phase-Locked Loops (II)

- ◆ When the frequency (that the signal frequency/phase is varying at) becomes comparable to the reference frequency
  - For example, if  $\omega_m = 0.25\omega_{REF}$
  
- ◆ Nonlinear operation
- ◆ Sampling delay results in additional phase shift → degrade stability
- ◆ Typically  $\omega_n$  is kept to be  $1/20 \sim 1/10 \omega_{REF}$


# Frequency Divider

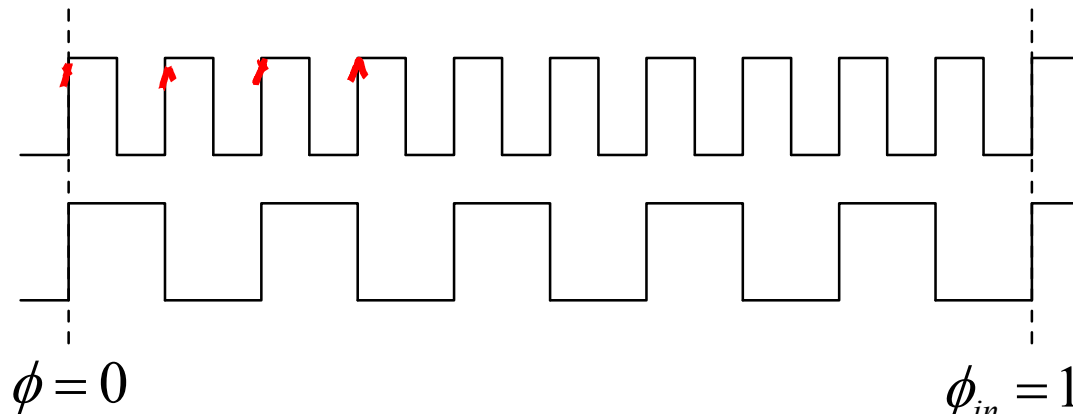 

$$\phi_{in} = 10 \cdot 2\pi$$

$$\phi_{in} = 5 \cdot 2\pi$$

 
- ◆ Usually implemented using digital circuits
- ◆ Both frequency and phase are divided by N


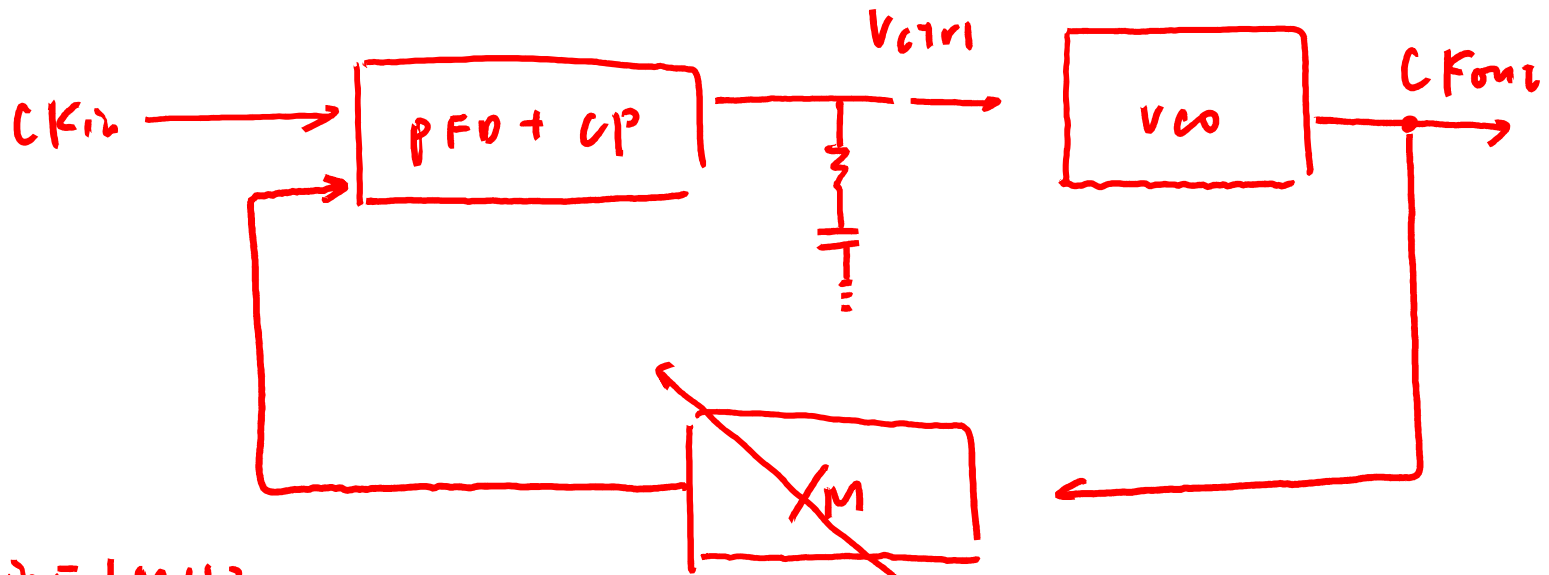
# With Frequency Divider in the Loop

- ◆ Input frequency can be different from output frequency

$$H_{loop}(s) = \frac{I_P}{2R} \left( \beta + \frac{1}{sC_1} \right) \frac{K_{VCO}}{s} \frac{1}{M}$$



$$CK_{in} = 1 \text{ MHz}$$

$$\text{with } M = 1000 \rightarrow CK_{out} = 1 \text{ GHz}$$

$$M = 999 \rightarrow CK_{out} = 999 \text{ MHz}$$

digital circuit  
with adjustable division  
ratio

output frequency can be adjusted with steps of  $f_{REF}$

## With Frequency Divider in the Loop

- ◆ Input frequency can be different from output frequency

- ◆ The transfer function: 
$$\frac{\phi_{out}}{\phi_{in}} = \frac{\frac{I_{CP}}{2\pi} \left( R + \frac{1}{sC_P} \right) \frac{K_{VCO}}{s}}{1 + \frac{I_{CP}}{2\pi} \left( R + \frac{1}{sC_P} \right) \frac{K_{VCO}}{M \cdot s}} = \frac{\frac{I_{CP} K_{VCO}}{2\pi C_P} (1 + sRC_P)}{s^2 + \frac{I_{CP} K_{VCO}}{2\pi M} Rs + \frac{I_{CP} K_{VCO}}{2\pi C_P M}}$$


$$\omega_n = \sqrt{\frac{I_{CP} K_{VCO}}{2\pi M C_P}} \text{ and } \zeta = \frac{R}{2} \sqrt{\frac{I_{CP} C_P K_{VCO}}{2\pi M}}$$

- ◆ Can be used for frequency synthesis
- Frequency adjustment set by reference

# Nonidealities in Phase-Locked Loops (I)

## ◆ Design considerations of PFD+CP

 1) Reset pulse width: in case with no pulse or very narrow pulse






# Nonidealities in Phase-Locked Loops (I)


## ◆ Design considerations of PFD+CP

 1) Reset pulse width: in case with no pulse or very narrow pulse



→ CP switches may not even get turned on

 
→ CP current may not settle in the short duration




# Nonidealities in Phase-Locked Loops (I)

## ◆ Design considerations of PFD+CP

 1) Reset pulse width: in case with no pulse or very narrow pulse



 
- CP switches may not even get turned on
- CP current may not settle in the short duration
- For very small phase error, PFD+CP fail to produce proportional outputs


 
## Nonidealities in Phase-Locked Loops (II)


- ◆ **Effect of dead zone**

→ negative feedback is broken with small phase error



- ◆ **Sufficiently wide reset pulse allows PFD+CP to settle**


→ Ready for small phase error

 
 
## Nonidealities in Phase-Locked Loops (II)


- ◆ **Effect of dead zone**

→ negative feedback is broken with small phase error



- ◆ **Sufficiently wide reset pulse allows PFD+CP to settle**

→ Ready for small phase error


 


# Nonidealities in Phase-Locked Loops (III)



◆ Design considerations of PFD+CP

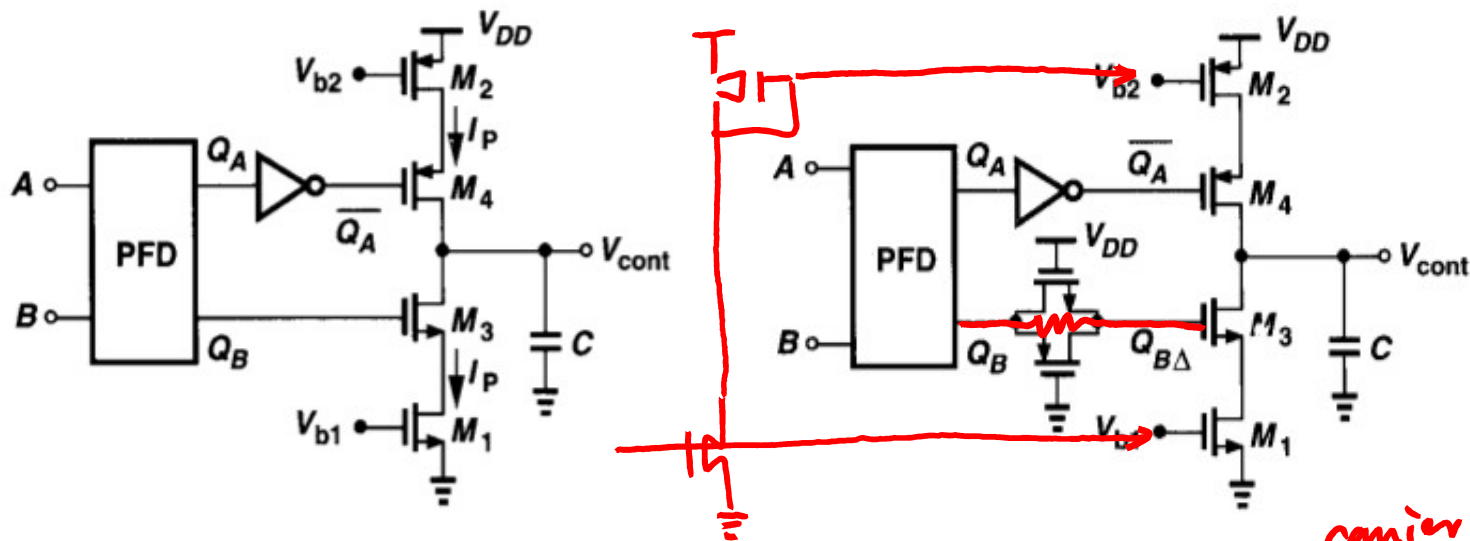 2) Skew in  $Q_A$  and  $Q_B$  pulses

- As the upper part of circuit is usually implemented using PMOS



@  $\Delta\phi = 0$

  


$\neq \Delta\phi = M$  output  
reference spur

## Nonidealities in Phase-Locked Loops (IV)

- ◆ Design considerations of PFD+CP

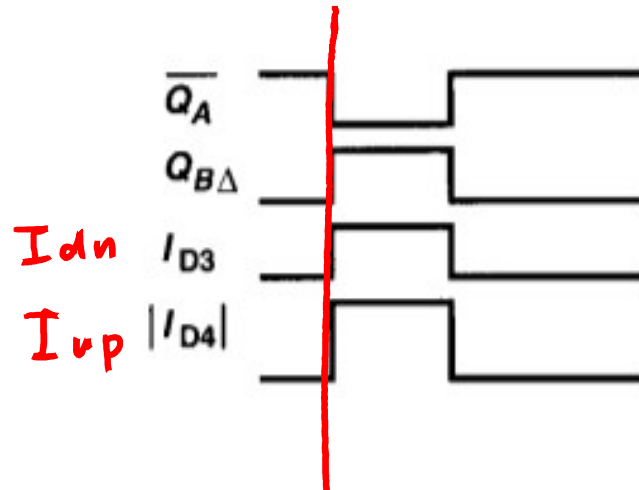- 3) Mismatch between up and down currents

- Even with perfect pulse alignment, for example, if  $I_{up} > I_{down}$




# Nonidealities in Phase-Locked Loops (IV)

- ◆ Design considerations of PFD+CP

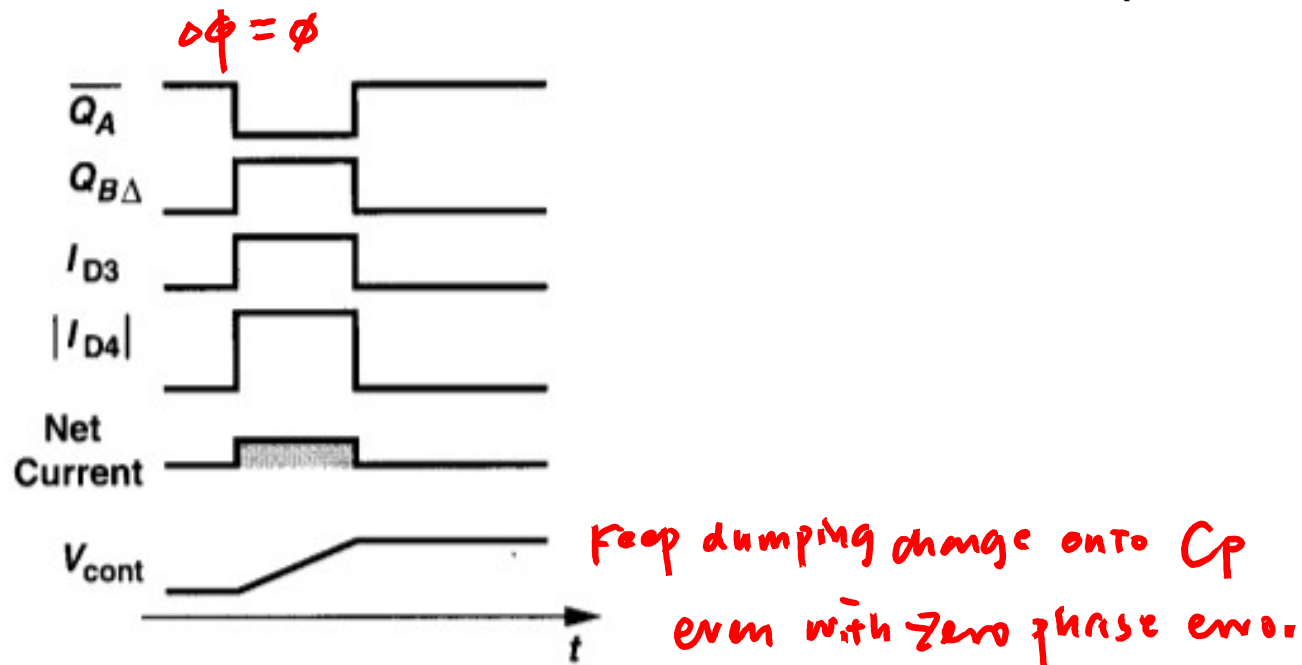- 3) Mismatch between up and down currents

- Even with perfect pulse alignment, for example, if  $I_{up} > I_{down}$




# Nonidealities in Phase-Locked Loops (IV)

- ◆ Design considerations of PFD+CP

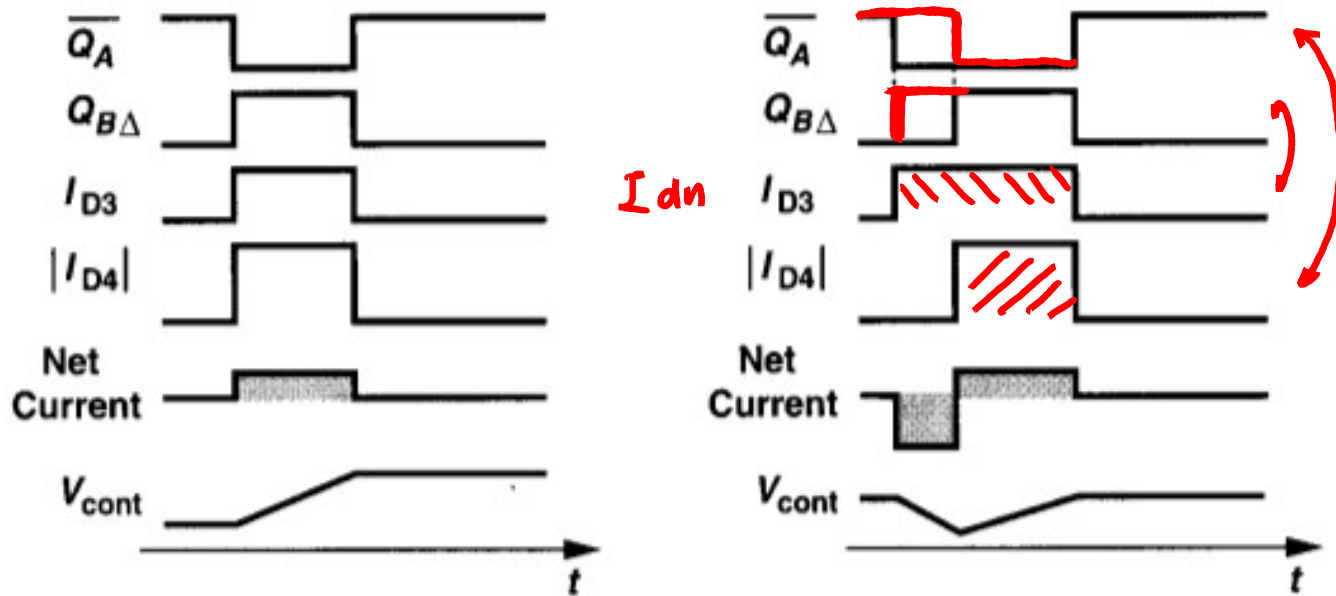- 3) Mismatch between up and down currents

- Even with perfect pulse alignment, for example, if  $I_{up} > I_{down}$




- Resulting in static phase error and  $V_{ctrl}$  ripple  $\rightarrow$  reference spur
- Difficult to maintain perfect match between  $I_{up}$  and  $I_{down}$  due to  $r_o$  of transistors  $\rightarrow$  worse for advanced technology



 
# Phase Noise and Jitter in Phase-Locked Loops (I)




- ◆ Total phase of a clean clock vs. a jittery clock



 - ◆ Different ways to characterize and quantify jitter
  - Cycle jitter, cycle-to-cycle jitter, long-term or absolute jitter




$\Rightarrow$

  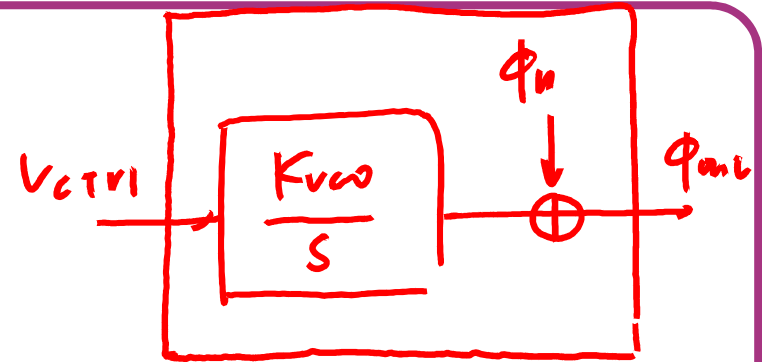

# Phase Noise and Jitter in Phase-Locked Loops (II)

- ◆ The rate at which the phase varies

 


- ◆ Two sources of jitter that are of most interest

- Jitter of the reference input
  - Jitter generated from the VCO
- $$\frac{\Phi_{out}}{\Phi_{in}}(s) = \frac{\frac{I_P K_{VCO}}{2\pi C_P} (R_P C_P s + 1)}{s^2 + \frac{I_P}{2\pi} K_{VCO} R_P s + \frac{I_P}{2\pi C_P} K_{VCO}}$$

 
# Phase Noise and Jitter in Phase-Locked Loops (III)

◆ Jitter from VCO  $\frac{\phi_{out}}{\phi_{n,vco}}(s) = \frac{1}{1 + H_{open}(s)}$

$$\frac{\Phi_{out}}{\Phi_{in}}(s) = \frac{\frac{I_P K_{VCO}}{2\pi C_P} (R_P C_P s + 1)}{s^2 + \frac{I_P}{2\pi} K_{VCO} R_{PS} + \frac{I_P}{2\pi C_P} K_{VCO}}$$


 
$$\frac{\Phi_{out}}{\Phi_{VCO}}(s) = \frac{s^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$



- ◆ Trade-off between noise contributions from different sources