

**EE3235 Analog IC Analysis & Design - I 2019. Fall.**

HW2

Due date : 2019. 10. 25 (Friday.) 23:59pm (upload to iLMS System)

First release : 2019. 10. 11


HW2 –Common Source

This homework is for you to design a **common source** stage. The results should include HSPICE simulations and hand calculations. The SPICE model is cic018.l. Please use the parameters from HSPICE simulation results for hand calculations.

Please note:

1. Please hand in your report using LMS.
2. Please note, **no delay allowed!!!**
3. Please generate your report with **pdf** format (AIC\_HW{X}\_StudentID.pdf). At first page please add your student ID and name. Try to make the information “readable”. (Note: Don’t use black color in background for your screen capture figures).
4. Please hand in the spice code file (AIC\_HW{X}\_StudentID.sp) with your report for each work. Do not include output file.
5. Please fill the results into HW2.xls. **(without this file, -20pt)**
6. Do not zip your whole package.

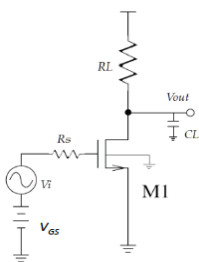**Please attach your spice code at the end of report.**



Please follow the rules as before.

In the common source, please use  $V_{DD}=1.5V$ . The source impedance  $R_s$  is assumed **10Kohm** and the loading capacitance  $C_L$  is **1.0pF**.

**(maximize the  $FoM_1$ )**

- (a) Please design the device size of  $M_1$ , load resistance  $R_L$ , and the bias voltage  $V_{GS}$ , to make the small signal voltage gain ( $v_{out}/v_i$ ) is **15**.
- (b) We define the figure of merit ( $FoM_1$ ) as “bandwidth (MHz) / bias current ( $\mu A$ )”. Please try your best.

**(determine the operation point)**

- (c) Please use `.op` command to print out its small signal parameters.
- (d) Please hand-calculate the gain value using SPICE parameters from (b).
- (e) Please sweep the gate DC voltage to draw its DC transfer curve. Please observe and mark the input-output linear transfer range around the selected  $V_{GS}$ .

**(get the frequency response)**

- (f) Please plot the frequency response of this gain stage. And mark the poles and zeros on the curve. (please use `.pz` command to get poles and zeros, and compare with hand calculation).
- (g) Please discuss your observations for best FOM<sub>1</sub>.

**(maximize the FoM<sub>2</sub>)**

- (h) We will use the “maximal small-signal voltage gain” as the figure of merit (FOM<sub>2</sub>). Please try your best.
- (i) Please discuss your observations for best FOM<sub>2</sub>.

For FoM <sub>1</sub> (fast speed and low power)	
M <sub>1</sub> Device Size (W/L)	
M <sub>1</sub> Bias Current (μA)	
M <sub>1</sub> Overdrive Voltage (mV)	
Load R (ohm)	
Small-Signal Voltage Gain (V/V)	15
Bandwidth (MHz)	
FoM <sub>1</sub> ( max (bandwidth (MHz) / bias current (μA) )	
For FoM <sub>2</sub> (highest gain)	
M <sub>1</sub> Device Size (W/L)	
M <sub>1</sub> Bias Current (μA)	
M <sub>1</sub> Overdrive Voltage (mV)	
Load R (ohm)	
Bandwidth (MHz)	
FoM <sub>2</sub> ( max small-signal voltage gain (V/V) )	