

EE3235 Analog IC Analysis & Design - I 2019. Fall.

HW4

Due date : 2019. 11. 22 (Fri) 23:59pm (upload to iLMS System)

First release : 2019. 11. 07


HW4 –Current DAC with Mirrors

In this homework is for you to design a current-steering digital-to-analog converter (CS-DAC) with binary-scaled current sources. The problem sets include HSPICE simulations compared with the ideal curve. The SPICE model is cic018.l.


Please note:

1. Please hand in your report using LMS.
2. Please note, **no delay allowed!!!**
3. **Please generate your report with pdf format (AIC_HW{X}_StudentID.pdf). At first page please add your student ID and name. Try to make the information “readable”.** (Note: Don’t use black color in background for your screen capture figures).
4. Please **hand in the spice code file (AIC_HW{X}_StudentID.sp)** with your report for each work. Do not include output file.
5. **Please fill the results into the table in the last page. (without this table, -20pt)**
6. Do not zip your whole package.


Please attached your spice code for each working item in your report, in addition to separate .sp file.

 

(Ideal 4-b CS-DAC)

 

(Cascoded current unit)

 

(Ideal DAC output)

In this differential pair circuit, please use $V_{DD}=1.5V$. The load impedance R_L is assumed **0.5Kohm** and the output full swing range is **0.75V**.

- (a) Please design your cascaded current unit to generate all the current level. (please use the multiple device size ratio, ie, x1, x2, x4, x8).
- (b) Please plot the ideal DAC output level and compare to your real circuit output.
- (c) Please calculate the DNL and INL error of each code.
- (d) Discuss your selection on circuit bias and device size, and the error between the ideal and the real outputs.

Working Item		Simulation result												
Vdd		1.5-V												
Reference I _o		0.1mA												
Reference size (W/L _{bottom} , W/L _{cascode})		1.5u/0.18u (bottom), 5u/0.18u (cascode) (x1, x2, x4, x8)												
Output load R _{out}		0.5 Kohm												
DAC unit size (W/L _{bottom} , W/L _{cascode})		1.5u/0.18u (bottom), 5u/0.18u (cascode), 2u/0.18u (switch) (x1, x2, x4, x8)												
Output voltage range (0.75)		0.744V												
DNL Error (%) [(this level – previous level) - ideal step] / ideal step (0.75V/15)														
I ₁	I ₂	I ₃	I ₄	I ₅	I ₆	I ₇	I ₈	I ₉	I ₁₀	I ₁₁	I ₁₂	I ₁₃	I ₁₄	I ₁₅
-0.4	-0.4	-0.4	-0.6	-0.4	-0.6	-0.6	-0.6	-0.6	-0.8	-0.8	-1	-1.4	-1.8	-2.2
INL Error (%) (this level – ideal level) / ideal step (0.75V/15)														
I ₁	I ₂	I ₃	I ₄	I ₅	I ₆	I ₇	I ₈	I ₉	I ₁₀	I ₁₁	I ₁₂	I ₁₃	I ₁₄	I ₁₅
0.4	0.8	1.2	1.8	2.2	2.8	3.4	4	4.6	5.4	6.2	7.2	8.6	10.4	12.6