

## Example


$V_{DD} = V_{SS} = 1.5V$ ,  $I = 0.4mA$ ,  $R_D = 2.5k\Omega$ . Minimum voltage across current source  $V_{CS} = 0.4V$   
For  $Q_1$  and  $Q_2$ :  $k_n = 4mA/V^2$ ,  $V_{tn} = 0.5V$ . Find  $V_S$ ,  $I_{D1}$ ,  $I_{D2}$ ,  $V_{D1}$ ,  $V_{D2}$  for 3 different  $V_{CM}$  below:

Due to symmetry,  $I_{D1} = I_{D2} = I/2$  for all 3  $V_{CM}$  values

$$V_{GS} = V_m + \sqrt{I/k_n} = 0.5 + 0.32 = 0.82V$$

$$V_{D1} = V_{D2} = V_{DD} - 0.5I \cdot R_D = 1.5 - 0.2 \times 2.5 = 1V$$
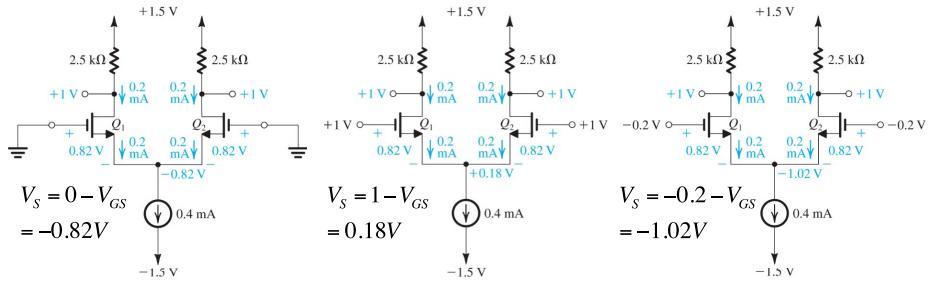
$$\text{Differential output } V_{D1} - V_{D2} = 0$$



Maximum  $V_{CM}$  should keep  $Q_1$  and  $Q_2$  in Saturation

$$V_{DS} > V_{GS} - V_m; \quad V_D - V_S > V_G - V_m; \quad V_{CM,\max} = V_{G,\max} = V_D + V_m = 1.5V$$

Minimum  $V_{CM}$  should keep  $V_S$  above minimum current source voltage,  $V_{CS}$

$$V_{CM,\min} = -V_{SS} + V_{CS,\min} + V_{GS} = -1.5 + 0.82 + 0.4 = -0.28V$$



18-5

## Operation with Differential Input Voltage

$$i_{D1} = \frac{k_n}{2} (v_{GS1} - V_t)^2; \quad i_{D2} = \frac{k_n}{2} (v_{GS2} - V_t)^2$$

$$\sqrt{i_{D1}} - \sqrt{i_{D2}} = \sqrt{\frac{k_n}{2}} (v_{GS1} - v_{GS2}) = \sqrt{\frac{k_n}{2}} v_{id}$$

square both sides, and recall  $i_{D1} + i_{D2} = I$


$$2\sqrt{i_{D1}i_{D2}} = I - \frac{k_n}{2} v_{id}^2$$

substitute  $i_{D2} = I - i_{D1}$ , solve quadratic equation:

$$i_{D1,2} = \frac{I}{2} \pm \sqrt{k_n I} \frac{v_{id}}{2} \sqrt{1 - \frac{(v_{id}/2)^2}{I/k_n}}$$

$$\frac{I}{2} = \frac{1}{2} k_n V_{OV}^2 \quad \Rightarrow \quad k_n = I / V_{OV}^2$$
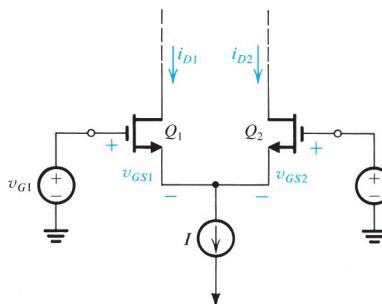
$$i_{D1,2} = \frac{I}{2} \pm \frac{I}{V_{OV}} \frac{v_{id}}{2} \sqrt{1 - \frac{(v_{id}/2)^2}{V_{OV}^2}}$$



18-6




## Operation with Differential Input Voltage

$$i_{D1,2} = \frac{I}{2} \pm \frac{I}{V_{OV}} \frac{v_{id}}{2} \sqrt{1 - \frac{(v_{id}/2)^2}{V_{OV}^2}}$$

Near  $v_{id} = 0$  :  
 $\sqrt{1 - \frac{(v_{id}/2)^2}{V_{OV}^2}} \approx 1$  (neglect high-order terms)

$$i_{D1} = \frac{I}{2} + \frac{I}{V_{OV}} \frac{v_{id}}{2}$$
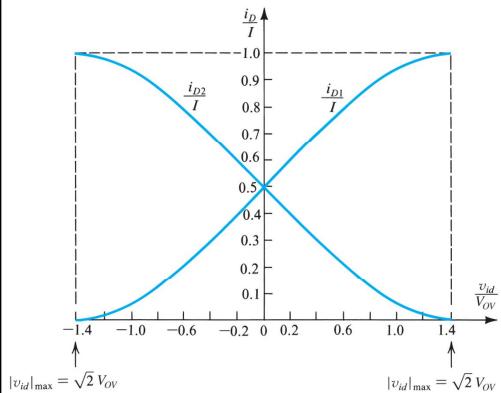
$$i_{D2} = \frac{I}{2} - \frac{I}{V_{OV}} \frac{v_{id}}{2}$$




18-7



*Cal*
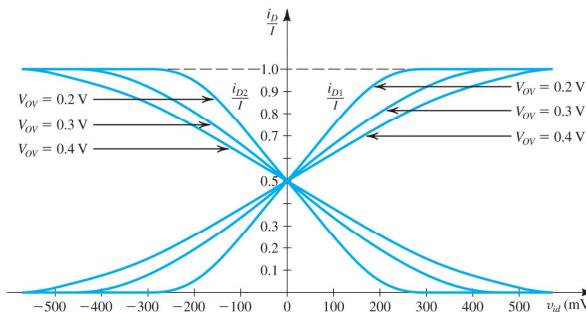
## Current of Differential Pair for Various Overdrive Voltage

$$i_{D1,2} = \frac{I}{2} \pm \frac{I}{V_{OV}} \frac{v_{id}}{2} \sqrt{1 - \frac{(v_{id}/2)^2}{V_{OV}^2}}$$



The linear range of operation of the MOS differential pair can be extended by operating the transistor at a higher value of  $V_{OV}$

18-8



*Cal*