

Lab Instruments, Passive Elements and Lab 1


- Instruments:
 - DC power supply, function generator, digital multimeter (DMM) and digital oscilloscope
- Coding of resistor and capacitor
- Wires and protoboard
- Lab 1 includes
 - DC measurement: Superposition, Thévenin's Theorem, maximum power transfer and Norton's Theorem
 - AC measurement: RL and RLC circuits

Grounding (接地)

- Ground
 - As a zero potential reference
 - The individual ground of all instruments and circuits should be connected to produce a unified ground during measurement
 - The ground resistance is desired to be small

DC Power Supply 直流電壓、電流供應器


- 注意：如右下角所提供的電壓或電流是相對於COM1埠

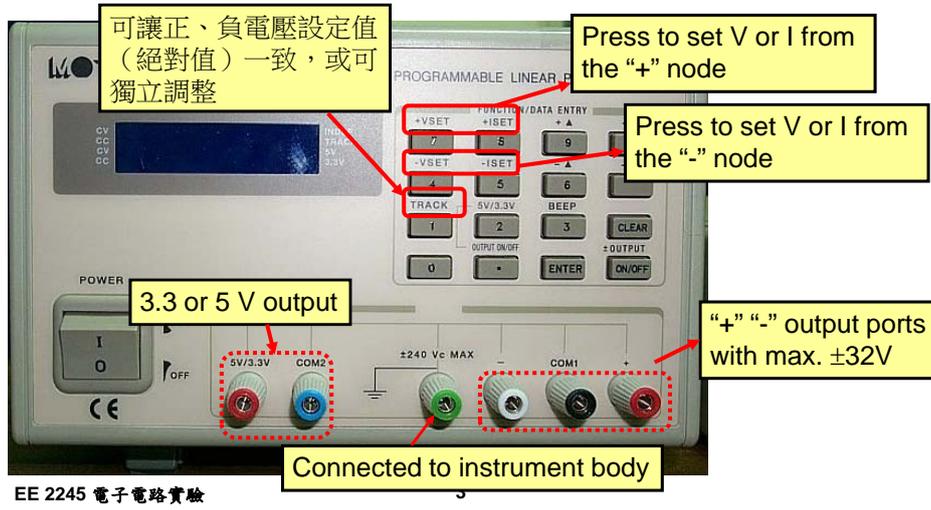

EE 2245 電子電路實驗

Function Generator (訊號產生器)


- It produces desired ac waveforms (sinusoidal, square wave, or triangle) as the input to circuit
- 本實驗室的訊號產生器本身有 $50\text{-}\Omega$ source impedance. 針對負載 R_L · 儀器有 $R_L = 50\text{ }\Omega$ 及高負載(High Z)的選項(default = $50\text{ }\Omega$)
 - For $R_L = 50\text{ }\Omega$: set $1 V_{p-p}$ as the output and you will get $2 V_{p-p}$ on the oscilloscope . Why?
 - For $R_L = \text{High Z}$: set $1 V_{p-p}$ as the output and you will get $1 V_{p-p}$

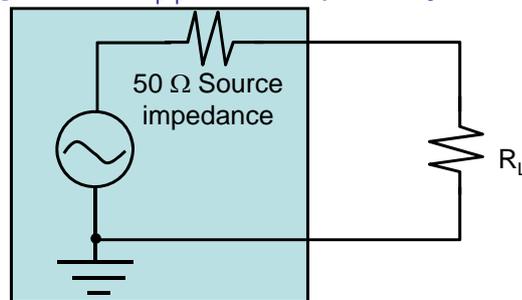

EE 2245 電子電路實驗

4

Front Panel 按鍵與功能

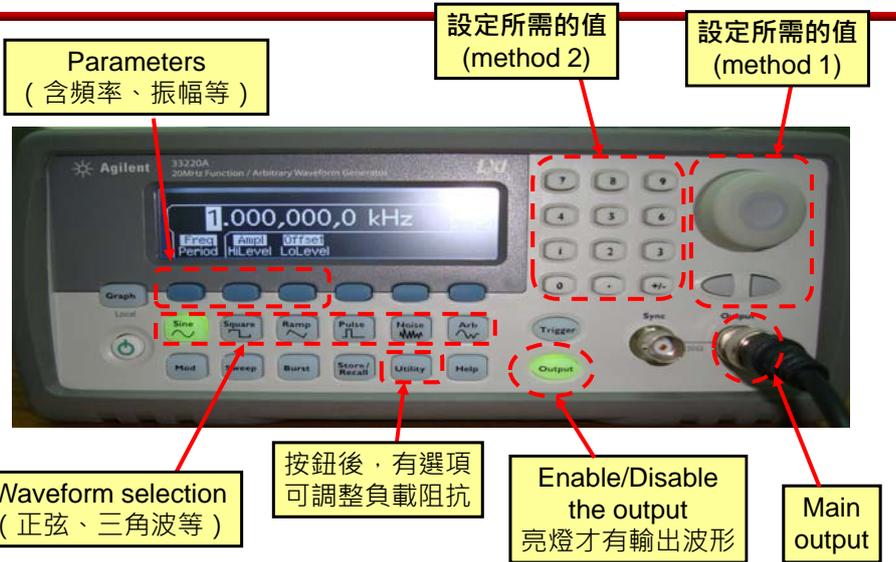

Digital Multimeter (DMM) 數位三用電表


- Capabilities: measure dc and ac electrical voltage, current, and resistance (一般以量直流為主)
 - The ac value is the root-mean-square (rms) value

$$V_{RMS} = \left[\frac{1}{T} \int_0^T v^2(t) dt \right]^{0.5}$$




Connections for Measurements (V, I, and R)

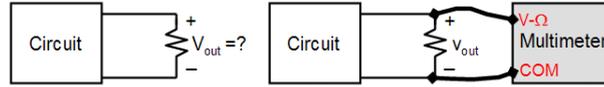
- Measurement of voltage: The multimeter connected in parallel



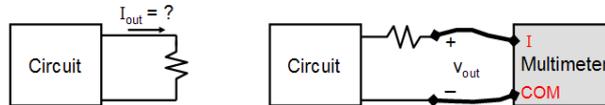- Measurement of current: The multimeter connected in series



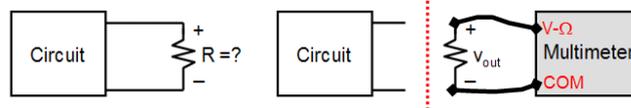
- Measurement of resistance: The resistor to be measured must be disconnected from the circuit



EE 2245 電子電路實驗

7


Voltage or Resistance Measurement

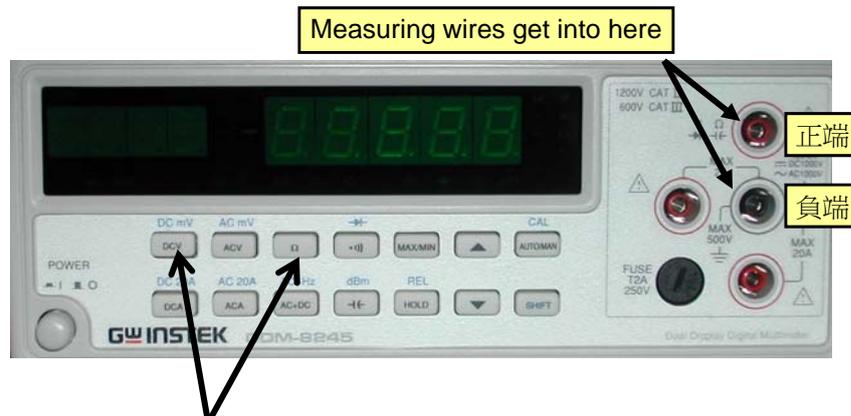

EE 2245 電子電路實驗


8

Current Measurement

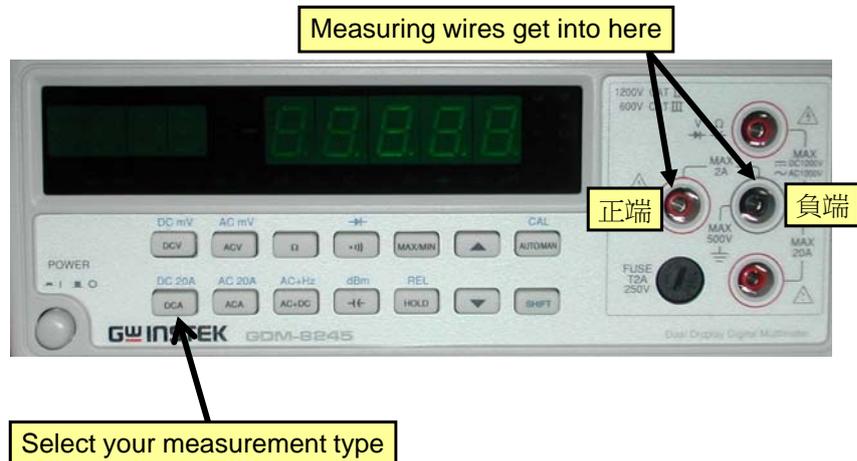


Oscilloscope (示波器)

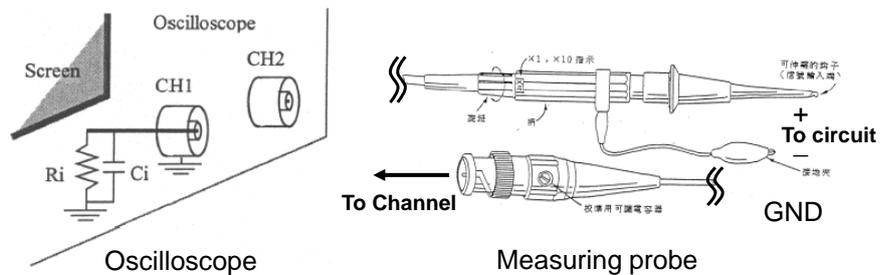- To display the voltage waveforms with respect to time
- 至少two channels (可顯示輸入及輸出波形)
- Analog type and digital type (現在幾乎都是數位示波器)
- 一般示波器 (頻率在數十MHz等級) 看進去的輸入電阻阻抗在MΩ以上(why?); 更高頻的示波器輸入電阻阻抗則有50 Ω的選項



Front Panel 功能與按鍵

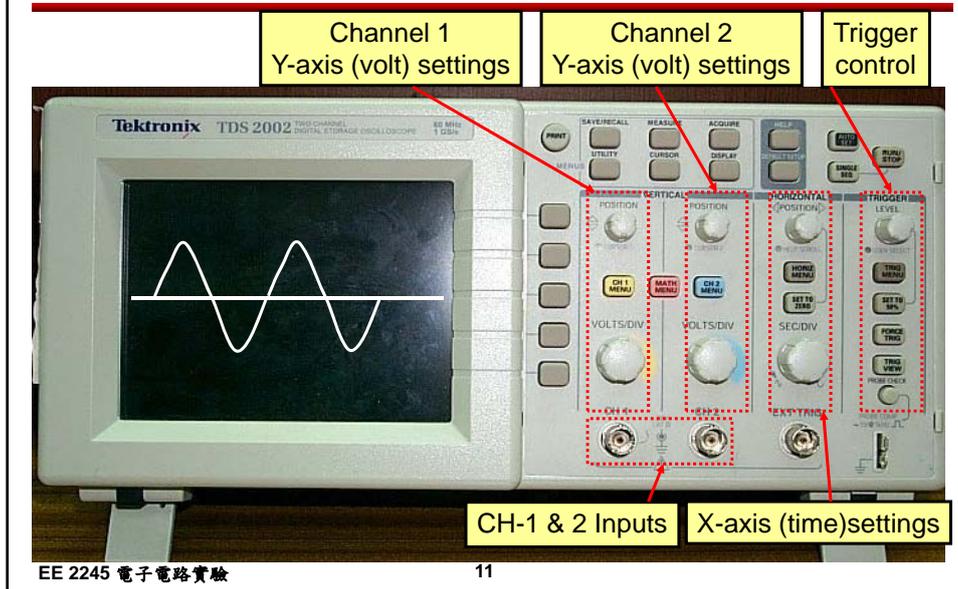


To Display the Waveform Properly, You Should:

- Have the proper X (time) and Y (voltage) settings
- Have the correct triggering settings (重要：根據以往經驗，超過百分之八十修過課的同學不會用trigger，對於以後做研究量測訊號會有影響)

Y-axis (Voltage) Settings : (耦合及探棒的選項最常需要注意到)

Once you press the "CH1 MENU" button you get:


按這些鈕來改變相對應的操作參數 (如耦合及探棒選項)

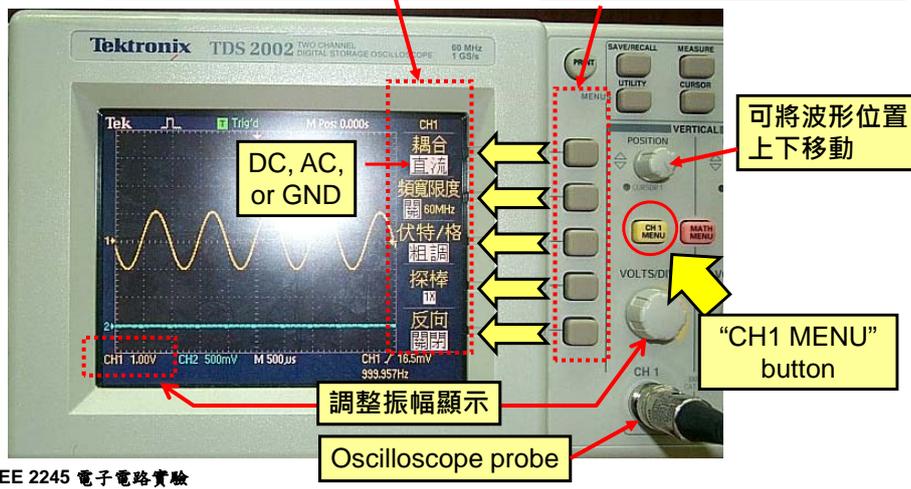

EE 2245 電子電路實驗

Cont'd: 耦合及探棒的選項

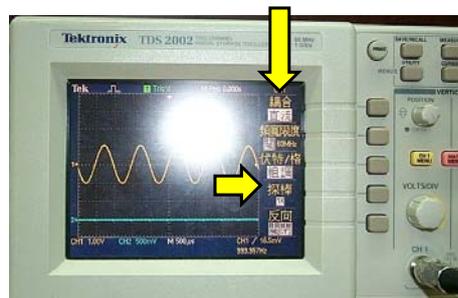- 耦合:
 - 直流耦合: 將波形的直流與交流完整輸出
 - 交流耦合: 將波形的直流去除, 僅輸出交流波形
 - 接地耦合: 顯示接地(0 V), 不顯示波形
- 探棒: 示波器的選項(1X, 10X等) 必須和量測用探棒你所選的選項(1X, 10X等) 相同, 不然你會觀察到量測波形振幅有十倍落差



EE 2245 電子電路實驗

14

X-axis (Time) Settings




EE 2245 電子電路實驗

15

Trigger

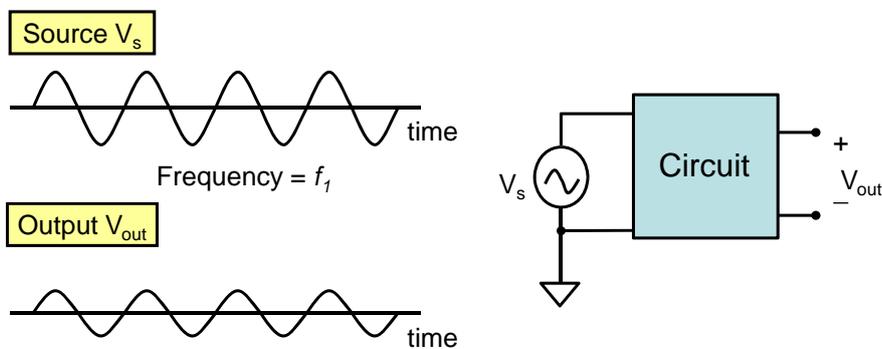- 一般常用電路的ac source (V_s)作為觸發訊號源(trigger) · 以便在示波器上得到輸出波形 V_{out} (因為 V_s 及 V_{out} 相同頻率、且 V_{out} 是來自於 V_s)
 - 因為每一台的ac source其訊號頻率相位會隨時間作少許漂移 · 所以 · 你不能用另外一台具相同頻率的ac source作觸發訊號源




EE 2245 電子電路實驗

16

Cont'd

- 有了相同頻率(f_1)的訊號作trigger，可得到較固定清晰的量測波形

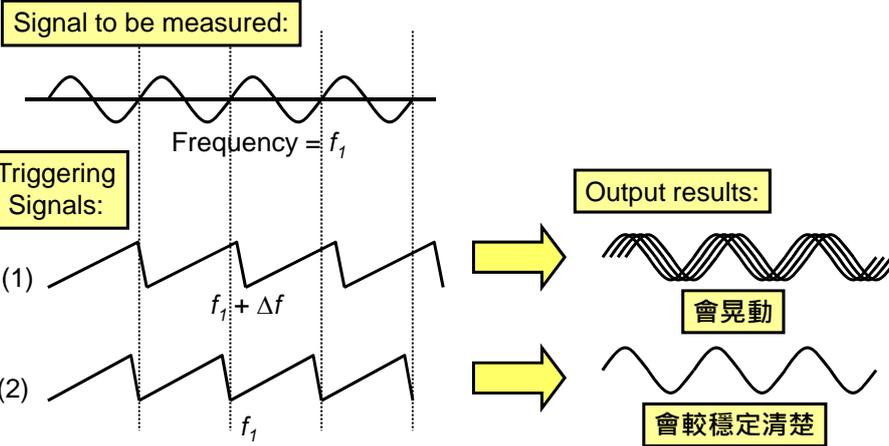

EE 2245 電子電路實驗

17

Trigger Control

Once you press the "TRIG MENU" button 即得到：

For changes, you press one of these

1. 最重要，信號源的設定
2. 調整 "TRIG MENU" 鍵之上的 "level" 旋鈕來得到不晃動的波形




EE 2245 電子電路實驗


18

Oscilloscope Probe

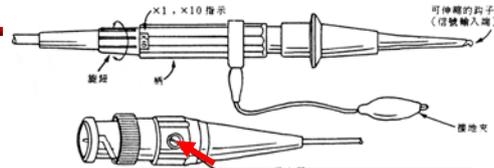- Two options: "x 1" and "x 10" (可在probe上調整)
- The "x10" probe is intended the lower the loading effect to the circuit under test
 - 10 times attenuation
- 請確認示波器及探針對於x 1或x 10的設定是一致，否則你會量到差十倍的訊號




Calibration (用起子旋轉，以校正Probe)

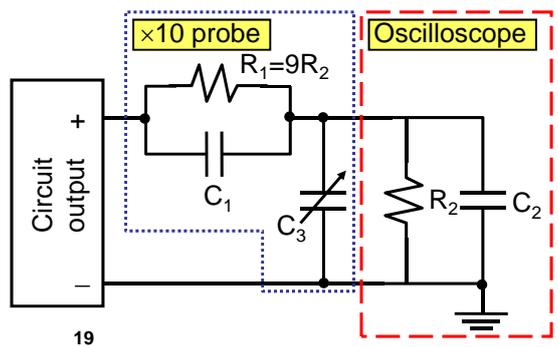


Calibration of Measuring Probe--由示波器所觀察到的波形來校正



OUTPUT PATTERNS

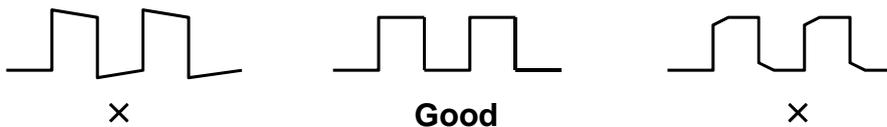

Resistor Color Code – 由電阻上的顏色環得知電阻值

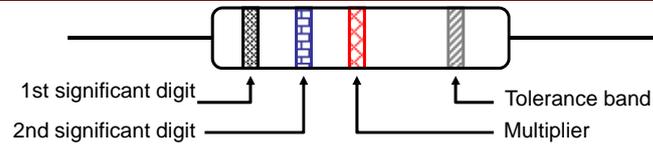


Color	1st and 2nd Digits	Multiplier	Tolerance (%)
Black	0	10^0	—
Brown	1	10^1	1
Red	2	10^2	2
Orange	3	10^3	—
Yellow	4	10^4	—
Green	5	10^5	0.5
Blue	6	10^6	0.25
Purple	7	10^7	—
Gray	8	10^8	—
White	9	10^9	—
Silver	—	0.01	10
Gold	—	0.1	5
No Color	—	—	20

EE 2245 電子電路實驗

21

Example

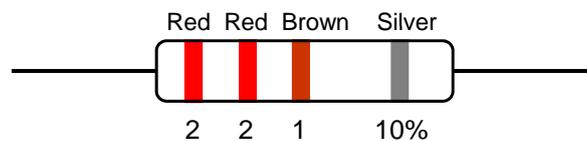

$$R_{\text{nominal}} = 22 \times 10^1 = 220 \Omega$$


$$\therefore R = 220 \pm (220 \times 10\%) \Omega = 198 \Omega \text{ to } 242 \Omega$$

EE 2245 電子電路實驗


22

Capacitor—如何辨識電容值？

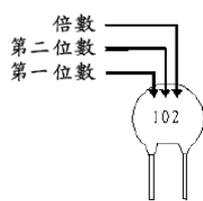
1. Use numbers. The minimum unit is pico-farad ($1 \text{ pf} = 10^{-12} \text{ F}$) for calculation



$$10 \times 10^2 \text{ pF}$$

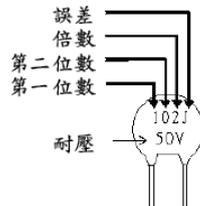

$$10 \times 10^2 \text{ pF} \pm 5\%$$

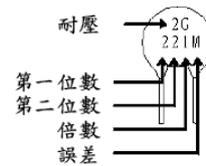

$$22 \times 10^1 \text{ pF} \pm 20\%$$

Code	H	J	K	L	M	N
Error (%)	3	5	10	15	20	30


2. Directly stamp on capacitors (for example: $0.1 \mu\text{F}$)

EE 2245 電子電路實驗

23

Wires

Red to the "+" and Black to the "-"

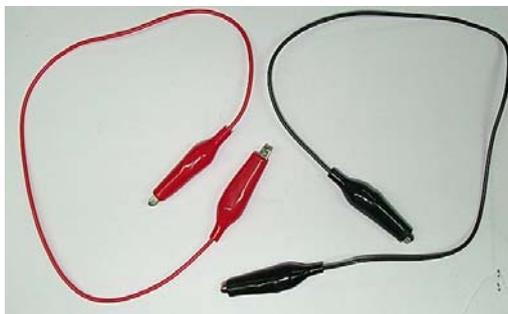

EE 2245 電子電路實驗

24

Coaxial Cable with BNC Connector



Coaxial cable: a type of wire that consists of a center wire surrounded by insulation and a grounded shield of braided wire. The shield minimizes electrical and radio-frequency interferences

用途：常接到function generator來將訊號送給電路

千萬注意：這條線與示波器量測用的線長相類似，不要將此兩種線及用途混淆

Bayonet Neill Concelman (BNC) Connector


EE 2245 電子電路實驗

25

Protoboard (Breadboard): Where You Build Circuits

含兩行兩行的插孔區塊：for connections to supply voltages and ground

含五行插孔區塊：For chips, passive elements, etc

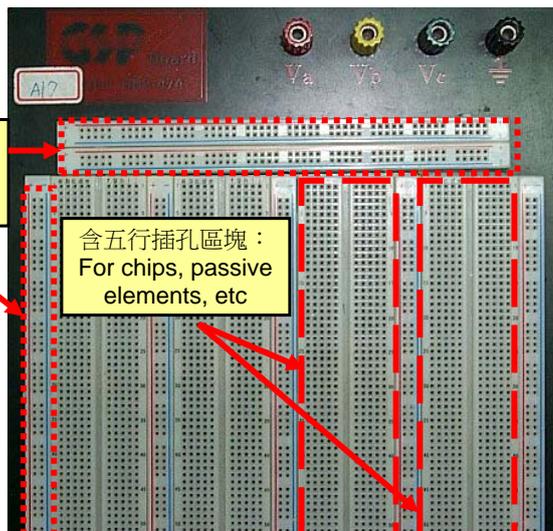


EE 2245 電子電路實驗


26

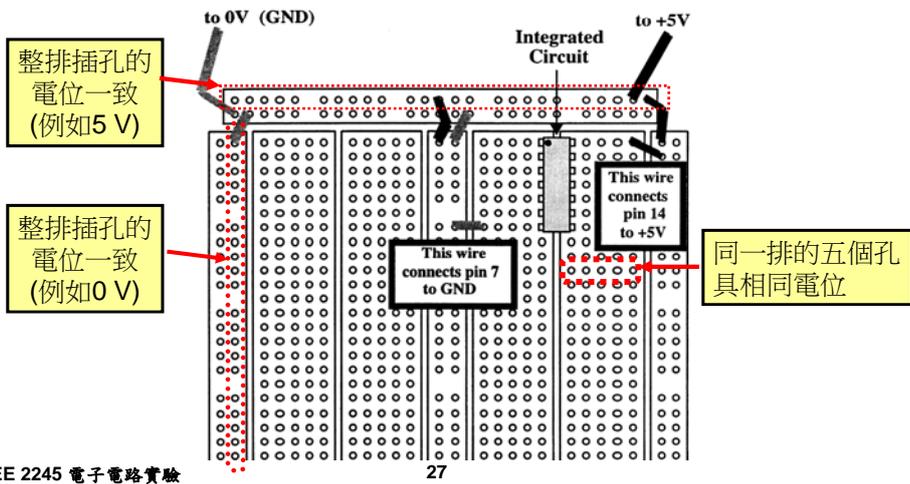Example

- Protoboard is designed such that supplied voltages can be conveniently accessed by circuits



Cont'd: Wiring on a Protoboard (請保持佈線的簡潔，以得到較佳的訊號品質)


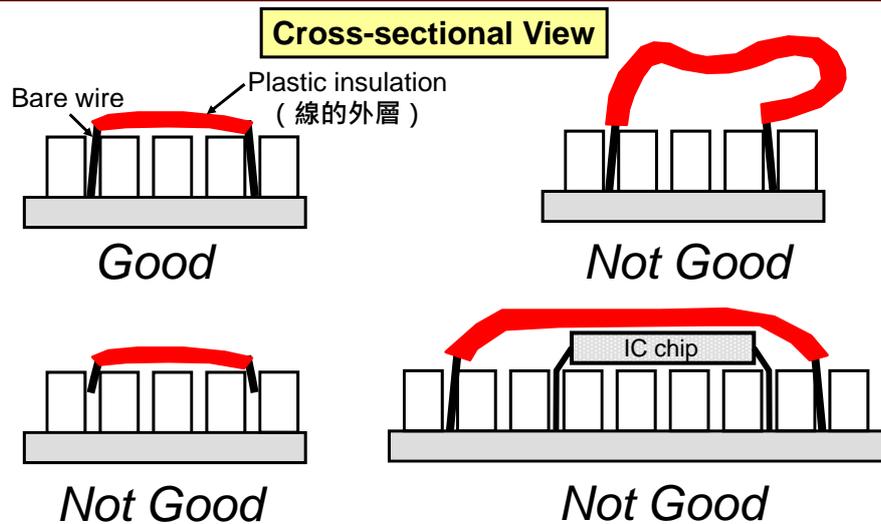


Lab 1

- DC measurement: Superposition, Thévenin's Theorem, maximum power transfer and Norton's Theorem
- AC measurement: RL and RLC circuits


Superposition

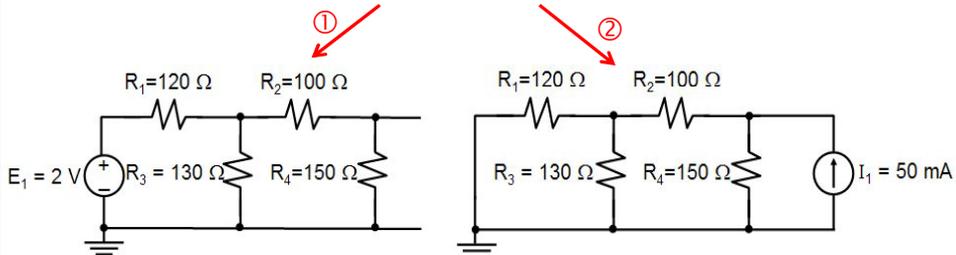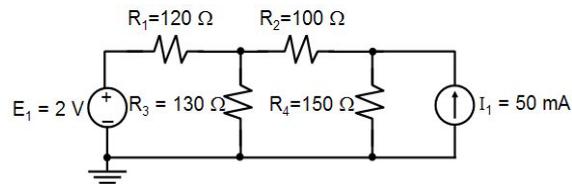- Verify the superposition principle: 分成①②各自計算電壓再加總



Thévenin's Theorem

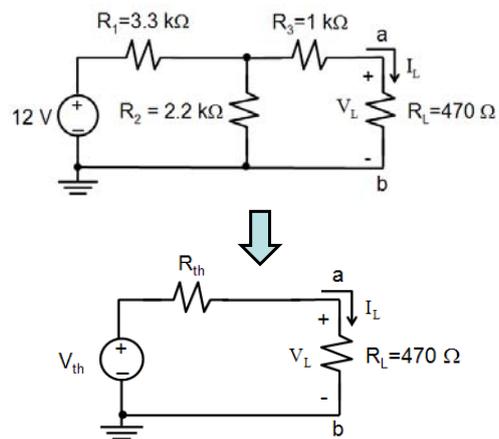- Learn how to use the theorem to simplify the circuit




EE 2245 電子電路實驗

31

From Thévenin to Maximum Power Transfer (DC Case)

- Find out the value of load resistance R_L to achieve maximum power transfer


$$R_L = R_{th}$$

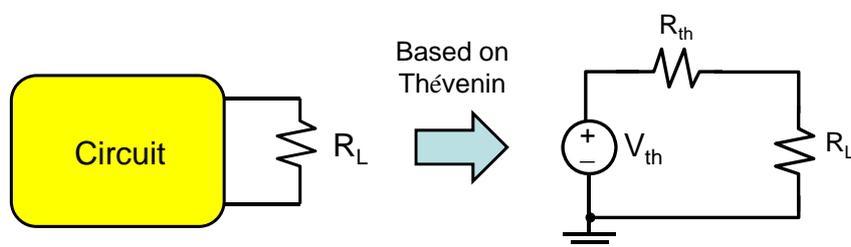

EE 2245 電子電路實驗

32


Cont'd

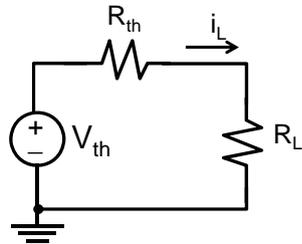


- The power absorbed by the load:

$$p_L =$$

Cont'd: AC Case

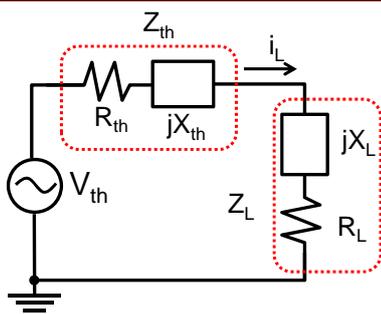

RL Circuit

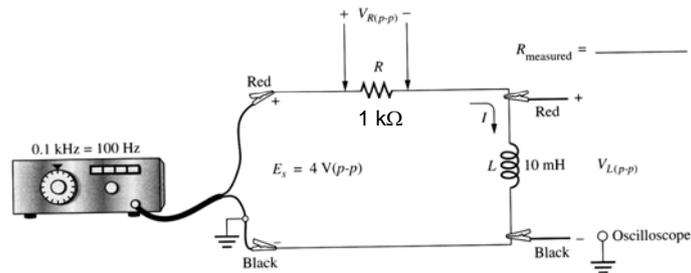

- Understand the phase difference in the measured V_R and V_L waveforms at different frequencies
- Based on the measured waveform amplitudes, can you say $E_s = V_R + V_L$?